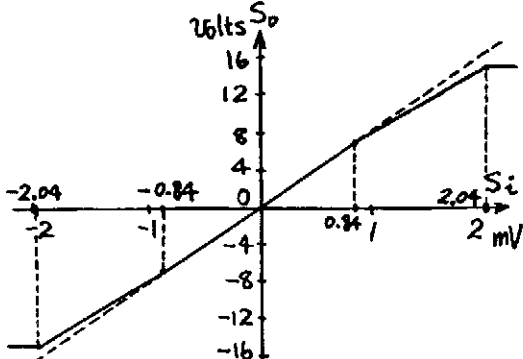


Homework Assignment No. 9 - Solutions

8.2


(a)  $A_1 = \frac{a_1}{1+a_1f} = \frac{50000}{1+5} \approx 8333$

$A_2 = \frac{20000}{1+2} = 6667$



(b)  $A_1 = \frac{50,000}{1+5000} = 9.998$

$A_2 = \frac{20,000}{1+2000} = 9.995$

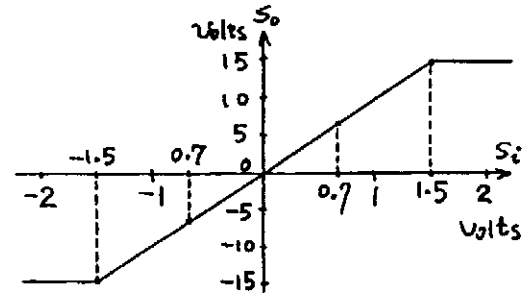

8.6(a)

From (8.66)

$Z_{ia} = \frac{R_F Z_i}{R_F + Z_i} = \frac{100 \times 500}{600} = 83.3 \text{ k}\Omega$

From (8.68)

$Z_{oa} = Z_o \parallel R_F \parallel R_L$   
 $= 200 \parallel 100 \text{ k} \parallel 15 \text{ k}$   
 $\approx 200 \Omega$

From (8.70)

$T = \left( \frac{10^5 \times 15 \times 10^3}{10^5 \times 15 \times 10^3 + 200 \times 10^3 + 200 \times 15 \times 10^3} \right) \times 75,000 \times \frac{500}{600}$   
 $= 61,560$


Thus with feedback

$Z_i = \frac{83.3 \text{ k}}{61,560} = 1.4 \Omega$

$Z_o = \frac{200}{61,560} = 0.0032 \Omega$

$A = \frac{1}{f} \frac{1}{1 + \frac{1}{T}} = \frac{100 \text{ k}\Omega}{1 + \frac{1}{61,560}}$   
 $= 99.998 \text{ k}\Omega$


8.7

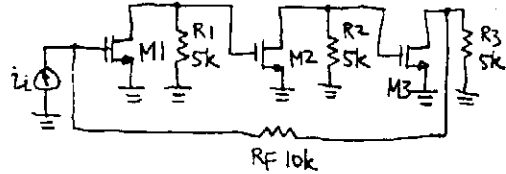

$g_m = \sqrt{2k' \frac{W}{L} I_D} = \sqrt{2 \times 60 \times 10^6 \times 100 \times 10^{-3}}$   
 $= 3.5 \times 10^{-3} \text{ A/V}$

$r_{o1} = \frac{1}{\lambda I_D} = \frac{50}{10^{-3}} = 50 \text{ k}\Omega$

(a)

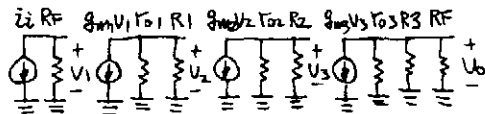

$a = \frac{V_o}{i_i} \Big|_{f=0} = R_F (-g_{m1} (r_{o1} \parallel R_1)) (-g_{m2} (r_{o2} \parallel R_2))$   
 $(-g_{m3} (r_{o3} \parallel R_3 \parallel R_F))$

$= -g_{m1}^3 (r_{o1} \parallel R_1)^2 R_F (r_{o2} \parallel R_2 \parallel R_F)$

$= -(3.5 \times 10^{-3})^3 (50 \text{ k} \parallel 15 \text{ k})^2 10 \text{ k} (50 \text{ k} \parallel 5 \text{ k} \parallel 10 \text{ k})$   
 $= -2.76 \times 10^7 \Omega$

$f = -\frac{i_{FB}}{V_o} = -\frac{1}{R_F} = -\frac{1}{10 \text{ k}\Omega}$

$a_f = 2.76 \times 10^3$

$\frac{V_o}{i_i} = \frac{a}{1 + a_f} = \frac{-2.76 \times 10^7}{1 + 2.76 \times 10^3} = -10 \text{ k}\Omega$

$R_i = \frac{R_F}{1 + a_f} = \frac{10 \text{ k}}{1 + 2.76 \times 10^3} = 16.4 \Omega$

$R_o = \frac{r_{o3} \parallel R_3 \parallel R_F}{1 + a_f} = \frac{50 \text{ k} \parallel 5 \text{ k} \parallel 10 \text{ k}}{1 + 2.76 \times 10^3} = 1.13 \Omega$

(b)

$a = -2.76 \times 10^7 \frac{R_F \parallel R_3}{R_F} = -2.76 \times 10^7 \frac{10 \text{ k} \parallel 5 \text{ k}}{10 \text{ k}}$


$= -2.51 \times 10^6 \Omega$

$a_f = 251$

$R_o = \frac{r_{o3} \parallel R_3 \parallel R_F}{1 + a_f} = \frac{50 \text{ k} \parallel 5 \text{ k} \parallel 10 \text{ k}}{1 + 251} = 12.4 \Omega$

8.8

(a) Basic amplifier

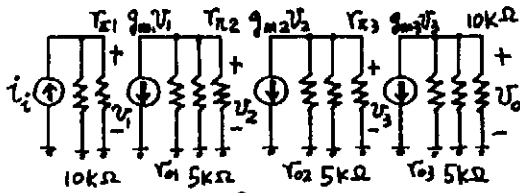

$$r_{\pi 1} = r_{\pi 2} = r_{\pi 3} = \frac{\beta}{g_m} = 5.2 \text{ k}\Omega$$

$$g_m = \frac{1}{26} V, r_o = 50 \text{ k}\Omega$$

$$R_1 = 10 \text{ k}\Omega \parallel r_{\pi 1} = \frac{5.2 \times 10}{15.2} = 3.42 \text{ k}\Omega$$

$$R_2 = r_{o1} \parallel 5 \text{ k}\Omega \parallel r_{\pi 2} = 2.42 \text{ k}\Omega$$

$$R_3 = r_{o2} \parallel 5 \text{ k}\Omega \parallel r_{\pi 3} = 2.42 \text{ k}\Omega$$

$$R_4 = r_{o3} \parallel 5 \text{ k}\Omega \parallel 10 \text{ k}\Omega = 3.13 \text{ k}\Omega$$

$$\begin{aligned} \therefore \frac{v_o}{i_i} &= -R_1 g_{m1} R_2 g_{m2} R_3 g_{m3} R_4 \\ &= -3.42 \frac{2420}{26} \frac{2420}{26} \frac{3130}{26} \text{ k}\Omega \\ &= -3.57 \times 10^9 \Omega = a \end{aligned}$$

$$f = -\frac{v_b}{v_o} = -\frac{1}{10 \text{ k}\Omega}$$

$$\begin{aligned} \therefore \text{overall } \frac{v_o}{i_i} &= \frac{a}{1+af} = \frac{-3.57 \times 10^9}{1+3.57 \times 10^5} \\ &= -10 \text{ k}\Omega \end{aligned}$$

$$\text{loop gain} = af = 3.57 \times 10^5$$

$$R_i = \frac{R_1}{1+af} = \frac{3420}{1+3.57 \times 10^5} = 0.0096 \Omega$$

$$R_o = \frac{R_4}{1+af} = \frac{3130}{1+3.57 \times 10^5} = 0.0088 \Omega$$

(b)

$$\text{New value of } R_1 = 3.42 \text{ k}\Omega \parallel 1 \text{ k}\Omega = 774 \Omega$$


$$\therefore a = -3.57 \times 10^9 \frac{774}{3420} = -808 \text{ M}\Omega$$

$$\therefore af = 808 \times 10^6 \times 10^{-4} = 8.08 \times 10^4$$

$$R_o = \frac{R_4}{1+af} = \frac{3130}{1+8.08 \times 10^4} = 0.0387 \Omega$$

8.11

Basic amplifier

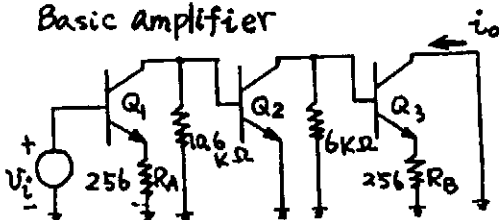

$$R_{E1} \parallel (R_F + R_{E2}) = 290 \parallel 2.19 \text{ k}\Omega = 256 \Omega$$

$$r_{\pi 1} = \frac{\beta}{g_m} = 52 \times 120 = 6.24 \text{ k}\Omega$$

$$r_{o1} = 80 \text{ k}\Omega$$

$$r_{\pi 2} = \frac{36 \times 120}{0.77} = 4.05 \text{ k}\Omega$$

$$r_{o2} = \frac{40}{0.77} = 52 \text{ k}\Omega$$

$$r_{\pi 3} = \frac{26 \times 120}{0.73} = 4.27 \text{ k}\Omega$$

$$r_{o3} = \frac{40}{0.73} = 54.8 \text{ k}\Omega$$

In forward gain calculation, neglect  $r_{o1}$  and  $r_{o3}$ .

For the basic amplifier,

$$\frac{i_o}{v_i} = \frac{g_{m1}}{1+g_{m1}R_A} R_1 g_{m2} R_2 \frac{g_{m3}}{1+g_{m3}R_B}$$

$$R_1 = 10.6 \text{ k}\Omega \parallel r_{\pi 2} = 2.93 \text{ k}\Omega$$

$$R_2 = r_{o2} \parallel 6 \text{ k}\Omega \parallel R_{i3}$$

$$R_{i3} = r_{\pi 3} (1+g_{m3}R_B)$$

$$= 4.27 \left( 1 + \frac{0.73}{26} \times 256 \right) = 35 \text{ k}\Omega$$

$$\therefore R_2 = 52 \text{ k}\Omega \parallel 6 \text{ k}\Omega \parallel 35 \text{ k}\Omega = 4.66 \text{ k}\Omega$$

$$\begin{aligned} \therefore \frac{i_o}{v_i} &= \frac{1}{52} \frac{1}{1+\frac{356}{52}} 2930 \frac{0.77}{26} 4660 \\ &\quad \times \frac{0.73}{26} \frac{1}{8.19} \end{aligned}$$

$$\therefore a = 4.5 \text{ A/V}$$

From (8.95)

$$\begin{aligned} f &= \frac{1}{\alpha_3} \frac{R_{E1} R_{E2}}{R_{E1} + R_{E2} + R_F} \\ &= \frac{1}{0.99} \frac{290 \times 290}{290 + 290 + 1900} \\ &= 34.25 \Omega \end{aligned}$$

$$\therefore \text{loop gain} = af = 4.5 \times 34.25 = 154$$

Overall gain with feedback

$$= \frac{a}{1+af} = \frac{4.5}{1+154} = \frac{4.5}{155} \text{ A/V}$$

$$\therefore \frac{i_o}{v_i} = 29 \text{ mA/V}$$

For the basic amplifier

Input resistance

$$\begin{aligned} r_{iA} &= r_{\pi 1} (1+g_{m1}R_A) \\ &= 6.24 \left( 1 + \frac{256}{52} \right) = 36.96 \text{ k}\Omega \end{aligned}$$

Output resistance

$$r_{oA} = r_{o3} \left( 1 + g_{m3}R_B \frac{r_{\pi 3}}{r_{\pi 3} + R_{S3}} \right)$$

$$R_{S3} = r_{o2} \parallel 6 \text{ k}\Omega = 5.38 \text{ k}\Omega$$

$$\begin{aligned} \therefore r_{oA} &= 54.8 \left( 1 + \frac{0.73}{26} 256 \frac{4.27}{4.27 + 5.38} \right) \\ &= 229 \text{ k}\Omega \end{aligned}$$

For the feedback amplifier

$$R_i = r_{iA} (1+af) = 36.96 \times 155 = 5.73 \text{ M}\Omega$$

$$R_o = r_{oA} (1+af) = 229 \times 155 = 35.5 \text{ M}\Omega$$