



Homework Assignment No. 11 - Solutions

Problem 1 - (10 points)

The simplified schematic of a feedback amplifier is shown. Use the method of feedback analysis to find V_2/V_1 , $R_{in} = V_1/I_1$, and $R_{out} = V_2/I_2$. Assume that all transistors are matched and that $g_m = 1\text{mA/V}$ and $r_{ds} = \infty$.

Solution

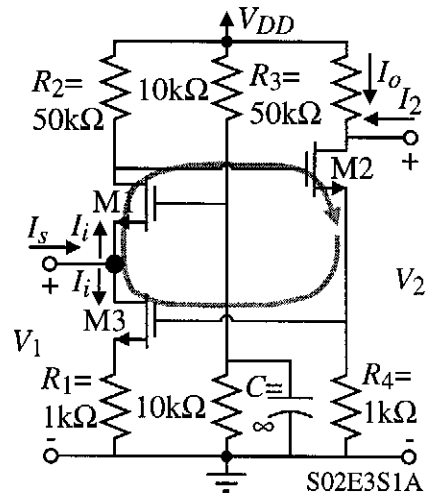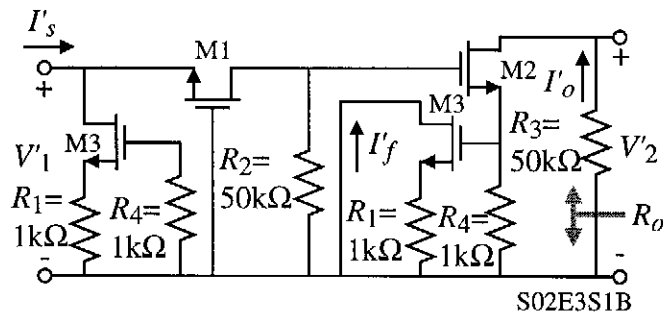This feedback circuit is shunt-series. We begin with the open-loop, quasi-ac model shown below.



The small-signal, open-loop model is:

$$\frac{I'_o}{I'_s} = \left(\frac{I'_o}{V_{gs2}} \right) \left(\frac{V_{gs2}}{V_{gs1}} \right) \left(\frac{V_{gs1}}{I'_s} \right)$$

$$V_{gs2} = -g_{m1}V_{gs1}R_2 - g_{m2}V_{gs2}R_4$$

or

$$\frac{V_{gs2}}{V_{gs1}} = \frac{-g_{m1}R_2}{1 + g_{m2}R_4} = -\frac{50}{2} = -25 \quad \therefore a = \frac{I'_o}{I'_s} = (g_{m2})(-25) \left(\frac{-1}{g_{m1}} \right) = 25\text{A/A}$$

$$f = \frac{I'_f}{I'_o} = \left(\frac{I'_f}{V_{gs3}} \right) \left(\frac{V_{gs3}}{I'_o} \right) = (g_{m3}) \left(\frac{R_4}{1 + g_{m3}R_1} \right) = (1\text{mA/V})(0.5\text{k}\Omega) = 0.5$$

$$\therefore af = 25 \cdot 0.5 = 12.5$$

$$R_i = \frac{v'_1}{I'_s} = \frac{1}{g_{m1}} = 1\text{k}\Omega \rightarrow R_{in} = R_{if} = \frac{R_i}{1 + af} = \frac{1000}{13.5} = 74.07\Omega$$

$$R_{out} = 50\text{k}\Omega \quad (R_3 \text{ is outside the feedback loop})$$


$$\frac{I'_o}{I'_s} = \frac{a}{1 + af} = \frac{25}{1 + 12.5} = 1.852 \text{ A/A} \rightarrow \frac{v_2}{v_1} = \frac{I'_o(-50\text{k}\Omega)}{I'_s(74.07\Omega)} = -1240.1 \text{ V/V}$$

Problem 2 - (10 points)

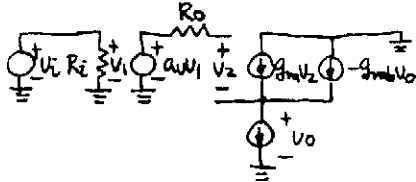Problem 8.30 of GHLM

(a)

The basic amplifier without the feedback signal inserted at the inverting input of the opamp



$$g_m = \sqrt{2k \frac{W}{L} I_D} = \sqrt{2 \times 180 \times 10^{-6} \times 100 \times 0.5 \times 10^{-3}}$$

$$= 4.2 \times 10^{-3} \text{ A/V}$$

$$g_{mb} = \frac{\gamma}{2\sqrt{2\phi_f + V_{SB}}} g_m = \frac{\gamma}{2\sqrt{2\phi_f}} g_m$$

$$= \frac{0.3}{2\sqrt{2 \times 0.3}} 4.2 \times 10^{-3} = 8.1 \times 10^{-4} \text{ A/V}$$

$$V_o = g_m (a_v V_i - V_o) \frac{1}{g_{mb}}$$

$$a = \frac{V_o}{V_i} = a_v \frac{g_m}{g_m + g_{mb}}$$

$$f = 1$$


$$a_f = a_v \frac{g_m}{g_m + g_{mb}} = 1000 \frac{4.2}{4.2 + 0.81} = 838$$

$$A = \frac{a}{1 + a_f} = \frac{838}{1 + 838} = 0.999$$

$$r_{ia} = R_i$$

$$R_{in} = r_{ia}(1 + a_f) = R_i(1 + a_f)$$
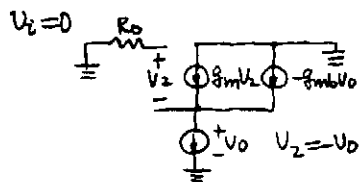
$$= 1\text{M}(1 + 838) = 839\text{M}\Omega$$




$$r_{oa} = \frac{1}{g_m} \parallel \frac{1}{g_{mb}} = \frac{1}{g_m + g_{mb}}$$

$$R_{out} = \frac{r_{oa}}{1 + a_f} = \frac{1}{g_m + g_{mb} (1 + a_f)}$$

$$= \frac{1}{4.2 \times 10^{-3} + 8.1 \times 10^{-4} (1 + 838)}$$

$$= 0.238 \Omega$$

(b)

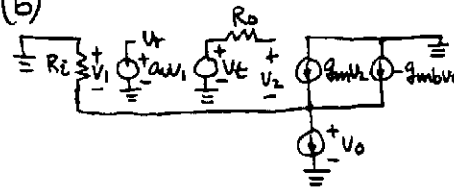

$$V_o = g_m (V_i - V_o) \left(\frac{1}{g_{mb}} \parallel R_i \right)$$

$$V_o = \frac{g_m}{\frac{1}{R_i} + g_m + g_{mb}}$$

$$R = a_v \frac{g_m}{\frac{1}{R_i} + g_m + g_{mb}}$$

$$\approx a_v \frac{g_m}{g_m + g_{mb}}$$

$$= 838$$

$$A_{vo} = \frac{V_o}{V_i} |_{a_v=0} = 1 \quad (V_i = 0 \text{ and } V_o = V_i)$$

$$d = \frac{V_{o1}}{V_i} |_{a_v=0} = \frac{\frac{1}{g_m} \parallel \frac{1}{g_{mb}}}{R_i + \frac{1}{g_m} \parallel \frac{1}{g_{mb}}}$$

$$= \frac{1}{g_m + g_{mb}}$$

$$\approx \frac{1}{(g_m + g_{mb}) R_i}$$

$$= \frac{1}{(4.2 \times 10^{-3} + 8.1 \times 10^{-4}) 10^6}$$


$$= 2.00 \times 10^{-4}$$

$$A = A_{vo} \frac{R}{1 + R} + \frac{d}{1 + R}$$

$$= 1 \frac{838}{1 + 838} + \frac{2.00 \times 10^{-4}}{1 + 838}$$

$$= 0.999$$

$$a_v = 0$$

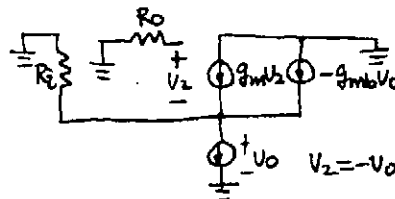

$$R_{in}(a_v=0) = R_i + \frac{1}{g_m} \parallel \frac{1}{g_{mb}} \approx R_i = 1\text{M}\Omega$$

$$R(\text{short}) = R = 838$$

$$R(\text{open}) = 0 \quad (V_i = 0)$$

$$R_{in} = R_{in}(a_v=0) \frac{1 + R(\text{short})}{1 + R(\text{open})} \approx R_i \frac{1 + R}{1 + 0}$$

$$= R_i(1 + R) = 1\text{M}(1 + 838) = 839\text{M}\Omega$$

$$R_{out}(a_v=0) = R_i \parallel \frac{1}{g_m} \parallel \frac{1}{g_{mb}} \approx \frac{1}{g_m} \parallel \frac{1}{g_{mb}}$$

$$= \frac{1}{4.2 \times 10^{-3} + 8.1 \times 10^{-4}} = 200 \Omega$$

$$R(\text{short}) = 0 \quad (V_o = 0)$$

$$R(\text{open}) = R$$

$$R_{out} = R_{out}(a_v=0) \frac{1 + R(\text{short})}{1 + R(\text{open})}$$

$$\approx \frac{1}{g_m + g_{mb}} \frac{1 + 0}{1 + R} = \frac{1}{g_m + g_{mb} (1 + R)}$$

$$= 200 \frac{1}{1 + 838} = 0.238 \Omega$$

Problem 3 - (10 points)

Use the Blackman's formula (see below) to calculate the small-signal output resistance of the stacked MOSFET configuration having identical drain-source drops for both transistors. Express your answer in terms of all the pertinent small-signal parameters and then simplify your answer if $g_m > g_{ds} > (1/R)$. Assume the MOSFETs are identical.

$$R_{out} = R_{out}(g_m=0) \left[\frac{1 + RR(\text{output port shorted})}{1 + RR(\text{output port open})} \right]$$

(You may use small-signal analysis if you wish but this circuit seems to be one of the rare cases where feedback analysis is more efficient.)

Solution

$$R_{out}(g_m=0) = 2R \parallel (r_{ds1} + r_{ds2}) = \frac{2R(r_{ds1} + r_{ds2})}{2R + r_{ds1} + r_{ds2}}$$

$RR(\text{port shorted}) = ?$

$$v_r = 0 - v_{s2} = -g_{m2}v_t \left(\frac{r_{ds1}r_{ds2}}{r_{ds1} + r_{ds2}} \right)$$

$$\Rightarrow RR(\text{port shorted}) = \frac{g_{m2}r_{ds1}r_{ds2}}{r_{ds1} + r_{ds2}}$$

$RR(\text{port open}) = ?$

$$v_r = -g_{m2}v_t \left(\frac{r_{ds2}(r_{ds1} + R)}{r_{ds1} + r_{ds2} + 2R} \right)$$



$$\Rightarrow RR(\text{port open}) = \frac{g_{m2}r_{ds2}(r_{ds1} + R)}{r_{ds1} + r_{ds2} + 2R}$$

$$\therefore R_{out} = \frac{2R(r_{ds1} + r_{ds2})}{2R + r_{ds1} + r_{ds2}} \left[\frac{1 + \frac{g_{m2}r_{ds1}r_{ds2}}{r_{ds1} + r_{ds2}}}{1 + \frac{g_{m2}r_{ds2}(r_{ds1} + R)}{r_{ds1} + r_{ds2} + 2R}} \right] = 2R \left(\frac{r_{ds1} + r_{ds2} + g_{m2}r_{ds1}r_{ds2}}{r_{ds1} + r_{ds2} + 2R + g_{m2}r_{ds2}(r_{ds1} + R)} \right)$$

Using the assumptions of $g_m > g_{ds} > (1/R)$ we can simplify R_{out} as

$$R_{out} \approx 2R \left(\frac{g_{m2}r_{ds1}r_{ds2}}{g_{m2}r_{ds2}R} \right) = \underline{\underline{2r_{ds1}}}$$

What is the insight? Well there are two feedback loops, one a series (the normal cascode) and one a shunt. Apparently they are working against each other and the effective output resistance is pretty much what it would be if there were two transistors in series without any feedback.

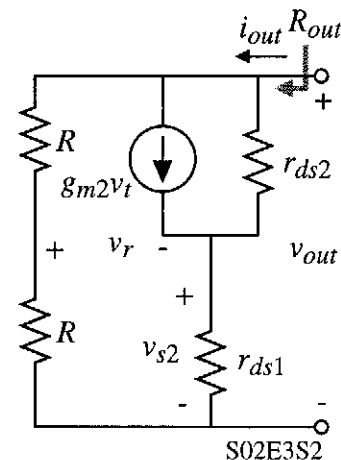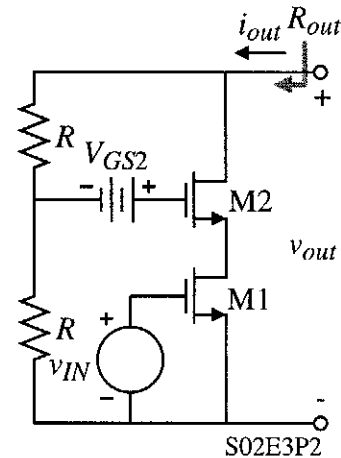


Problem 4 – (10 points)

Find the dominant roots of the MOS follower and the BJT follower for the buffered, class-A op amp of Ex. 7.1-2. Use the capacitances of Table 3.2-1. Compare these root locations with the fact that $GB = 5\text{MHz}$? Assume the capacitances of the BJT are $C_\pi = 10\text{pF}$ and $C_\mu = 1\text{pF}$.

Solution

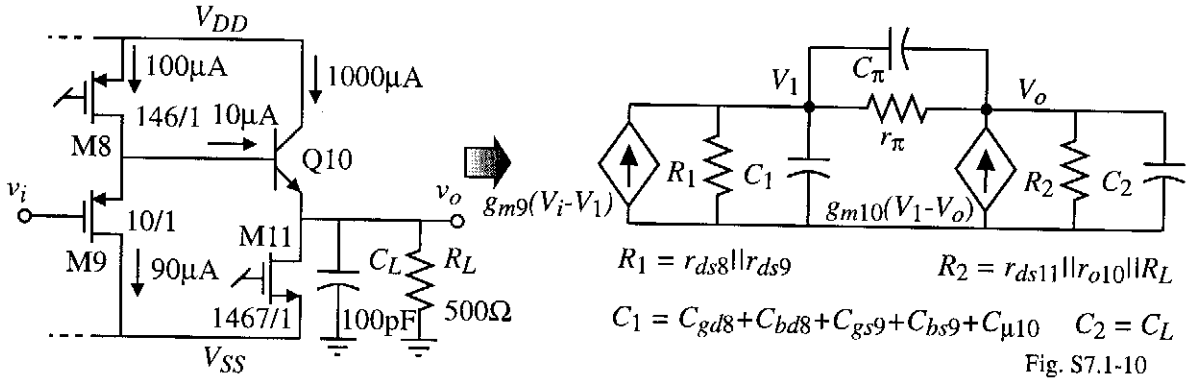The model of just the output buffer of Ex. 7.1-2 is shown.



The nodal equations can be written as,

$$g_{m9}V_i = (g_{m9} + G_1 + g_{\pi 10} + sC_{\pi 10} + sC_1)V_1 - (g_{\pi 10} + sC_{\pi 10})V_o$$

$$0 = -(g_{m10} + g_{\pi 10} + sC_{\pi 10})V_1 + (g_{m10} + G_2 + g_{\pi 10} + sC_{\pi 10} + sC_2)V_o$$

Solving for V_o/V_i gives,

$$\frac{V_o}{V_i} = \frac{g_{m9}(g_{m10} + g_{\pi 10} + sC_{\pi 10})}{(g_{\pi 10} + sC_{\pi 10})(g_{m9} + G_1 + G_2 + sC_1 + sC_2) + (g_{m10} + G_2 + sC_2)(g_{m9} + G_1 + sC_1)}$$

$$\frac{V_o}{V_i} = \frac{g_{m9}(g_{m10} + g_{\pi 10} + sC_{\pi 10})}{a_0 + sa_1 + s^2a_2}$$

where

$$a_0 = g_{m9}g_{\pi 10} + g_{\pi 10}G_1 + g_{\pi 10}G_2 + g_{m9}g_{m10} + g_{m10}G_1 + g_{m9}G_2 + G_1G_2$$

$$a_1 = g_{m9}C_{\pi 10} + G_1C_{\pi 10} + G_2C_{\pi 10} + g_{\pi 10}C_1 + g_{\pi 10}C_2 + g_{m10}C_1 + G_2C_1 + g_{m9}C_2 + G_1C_2$$

$$a_2 = C_{\pi 10}C_1 + C_{\pi 10}C_2 + C_1C_2$$

The numerical value of the small signal parameters are:

$$g_{m10} = \frac{1\text{mA}}{25.9\text{mV}} = 38.6\text{mS}, \quad G_2 = 2\text{mS}, \quad g_{\pi 10} = 386\mu\text{S}, \quad g_{m9} = \sqrt{2 \cdot 50 \cdot 10 \cdot 90} = 300\mu\text{S},$$

$$G_1 = g_{ds8} + g_{ds9} = 0.05 \cdot 100\mu\text{A} + 0.05 \cdot 90\mu\text{A} = 9.5\mu\text{S}$$

$$C_2 = 100\text{pF}, \quad C_{\pi 10} = 10\text{pF}, \quad C_1 = C_{gs9} + C_{bs9} + C_{bd8} + C_{gd8} + C_{\mu 10}$$

$$C_{gs9} = C_{ov} + 0.667C_{ox}W_9L_9 = (220 \times 10^{-12})(10 \times 10^{-6})$$

$$+ 0.667(24.7 \times 10^{-4})(10 \times 10^{-12}) = 18.7\text{fF}$$

Problem 7.1-10 – Continued

$$C_{bs9} = 560 \times 10^{-6} (30 \times 10^{-12}) + 350 \times 10^{-12} (26 \times 10^{-6}) = 25.9 \text{ fF}$$

(Assumed area = $3 \mu\text{m} \times 10 \mu\text{m} = 30 \mu\text{m}^2$ and perimeter is $3 \mu\text{m} + 10 \mu\text{m} + 3 \mu\text{m} + 10 \mu\text{m} = 26 \mu\text{m}$)

$$C_{bd8} = 560 \times 10^{-6} (438 \times 10^{-12}) + 350 \times 10^{-12} (298 \times 10^{-6}) = 349 \text{ fF}$$

$$C_{gd8} = C_{ov} = (220 \times 10^{-12}) (146 \times 10^{-6}) = 32.1 \text{ fF}$$

$$\therefore C_1 = 18.7 \text{ fF} + 25.9 \text{ fF} + 349 \text{ fF} + 32.1 \text{ fF} + 1000 \text{ fF} = 1.43 \text{ pF}$$

(We have ignored any reverse bias influence on pn junction capacitors.)

The dominant terms of a_0 , a_1 , and a_2 based on these values are shown in boldface above.

$$\therefore \frac{V_o}{V_i} \approx \frac{g_{m9}(g_{m10} + g_{\pi10} + sC_{\pi10})}{g_{m9}g_{m10} + g_{\pi10}G_2 + s(G_2C_{\pi10} + g_{\pi10}C_2 + g_{m10}C_1 + g_{m9}C_2) + s^2C_2C_{\pi10}}$$

$$\frac{V_o}{V_i} = \frac{g_{m9}g_{m10}}{g_{m9}g_{m10} + g_{\pi10}G_2} \left[\frac{1 + \frac{sC_{\pi10}}{g_{m10}}}{1 + s \left(\frac{G_2C_{\pi10} + g_{\pi10}C_2 + g_{m10}C_1 + g_{m9}C_2}{g_{m9}g_{m10} + g_{\pi10}G_2} \right) + s^2 \frac{C_2C_{\pi10}}{g_{m9}g_{m10} + g_{\pi10}G_2}} \right]$$

Assuming negative real axis roots widely spaced gives,

$$p_1 = -\frac{1}{a} = \frac{-(g_{m9}g_{m10} + g_{\pi10}G_2)}{G_2C_{\pi10} + g_{\pi10}C_2 + g_{m10}C_1 + g_{m9}C_2} = -\frac{1.235 \times 10^{-5}}{1.465 \times 10^{-13}} = \underline{\underline{-84.3 \times 10^6 \text{ rads/sec.}}}$$

$$= -13.4 \text{ MHz}$$

$$p_2 = -\frac{a}{b} = \frac{-(G_2C_{\pi10} + g_{\pi10}C_2 + g_{m10}C_1 + g_{m9}C_2)}{C_2C_{\pi10}} = -\frac{1.465 \times 10^{-13}}{100 \times 10^{-12} \cdot 10 \times 10^{-12}}$$

$$= \underline{\underline{-146.5 \times 10^6 \text{ rads/sec.}} \rightarrow -23.32 \text{ MHz}}$$

$$z_1 = -\frac{g_{m10}}{C_{\pi10}} = -\frac{38.6 \times 10^{-3}}{10 \times 10^{-12}} = \underline{\underline{-3.86 \times 10^9 \text{ rads/sec.}} \rightarrow -614 \text{ MHz}}$$

We see that neither p_1 or p_2 is greater than $10GB$ if $GB = 5 \text{ MHz}$ so they will deteriorate the phase margin of the amplifier of Ex. 7.1-2.

Problem 5 - (10 points)

Find the GB of a two-stage op amp using Miller compensation using a nulling resistor that has 60° phase margin where the second pole is -10×10^6 rads/sec and two higher poles both at -100×10^6 rads/sec. Assume that the RHP zero is used to cancel the second pole and that the load capacitance stays constant. If the input transconductance is $500 \mu\text{A/V}$, what is the value of C_c ?

Solution

The resulting higher-order poles are two at -100×10^6 radians/sec. The resulting phase margin expression is,

$$\text{PM} = 180^\circ - \tan^{-1}(A_v(0)) - 2 \tan^{-1}\left(\frac{GB}{10^7}\right) = 90^\circ - 2 \tan^{-1}\left(\frac{GB}{10^7}\right) = 60^\circ$$

$$\therefore 30^\circ = 2 \tan^{-1}\left(\frac{GB}{10^7}\right) \rightarrow \left(\frac{GB}{10^7}\right) = \tan(15^\circ) = 0.2679$$

$$GB = 2.679 \times 10^7 = \frac{g_{m1}}{C_c} \rightarrow C_c = \frac{500 \times 10^{-6}}{26.79 \times 10^7} = \underline{\underline{18.66 \text{ pF}}}$$