

Homework Assignment No. 12

Due Friday, April 11, 2003 in class

Problem 1 - (10 points)


Problem 7.3-7 of Allen and Holberg, 2nd edition

Problem 2 – (10 points)

Calculate the small-signal voltage gain, the SR ($C_L = 1\text{pF}$), and the P_{diss} for the op amp shown where $I_5 = 100\text{nA}$ and all transistors M1-M11 have a W/L of $10\mu\text{m}/1\mu\text{m}$ and $V_{DD} = -V_{SS} = 1.5\text{V}$. If the minimum voltage across the drain-source of M6 and M7 are to be 0.1V , design the W/L ratios of M12-M15 that give the maximum plus and minus output voltage swing assuming that transistors M12 and M15 have a current of 50nA . The transistors are working in weak inversion and are modeled by the large signal model of

$$i_D = \frac{W}{L} I_{D0} \exp\left(\frac{v_{GS}}{nV_t}\right)$$

where $I_{D0} = 2\text{nA}$ for PMOS and NMOS and $n_P = 2.5$ and $n_N = 1.5$. Assume $V_t = 26\text{mV}$ and $\lambda_N = 0.4\text{V}^{-1}$ and $\lambda_P = 0.5\text{V}^{-1}$.

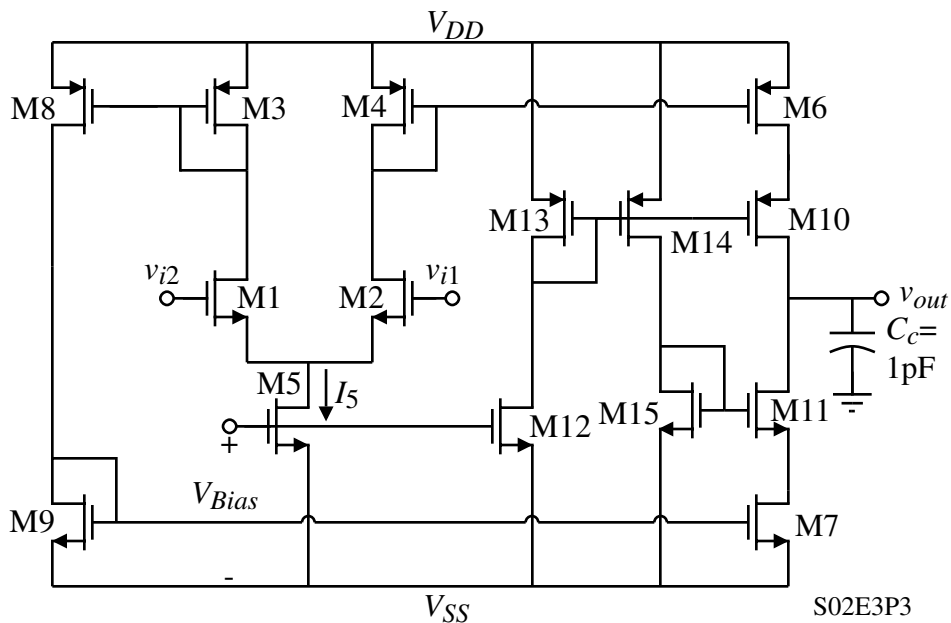

Problem 3 – (10 points)

Problem 7.4-3 of Allen and Holberg, 2nd edition

Problem 4 - (10 points)

Problem 7.5-5 of Allen and Holberg, 2nd edition

