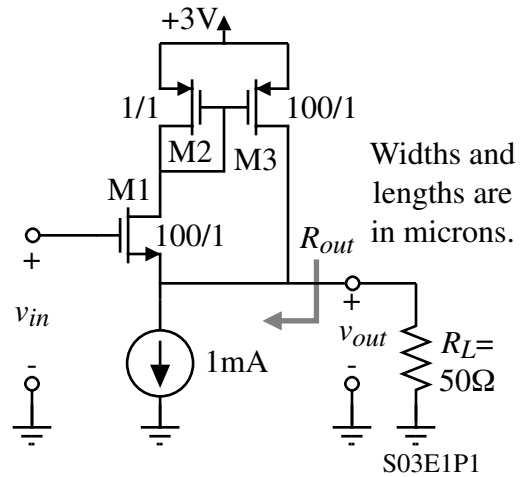


Problem 4 - (10 points)

Find an algebraic expression for the voltage gain, v_{out}/v_{in} , and the output resistance, R_{out} , of the source follower shown in terms of the small-signal model parameters, g_m and R_L (ignore r_{ds}). If the bias current is 1mA find the numerical value of the voltage gain and the output resistance. Assume that $K_N' = 110\mu\text{A}/\text{V}^2$, $V_{TN} = 0.7\text{V}$, and $K_P' = 50\mu\text{A}/\text{V}^2$, $V_{TP} = -0.7\text{V}$.

Problem 5 (40 points) - Design Problem #1

You are to design a CMOS output amplifier having a single-ended input and single-ended output and a voltage gain of +1. This amplifier is to use $\pm 2\text{V}$ power supplies and all W/L values should be between 1 and 100. You may only use MOSFETs or substrate or vertical BJTs (only one type, NPN) in your design with the exception of a load capacitor (C_L) and load resistor (R_L). You should use the following model parameters for SPICE. Use $\beta_F = 100$ and $I_s = 10\text{fA}$ for the BJT.

	K' ($\mu\text{A}/\text{V}^2$)	V_T (V)	$\gamma(\sqrt{V})$	$2\phi_F$ (V)	λ (V^{-1})
NMOS	110	0.7	0.4	0.7	0.04(L=1 μm) 0.01(L=2 μm)
PMOS	50	-0.7	0.57	0.8	0.05(L=1 μm) 0.01(L=2 μm)

The various definitions used in the specifications of this design are:

- 1.) Slew rate (SR) is the smallest \pm output voltage rate across a 1nF load capacitance when the output voltage is between $\pm 1\text{V}$.
- 2.) The peak output voltage (V_P) is the maximum \pm deviation from the quiescent output voltage when a sinusoid is applied to the input and a 100 Ω resistor is attached to the output.
- 3.) Efficiency in percent (η) is defined as

$$\eta = \left(\frac{\text{Power to the load resistor of } 100\Omega}{\text{Power from the supplies}} \right) \times 100$$

- 4.) Voltage gain (A_v) is the output voltage (peak-to-peak) over the input voltage (peak-to-peak) when the output is loaded with a 100 Ω load resistor.

Your score for this problem will be determined as follows:

$$\text{SCORE} = 1.0 \times 10^6 \cdot \min[SR, 10\text{V}/\mu\text{s}] + 10 \cdot \min[V_P, 1] + 0.4 \cdot \min[\eta, 25] + \frac{10}{|A_v - 1| + 1}$$