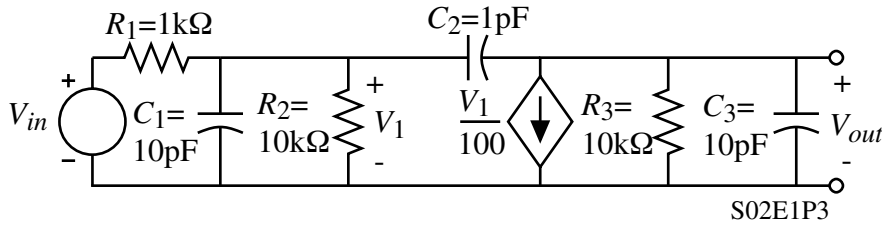


Homework Assignment No. 4 - Solutions

Problem 1

Find the midband voltage gain and the -3dB frequency in Hertz for the circuit shown.



Solution

The midband gain is given as,

$$\frac{V_{out}}{V_{in}} = - \left(\frac{10\text{k}\Omega}{100} \right) \left(\frac{10\text{k}\Omega}{11\text{k}\Omega} \right) = \underline{\underline{-90.91\text{V/V}}}$$

To find the -3dB frequency requires finding the 3 open-circuit time constants.

R_{C10} :

$$R_{C10} = 1\text{k}\Omega \parallel 10\text{k}\Omega = 0.9091\text{k}\Omega \quad \rightarrow \quad R_{C10}C_1 = 0.9091 \cdot 10\text{ns} = 9.09\text{ns}$$

R_{C20} :

$$\begin{aligned} v_t &= i_t R_{C10} + R_3(i_t + 0.01V_1) \\ &= i_t(R_{C10} + R_3 + 0.01R_{C10}R_3) \\ \therefore R_{C20} &= R_{C10} + R_3 + 0.01R_{C10}R_3 \\ &= 0.9091 \end{aligned}$$

$$10(1 + 0.01 \cdot 909.1)\text{k}\Omega = 101.82\text{k}\Omega$$


$$R_{C20}C_2 = 101.82 \cdot 1\text{ns} = 101.82\text{ns}$$

R_{C30} :

$$R_{C30} = 10\text{k}\Omega \quad \rightarrow \quad R_{C30}C_3 = 10 \cdot 10\text{ns} = 100\text{ns}$$


$$\Sigma T_0 = (9.091 + 101.82 + 100)\text{ns} = 210.91\text{ns} \quad \rightarrow \quad \omega_{-3\text{dB}} = \frac{1}{\Sigma T_0} = 4.74 \times 10^6 \text{ rad/s}$$

$$f_{-3\text{dB}} = \frac{4.74 \times 10^6}{2\pi} = \underline{\underline{754.6\text{kHz}}}$$

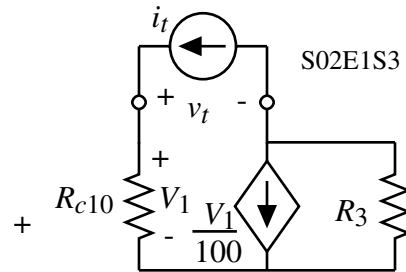


Problem 2 – (10 points)

Find the midband voltage gain and the exact value of the two poles of the voltage transfer function for the circuit shown. Assume that $R_I = 1\text{k}\Omega$, $R_L = 10\text{k}\Omega$, $g_m = 1\text{mS}$, $C_{gs} = 5\text{pF}$ and $C_{gd} = 1\text{pF}$. Ignore r_{ds} .

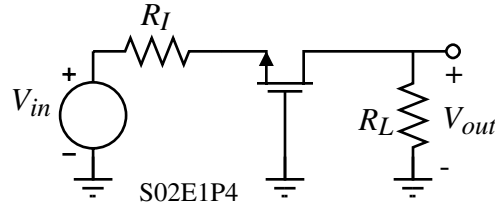**Solution**

The best approach to this problem is a direct analysis.

Small-signal model:

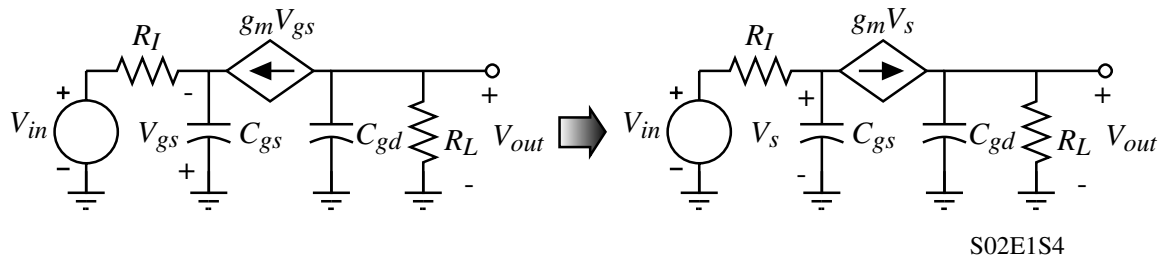

$$V_{out} = g_m Z_L V_s \quad \text{where} \quad Z_L = \frac{1}{sR_L C_{gd} + 1} \quad \text{and} \quad \frac{V_{in} - V_s}{R_I} = g_m V_s + sC_{gs} V_s$$

Solving for V_s from the second equation gives,

$$V_s = \frac{V_{in}}{1 + g_m R_I + sC_{gs} R_I}$$

Substituting V_s in the first equation gives,


$$\begin{aligned} V_{out} &= g_m Z_L \frac{V_{in}}{1 + g_m R_I + sC_{gs} R_I} \rightarrow \frac{V_{out}}{V_{in}} = g_m \left(\frac{1}{sR_L C_{gd} + 1} \right) \left(\frac{1}{1 + g_m R_I + sC_{gs} R_I} \right) \\ &= \left(\frac{g_m R_L}{1 + g_m R_I} \right) \left(\frac{1}{sR_L C_{gd} + 1} \right) \left(\frac{1}{\frac{sC_{gd} R_I}{1 + g_m R_I} + 1} \right) = \text{MBG} \left(\frac{1}{1 - \frac{s}{p_1}} \right) \left(\frac{1}{1 - \frac{s}{p_2}} \right) \end{aligned}$$

$$\therefore \text{MBG} = \left(\frac{g_m R_L}{1 + g_m R_I} \right) = \left(\frac{1 \cdot 10}{1 + 1 \cdot 1} \right) = \underline{\underline{5V/V}}$$

$$p_1 = -\frac{1}{R_L C_{gd}} = -\frac{1}{10 \cdot 1\text{ns}} = \underline{\underline{-10^8 \text{ rad/s}}} \quad \text{and} \quad p_2 = -\frac{1 + g_m R_I}{R_I C_{gs}} = -\frac{1 + 1}{1 \cdot 5\text{ns}} = \underline{\underline{-4 \times 10^8 \text{ rad/s}}}$$

7.21

(a)

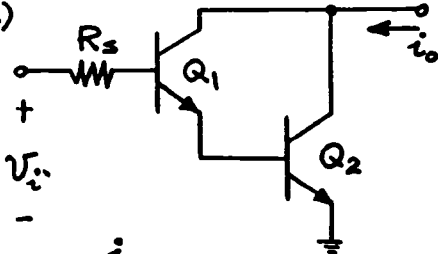

$$G_m = \frac{i_o}{V_i} \approx \frac{1}{2} g_{m2} = \frac{1}{2} \frac{1}{26}$$

$$= \frac{1}{52} \text{ A/V} \quad \text{--- both circuits}$$

$$R_i \approx r_{\pi 1} (1 + g_{m1} r_{\pi 2}) = 2 r_{\pi 1} = 2 \frac{\beta}{g_{m1}}$$

$$= 2 \times 100 \times 2.6 \text{ k}\Omega = 520 \text{ k}\Omega$$

--- both Circuits

$$\therefore \frac{V_o}{V_i} = - \frac{R_i}{R_i + R_s} G_m R_L$$

$$= - \frac{520}{620} \times \frac{1}{52} \times 3000$$

$$= -48.4 \quad \text{--- both circuits}$$

(b) Darlington

$$R_{C50} = R_L = 3 \text{ k}\Omega \quad \text{for } Q_1 \text{ and } Q_2$$

$$\therefore R_{C50} (C_{e51} + C_{e52}) = 3 \times 2 = 6 \text{ ns}$$

$$R_{\pi 01} = r_{\pi 1} \parallel \frac{R_s + R_E}{1 + g_{m1} R_E} = r_{\pi 1} \parallel \frac{R_s + r_{\pi 2}}{1 + g_{m1} r_{\pi 2}}$$

$$= 260 \text{ k}\Omega \parallel \frac{102.6 \text{ k}\Omega}{2} = 42.9 \text{ k}\Omega$$

$$C_{\pi} + C_{\mu} = \frac{g_m}{2\pi f_T} = \frac{1}{26} \frac{1}{2\pi \times 500 \times 10^6}$$

$$= 12.2 \text{ pF} \quad \text{at } I_c = 1 \text{ mA}$$

$$\therefore C_{\pi} = 11.8 \text{ pF} \quad \text{at } I_c = 1 \text{ mA}$$

$$C_b = 9.8 \text{ pF}$$

$$\therefore C_{b1} = 0.1 \text{ pF}, \therefore C_{\pi 1} = 2.1 \text{ pF}$$

$$\therefore C_{\pi 1} R_{\pi 01} = 2.1 \times 42.9 = 90.1 \text{ ns}$$

$$R_{\mu 01} = R_x + R_L + G_m R_x R_L$$

$$R_x = R_i \parallel R_s = 520 \text{ k}\Omega \parallel 100 \text{ k}\Omega = 83.9 \text{ k}\Omega$$

$$\therefore R_{\mu 01} = 83.9 + 3 + \frac{1}{52} \times 3000 \times 83.9$$

$$= 4.93 \text{ M}\Omega$$

$$\therefore C_{\mu 1} R_{\mu 01} = 0.4 \times 4.93 \times 10^3 = 1972 \text{ ns}$$

$$C_{\pi 2} = 11.8 \text{ pF}$$

$$R_{\pi 02} = r_{\pi 2} \parallel \left(\frac{1}{g_{m1}} + \frac{R_s}{\beta_1} \right)$$

$$= 2.6 \text{ k}\Omega \parallel \left(2.6 \text{ k}\Omega + \frac{100 \text{ k}\Omega}{100} \right)$$

$$= 2.6 \text{ k}\Omega \parallel 3.6 \text{ k}\Omega = 1.51 \text{ k}\Omega$$

$$\therefore C_{\pi 2} R_{\pi 02} = 17.8 \text{ ns}$$

$$R_{\mu 0} = R_{\pi 02} + R_L + g_{m2} R_L R_{\pi 02}$$

$$= 1.51 + 3 + \frac{3000}{26} \times 1.51$$

$$= 179 \text{ k}\Omega$$

$$\therefore C_{\mu 2} R_{\mu 02} = 0.4 \times 179 = 71 \text{ ns}$$

$$\therefore \sum T_o = 6 + 90 + 1972 + 18 + 71$$

$$= 2157 \text{ ns}$$

$$\therefore f_{-3\text{dB}} = \frac{1}{2\pi \sum T_o} = 73.8 \text{ kHz}$$

Common-collector - Common emitter

$$R_{C50} C_{C52} = 3 \text{ ns}$$

$$R_{C50} C_{C51} = 0$$

$$C_{\pi 1} R_{\pi 01} = 90.1 \text{ ns}$$

$$C_{\pi 2} R_{\pi 02} = 17.8 \text{ ns}$$

$$C_{\mu 2} R_{\mu 02} = 71 \text{ ns}$$

$$R_{\mu 01} = R_i \parallel R_s = 83.9 \text{ k}\Omega$$

$$\therefore C_{\mu 1} R_{\mu 01} = 0.4 \times 83.9 = 33.6 \text{ ns}$$


$$\therefore \sum T_o = 3 + 90.1 + 17.8 + 71 + 33.6$$

$$= 215.5 \text{ ns}$$

$$\therefore f_{-3\text{dB}} = \frac{1}{2\pi \sum T_o} = 738 \text{ kHz}$$

7.22

(a)

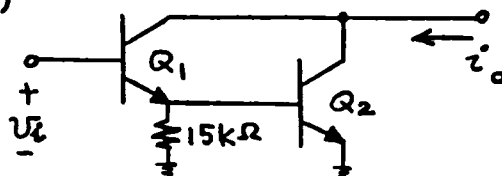

7-23

Effective value of $r_{\pi 2} = 15k \parallel 2.6k$

$$G_m = \frac{i_o}{v_i} \approx \frac{g_{m1} R_E}{g_{m1} R_E + 1} \times g_{m2}$$

$$R_E = 2.2k\Omega$$

$$\therefore G_m = \frac{\frac{0.05}{26} \times 2200}{1 + \frac{0.05}{26} \times 2200} \times \frac{1}{26}$$

= 31.2 mA/V — for both circuits

$$R_i = r_{\pi 1} (1 + g_{m1} R_E)$$

$$= \frac{100 \times 26}{0.05} \left(1 + \frac{0.05}{26} \times 2200 \right) = 274k\Omega$$

$$\therefore \frac{v_o}{v_i} = - \frac{R_i}{R_i + R_s} G_m R_L$$

$$= - \frac{274}{274 + 100} \times 31.2 \times 10^3 \times 3000$$

= -68.6 — for both circuits

(b) $I_{C1} = 50\mu A \therefore C_{b1} = 0.5pF$

$$C_{\pi 1} = 2.5pF$$

Darlington

$$R_{C50} = R_L = 3k\Omega$$

$$\therefore R_{C50} (C_{C51} + C_{C52}) = 3 \times 2 = 6ns$$

$$R_{\pi 01} = r_{\pi 1} \parallel \frac{R_s + R_E}{1 + g_{m1} R_E}$$

$$= 52k \parallel \frac{102.2k}{1 + 4.27} = 14.1k\Omega$$

$$\therefore C_{\pi 1} R_{\pi 01} = 2.5 \times 14.1 = 35.3ns$$

$$R_{\mu 01} = R_x + R_L + G_m R_x R_L$$

$$R_x = R_i \parallel R_s = 274 \parallel 100 = 73.3k\Omega$$

$$\therefore R_{\mu 01} = 73.3 + 3 + 31.2 \times 73.3 \times 3$$

$$= 6.94M\Omega$$

$$\therefore C_{\mu 1} R_{\mu 01} = 0.4 \times 6940 = 2776ns$$

$$R_{\pi 02} = r_{\pi 2} \parallel \left(\frac{1}{g_{m1}} + \frac{R_s}{\beta_1} \right)$$

$$= 2.6k \parallel \left(520 + \frac{100k}{100} \right)$$

$$= 2.6k \parallel 1.52k = 959\Omega$$

$$\therefore C_{\pi 2} R_{\pi 02} = 11.8 \times 0.959 = 11.3ns$$

$$R_{\mu 02} = R_{\pi 02} + R_L + g_{m2} R_L R_{\pi 02}$$

$$= 0.959 + 3 + \frac{3000}{26} \times 0.959$$

$$= 114.6k\Omega$$

$$\therefore C_{\mu 2} R_{\mu 02} = 0.4 \times 114.6 = 45.8ns$$

$$\therefore \Sigma T_o = 6 + 35.3 + 2776 + 11.3 + 45.8$$

$$= 2874ns$$

$$\therefore f_{-3dB} = \frac{1}{2\pi \Sigma T_o} = 55.4kHz$$

Common-collector - Common emitter

$$R_{C50} C_{C52} = 3ns$$

$$R_{C50} C_{C51} = 0$$

$$C_{\pi 1} R_{\pi 01} = 35.3ns$$

$$C_{\pi 2} R_{\pi 02} = 11.3ns$$

$$C_{\mu 2} R_{\mu 02} = 45.8ns$$

$$R_{\mu 01} = R_i \parallel R_s = 274 \parallel 100 = 73.3k\Omega$$

$$\therefore C_{\mu 1} R_{\mu 01} = 0.4 \times 73.3 = 29.3ns$$


$$\therefore \Sigma T_o = 3 + 35.3 + 11.3 + 45.8 + 29.3$$

$$= 124.7ns$$

$$\therefore f_{-3dB} = \frac{1}{2\pi \Sigma T_o} = 1.28MHz$$

7.23

(a)

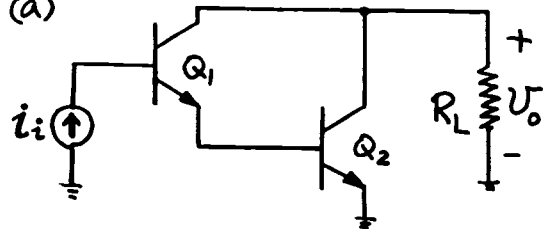

In both cases

$$\frac{v_o}{i_i} \approx -\beta_1 \beta_2 R_L = -100 \times 100 \times 3k = -30M\Omega$$


$$R_i = r_{\pi 1} (1 + g_{m1} r_{\pi 2}) = 520k\Omega$$

(b) Darlington


$$R_{C50} (C_{C51} + C_{C52}) = 6ns$$

7.27

Half-circuits (ac)

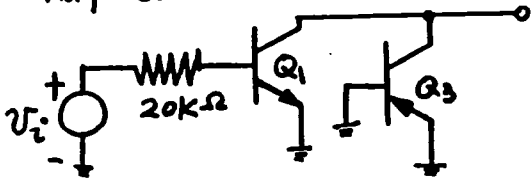

Equivalent

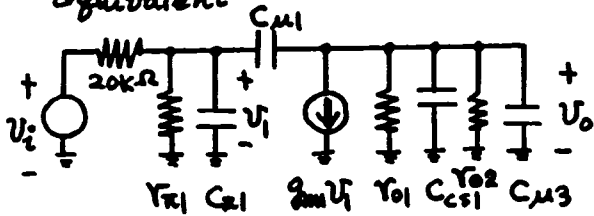

$$I_{C6} = \frac{9.4}{20} = 470 \mu\text{A}$$

$$I_{C5} = \frac{V_T}{R_E} \ln \frac{I_{C6}}{I_{C5}} = 2.6 \ln \frac{470}{I_{C5}} \mu\text{A}$$

$$= 10 \mu\text{A}$$

$$\therefore I_{C1} = I_{C3} = I_{C5}/2 = 5 \mu\text{A}$$

$$\frac{Q_1}{r_{o1}} = \frac{V_A}{I_{C1}} = \frac{120}{5} = 24 \text{ M}\Omega$$

$$r_{\pi 1} = \frac{\beta}{g_{m1}} = 200 \times \frac{26}{0.005} = 1.04 \text{ M}\Omega$$

$$C_{\mu 1} = \frac{0.7}{\sqrt{1 + \frac{5}{0.55}}} = 0.22 \text{ pF}$$

$$C_{cs1} = \frac{2}{\sqrt{1 + \frac{15}{0.55}}} = 0.38 \text{ pF}$$

$$C_{\pi 1} + C_{\mu 1} = \frac{f_m}{2\pi f_T} = \frac{1}{2\pi \times 26 \times 500 \times 10^6}$$

$$= 12.2 \text{ pF at } 1 \text{ mA}$$

$$\therefore C_{\pi 1} = 12 \text{ pF at } 1 \text{ mA}$$

$$C_{\mu 1} = 9 \text{ pF at } 1 \text{ mA}$$

$$\approx 0 \text{ at } 5 \mu\text{A}$$

$$\therefore C_{\pi 1} = 3 \text{ pF at } 5 \mu\text{A}$$

$$\frac{Q_3}{r_{o3}} = \frac{50}{5} = 10 \text{ M}\Omega$$

$$C_{\mu 3} = \frac{1}{\sqrt{1 + \frac{4.4}{0.55}}} = 0.33 \text{ pF}$$

$$\frac{v_o}{v_i} = - \frac{r_{\pi 1}}{r_{\pi 1} + R_S} g_{m1} r_o$$

$$r_o = r_{o1} \parallel r_{o3} = 24 \parallel 10 = 7.06 \text{ M}\Omega$$

$$\frac{v_o}{v_i} = - \frac{1.04}{1.06} \times \frac{0.005}{26} \times 7.06 \times 10^6$$

$$= -1332$$

$$R_{\pi o1} = r_{\pi 1} \parallel R_S = 1 \text{ M} \parallel 20 \text{ k} = 19.6 \text{ k}\Omega$$

$$\therefore C_{\pi 1} R_{\pi o1} = 3 \times 19.6 = 59 \text{ ns}$$

$$R_{\mu o1} = R_{\pi o1} + r_o + g_{m1} R_{\pi o1} r_o$$

$$R_{\mu o1} = 19.6 \text{ k} + 7.06 \text{ M} + \frac{0.005}{26} \times 19600 \times 7.06 \text{ M}$$

$$= 33.7 \text{ M}\Omega$$

$$\therefore C_{\mu 1} R_{\mu o1} = 0.22 \times 33.7 = 7.41 \mu\text{s}$$

$$(C_{cs1} + C_{\mu 3}) r_o = 0.71 \times 7.06 = 5.0 \mu\text{s}$$

$$\therefore \Sigma T_o = 0.06 + 7.41 + 5 = 12.47 \mu\text{s}$$

$$\therefore f_{-3dB} = \frac{1}{2\pi \Sigma T_o} = 12.8 \text{ kHz}$$

7-42

7-37 (a)

$$V_0 = 2.5 \text{ V dc}$$

$$V_{GS2} = 2.5 \text{ V}$$

$$\begin{aligned} V_{t2} &= V_{t0} + \gamma(\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f}) \\ &= 0.7 + 0.4(\sqrt{0.6 + 2.5} - \sqrt{0.6}) \\ &= 1.09 \text{ V} \end{aligned}$$


$$\begin{aligned} I_D &= \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right)_2 (V_{GS2} - V_{t2})^2 \\ &= \frac{60 \mu}{2} \frac{4}{1} (2.5 - 1.09)^2 \\ &= 237 \mu\text{A} \end{aligned}$$

$$\begin{aligned} \frac{V_0}{V_i} &= \frac{-g_{m1}}{g_{m2} + g_{mb2}} = \frac{-1.69 \text{ m}}{337 \mu + 38.3 \mu} \\ &= -4.5 \end{aligned}$$

$$\begin{aligned} g_{m1} &= \sqrt{2I_D \mu C_{ox} \frac{W}{L}} \\ &= \sqrt{2(237 \mu)(60 \mu)(100)} \\ &= 1.69 \text{ mA/V} \end{aligned}$$

$$\begin{aligned} g_{m2} &= \sqrt{2(237 \mu)(60 \mu)(4)} \\ &= 337 \mu\text{A/V} \end{aligned}$$
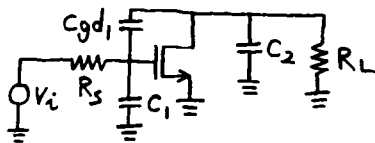
$$\begin{aligned} g_{mb2} &= \frac{g_{m2} \gamma}{2\sqrt{2\phi_f + V_{SB}}} = \frac{g_{m2} 0.4}{2\sqrt{0.6 + 2.5}} \\ &= 38.3 \mu\text{A/V} \end{aligned}$$



$$C_{ox} = 1.73 \frac{\text{fF}}{\mu^2}$$

$$\begin{aligned} C_{gs1} &= \frac{2}{3} WL C_{ox} + C_{ol} W \\ &= 115 \text{ fF} + 30 \text{ fF} = 145 \text{ fF} \end{aligned}$$

$$\begin{aligned} C_{gs2} &= \frac{2}{3} WL C_{ox} + C_{ol} W \\ &= 4.61 \text{ fF} + 1.2 \text{ fF} \\ &= 5.8 \text{ fF} \end{aligned}$$

$$C_{db1} = \frac{0.8(100)}{\sqrt{1 + \frac{2.5}{0.6}}} = 35.2 \text{ fF}$$

$$C_{gd1} = C_{ol} W = 30 \text{ fF}$$

$$C_{sb2} = \frac{0.8(4)}{\sqrt{1 + \frac{2.5}{0.6}}} = 1.41 \text{ fF}$$

$$C_1 = C_{gs1} = 145 \text{ fF}$$

$$\begin{aligned} C_2 &= C_{db1} + C_{sb2} + C_{gs2} + C_L \\ &= 142 \text{ fF} \end{aligned}$$

$$C_1 R_s = 145 \text{ ps}$$

$$\begin{aligned} C_2 R_L &= 142 \text{ fF}(2665 \Omega) \\ &= 378 \text{ ps} \end{aligned}$$

$$\begin{aligned} C_{gd1}(R_s + R_L + g_m R_s R_L) \\ &= 30(1\text{k} + 2665 + 1.69\text{m}(1\text{k})(2665)) \text{ f} \\ &= 245 \text{ ps} \end{aligned}$$

$$\begin{aligned} f_{-3\text{dB}} &= \frac{1}{2\pi} \frac{10^{12}}{145 + 378 + 245} \\ &= 207 \text{ MHz} \end{aligned}$$

(b)

$$R_{sx} = \frac{1}{E_c \mu C_{ox} W}$$

$$\begin{aligned} m_1 R_{sx} &= \frac{1}{1.5\text{M} \cdot 60 \mu \cdot 100 \mu} \\ &= 111 \Omega \end{aligned}$$

7-43

$$m_2 R_{sx} = \frac{1}{1.5M \cdot 60\mu \cdot 4\mu}$$

$$= 2.78 \text{ k}$$

$$R_L' = R_{sx2} + \frac{1}{g_{m2} + g_{mb2}}$$

$$= 2.78 \text{ k} + 2.66 \text{ k}$$

$$= 5.44 \text{ k}$$

$$g_{m1}' = \frac{g_{m1}}{1 + g_{m1} R_{sx1}}$$

$$= 1.42 \text{ mA/V}$$

$$\frac{V_o}{V_i} = -g_{m1}' R_L' = -7.74$$

$$C_1 R_s = 145 \text{ ps unchanged}$$

$$C_2 R_L' = C_2 R_L \frac{R_L'}{R_L}$$

$$= 378 \text{ ps (2.04)}$$

$$= 772 \text{ ps}$$

$$C_{gd1} (R_s + R_L' + g_{m1}' R_L' R_s)$$

$$= 30 \text{ f} (1 \text{ k} + 5.44 \text{ k} + 1.42 \text{ m} (5.44 \text{ k}) (1 \text{ k}))$$

$$= 425 \text{ ps}$$

$$f_{-3\text{dB}} = \frac{1}{2\pi} \frac{10^{12}}{145 + 772 + 425}$$

$$= 119 \text{ MHz}$$

```

NMOS AMP
VDD 1 0 5V
M2 1 1 2 0 NMOS2 W=4U L=1U
M1 2 3 0 0 NMOS W=100U L=1U
CLOAD 2 0 100PF
RS 4 3 1K
VI 4 0 0.981V AC
.PLOT AC VDB(2)
.PLOT AC VP(2)
.AC DEC 15 1MEG 2GIG
.MODEL NMOS NMOS KP=60U VTO=0.7 LAMBDA=0 LD=0 GAMMA=0.4
+ TOX=20NM CGSO=300PF CGDO=300PF CBD=80PF CBS=80PF
.MODEL NMOS2 NMOS KP=60U VTO=0.7 LAMBDA=0 LD=0 GAMMA=0.4
+ TOX=20NM CGSO=300PF CGDO=300PF CBD=3.2PF CBS=3.2PF
.OPTIONS NOPAGE NOMOD
.WIDTH OUT=80
.OPTIONS SPICE
.OP
.END

```

```

***** OPERATING POINT INFORMATION      TNOM= 27.000 TEMP= 27.000
+0:1      = 5.000E+00 0:2      = 2.500E+00 0:3      = 9.810E-01
+0:4      = 9.810E-01

```

```

**** MOSFETS
ELEMENT 0:M2      0:M1
MODEL   0:NMOS2  0:NMOS
ID      2.369E-04 2.369E-04
IBS     -2.501E-14 0.
IBD     -5.000E-14 -2.501E-14
VGS     2.499E+00 9.810E-01
VDS     2.499E+00 2.500E+00
VBS     -2.500E+00 0.
VTH     1.094E+00 7.000E-01
VDSAT   1.405E+00 2.810E-01
BETA    2.400E-04 6.000E-03
GAM KFF 4.000E-01 4.000E-01
GM      3.372E-04 1.686E-03
GMB     3.830E-05 4.353E-04
CITOT   2.411E-15 6.996E-14
CGTOT   7.037E-15 1.780E-13
CSTOT   7.380E-15 2.251E-13
CBTOT   2.774E-15 1.217E-13
CGS     5.804E-15 1.451E-13
CGD     1.223E-15 3.058E-14

```

```

***** AC ANALYSIS      TNOM= 27.000 TEMP= 27.000

```

FREQ	VDB(2)	VP(2)
(A)	-2.000E+01	-1.000E+01
	0.	1.000E+01
		2.000E+01
1.000E+06	1.30E+01	A
1.165E+06	1.30E+01	A
1.359E+06	1.30E+01	A
1.584E+06	1.30E+01	A
1.847E+06	1.30E+01	A
2.154E+06	1.30E+01	A
2.511E+06	1.30E+01	A
2.928E+06	1.30E+01	A
3.414E+06	1.30E+01	A
3.981E+06	1.30E+01	A
4.641E+06	1.30E+01	A
5.411E+06	1.30E+01	A
6.309E+06	1.30E+01	A
7.356E+06	1.30E+01	A
8.577E+06	1.30E+01	A
1.000E+07	1.30E+01	A
1.165E+07	1.30E+01	A
1.359E+07	1.30E+01	A
1.584E+07	1.30E+01	A
1.847E+07	1.30E+01	A
2.154E+07	1.30E+01	A
2.511E+07	1.30E+01	A
2.928E+07	1.29E+01	A
3.414E+07	1.29E+01	A
3.981E+07	1.29E+01	A
4.641E+07	1.29E+01	A
5.411E+07	1.28E+01	A
6.309E+07	1.27E+01	A
7.356E+07	1.26E+01	A
8.577E+07	1.25E+01	A
1.000E+08	1.23E+01	A
1.165E+08	1.20E+01	A
1.359E+08	1.17E+01	A
1.584E+08	1.14E+01	A
1.847E+08	1.09E+01	A
2.154E+08	1.03E+01	A
2.511E+08	9.66E+00	A
2.928E+08	8.86E+00	A
3.414E+08	7.93E+00	A
3.981E+08	6.90E+00	A
4.641E+08	5.75E+00	A
5.411E+08	4.50E+00	A
6.309E+08	3.14E+00	A
7.356E+08	1.67E+00	A
8.577E+08	9.97E-02	A
1.000E+09	-1.58E+00	A
1.165E+09	-3.38E+00	A
1.359E+09	-5.28E+00	A
1.584E+09	-7.30E+00	A
1.847E+09	-9.40E+00	A
2.154E+09	-1.15E+01	A

FREQ	VP(2)	5.000E+01	1.000E+02	1.500E+02	2.000E+02
(A)	0.				
1.000E+06	1.79E+02				A
1.165E+06	1.79E+02				A
1.359E+06	1.79E+02				A
1.584E+06	1.79E+02				A
1.847E+06	1.79E+02				A
2.154E+06	1.79E+02				A
2.511E+06	1.79E+02				A
2.928E+06	1.79E+02				A
3.414E+06	1.79E+02				A
3.981E+06	1.78E+02				A
4.641E+06	1.78E+02				A
5.411E+06	1.78E+02				A
6.309E+06	1.78E+02				A
7.356E+06	1.77E+02				A
8.577E+06	1.77E+02				A
1.000E+07	1.77E+02				A
1.165E+07	1.76E+02				A
1.359E+07	1.76E+02				A
1.584E+07	1.75E+02				A
1.847E+07	1.74E+02				A
2.154E+07	1.73E+02				A
2.511E+07	1.72E+02				A
2.928E+07	1.71E+02				A
3.414E+07	1.70E+02				A
3.981E+07	1.68E+02				A
4.641E+07	1.66E+02				A
5.411E+07	1.64E+02				A
6.309E+07	1.62E+02				A
7.356E+07	1.59E+02				A
8.577E+07	1.55E+02				A
1.000E+08	1.52E+02				A
1.165E+08	1.48E+02				A
1.359E+08	1.43E+02				A
1.584E+08	1.38E+02				A
1.847E+08	1.33E+02				A
2.154E+08	1.27E+02				A
2.511E+08	1.21E+02				A
2.928E+08	1.14E+02				A
3.414E+08	1.08E+02				A
3.981E+08	1.01E+02				A
4.641E+08	9.45E+01				A
5.411E+08	8.76E+01				A
6.309E+08	8.07E+01				A
7.356E+08	7.36E+01				A
8.577E+08	6.65E+01				A
1.000E+09	5.93E+01				A
1.165E+09	5.20E+01				A
1.359E+09	4.48E+01				A
1.584E+09	3.76E+01				A
1.847E+09	3.05E+01				A
2.154E+09	2.35E+01				A

7-45

```

NMOS AMP, EXAMINE SMALL SIGNAL BANDWIDTH AS DC VIN VARIES
VDD 1 0 5V
M2 1 1 2 0 NMOS2 W=4U L=1U
M1 2 3 0 0 NMOS W=100U L=1U
CLOAD 2 0 100FF
RS 4 3 1K
VI 4 0 0.5V AC
.PLOT AC VDB(2)
.PLOT AC VP(2)
.AC DEC 15 1MEG 2GIG
.MODEL NMOS NMOS KP=60U VTO=0.7 LAMBDA=0 LD=0 GAMMA=0.4
+ TOX=20NM CGSO=300PF CGDO=300PF CRD=80FF CBS=80FF
.MODEL NMOS2 NMOS KP=60U VTO=0.7 LAMBDA=0 LD=0 GAMMA=0.4
+ TOX=20NM CGSO=300PF CGDO=300PF CRD=3.2FF CBS=3.2FF
.OPTIONS NOPAGE NOMOD
.WIDTH OUT=80
.OPTIONS SPICE
.OP
.END

```

***** AC ANALYSIS

TNOM= 27.000 TEMP= 27.000

FREQ	VDB(2)				
(A)	-2.000E+01	-1.800E+01	-1.600E+01	-1.400E+01	-1.200E+01
3.981E+07	-1.50E+01	+	+	+	+
4.641E+07	-1.50E+01	+	+	A+	+
5.411E+07	-1.50E+01	+	+	A+	+
6.309E+07	-1.50E+01	+	+	A+	+
7.356E+07	-1.50E+01	+	+	A+	+
8.577E+07	-1.50E+01	+	+	A+	+
1.000E+08	-1.51E+01	-----	-----	A-	-----
1.165E+08	-1.51E+01	+	+	A+	+
1.359E+08	-1.51E+01	+	+	A+	+
1.584E+08	-1.51E+01	+	+	A+	+
1.847E+08	-1.51E+01	+	+	A+	+
2.154E+08	-1.51E+01	+	+	A+	+
2.511E+08	-1.52E+01	+	+	A+	+
2.928E+08	-1.52E+01	+	+	A+	+
3.414E+08	-1.52E+01	+	+	A+	+
3.981E+08	-1.53E+01	+	+	A+	+
4.641E+08	-1.54E+01	-----	-----	A-	-----
5.411E+08	-1.56E+01	+	+	A+	+
6.309E+08	-1.57E+01	+	+	A+	+
7.356E+08	-1.60E+01	+	+	A+	+
8.577E+08	-1.62E+01	+	+	A+	+
1.000E+09	-1.66E+01	+	+	A+	+
1.165E+09	-1.71E+01	+	A+	+	+

```

NMOS AMP
VDD 1 0 5V
M2 1 1 2 0 NMOS2 W=4U L=1U
M1 2 3 0 0 NMOS W=100U L=1U
CLOAD 2 0 100FF
RS 4 3 1K
VI 4 0 1.5V AC
.PLOT AC VDB(2)
.PLOT AC VP(2)
.AC DEC 15 1MEG 2GIG
.MODEL NMOS NMOS KP=60U VTO=0.7 LAMBDA=0 LD=0 GAMMA=0.4
+ TOX=20NM CGSO=300PF CGDO=300PF CRD=80FF CBS=80FF
.MODEL NMOS2 NMOS KP=60U VTO=0.7 LAMBDA=0 LD=0 GAMMA=0.4
+ TOX=20NM CGSO=300PF CGDO=300PF CRD=3.2FF CBS=3.2FF
.OPTIONS NOPAGE NOMOD
.WIDTH OUT=80
.OPTIONS SPICE
.OP
.END

```

***** AC ANALYSIS

TNOM= 27.000 TEMP= 27.000

FREQ	VDB(2)				
(A)	-1.500E+01	-1.000E+01	-5.000E+00	0.	5.000E+00
2.928E+06	2.29E-01	+	+	+	+
3.414E+06	2.29E-01	+	+	+	+
3.981E+06	2.29E-01	+	+	+	+
4.641E+06	2.28E-01	-----	-----	A-	-----
5.411E+06	2.28E-01	+	+	+	+
6.309E+06	2.28E-01	+	+	+	+
7.356E+06	2.28E-01	+	+	+	+
8.577E+06	2.27E-01	+	+	+	+
1.000E+07	2.27E-01	+	+	+	+
1.165E+07	2.26E-01	+	+	+	+
1.359E+07	2.25E-01	+	+	+	+
1.584E+07	2.24E-01	+	+	+	+
1.847E+07	2.22E-01	+	+	+	+
2.154E+07	2.19E-01	-----	-----	A-	-----
2.511E+07	2.16E-01	+	+	+	+
2.928E+07	2.11E-01	+	+	+	+
3.414E+07	2.04E-01	+	+	+	+
3.981E+07	1.96E-01	+	+	+	+
4.641E+07	1.84E-01	+	+	+	+
5.411E+07	1.68E-01	+	+	+	+
6.309E+07	1.46E-01	+	+	+	+
7.356E+07	1.16E-01	+	+	+	+
8.577E+07	7.64E-02	+	+	+	+
1.000E+08	2.29E-02	-----	-----	A-	-----
1.165E+08	-4.89E-02	+	+	+	+
1.359E+08	-1.45E-01	+	+	+	+
1.584E+08	-2.72E-01	+	+	+	+
1.847E+08	-4.39E-01	+	+	+	+
2.154E+08	-6.56E-01	+	+	+	+
2.511E+08	-9.36E-01	+	+	+	+
2.928E+08	-1.29E+00	+	+	+	+
3.414E+08	-1.73E+00	+	+	+	+
3.981E+08	-2.26E+00	+	+	+	+
4.641E+08	-2.91E+00	-----	-----	A-	-----

```

NMOS AMP
VDD 1 0 5V
M2 1 1 2 0 NMOS2 W=4U L=1U
M1 2 3 0 0 NMOS W=100U L=1U
CLOAD 2 0 100FF
RS 4 3 1K
VI 4 0 2V AC
.PLOT AC VDB(2)
.PLOT AC VP(2)
.AC DEC 15 1MEG 2GIG
.MODEL NMOS NMOS KP=60U VTO=0.7 LAMBDA=0 LD=0 GAMMA=0.4
+ TOX=20NM CGSO=300FF CGDO=300FF CBD=80FF CBS=80FF
.MODEL NMOS2 NMOS KP=60U VTO=0.7 LAMBDA=0 LD=0 GAMMA=0.4
+ TOX=20NM CGSO=300FF CGDO=300FF CBD=3.2FF CBS=3.2FF
.OPTIONS NOPAGE NOMOD
.WIDTH OUT=80
.OPTIONS SPICE
.OP
.END
    
```

***** AC ANALYSIS TRON= 27.000 TEMP= 27.000

FREQ	VDB(2)					
(A)		-2.500E+01	-2.000E+01	-1.500E+01	-1.000E+01	-5.000E+00
2.511E+07	-1.31E+01	+	+	+	A	+
2.928E+07	-1.31E+01	+	+	+	A	+
3.414E+07	-1.31E+01	+	+	+	A	+
3.981E+07	-1.31E+01	+	+	+	A	+
4.641E+07	-1.31E+01	+	+	+	A	+
5.411E+07	-1.31E+01	+	+	+	A	+
6.309E+07	-1.31E+01	+	+	+	A	+
7.356E+07	-1.31E+01	+	+	+	A	+
8.577E+07	-1.32E+01	+	+	+	A	+
1.000E+08	-1.32E+01	+	+	+	A	+
1.165E+08	-1.32E+01	+	+	+	A	+
1.359E+08	-1.33E+01	+	+	+	A	+
1.584E+08	-1.34E+01	+	+	+	A	+
1.847E+08	-1.34E+01	+	+	+	A	+
2.154E+08	-1.36E+01	+	+	+	A	+
2.511E+08	-1.37E+01	+	+	+	A	+
2.928E+08	-1.40E+01	+	+	+	A	+
3.414E+08	-1.42E+01	+	+	+	A	+
3.981E+08	-1.46E+01	+	+	+	A	+
4.641E+08	-1.50E+01	+	+	+	A	+
5.411E+08	-1.55E+01	+	+	+	A	+
6.309E+08	-1.61E+01	+	+	+	A	+
7.356E+08	-1.68E+01	+	+	+	A	+

```

NMOS AMP
VDD 1 0 5V
M2 1 1 2 0 NMOS2 W=4U L=1U
M1 2 3 0 0 NMOS W=100U L=1U
CLOAD 2 0 100FF
RS 4 3 1K
VI 4 0 3V AC
.PLOT AC VDB(2)
.PLOT AC VP(2)
.AC DEC 15 1MEG 2GIG
.MODEL NMOS NMOS KP=60U VTO=0.7 LAMBDA=0 LD=0 GAMMA=0.4
+ TOX=20NM CGSO=300FF CGDO=300FF CBD=80FF CBS=80FF
.MODEL NMOS2 NMOS KP=60U VTO=0.7 LAMBDA=0 LD=0 GAMMA=0.4
+ TOX=20NM CGSO=300FF CGDO=300FF CBD=3.2FF CBS=3.2FF
.OPTIONS NOPAGE NOMOD
.WIDTH OUT=80
.OPTIONS SPICE
.OP
.END
    
```

***** AC ANALYSIS TRON= 27.000 TEMP= 27.000

FREQ	VDB(2)					
(A)		-3.000E+01	-2.800E+01	-2.600E+01	-2.400E+01	-2.200E+01
4.641E+07	-2.38E+01	+	+	+	+	A
5.411E+07	-2.38E+01	+	+	+	+	A
6.309E+07	-2.38E+01	+	+	+	+	A
7.356E+07	-2.38E+01	+	+	+	+	A
8.577E+07	-2.38E+01	+	+	+	+	A
1.000E+08	-2.38E+01	+	+	+	+	A
1.165E+08	-2.38E+01	+	+	+	+	A
1.359E+08	-2.39E+01	+	+	+	+	A
1.584E+08	-2.39E+01	+	+	+	+	A
1.847E+08	-2.40E+01	+	+	+	+	A
2.154E+08	-2.41E+01	+	+	+	+	A
2.511E+08	-2.42E+01	+	+	+	+	A
2.928E+08	-2.43E+01	+	+	+	+	A
3.414E+08	-2.45E+01	+	+	+	+	A
3.981E+08	-2.47E+01	+	+	+	+	A
4.641E+08	-2.50E+01	+	+	+	+	A
5.411E+08	-2.53E+01	+	+	+	+	A
6.309E+08	-2.57E+01	+	+	+	+	A
7.356E+08	-2.61E+01	+	+	+	+	A
8.577E+08	-2.65E+01	+	+	+	+	A
1.000E+09	-2.70E+01	+	+	+	+	A

7-47

```

NMOS AMP
VDD 1 0 5V
M2 1 1 2 0 NMOS2 W=4U L=1U
M1 2 3 0 0 NMOS W=100U L=1U
CLOAD 2 0 100PF
RS 4 3 1K
VI 4 0 4V AC
.PLOT AC VDB(2)
.PLOT AC VP(2)
.AC DEC 15 1MEG 2GIG
.MODEL NMOS NMOS KP=60U VTO=0.7 LAMBDA=0 LD=0 GAMMA=0.4
+ TOX=20NM CGSO=300PF CGDO=300PF CBD=80FF CBS=80FF
.MODEL NMOS2 NMOS KP=60U VTO=0.7 LAMBDA=0 LD=0 GAMMA=0.4
+ TOX=20NM CGSO=300PF CGDO=300PF CBD=3.2FF CBS=3.2FF
.OPTIONS NOPAGE NOMOD
.WIDTH OUT=80
.OPTIONS SPICE
.OP
.END

```

***** AC ANALYSIS THOM= 27.000 TEMP= 27.000

FREQ	VDB(2)				
1A		-3.800E+01	-3.600E+01	-3.400E+01	-3.200E+01
4.641E+07	-3.00E+01	+	+	+	+
5.411E+07	-3.00E+01	+	+	+	+
6.309E+07	-3.00E+01	+	+	+	+
7.356E+07	-3.00E+01	+	+	+	+
8.577E+07	-3.00E+01	+	+	+	+
1.000E+08	-3.00E+01	+	+	+	+
1.165E+08	-3.01E+01	+	+	+	+
1.359E+08	-3.01E+01	+	+	+	+
1.584E+08	-3.01E+01	+	+	+	+
1.847E+08	-3.01E+01	+	+	+	+
2.154E+08	-3.02E+01	+	+	+	+
2.511E+08	-3.02E+01	+	+	+	+
2.928E+08	-3.03E+01	+	+	+	+
3.414E+08	-3.04E+01	+	+	+	+
3.981E+08	-3.05E+01	+	+	+	+
4.641E+08	-3.07E+01	+	+	+	+
5.411E+08	-3.08E+01	+	+	+	+
6.309E+08	-3.10E+01	+	+	+	+
7.356E+08	-3.12E+01	+	+	+	+
8.577E+08	-3.14E+01	+	+	+	+
1.000E+09	-3.16E+01	+	+	+	+
1.165E+09	-3.18E+01	+	+	+	+
1.359E+09	-3.19E+01	+	+	+	+
1.584E+09	-3.21E+01	+	+	+	+
1.847E+09	-3.22E+01	+	+	+	+
2.154E+09	-3.23E+01	+	+	+	+
2.511E+09	-3.24E+01	+	+	+	+
2.928E+09	-3.25E+01	+	+	+	+
3.414E+09	-3.26E+01	+	+	+	+
3.981E+09	-3.28E+01	+	+	+	+
4.641E+09	-3.29E+01	+	+	+	+
5.411E+09	-3.31E+01	+	+	+	+
6.309E+09	-3.33E+01	+	+	+	+
7.356E+09	-3.35E+01	+	+	+	+

```

NMOS AMP
VDD 1 0 5V
M2 1 1 2 0 NMOS2 W=4U L=1U
M1 2 3 0 0 NMOS W=100U L=1U
CLOAD 2 0 100PF
RS 4 3 1K
VI 4 0 5V AC
.PLOT AC VDB(2)
.PLOT AC VP(2)
.AC DEC 15 1MEG 2GIG
.MODEL NMOS NMOS KP=60U VTO=0.7 LAMBDA=0 LD=0 GAMMA=0.4
+ TOX=20NM CGSO=300PF CGDO=300PF CBD=80FF CBS=80FF
.MODEL NMOS2 NMOS KP=60U VTO=0.7 LAMBDA=0 LD=0 GAMMA=0.4
+ TOX=20NM CGSO=300PF CGDO=300PF CBD=3.2FF CBS=3.2FF
.OPTIONS NOPAGE NOMOD
.WIDTH OUT=80
.OPTIONS SPICE
.OP
.END

```

***** AC ANALYSIS THOM= 27.000 TEMP= 27.000

FREQ	VDB(2)				
A		-6.000E+01	-5.000E+01	-4.000E+01	-3.000E+01
3.414E+08	-3.46E+01	+	+	+	+
3.981E+08	-3.46E+01	+	+	+	+
4.641E+08	-3.46E+01	+	+	+	+
5.411E+08	-3.46E+01	+	+	+	+
6.309E+08	-3.46E+01	+	+	+	+
7.356E+08	-3.46E+01	+	+	+	+
8.577E+08	-3.46E+01	+	+	+	+
1.000E+09	-3.46E+01	+	+	+	+
1.165E+09	-3.47E+01	+	+	+	+
1.359E+09	-3.47E+01	+	+	+	+
1.584E+09	-3.47E+01	+	+	+	+
1.847E+09	-3.47E+01	+	+	+	+
2.154E+09	-3.47E+01	+	+	+	+
2.511E+09	-3.47E+01	+	+	+	+
2.928E+09	-3.48E+01	+	+	+	+
3.414E+09	-3.48E+01	+	+	+	+
3.981E+09	-3.49E+01	+	+	+	+
4.641E+09	-3.50E+01	+	+	+	+
5.411E+09	-3.51E+01	+	+	+	+
6.309E+09	-3.52E+01	+	+	+	+
7.356E+09	-3.54E+01	+	+	+	+
8.577E+09	-3.56E+01	+	+	+	+
1.000E+10	-3.59E+01	+	+	+	+
1.165E+10	-3.62E+01	+	+	+	+
1.359E+10	-3.67E+01	+	+	+	+
1.584E+10	-3.72E+01	+	+	+	+
1.847E+10	-3.79E+01	+	+	+	+
2.154E+10	-3.86E+01	+	+	+	+
2.511E+10	-3.95E+01	+	+	+	+