

LECTURE 290 – FEEDBACK CIRCUIT ANALYSIS USING RETURN RATIO

(READING: GHLM – 599-613)

Objective

The objective of this presentation is:

- 1.) Illustrate the method of using return ratio to analyze feedback circuits
- 2.) Demonstrate using examples

Outline

- Concept of return ratio
- Closed-loop gain using return ratio
- Closed-loop impedance using return ratio
- Summary

Concept of Return Ratio

Instead of using two-port analysis, return ratio takes advantage of signal flow graph theory.

The return ratio for a dependent source in a feedback loop is found as follows:

- 1.) Set all independent sources to zero.
- 2.) Change the dependent source to an independent source and define the controlling variable as, s_r , and the source variable as s_t .
- 3.) Calculate the return ratio designated as $RR = -s_r/s_t$.


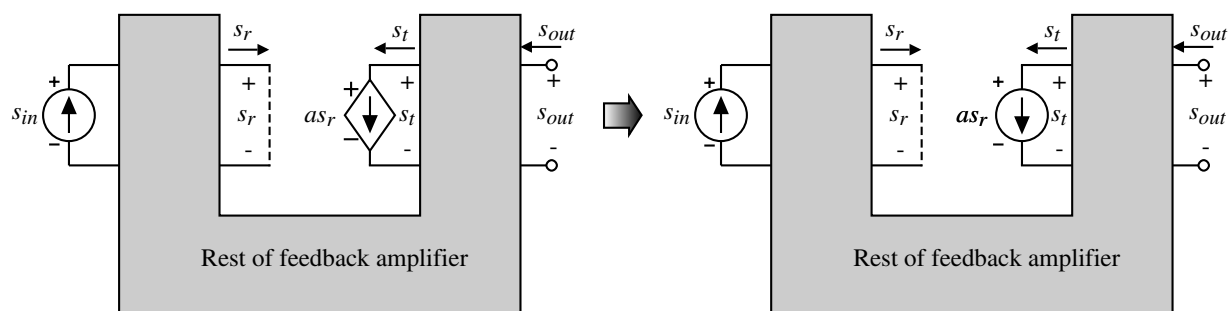


Fig. 290-01

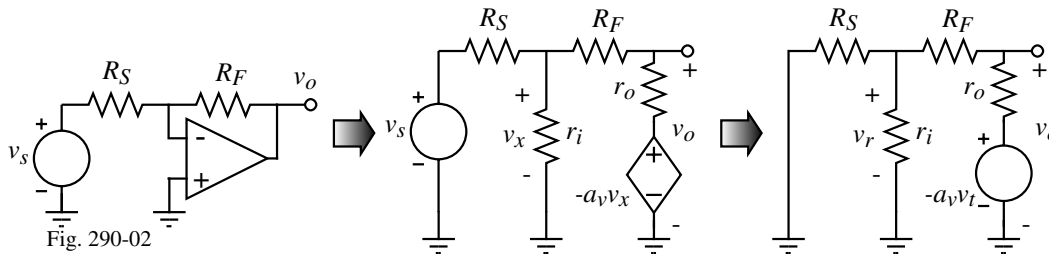Example 1 – Calculation of Return Ratio

Find the return ratio of the op amp with feedback shown if the input resistance of the op amp is r_i , the output resistance is r_o , and the voltage gain is a_v .



Solution

$$v_r = \frac{(-a_v v_t) R_S \parallel r_i}{r_o + R_F + R_S \parallel r_i} \quad \rightarrow \quad RR = -\frac{v_r}{v_t} = \frac{(a_v) R_S \parallel r_i}{r_o + R_F + R_S \parallel r_i}$$

Closed-Loop Gain Using Return Ratio

Consider the following general feedback amplifier:

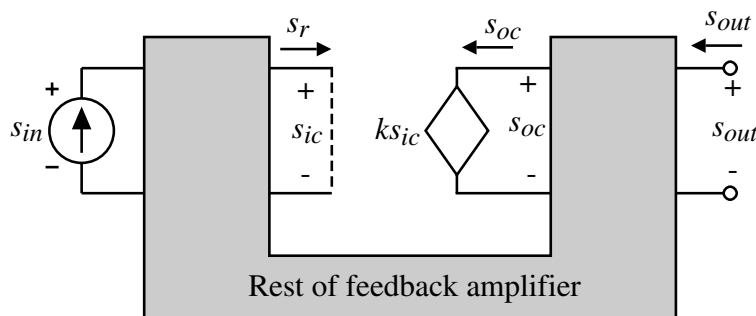


Fig. 290-03

Note that $s_{oc} = k s_{ic}$.

Assume the amplifier is linear and express s_{ic} and s_{out} as linear functions of the two sources, s_{in} and s_{oc} .

$$s_{ic} = B_1 s_{in} - H s_{oc}$$

$$s_{out} = d s_{in} + B_2 s_{oc}$$

where B_1 , B_2 , and H are defined as

$$B_1 = \left. \frac{s_{ic}}{s_{in}} \right|_{s_{oc}=0} = \left. \frac{s_{ic}}{s_{in}} \right|_{k=0}, \quad B_2 = \left. \frac{s_{out}}{s_{oc}} \right|_{s_{in}=0}, \quad \text{and} \quad H = - \left. \frac{s_{ic}}{s_{oc}} \right|_{s_{in}=0}$$

Closed-Loop Gain Using Return Ratio – Continued

Interpretation:

B_1 is the transfer function from the input to the controlling signal with $k = 0$.

B_2 is the transfer function from the controlling signal to the output with $s_{in} = 0$.

H is the transfer function from the output of the dependent source to the controlling signal with $s_{in} = 0$ and multiplied times a -1 .

d is defined as,

$$d = \left. \frac{s_{out}}{s_{in}} \right|_{s_{oc}=0} = \left. \frac{s_{out}}{s_{in}} \right|_{k=0}$$

d is the direct signal feedthrough when the controlled source in A is set to zero ($k=0$)

Closed-loop gain (s_{out}/s_{in}) can be found as,

$$s_{ic} = B_1 s_{in} - H s_{oc} = B_1 s_{in} - kH s_{ic} \quad \rightarrow \quad \frac{s_{ic}}{s_{in}} = \frac{B_1}{1 + kH}$$

$$s_{out} = d s_{in} + B_2 s_{oc} = d s_{in} + kB_2 s_{ic} = d s_{in} + \frac{B_1 kB_2}{1 + kH} s_{in}$$

$$2.) \quad A = \frac{s_{out}}{s_{in}} = \frac{B_1 kB_2}{1 + kH} + d = \frac{B_1 kB_2}{1 + RR} + d = \frac{g}{1 + RR} + d$$

where $RR = kH$ and $g = B_1 kB_2$ (gain from s_{in} to s_{out} if $H = 0$ and $d = 0$)

Closed-Loop Gain Using Return Ratio – Continued

Further simplification:

$$A = \frac{g}{1 + RR} + d = \frac{g + d(1 + RR)}{1 + RR} = \frac{g + d \cdot RR}{1 + RR} + \frac{d}{1 + RR} = \frac{\left(\frac{g}{RR} + d\right)RR}{1 + RR} + \frac{d}{1 + RR}$$

Define

$$A_\infty = \frac{g}{RR} + d$$

$$3.) \quad A = A_\infty \frac{RR}{1 + RR} + \frac{d}{1 + RR}$$

Note that as $RR \rightarrow \infty$, that $A = A_\infty$.

A_∞ is the closed-loop gain when the feedback circuit is ideal (i.e., $RR \rightarrow \infty$ or $k \rightarrow \infty$).

Block diagram of the new formulation:

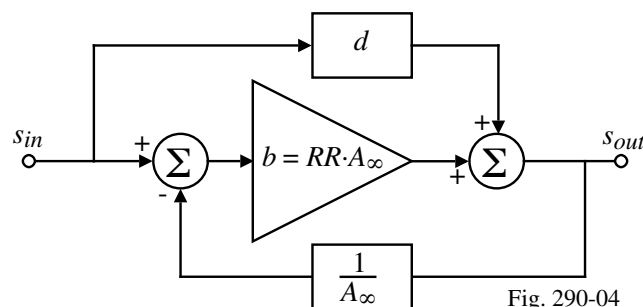


Fig. 290-04



Note that $b = RR \cdot A_\infty$ is called the effective gain of the feedback amplifier.

Example 2 – Use of Return Ratio Approach to Calculate the Closed-Loop Gain

Find the closed-loop gain and the effective gain of the transistor feedback amplifier shown using the previous formulas. Assume that the BJT $g_m = 40\text{mS}$, $r_\pi = 5\text{k}\Omega$, and $r_o = 1\text{M}\Omega$.

Solution

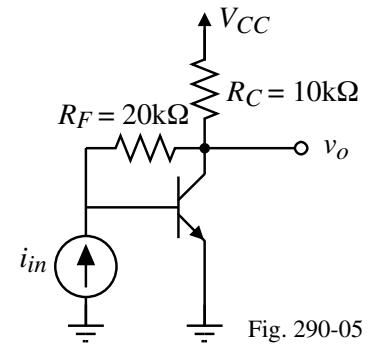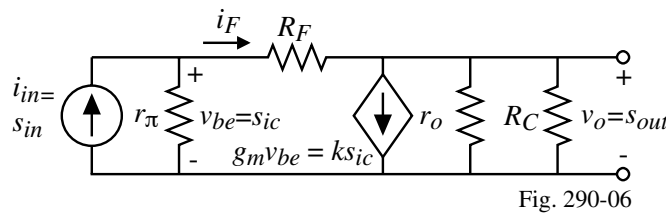The small-signal model suitable for calculating A_∞ and d is shown.



$$A_\infty = \left. \frac{s_{out}}{s_{in}} \right|_{k=\infty} = \left. \frac{v_o}{i_{in}} \right|_{g_m=\infty} = ? \quad \text{Remember that } A = \frac{a}{1+af} \rightarrow \frac{1}{f} \text{ as } a \rightarrow \infty.$$


$$f = \left. \frac{v_o}{i_F} \right|_{v_{in}=0} = \frac{-1}{R_F} \quad \text{Therefore, } A_\infty = -R_F = -20\text{k}\Omega$$

$$d = \left. \frac{s_{out}}{s_{in}} \right|_{k=0} = \left. \frac{v_o}{i_{in}} \right|_{g_m=0} = \frac{r_\pi}{r_\pi + R_F + (r_o \parallel R_C)} (r_o \parallel R_C)$$

$$= \frac{5\text{k}\Omega}{5\text{k}\Omega + 20\text{k}\Omega + 1\text{M}\Omega \parallel 10\text{k}\Omega} (1\text{M}\Omega \parallel 10\text{k}\Omega) = 1.42\text{k}\Omega$$

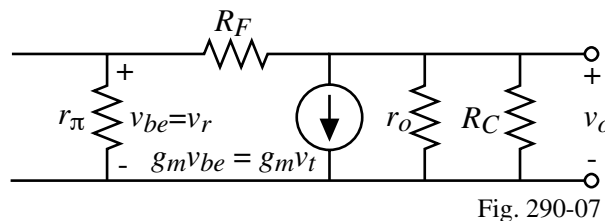Example 2 – Continued

What is left is to calculate the RR . A small-signal model for this is shown below.



$$v_r = (-g_m v_t) \left(\frac{r_o \parallel R_C}{r_\pi + R_F + r_o \parallel R_C} \right) r_\pi \quad \rightarrow \quad \frac{v_r}{v_t} = (-g_m r_\pi) \left(\frac{r_o \parallel R_C}{r_\pi + R_F + r_o \parallel R_C} \right)$$

$$RR = -\frac{v_r}{v_t} = (g_m r_\pi) \left(\frac{r_o \parallel R_C}{r_\pi + R_F + r_o \parallel R_C} \right) = (200) \left(\frac{1\text{M}\Omega \parallel 10\text{k}\Omega}{5\text{k}\Omega + 20\text{k}\Omega + 1\text{M}\Omega \parallel 10\text{k}\Omega} \right) = 56.74$$

Now, the closed loop gain is found to be,

$$A = A_\infty \frac{RR}{1+RR} + \frac{d}{1+RR} = (-20\text{k}\Omega) \left(\frac{56.74}{1+56.74} \right) + \left(\frac{1.4\text{k}\Omega}{1+56.74} \right) = -19.63\text{k}\Omega$$

The effective gain is given as,

$$b = RR \cdot A_\infty = 56.74(-20\text{k}\Omega) = -1135\text{k}\Omega$$

Closed-Loop Impedance Formula using the Return Ratio (Blackman's Formula)

Consider the following linear feedback circuit where the impedance at port X is to be calculated.

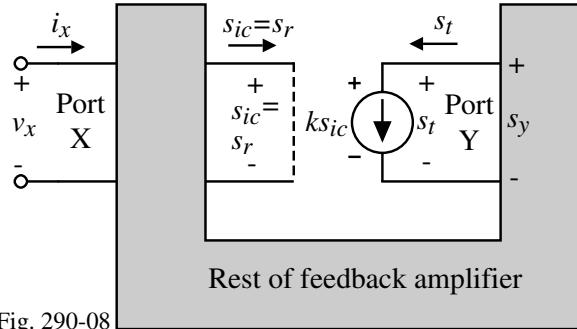


Fig. 290-08

Expressing the signals, v_x and s_{ic} as linear functions of the signals i_x and s_y gives,

$$v_x = a_1 i_x + a_2 s_y$$

$$s_{ic} = a_3 i_x + a_4 s_y$$

The impedance looking into port X when $k = 0$ is,

$$Z_{port}(k=0) = \left. \frac{v_x}{i_x} \right|_{k=0} = \left. \frac{v_x}{i_x} \right|_{s_y=0}$$

Closed-Loop Impedance Formula using the Return Ratio – Continued

Next, compute the RR for the controlled source, k , under two different conditions.

1.) The first condition is when port X is open ($i_x = 0$).

$$s_{ic} = a_4 s_y = a_4 s_t$$

Also,

$$s_r = k s_{ic} \quad \rightarrow \quad s_r = k a_4 s_t \quad \rightarrow \quad RR(\text{port open}) = -\frac{s_r}{s_t} = -k a_4$$

2.) The second condition is when port X is shorted ($v_x = 0$).

$$i_x = -\frac{a_2}{a_1} s_y = -\frac{a_2}{a_1} s_t$$

$$\therefore s_{ic} = a_3 i_x + a_4 s_y = \left(a_4 - \frac{a_2 a_3}{a_1} \right) s_t$$

The return signal is

$$s_r = k s_{ic} = k \left(a_4 - \frac{a_2 a_3}{a_1} \right) s_t \quad \rightarrow \quad RR(\text{port shorted}) = -\frac{s_r}{s_t} = -k \left(a_4 - \frac{a_2 a_3}{a_1} \right)$$

3.) The port impedance can be found as (Blackman's formula),

$$4.) \quad Z_{port} = \frac{v_x}{i_x} = a_1 \left(\frac{1 - k \left(a_4 - \frac{a_2 a_3}{a_1} \right)}{1 - a_4} \right) \Rightarrow \boxed{Z_{port} = Z_{port}(k=0) \left[\frac{1 + RR(\text{port shorted})}{1 + RR(\text{port open})} \right]}$$

Example 3 – Application of Blackman’s Formula

Use Blackman’s formula to calculate the output resistance of Example 2.

Solution

We must calculate three quantities. They are $R_{out}(g_m=0)$, $RR(\text{output port shorted})$, and $RR(\text{output port open})$. Use the following model for calculations:

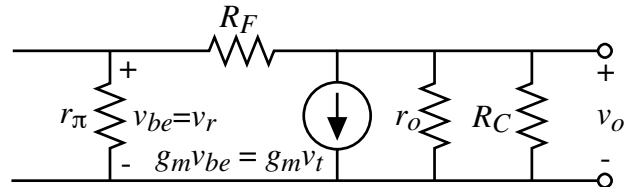


Fig. 290-07

$$R_{out}(g_m=0) = r_o \parallel R_C \parallel (r_\pi + R_F) = 7.09\text{k}\Omega$$

$$RR(\text{output port shorted}) = 0 \text{ because } v_r = 0.$$

$$RR(\text{output port open}) = RR \text{ of Example 2} = 56.74$$

$$\therefore R_{out} = R_{out}(g_m=0) \left[\frac{1 + RR(\text{port shorted})}{1 + RR(\text{port open})} \right] = 7.09\text{k}\Omega \left(\frac{1}{1+56.74} \right) = 129\Omega$$

Example 4 – Output Resistance of a Super-Source Follower

Find an expression for the small-signal output resistance of the circuit shown.

Solution

The appropriate small-signal model is shown where $g_{m2} = k$.

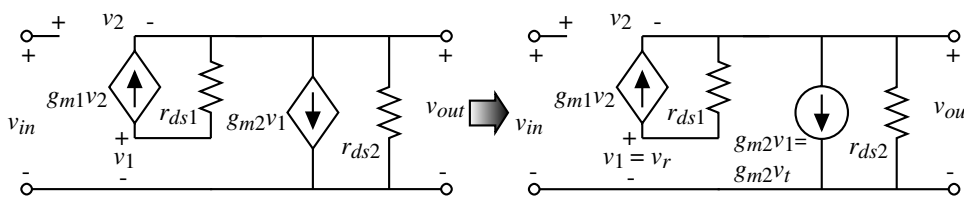


Fig. 290-10

$$R_{out}(g_{m2}=0) = r_{ds2} \quad \text{and} \quad RR(\text{output port shorted}) = 0 \text{ because } v_t = 0.$$

$$RR(\text{output port open}) = -\frac{s_r}{s_t} = -\frac{v_r}{v_t}$$

$$v_r = v_{out} - (g_{m1}v_2)r_{ds1} = v_{out} - g_{m1}r_{ds1}(-v_{out}) = v_{out}(1 + g_{m1}r_{ds1})$$

$$v_{out} = -g_{m2}r_{ds2}v_t \quad \rightarrow \quad v_r = -(1 + g_{m1}r_{ds1})g_{m2}r_{ds2}v_t$$

$$RR(\text{output port open}) = -\frac{v_r}{v_t} = (1 + g_{m1}r_{ds1})g_{m2}r_{ds2}$$

$$\therefore R_{out} = R_{out}(g_{m2}=0) \left[\frac{1 + RR(\text{port shorted})}{1 + RR(\text{port open})} \right] = r_{ds2} \left(\frac{1+0}{1+(1 + g_{m1}r_{ds1})g_{m2}r_{ds2}} \right) \approx \frac{1}{g_{m1}r_{ds1}g_{m2}}$$

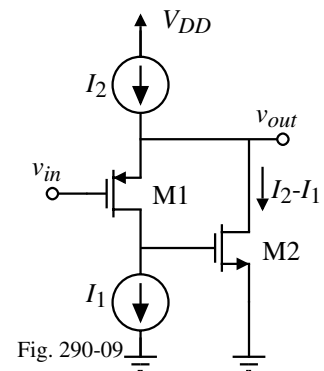


Fig. 290-09

SUMMARY

- Return ratio is associated with a dependent source. If the dependent source is converted to an independent source, then the return ratio is the gain from the dependent source variable to the previously controlling variable.
- The closed-loop gain of a linear, negative feedback system can be expressed as

$$A = A_{\infty} \frac{RR}{1 + RR} + \frac{d}{1 + RR}$$

where

A_{∞} = the closed-loop gain when the loop gain is infinite

RR = the return ratio

d = the closed-loop gain when the amplifier gain is zero

- The resistance at a port can be found from Blackman's formula which is

$$Z_{\text{port}} = Z_{\text{port}}(k=0) \left[\frac{1 + RR(\text{port shorted})}{1 + RR(\text{port open})} \right]$$

where k is the gain of the dependent source chosen for the return ratio calculation

- This stuff is all great but of *little use as far as calculations are concerned*.

Small-signal analysis is generally quicker and easier than the two-port approach or the return ratio approach.

- Why study feedback? Because it is a great tool for understanding a circuit and for knowing how to modify the performance in design.