

Homework Assignment No. 5

Due Monday, February 14, 2005 in class (because of Exam 1, you may turn in by 2/16)

Problem 1 - (10 points - Problem 6.2-8 of A&H)


A two-stage, Miller-compensated CMOS op amp has a RHP zero at $20GB$, a dominant pole due to the Miller compensation, a second pole at p_2 and a mirror pole at $-3GB$. (a) If GB is 1MHz, find the location of p_2 corresponding to a 45° phase margin. (b) Assume that in part (a) that $|p_2| = 2GB$ and a nulling resistor is used to cancel p_2 . What is the new phase margin assuming that $GB = 1\text{MHz}$? (c) Using the conditions of (b), what is the phase margin if C_L is increased by a factor of 4?

Problem 2 – (10 points - Problem 6.2-10 of A&H)

For the two-stage op amp of Fig. 6.2-8, find W_1/L_1 , W_6/L_6 , and C_c if $GB = 1\text{MHz}$, $|p_2| = 5\text{GB}$, $z = 3\text{GB}$ and $C_L = C_2 = 20\text{pF}$. Use the parameter values of Table 3.1-2 and consider only the two-pole model of the op amp. The bias current in M5 is $40\mu\text{A}$ and in M7 is $320\mu\text{A}$.

Problem 3 – (10 points – Problem 6.2-11 of A&H)


In the figure shown, assume that $R_I = 150\text{k}\Omega$, $R_{II} = 100\text{k}\Omega$, $g_{mII} = 500\mu\text{S}$, $C_I = 1\text{pF}$, $C_{II} = 5\text{pF}$, and $C_c = 30\text{pF}$. Find the value of R_z and the locations of all roots for (a) the case where the zero is moved to infinity and (b) the case where the zero cancels the highest pole.

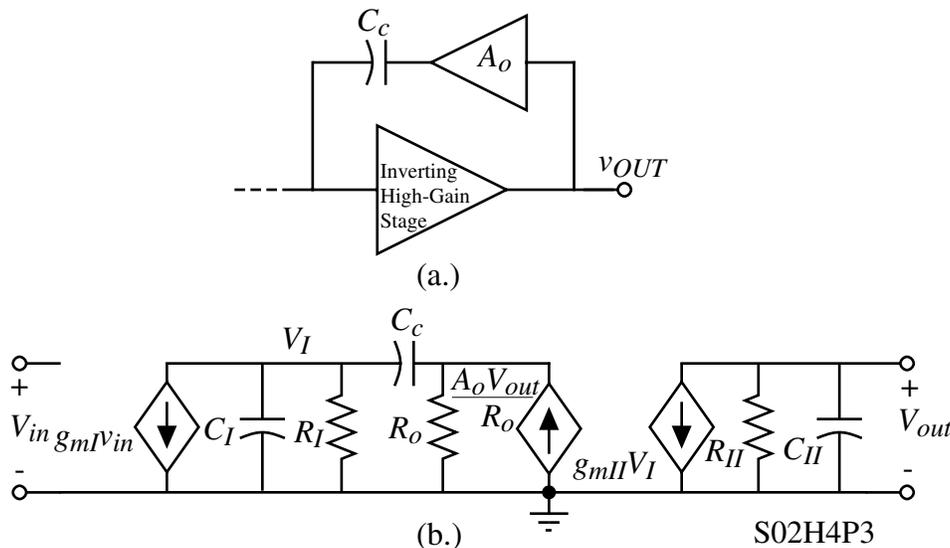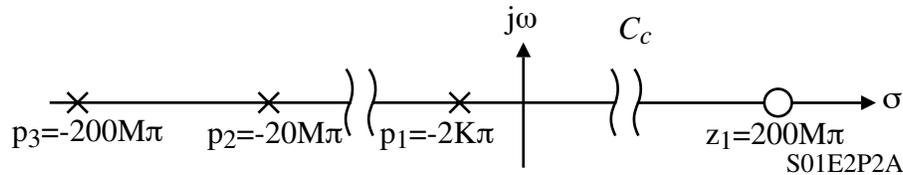

Problem 4 – (10 points)

The poles and zeros of a Miller compensated, two-stage op amp are shown below.

- (a.) If the influence of p_3 and z_1 are ignored, what is the GB in MHz of this op amp for 60° phase margin?
- (b.) What is the value of $A_v(0)$? What is the value of C_c if $g_{m1}=g_{m2}=500\mu\text{S}$?
- (c.) If p_2 is moved to p_3 , what is the new GB in MHz for 60° phase margin? What is the new C_c if the input transconductances are the same as in (b.)?

Problem 5 – (10 points)

A self-compensated op amp has three higher order poles grouped closely around -1×10^9 radians/sec. What should be the GB of this op amp in Hz to achieve a 60° phase margin? If the low frequency gain of the op amp is 80dB, where is the location of the dominant pole, p_1 ? If the output resistance of this amplifier is $10\text{M}\Omega$, what is the value of C_L that will give this location for p_1 ? (Ignore any other capacitance at the output for this part of the problem).