

# LECTURE 010 – ECE 4430 REVIEW I

## (READING: GHLM - Chap. 1)

### **Objective**

The objective of this presentation is:

- 1.) Identify the prerequisite material as taught in ECE 4430
- 2.) Insure that the students of ECE 6412 are adequately prepared

### **Outline**

- Models for Integrated-Circuit Active Devices
- Bipolar, MOS, and BiCMOS IC Technology
- Single-Transistor and Multiple-Transistor Amplifiers
- Transistor Current Sources and Active Loads

## MODELS FOR INTEGRATED-CIRCUIT ACTIVE DEVICES

### PN Junctions - Step Junction

Barrier potential-

$$\psi_o = \frac{kT}{q} \ln\left(\frac{N_A N_D}{n_i^2}\right) = V_t \ln\left(\frac{N_A N_D}{n_i^2}\right) = U_T \ln\left(\frac{N_A N_D}{n_i^2}\right)$$

Depletion region widths-

$$\left. \begin{aligned} W_1 &= \sqrt{\frac{2\epsilon_{si}(\psi_o - v_D)N_D}{qN_A(N_A + N_D)}} \\ W_2 &= \sqrt{\frac{2\epsilon_{si}(\psi_o - v_D)N_A}{qN_D(N_A + N_D)}} \end{aligned} \right\} W \propto \sqrt{\frac{1}{N}}$$

Depletion capacitance-

$$C_j = A \sqrt{\frac{\epsilon_{si} q N_A N_D}{2(N_A + N_D)}} \frac{1}{\sqrt{\psi_o - v_D}} = \frac{C_{j0}}{\sqrt{1 - \frac{v_D}{\psi_o}}}$$

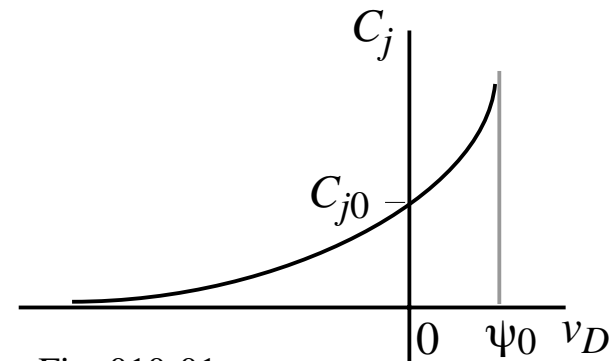


Fig. 010-01

## PN-Junctions - Graded Junction

Graded junction:

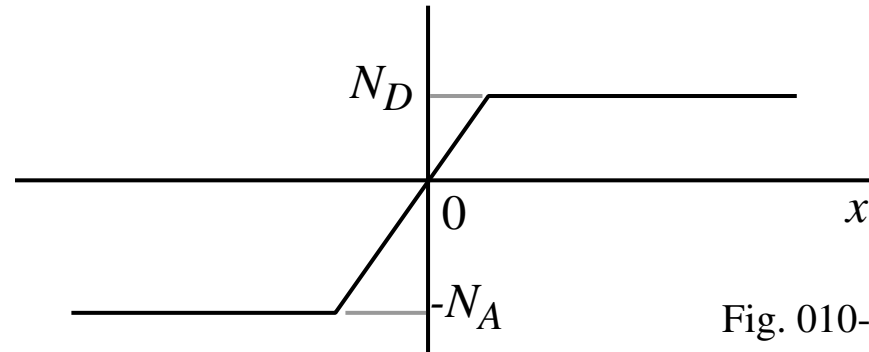


Fig. 010-02

Above expressions become:

Depletion region widths-

$$\left. \begin{aligned} W_1 &= \left( \frac{2\epsilon_{si}(\psi_o - v_D)N_D}{qN_D(N_A + N_D)} \right)^m \\ W_2 &= \left( \frac{2\epsilon_{si}(\psi_o - v_D)N_A}{qN_D(N_A + N_D)} \right)^m \end{aligned} \right\} W \propto \left( \frac{1}{N} \right)^m$$

Depletion capacitance-

$$C_j = A \left( \frac{\epsilon_{si}qN_A N_D}{2(N_A + N_D)} \right)^m \frac{1}{(\psi_o - v_D)^m} = \frac{C_{j0}}{\left( 1 - \frac{v_D}{\psi_o} \right)^m}$$

where  $0.33 \leq m \leq 0.5$ .


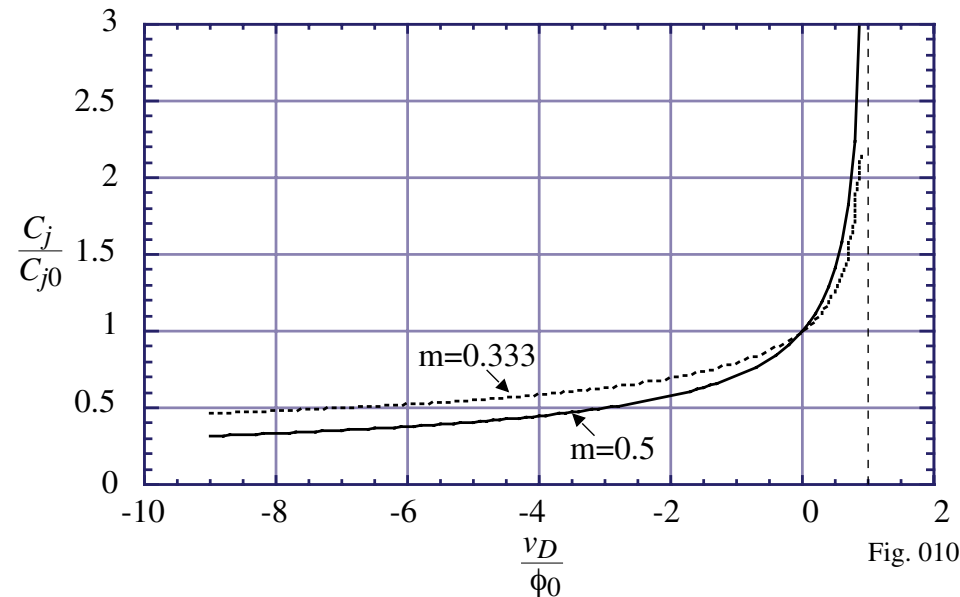



Fig. 010-03
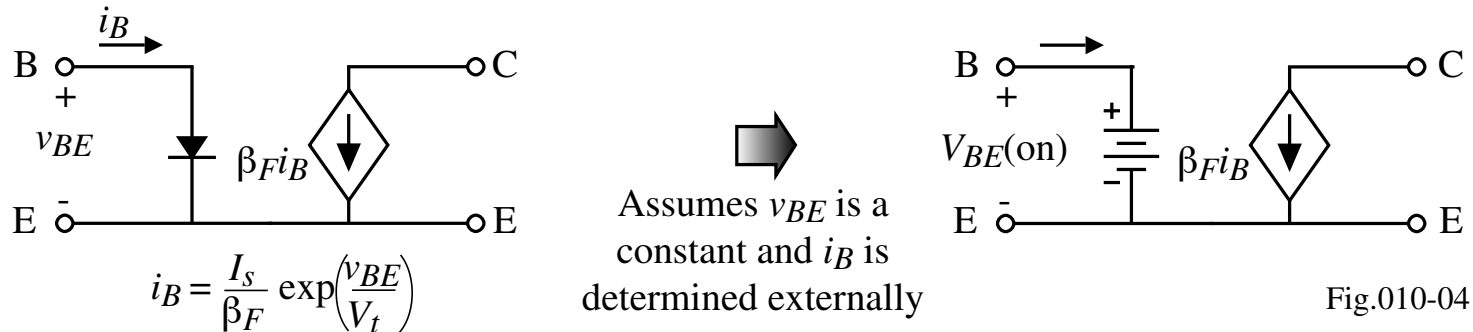
## Large Signal Model for the BJT in the Forward Active Region

Large-signal model for a *npn* transistor:



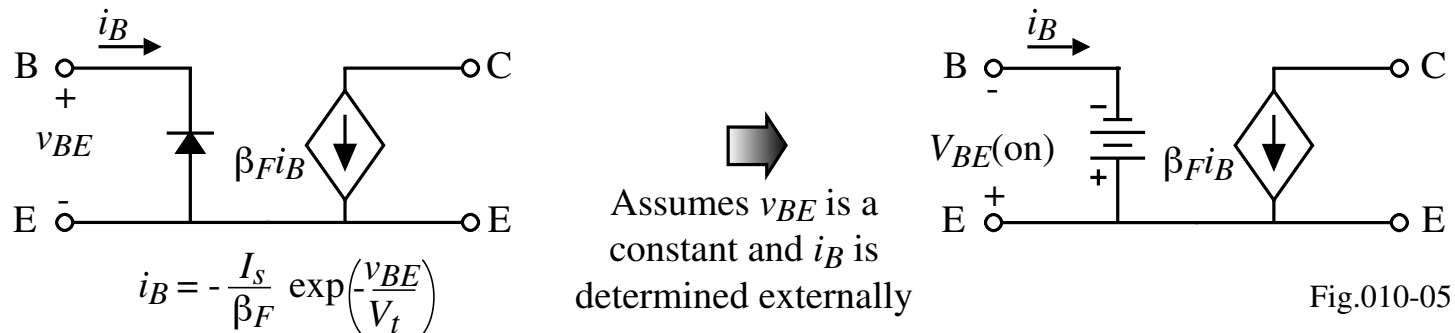Large-signal model for a *pnp* transistor:



Early Voltage:

Modified large signal model becomes

$$i_C = I_S \left( 1 + \frac{v_{CE}}{V_A} \right) \exp\left(\frac{v_{BE}}{V_t}\right)$$

## The Ebers-Moll Equations

The reciprocity condition allows us to write,

$$\alpha_F I_{EF} = \alpha_R I_{CR} = I_S$$

Substituting into a previous form of the Ebers-Moll equations gives,

$$i_C = I_S \left( \exp \frac{v_{BE}}{V_t} + 1 \right) - \frac{I_S}{\alpha_R} \left( \exp \frac{v_{BC}}{V_t} + 1 \right)$$

and

$$i_E = -\frac{I_S}{\alpha_F} \left( \exp \frac{v_{BE}}{V_t} + 1 \right) + I_S \left( \exp \frac{v_{BC}}{V_t} + 1 \right)$$

These equations are valid for all four regions of operation of the BJT.

Also:

- Dependence of  $\beta_F$  as a function of collector current
- The temperature coefficient of  $\beta_F$  is,

$$\text{TC}_F = \frac{1}{\beta_F} \frac{\partial \beta_F}{\partial T} \approx +7000 \text{ppm}/^\circ\text{C}$$

## Simple Small Signal BJT Model

Implementing the above relationships,  $i_c = g_m v_i + g_o v_{ce}$ , and  $v_i = r_\pi i_b$ , into a schematic model gives,

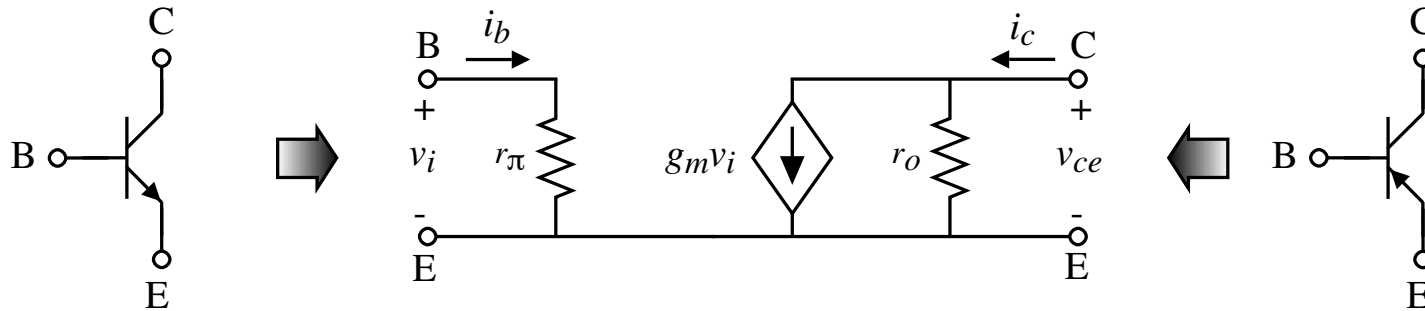


Fig. 010-06

Note that the small signal model is the same for either a *npn* or a *pnp* BJT.

Example:

Find the small signal input resistance,  $R_{in}$ , the output resistance,  $R_{out}$ , and the voltage gain of the common emitter BJT if the BJT is unloaded ( $R_L = \infty$ ),  $v_{out}/v_{in}$ , the dc collector current is 1mA, the Early voltage is 100V, and  $\beta_o = 100$  at room temperature.

$$g_m = \frac{I_C}{V_t} = \frac{1\text{mA}}{26\text{mV}} = \frac{1}{26} \text{ mhos or Siemens} \quad R_{in} = r_\pi = \frac{\beta_o}{g_m} = 100 \cdot 26 = 2.6\text{k}\Omega$$

$$R_{out} = r_o = \frac{V_A}{I_C} = \frac{100\text{V}}{1\text{mA}} = 100\text{k}\Omega \quad \frac{v_{out}}{v_{in}} = -g_m r_o = -26\text{mS} \cdot 100\text{k}\Omega = -2600\text{V/V}$$

## Complete Small Signal BJT Model

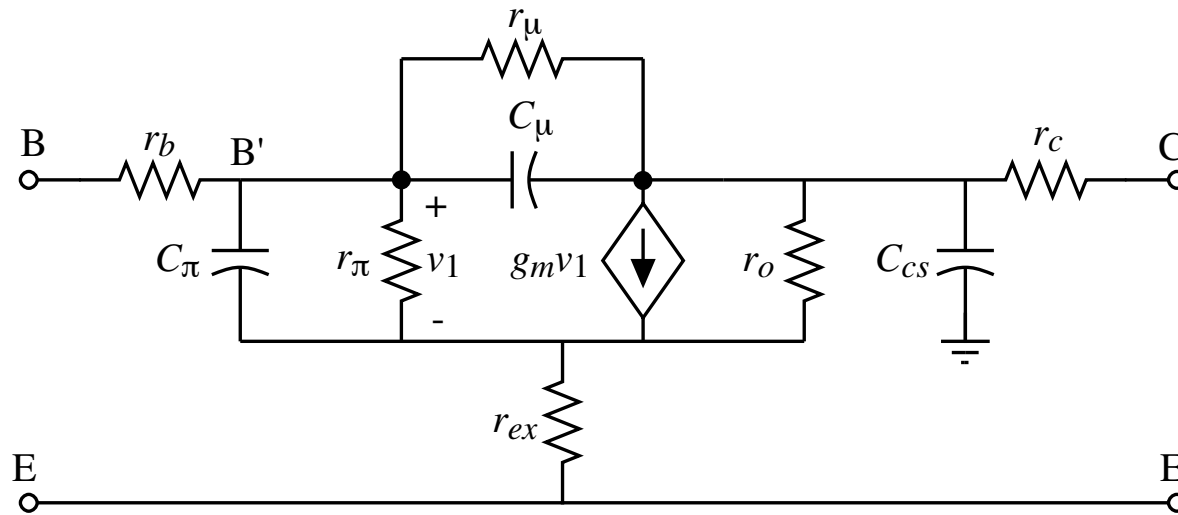


Fig. 010-07

The capacitance,  $C_\pi$ , consists of the sum of  $C_{je}$  and  $C_b$ .

$$C_\pi = C_{je} + C_b$$

## Example 1

Derive the complete small signal equivalent circuit for a BJT at  $I_C = 1\text{mA}$ ,  $V_{CB} = 3\text{V}$ , and  $V_{CS} = 5\text{V}$ . The device parameters are  $C_{je0} = 10\text{fF}$ ,  $n_e = 0.5$ ,  $\psi_{0e} = 0.9\text{V}$ ,  $C_{\mu0} = 10\text{fF}$ ,  $n_c = 0.3$ ,  $\psi_{0c} = 0.5\text{V}$ ,  $C_{cs0} = 20\text{fF}$ ,  $n_s = 0.3$ ,  $\psi_{0s} = 0.65\text{V}$ ,  $\beta_o = 100$ ,  $\tau_F = 10\text{ps}$ ,  $V_A = 20\text{V}$ ,  $r_b = 300\Omega$ ,  $r_c = 50\Omega$ ,  $r_{ex} = 5\Omega$ , and  $r_\mu = 10\beta_o r_o$ .

### Solution

Because  $C_{je}$  is difficult to determine and usually an insignificant part of  $C_\pi$ , let us approximate it as  $2C_{je0}$ .

$$\therefore C_{je} = 20\text{fF}$$

$$C_\mu = \frac{C_{\mu0}}{\left(1 + \frac{V_{CB}}{\psi_{0c}}\right)^{n_e}} = \frac{10\text{fF}}{\left(1 + \frac{3}{0.5}\right)^{0.3}} = 5.6\text{fF} \quad \text{and} \quad C_{cs} = \frac{C_{cs0}}{\left(1 + \frac{V_{CS}}{\psi_{0s}}\right)^{n_s}} = \frac{20\text{fF}}{\left(1 + \frac{5}{0.65}\right)^{0.3}} = 10.5\text{fF}$$

$$g_m = \frac{I_C}{V_t} = \frac{1\text{mA}}{26\text{mV}} = 38\text{mA/V} \quad C_b = \tau_F g_m = (10\text{ps})(38\text{mA/V}) = 0.38\text{pF}$$

$$\therefore C_\pi = C_b + C_{je} = 0.38\text{pF} + 0.02\text{pF} = 0.4\text{pF}$$

$$r_\pi = \frac{\beta_o}{g_m} = 100 \cdot 26\Omega = 2.6\text{k}\Omega, \quad r_o = \frac{V_A}{I_C} = \frac{20\text{V}}{1\text{mA}} = 20\text{k}\Omega \quad \text{and} \quad r_\mu = 10\beta_o r_o = 20\text{M}\Omega$$

## Transition Frequency, $f_T$

$f_T$  is the frequency where the magnitude of the short-circuit, common-emitter current = 1.

Circuit and model:

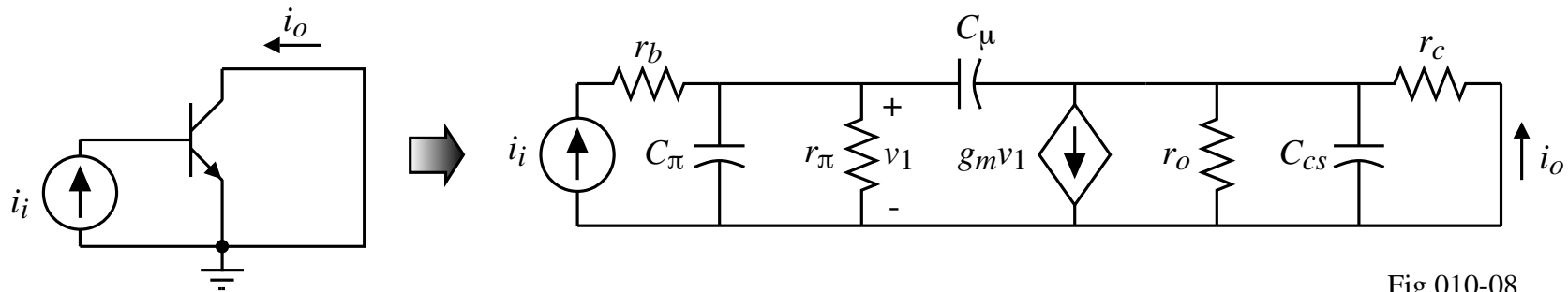


Fig.010-08

Assume that  $r_c \approx 0$ . As a result,  $r_o$  and  $C_{cs}$  have no effect.

$$V_1 \approx \frac{r_\pi}{1 + r_\pi(C_\pi + C_\mu)s} I_i \quad \text{and} \quad I_o \approx g_m V_1 \Rightarrow \frac{I_o(j\omega)}{I_i(j\omega)} = \frac{g_m r_\pi}{1 + g_m r_\pi \frac{(C_\pi + C_\mu)s}{g_m}} = \frac{\beta_o}{1 + \beta_o \frac{(C_\pi + C_\mu)s}{g_m}}$$

$$\text{Now,} \quad \beta(j\omega) = \frac{I_o(j\omega)}{I_i(j\omega)} = \frac{\beta_o}{1 + \beta_o \frac{(C_\pi + C_\mu)j\omega}{g_m}}$$

At high frequencies,

$$\beta(j\omega) \approx \frac{g_m}{j\omega (C_\pi + C_\mu)} \Rightarrow \text{When } |\beta(j\omega)| = 1 \text{ then } \omega_T = \frac{g_m}{C_\pi + C_\mu} \text{ or } f_T = \frac{1}{2\pi} \frac{g_m}{C_\pi + C_\mu}$$

## JFET Large Signal Model

Large signal model:

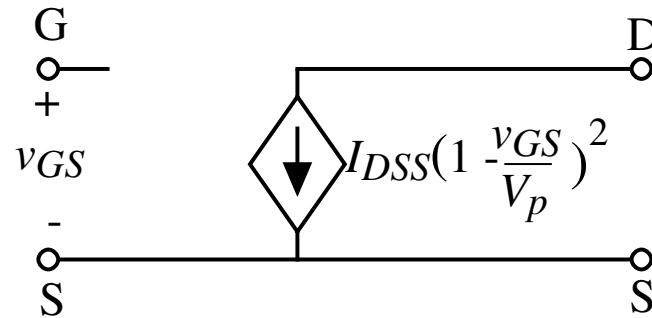


Fig. 010-09

Incorporating the channel modulation effect:


$$i_D = I_{DSS} \left(1 - \frac{v_{GS}}{V_p}\right)^2 (1 + \lambda v_{DS}) \quad , \quad v_{DS} \geq v_{GS} - V_p$$

Signs for the JFET variables:

Type of JFET	$V_p$	$I_{DSS}$	$v_{GS}$
$p$ -channel	Positive	Negative	Normally positive
$n$ -channel	Negative	Positive	Normally negative

## Frequency Independent JFET Small Signal Model

Schematic:

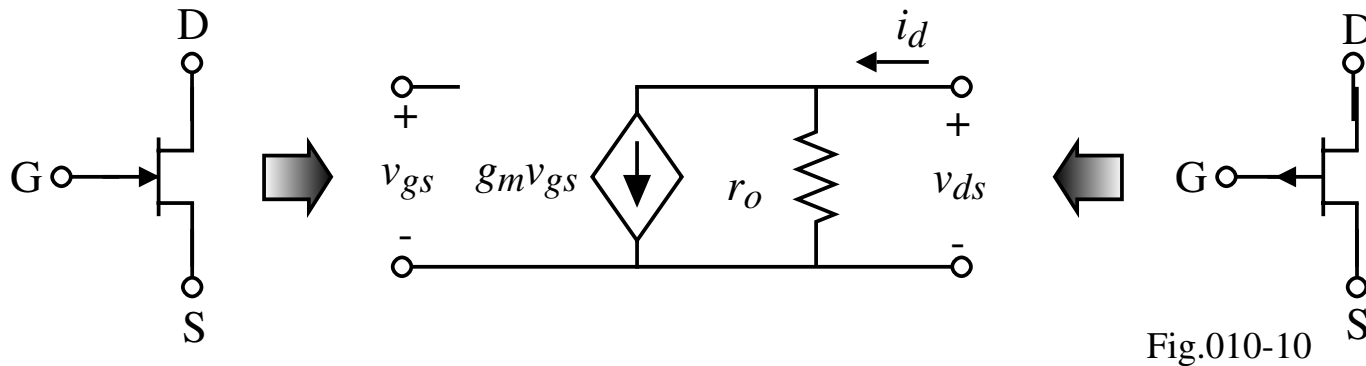

Parameters:

$$g_m = \left. \frac{di_D}{dv_{GS}} \right|_Q = - \frac{2I_{DSS}}{V_p} \left( 1 - \frac{V_{GS}}{V_p} \right) = g_{m0} \left( 1 - \frac{V_{GS}}{V_p} \right)$$

where

$$g_{m0} = - \frac{2I_{DSS}}{V_p}$$

$$r_o = \left. \frac{di_D}{dv_{DS}} \right|_Q = \lambda I_{DSS} \left( 1 - \frac{V_{GS}}{V_p} \right)^2 \approx \frac{1}{\lambda I_D}$$

Typical values of  $I_{DSS}$  and  $V_p$  for a  $p$ -channel JFET are  $-1\text{mA}$  and  $2\text{V}$ , respectively.

With  $\lambda = 0.02\text{V}^{-1}$  and  $I_D = 1\text{mA}$  we get  $g_m = 1\text{mA/V}$  or  $1\text{mS}$  and  $r_o = 50\text{k}\Omega$ .

## Frequency Dependent JFET Small Signal Model

Complete small signal model:

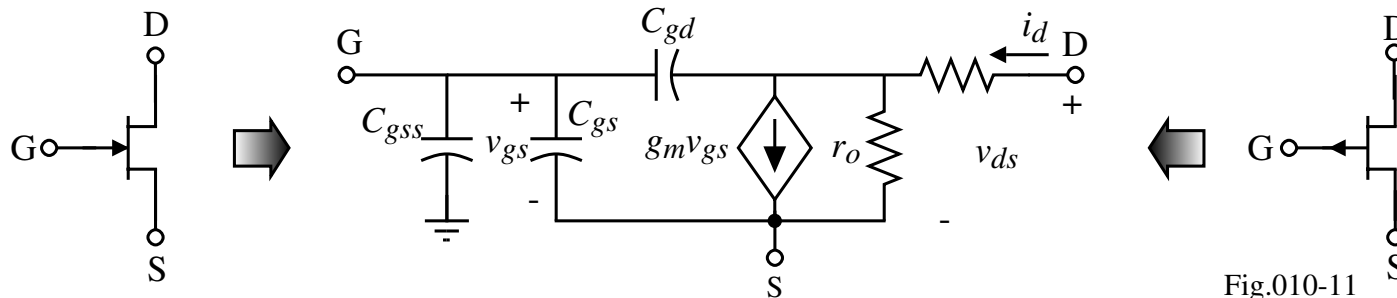


Fig.010-11

All capacitors are reverse biased depletion capacitors given as,

$$C_{gs} = \frac{C_{gs0}}{\left(1 + \frac{V_{GS}}{\psi_o}\right)^{1/3}} \quad (\text{capacitance from source to } \textit{top} \text{ and } \textit{bottom} \text{ gates})$$

$$C_{gd} = \frac{C_{gd0}}{\left(1 + \frac{V_{GD}}{\psi_o}\right)^{1/3}} \quad (\text{capacitance from drain to } \textit{top} \text{ and } \textit{bottom} \text{ gates})$$

$$C_{gss} = \frac{C_{gss0}}{\left(1 + \frac{V_{GSS}}{\psi_o}\right)^{1/2}} \quad (\text{capacitance from the gate (p-base) to substrate})$$

$$\therefore f_T = \frac{1}{2\pi} \frac{g_m}{C_{gs} + C_{gd} + C_{gss}} = 30\text{MHz} \quad \text{if } g_m = 1\text{mA/V} \text{ and } C_{gs} + C_{gd} + C_{gss} = 5\text{pF}$$

## Simple Large Signal MOSFET Model

N-channel reference convention:

Non-saturation-

$$i_D = \frac{W\mu_o C_{ox}}{L} \left[ (v_{GS} - V_T)v_{DS} - \frac{v_{DS}^2}{2} \right] (1 + \lambda v_{DS}), \quad 0 < v_{DS} < v_{GS} - V_T$$

Saturation-

$$i_D = \frac{W\mu_o C_{ox}}{L} \left[ (v_{GS} - V_T)v_{DS(sat)} - \frac{v_{DS(sat)}^2}{2} \right] (1 + \lambda v_{DS})$$

$$= \frac{W\mu_o C_{ox}}{2L} (v_{GS} - V_T)^2 (1 + \lambda v_{DS}), \quad 0 < v_{GS} - V_T < v_{DS}$$

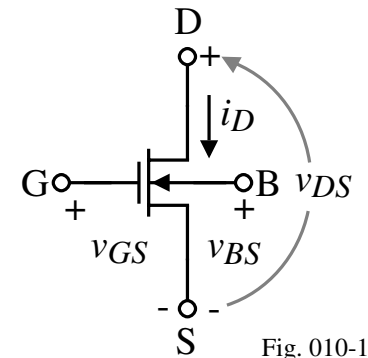


Fig. 010-12

where:

$\mu_o$  = zero field mobility (cm<sup>2</sup>/volt·sec)

$C_{ox}$  = gate oxide capacitance per unit area (F/cm<sup>2</sup>)

$\lambda$  = channel-length modulation parameter (volts<sup>-1</sup>)

$$V_T = V_{T0} + \gamma(\sqrt{2|\phi_f| + |v_{BS}|} - \sqrt{2|\phi_f|})$$

$V_{T0}$  = zero bias threshold voltage


$\gamma$  = bulk threshold parameter (volts<sup>-0.5</sup>)

$2|\phi_f|$  = strong inversion surface potential (volts)

For p-channel MOSFETs, use n-channel equations with p-channel parameters and invert current.

# MOSFET Small-Signal Model

Complete schematic model:

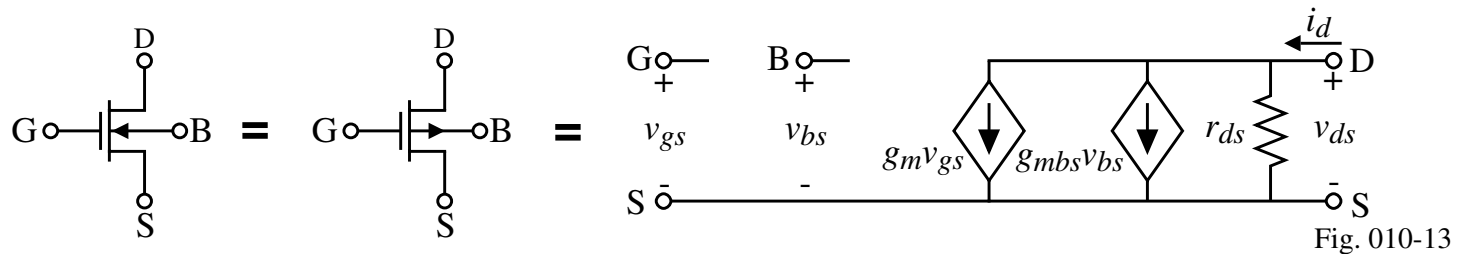


where

$$g_m \equiv \left. \frac{di_D}{dv_{GS}} \right|_Q = \beta(V_{GS} - V_T) = \sqrt{2\beta I_D}$$

$$g_{ds} \equiv \left. \frac{di_D}{dv_{DS}} \right|_Q = \frac{\lambda i_D}{1 + \lambda v_{DS}} \approx \lambda i_D$$

$$\text{and } g_{mbs} = \left. \frac{\partial i_D}{\partial v_{BS}} \right|_Q = \left( \frac{\partial i_D}{\partial v_{GS}} \right) \left( \frac{\partial v_{GS}}{\partial v_{BS}} \right) \Big|_Q = \left( - \frac{\partial i_D}{\partial v_T} \right) \left( \frac{\partial v_T}{\partial v_{BS}} \right) \Big|_Q = \frac{g_m \gamma}{2\sqrt{2|\phi_F| - V_{BS}}} = \eta g_m$$

Simplified schematic model:

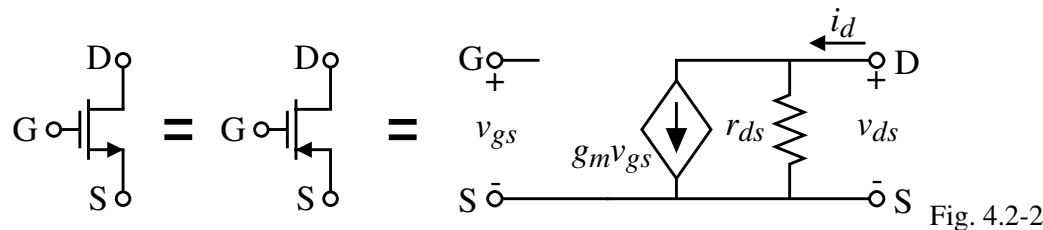

Extremely important assumption:

$$g_m \approx 10g_{mbs} \approx 100g_{ds}$$

## MOSFET Depletion Capacitors - $C_{BS}$ and $C_{BD}$

Model:

$$C_{BS} = \frac{CJ \cdot AS}{\left(1 - \frac{V_{BS}}{PB}\right)^{MJ}} + \frac{CJSW \cdot PS}{\left(1 - \frac{V_{BS}}{PB}\right)^{MJSW}}, \quad V_{BS} \leq FC \cdot PB$$

and

$$C_{BS} = \frac{CJ \cdot AS}{(1 - FC)^{1+MJ}} \left(1 - (1+MJ)FC + MJ \frac{V_{BS}}{PB}\right) + \frac{CJSW \cdot PS}{(1 - FC)^{1+MJSW}} \left(1 - (1+MJSW)FC + MJSW \frac{V_{BS}}{PB}\right),$$

$$V_{BS} > FC \cdot PB$$

where

$AS$  = area of the source

$PS$  = perimeter of the source

$CJSW$  = zero bias, bulk source sidewall capacitance

$MJSW$  = bulk-source sidewall grading coefficient

For the bulk-drain depletion capacitance replace "S" by "D" in the above equations.

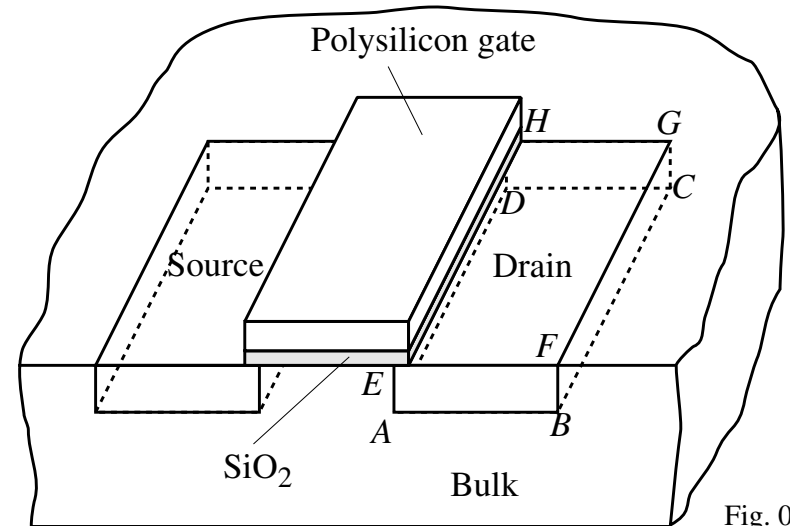


Fig. 010-14

Drain bottom = ABCD

Drain sidewall = ABFE + BCGF + DCGH + ADHE

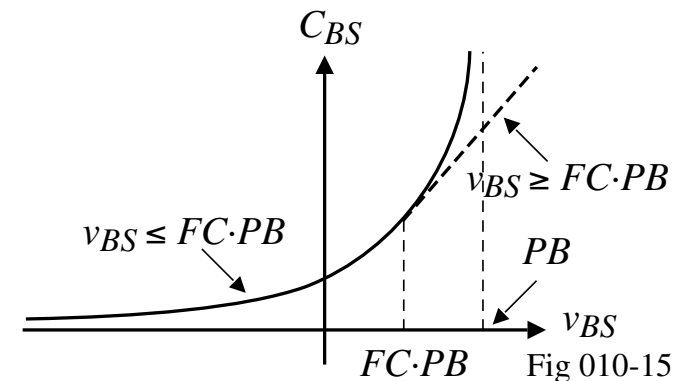


Fig 010-15

## MOSFET Intrinsic Capacitors - $C_{GD}$ , $C_{GS}$ and $C_{GB}$

Cutoff Region:

$$C_{GB} = C_2 + 2C_5 = C_{ox}(W_{eff})(L_{eff}) + 2CGBO(L_{eff})$$

$$C_{GS} = C_1 \approx C_{ox}(LD)W_{eff} = CGSO(W_{eff})$$

$$C_{GD} = C_3 \approx C_{ox}(LD)W_{eff} = CGDO(W_{eff})$$

Saturation Region:

$$C_{GB} = 2C_5 = CGBO(L_{eff})$$

$$C_{GS} = C_1 + (2/3)C_2 = C_{ox}(LD + 0.67L_{eff})(W_{eff})$$

$$= CGSO(W_{eff}) + 0.67C_{ox}(W_{eff})(L_{eff})$$

$$C_{GD} = C_3 \approx C_{ox}(LD)W_{eff} = CGDO(W_{eff})$$

Active Region:

$$C_{GB} = 2C_5 = 2CGBO(L_{eff})$$

$$C_{GS} = C_1 + 0.5C_2 = C_{ox}(LD + 0.5L_{eff})(W_{eff})$$

$$= (CGSO + 0.5C_{ox}L_{eff})W_{eff}$$

$$C_{GD} = C_3 + 0.5C_2 = C_{ox}(LD + 0.5L_{eff})(W_{eff})$$

$$= (CGDO + 0.5C_{ox}L_{eff})W_{eff}$$

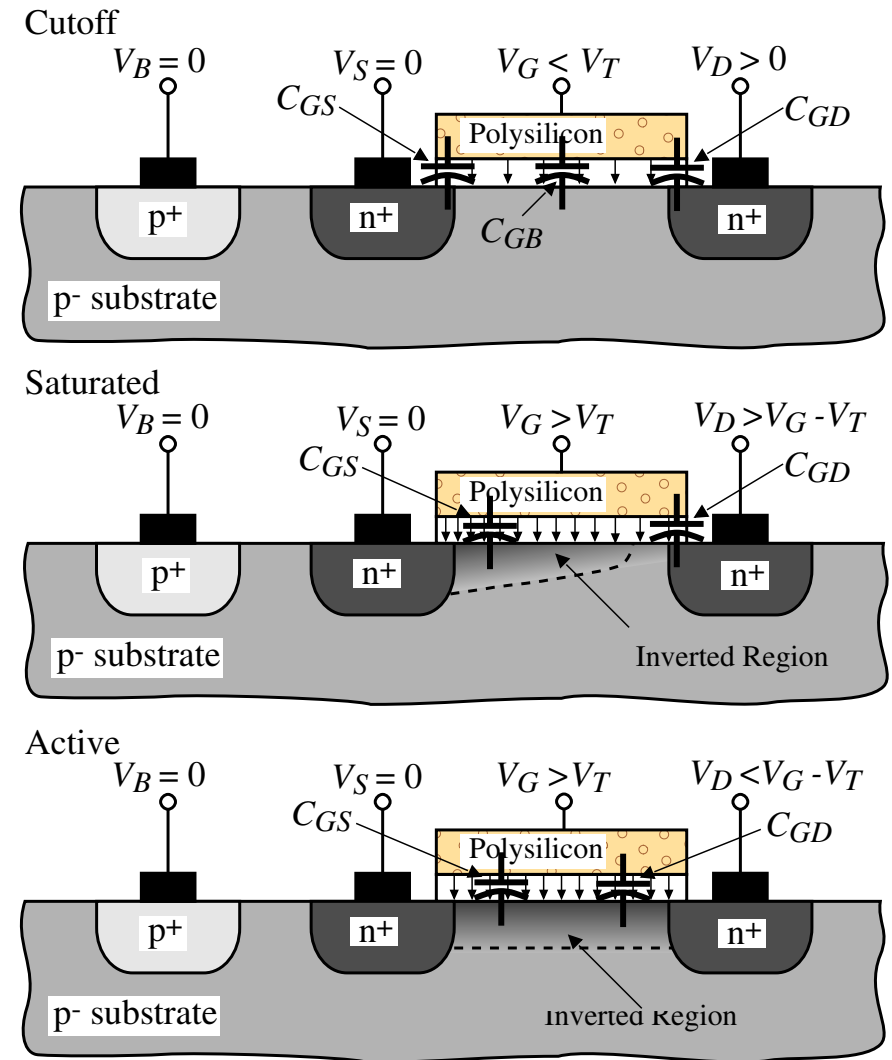


Fig 010-16

## Small-Signal Frequency Dependent Model

The depletion capacitors are found by evaluating the large signal capacitors at the DC operating point.

The charge storage capacitors are constant for a specific region of operation.

Gainbandwidth of the MOSFET:

Assume  $V_{SB} = 0$  and the MOSFET is in saturation,

$$f_T = \frac{1}{2\pi} \frac{g_m}{C_{gs} + C_{gd}} \approx \frac{1}{2\pi} \frac{g_m}{C_{gs}}$$

Recalling that

$$C_{gs} \approx \frac{2}{3} C_{ox} WL \quad \text{and} \quad g_m = \mu_o C_{ox} \frac{W}{L} (V_{GS} - V_T)$$

gives

$$f_T = \frac{3}{4\pi} \frac{\mu_o}{L^2} (V_{GS} - V_T)$$

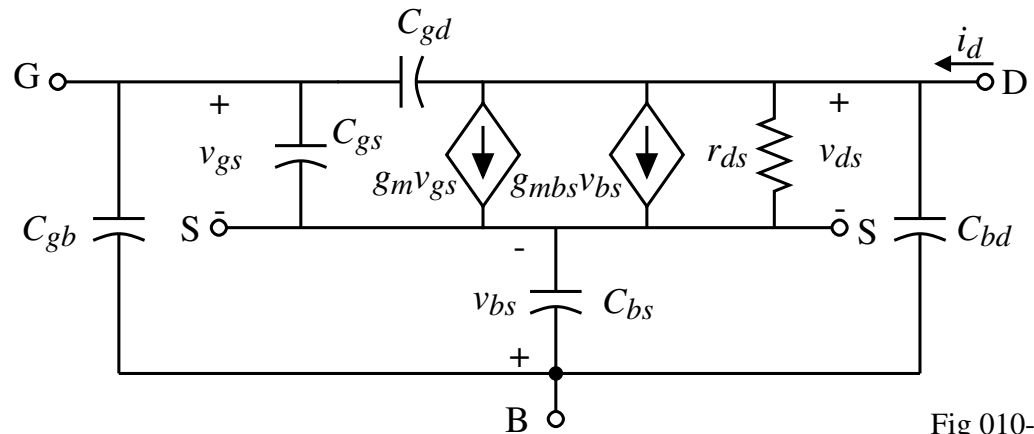


Fig 010-17

## Subthreshold MOSFET Model

Weak inversion operation occurs when the applied gate voltage is below  $V_T$  and pertains to when the surface of the substrate beneath the gate is weakly inverted.

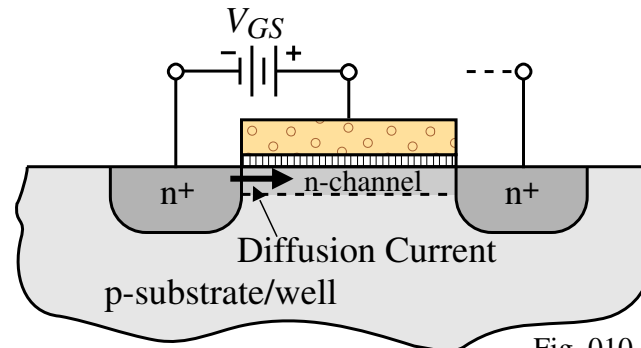


Fig. 010-18

Regions of operation according to the surface potential,  $\phi_S$ .

$\phi_S < \phi_F$  : Substrate not inverted

$\phi_F < \phi_S < 2\phi_F$  : Channel is weakly inverted (diffusion current)

$2\phi_F < \phi_S$  : Strong inversion (drift current)

Drift current versus diffusion current in a MOSFET:

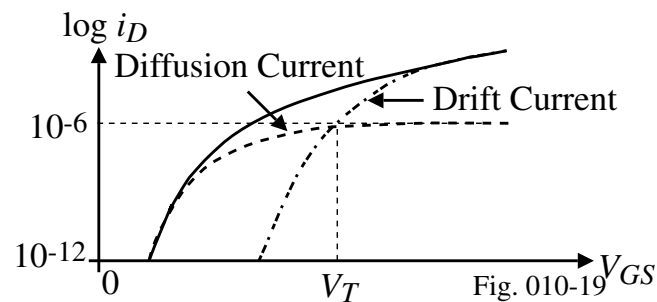


Fig. 010-19

## Large-Signal Model for Subthreshold

Model:

$$i_D = K_x \frac{W}{L} e^{v_{GS}/nV_t} (1 - e^{-v_{DS}/V_t}) (1 + \lambda v_{DS})$$

where

$K_x$  is dependent on process parameters and the bulk-source voltage

$$n \approx 1.5 - 3$$

and

$$V_t = \frac{kT}{q}$$

If  $v_{DS} > 0$ , then

$$i_D = K_x \frac{W}{L} e^{v_{GS}/nV_t} (1 + \lambda v_{DS})$$

Small-signal model:

$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_Q = \frac{qI_D}{nkT}$$

$$g_{ds} = \left. \frac{\partial i_D}{\partial v_{DS}} \right|_Q \approx \frac{I_D}{V_A}$$

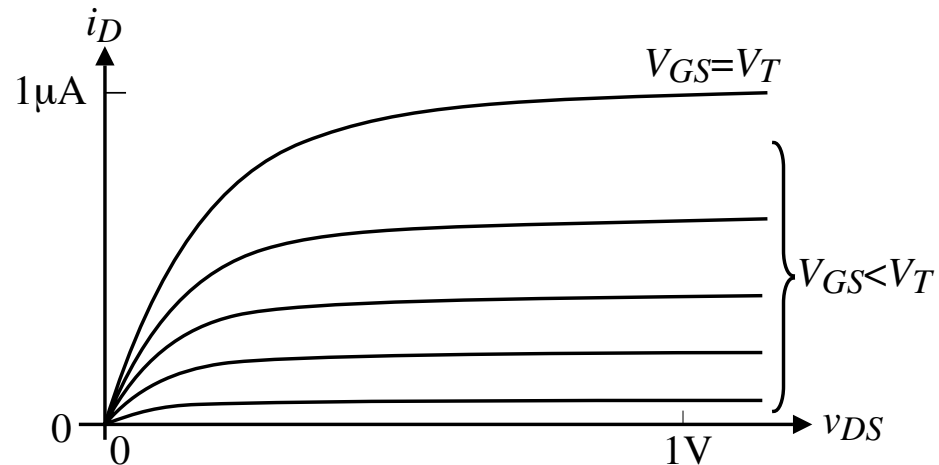


Fig 010-20

## SUMMARY

- Models
  - Large-signal
  - Small-signal
- Components
  - pn Junction
  - BJT
  - MOSFET
    - Strong inversion
    - Weak inversion
  - JFET
- Capacitors
  - Depletion
  - Parallel plate