

GEORGIA INSTITUTE OF TECHNOLOGY  
School of Electrical and Computer Engineering

Course ECE 2040  
Circuit Analysis

Assigned: April 6, 2001  
Due: April 13, 2001

**Problem Set #11**

---

**Reading:** Read the following sections from the class notes:

Chapter 8, Sections 8.3

Chapter 9, Sections 9.2.2, 9.3

**Reading:** Some of same topics are discussed in Dorf and Svoboda:

Chapter 10, Section 10.10 (node and mesh equations)

Chapter 11, Sections 11.3, 11.8 (power and complex amplitudes)


Chapter 16, Section 16.6 (frequency responses)

---

**Announcement:** Quiz #4 will be held during the class hour on Wednesday, April 18, 2001. It will be a closed book test, although calculators are permitted. You may also bring one 8.5 by 11.0 inch sheet of *handwritten* notes. It will cover problem sets 9–11.

---

**Problem 11.1:** For the circuit below find  $v(t)$ .

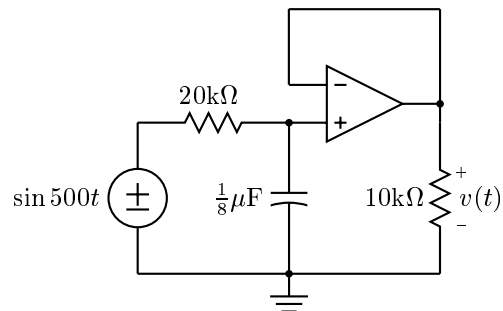

**Problem 11.2:** For the circuit in Figure 1 find  $v(t)$  when  $v_s(t) = \cos(\omega t)$ .

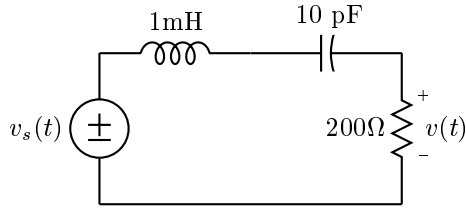


Figure 1: Circuit for Problem 11.2.

**Problem 11.3:** For the circuit in Figure 2 what is the average power supplied by the current source?

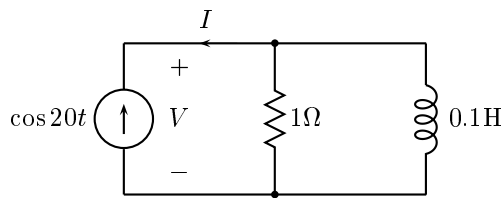


Figure 2: Circuit for Problem 11.3.

**Problem 11.4:** Determine the values of  $R$  and  $L$  for the circuit in Figure 3 that cause the maximum amount of power to be delivered to the load.


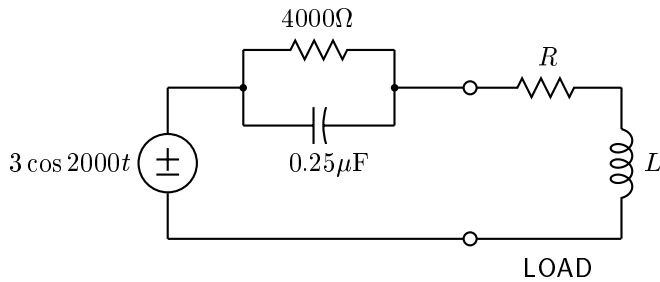



Figure 3: Circuit for Problem 11.4.

**Problem 11.5:**

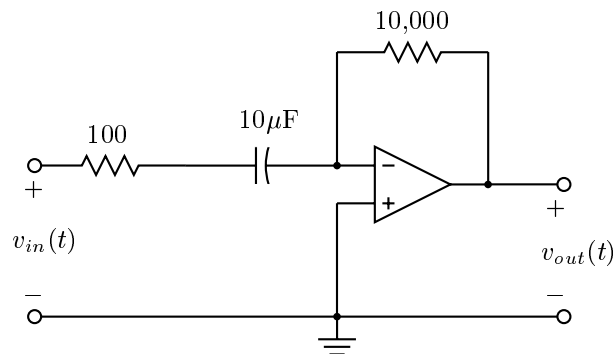

- (a) Calculate the frequency response of the above circuit.
- (b) Plot the magnitude response.
- (c) Plot the phase response.

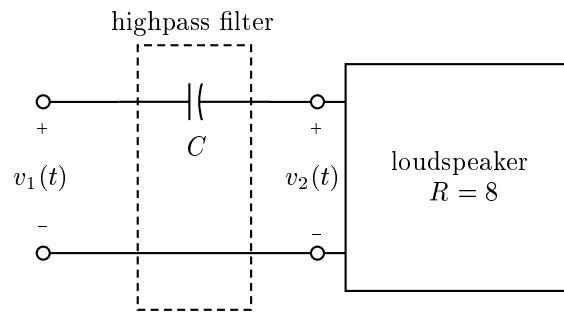**Problem 11.6:** Many loudspeaker systems consist of two loudspeakers: the woofer, which reproduces the low frequency part of the signal, and the tweeter, which reproduces the high frequency part of the signal. A crossover network is used to select the high frequency part of the signal and feed it into the tweeter. Such a network functions as a highpass filter. The entire audio signal is applied at the terminals  $a - a'$ .



- (a) Assuming that the equivalent circuit for the tweeter consists of just a resistor with a resistance of  $R$ , plot the pole-zero pattern of the system function that relates  $v_2(t)$  to  $v_1(t)$  and sketch the frequency response curves (magnitude and angle).
- (b) If  $R = 8\Omega$ , find the value of the capacitance  $C$  so that the half-power frequency of the highpass filter is 5 kHz ( $= 2\pi(5000)$  rad/s).