

GEORGIA INSTITUTE OF TECHNOLOGY
School of Electrical and Computer Engineering

Course ECE 2040
Circuit Analysis

Assigned: January 26, 2001

Due: February 2, 2001

Problem Set #3

Reading: Read the following sections from the class notes:
Chapter 2, Sections 2.1, 2.3

Reading: Some of same topics are discussed in Dorf and Svoboda:
Chapter 4, Sections 4.3–4.5; (node method)
Chapter 5, Sections 5.4; (superposition of sources)

Problem 3.1: This problem will solve the circuit in Figure 1 using the Simplified Exhaustive Method using both voltage and current variables. In addition to the three voltage variables

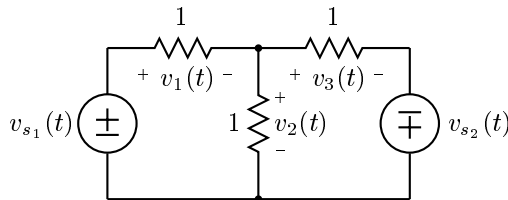


Figure 1: Circuit for Problem 3.1.

that are indicated, define current variables $i_1(t)$, $i_2(t)$, and $i_3(t)$ flowing through the three resistors with reference directions defined according to the default sign conventions. Let $i_1(t)$ be the current through the resistor with voltage drop $v_1(t)$, etc.

- Write a sufficient set of KCL equations to constrain the currents. Write these equations in terms of the current variables $i_1(t)$, $i_2(t)$, and $i_3(t)$.
- Write a sufficient set of KVL equations to constrain the voltage drops. Write these equations in terms of the voltage variables $v_1(t)$, $v_2(t)$, and $v_3(t)$.
- Write the element relations for the three resistors. Write these with both the voltage and current variables on the left-sides of the equations, since these are both element variables.
- Put these equations in matrix-vector form. Define the vector of variables as

$$\mathbf{x} = \begin{bmatrix} v_1(t) \\ v_2(t) \\ v_3(t) \\ i_1(t) \\ i_2(t) \\ i_3(t) \end{bmatrix}.$$

Solve these equations for the complete set of element variables.

- Problem 3.2:** (a) For the circuit in Figure 2, what is the minimum number of KCL equations that need to be written to specify the equilibrium solution?
- (b) Select one of the nodes of the basic network as the ground node and label it. Define node potentials at the remaining nodes of the basic network and write a KCL equation at each of these nodes in terms of the node potentials (and the source waveforms).
- (c) Put your equations in matrix-vector form with the node potentials as unknowns. You do not need to solve the equations.

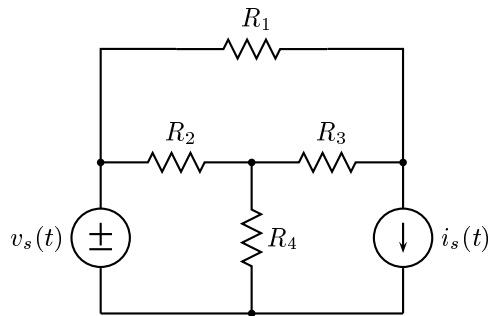


Figure 2: Circuit for Problem 3.2.

- Problem 3.3:** In this problem we solve the circuit in Figure 3 using the node method.

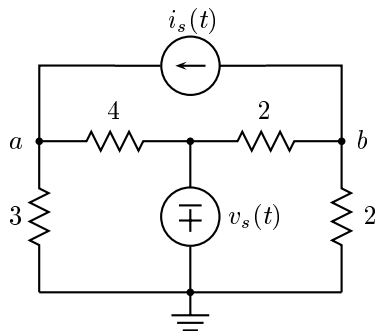


Figure 3: Circuit for Problem 3.3.

- (a) Write the KCL equations at nodes a and b in terms of the node potentials at those nodes, $e_a(t)$ and $e_b(t)$.
- (b) Put your equations in matrix-vector form by supplying the missing constants in the framework below.

$$\begin{bmatrix} \quad \\ \quad \end{bmatrix} \begin{bmatrix} e_a(t) \\ e_b(t) \end{bmatrix} = \begin{bmatrix} \quad \\ \quad \end{bmatrix} i_s(t) + \begin{bmatrix} \quad \\ \quad \end{bmatrix} v_s(t)$$

- (c) Solve them for $e_a(t)$ and $e_b(t)$.

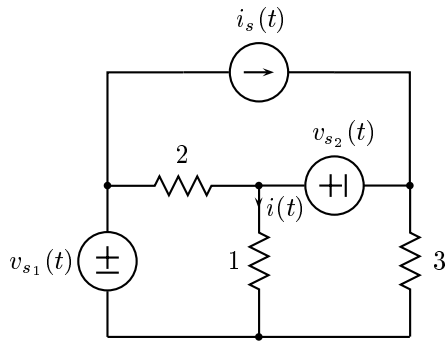


Figure 4: Circuit for Problem 3.4.

Problem 3.4: Solve for $i(t)$ in the circuit in Figure 4.

Problem 3.5: In the circuit in Figure 5

- Compute the power supplied by the voltage source. (Note: The power supplied is the negative of the power dissipated.)
- Compute the power supplied by the current source.

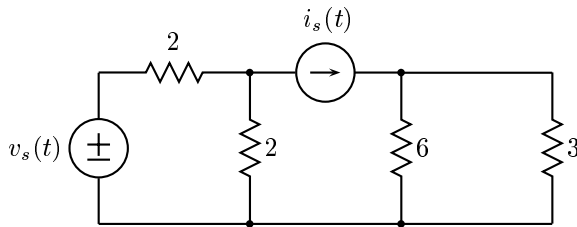


Figure 5: Circuit for Problem 3.5.

Problem 3.6: In the circuit in Figure 6 determine $v(t)$ in terms of $i_s(t)$.

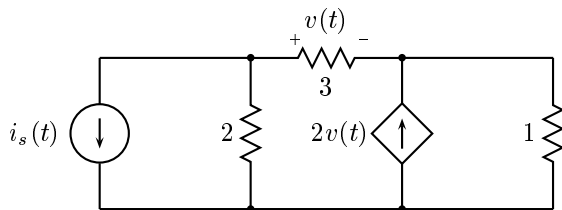


Figure 6: Circuit for Problem 3.6.