

GEORGIA INSTITUTE OF TECHNOLOGY
School of Electrical and Computer Engineering

Course ECE 2040
Circuit Analysis

March 16, 2001

Problem Set #8–Solutions

Problem 8.1: In the circuit of Figure 1 the source voltage is $v_s(t) = e^{-2t}$ for $t > 0$ and $v_c(0) = 1$ V.

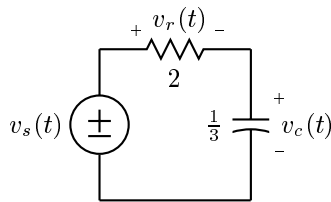


Figure 1: Circuit for Problem 8.1.

- (a) Write the differential equation whose solution is the equilibrium solution for $v_c(t)$.
- (b) Write the differential equation whose solution is the equilibrium solution for $v_r(t)$ and determine the value of $v_r(0)$.

Solution:

- (a) We can begin with a statement of KVL.

$$v_r(t) + v_c(t) = v_s(t).$$

We know, however, that

$$\begin{aligned} v_r(t) &= 2i_r(t) \\ &= 2i_c(t) \\ &= 2 \cdot \frac{1}{3} \frac{dv_c(t)}{dt}. \end{aligned}$$

Therefore,

$$\frac{2}{3} \frac{dv_c(t)}{dt} + v_c(t) = v_s(t)$$

or

$$\frac{dv_c(t)}{dt} + \frac{3}{2}v_c(t) = \frac{3}{2}v_s(t) = \frac{3}{2}e^{-2t}, \quad t > 0.$$

- (b) Since $v_c(t) = v_s(t) - v_r(t)$, we can substitute into the solution of part (a).

$$\frac{dv_s(t)}{dt} - \frac{dv_r(t)}{dt} + \frac{3}{2}v_s(t) - \frac{3}{2}v_r(t) = \frac{3}{2}v_s(t).$$

Substituting for the known input and simplifying gives

$$\frac{dv_r(t)}{dt} + \frac{3}{2}v_r(t) = \frac{dv_s(t)}{dt} = -2e^{-2t}, \quad t > 0.$$

At $t = 0$

$$v_s(0) = 1, v_c(0) = 1 \implies v_r(0) = 0.$$

Problem 8.2: Determine $v_{out}(t)$ for $t > 0$ for the circuit in Figure 2 if $v_{out}(0) = 0$.


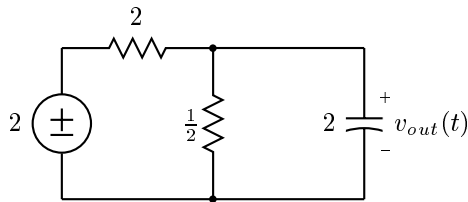


Figure 2: Circuit for Problem 8.2.

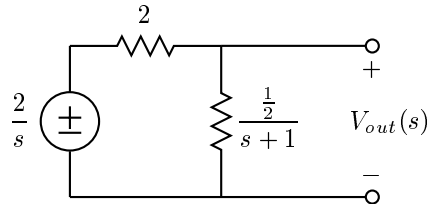Solution: We begin by redrawing the circuit in the Laplace domain and replacing the parallel resistor and capacitor by their equivalent impedance.



We can now determine $V_{out}(s)$ by using a voltage divider.

$$\begin{aligned} V_{out}(s) &= \frac{\frac{1}{s+1}}{2 + \frac{1}{s+1}} \cdot \frac{2}{s} = \frac{\frac{1}{2}}{s(s + \frac{5}{4})} \\ &= \frac{A}{s} + \frac{B}{s + \frac{5}{4}} \end{aligned}$$

$$A = \lim_{s \rightarrow 0} \frac{\frac{1}{2}}{s + \frac{5}{4}} = \frac{2}{5}$$

$$B = \lim_{s \rightarrow -\frac{5}{4}} \frac{\frac{1}{2}}{s} = -\frac{2}{5}$$

Therefore,

$$v_{out}(t) = \frac{2}{5}(1 - e^{-1.25t}), \quad t > 0$$

Problem 8.3: For the circuit shown in Figure 3.

- (a) Find $v_r(t)$ for $t > 0$ if $i_\ell(0) = 0$.
 (b) Find $v_r(t)$ for $t > 0$ if $i_\ell(0) = 5$.

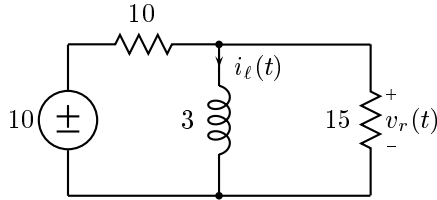


Figure 3: Circuit for Problem 8.3.

Solution:

- (a) At $t = 0$ the inductor looks like an open circuit.

$$v_r(0) = \frac{15}{25} \cdot 10 = 6$$

At $t = \infty$ the inductor looks like a short circuit.

$$v_r(\infty) = 0.$$


We turn off the source to determine the time constant

$$\tau = \frac{L}{R_{eq}} = \frac{3}{6} = \frac{1}{2}.$$

Therefore,

$$v_r(t) = 6e^{-2t} \quad t \geq 0.$$

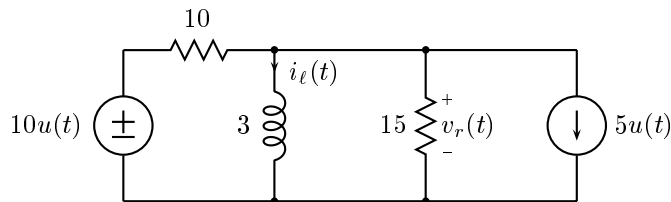- (b) We can incorporate a current source to handle the initial condition. This changes the circuit to



The time constant is the same as before. The value at $t = \infty$ is also the same as before. At $t = 0$

$$v_r(0) = 6 - 30 = -24.$$

Therefore,

$$v_r(t) = -24e^{-2t} \quad t \geq 0.$$

Problem 8.4: For the circuit in Figure 4, let $i_s(t) = 1$ for $t > 0$ and assume that at $t = 0$ the current through the inductor is zero and that the voltage drop across the capacitor terminals is 1 volt.

- (a) Redraw the circuit in the Laplace domain.
 (b) Determine $V(s)$, the Laplace transform of the resistor voltage.
 (c) Determine $v(t)$ for $t > 0$.


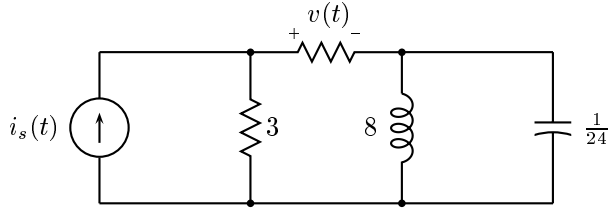


Figure 4: Circuit for Problem 8.4.

Solution:

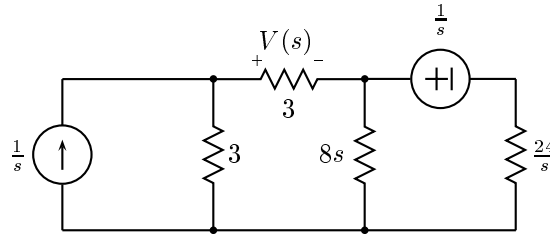- (a) We replace the inductor and capacitor by impedances and insert a voltage source to realize the initial voltage on the capacitor.



- (b) Let $\frac{1}{s}$, $I_\alpha(s)$, and $I_\beta(s)$ be mesh currents in the three meshes. Then, if we write KVL equations over the two rightmost meshes, we get

$$3[I_\alpha(s) - \frac{1}{s}] + 3I_\alpha(s) + 8s[I_\alpha(s) - I_\beta(s)] = 0$$

$$8s[I_\beta(s) - I_\alpha(s)] + \frac{24}{s}I_\beta(s) = -\frac{1}{s}.$$

We can rewrite these as

$$[8s + 6]I_\alpha(s) - 8sI_\beta(s) = \frac{3}{s}$$

$$-8sI_\alpha(s) + [8s + \frac{24}{s}]I_\beta(s) = -\frac{1}{s}$$

If we add the two equations together we get

$$6I_\alpha(s) + \frac{24}{s}I_\beta(s) = \frac{1}{s}$$

from which

$$I_\beta(s) = -\frac{s}{4}I_\alpha(s) + \frac{1}{3s}$$

If we substitute this result into the first equation, we get

$$I_\alpha(s) = \frac{\frac{4}{3}s + \frac{3}{2}}{s(s^2 + 4s + 3)}$$

Finally,

$$V(s) = 3I_\alpha(s) = \frac{4s + \frac{9}{2}}{s(s^2 + 4s + 3)}$$

(c) $V(s) = \frac{3}{s} + \frac{-\frac{1}{4}}{s+1} + \frac{-\frac{5}{4}}{s+3}$. Therefore,

$$v(t) = \frac{3}{2} - \frac{1}{4}e^{-t} - \frac{5}{4}e^{-3t}, \quad t > 0$$

Problem 8.5: In the circuit in Figure 5 solve for $v(t)$ for $t > 0$. Assume that the circuit is at initial rest.

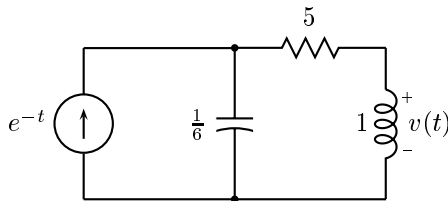


Figure 5: Circuit for Problem 8.5.

Solution: Clearly

$$V(s) = sI_\ell(s)$$

and we can determine $I_\ell(s)$ by using a current divider. Therefore,

$$V(s) = s \left(\frac{\frac{6}{s}}{s + 5 + \frac{6}{s}} \right) \left(\frac{1}{s + 1} \right) = \frac{6s}{(s + 1)(s + 2)(s + 3)}.$$

Performing a partial fraction expansion gives

$$V(s) = \frac{-3}{s + 1} + \frac{12}{s + 2} + \frac{-9}{s + 3}$$

and

$$v(t) = (-3e^{-t} + 12e^{-2t} - 9e^{-3t}) u(t).$$

The response is zero for $t < 0$ because the input is zero in that range.

Problem 8.6: In the circuit below, $v_c(0) = 8\text{V}$ and $i_\ell(0) = 4\text{A}$. Find $i_\ell(t)$ for $t > 0$.

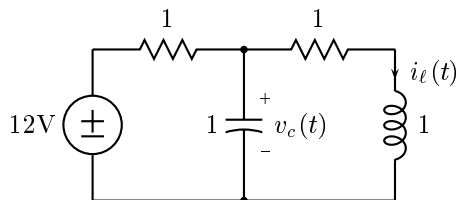


Figure 6: Circuit for Problem 8.6.

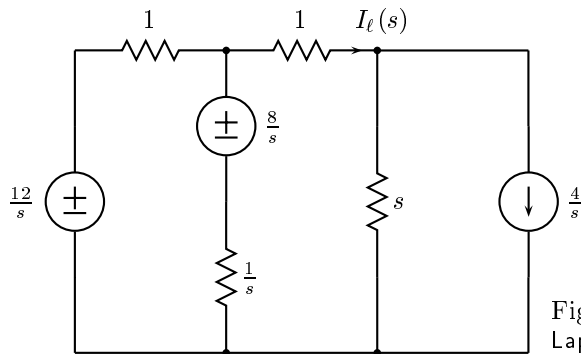


Figure 7: Circuit redrawn in the Laplace domain.

Solution: In the Laplace domain the circuit can be drawn as shown in Figure 7. Let us attack this circuit using the mesh method. Let the mesh current in the left mesh be $I(s)$, in the center mesh it is the variable of interest $I_\ell(s)$, and in the right mesh we use $\frac{4}{s}$. Then the two KCL equations are

$$-\frac{12}{s} + I(s) + \frac{8}{s} + \frac{1}{s}[I(s) - I_\ell(s)] = 0$$

$$\frac{1}{s}[I_\ell(s) - I(s)] - \frac{8}{s} + I_\ell(s) + s[I_\ell(s) - \frac{4}{s}] = 0.$$

These can be simplified to

$$I(s)[s + 1] - I_\ell(s) = 4$$

$$-I(s) + [s^2 + s + 1]I_\ell(s) = 4s + 8.$$

Solving for $I_\ell(s)$

$$I_\ell(s) = \frac{4(s^2 + 3s + 3)}{(s^2 + 2s + 2)s} = \frac{6}{s} + \frac{-1 - j}{s + 1 - j} + \frac{-1 + j}{s + 1 + j}.$$

Therefore, for $t > 0$

$$i_\ell(t) = 6 + \sqrt{2}e^{-j3\pi/4}e^{-t}e^{jt} + \sqrt{2}e^{j3\pi/4}e^{-t}e^{-jt}$$

$$= 6 + 2\sqrt{2}e^{-t}\cos(t - \frac{3\pi}{4}).$$
