

GEORGIA INSTITUTE OF TECHNOLOGY  
School of Electrical and Computer Engineering

Course ECE 2040  
Circuit Analysis

November 17, 2000

**Problem Set #12–Solutions**

**Problem 12.1:** Find  $v_{out}(t)$  if  $v_{in}(t) = 3 + 4 \sin(1000t)$ . The terminals are *open-circuited*.


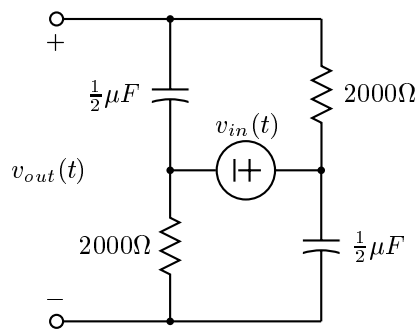


Figure 1: Circuit for Problem 12.1.

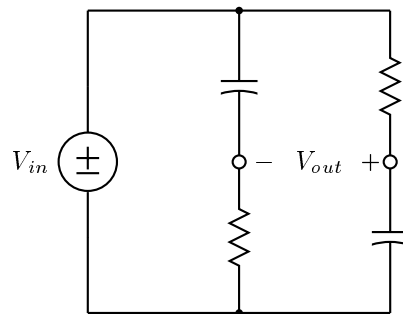**Solution:** We can redraw this circuit as



Then

$$\begin{aligned} V_{out} &= \left( \frac{\frac{1}{jC\omega}}{\frac{1}{jC\omega} + R} - \frac{R}{\frac{1}{jC\omega} + R} \right) V_{in} \\ &= \frac{1 - jRC\omega}{1 + jRC\omega} V_{in} \end{aligned}$$

Now, we observe

$$\begin{aligned} \omega = 0 : \quad V_{out} &= V_{in} \\ \omega = 1000 : \quad V_{out} &= \frac{1 - j}{1 + j} V_{in} = e^{-j\frac{\pi}{2}} V_{in} \end{aligned}$$

Therefore,

$$v_{out}(t) = 3 + 4 \sin(1000t - \frac{\pi}{2}) = 3 - 4 \cos(1000t).$$


---

**Problem 12.2:** Determine  $i(t)$  for all  $t$  for the circuit in Figure 2.

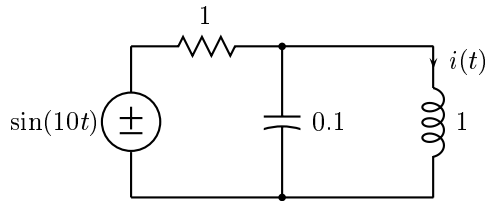


Figure 2: Circuit for Problem 12.2.

---

**Solution:**

$$H(j\omega) = \frac{I}{V_s} = \frac{1}{j\omega} \cdot \frac{\frac{10}{j\omega + j\omega}}{\frac{10}{j\omega + j\omega} + 1} = \frac{10}{10 - \omega^2 + j10\omega}$$

Letting  $\omega = 10$  gives


$$H(j10) = \frac{10}{10 - 100 + j100} = \frac{1}{\sqrt{181}} e^{j \tan^{-1}(\frac{10}{9}) - j\pi}$$

Therefore,

$$i(t) = \frac{1}{\sqrt{181}} \sin(10t + \tan^{-1}(\frac{10}{9})) = 0.074 \sin(10t + \tan^{-1}(\frac{10}{9}))$$


---

**Problem 12.3:**

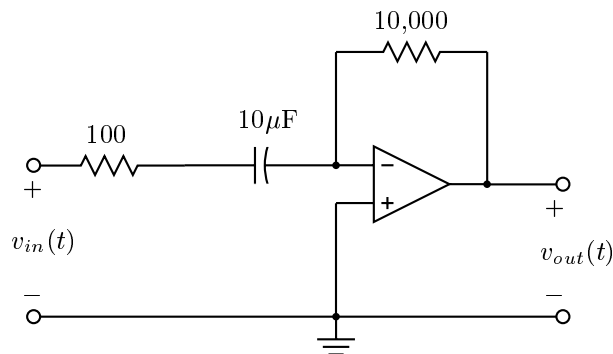

(a) Calculate the frequency response of the above circuit.



- (b) Plot the magnitude response.  
(c) Plot the phase response.

---

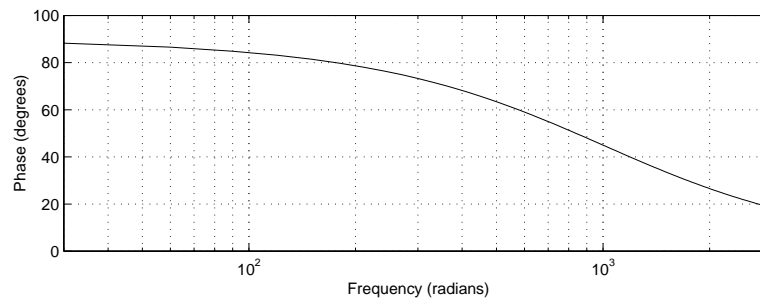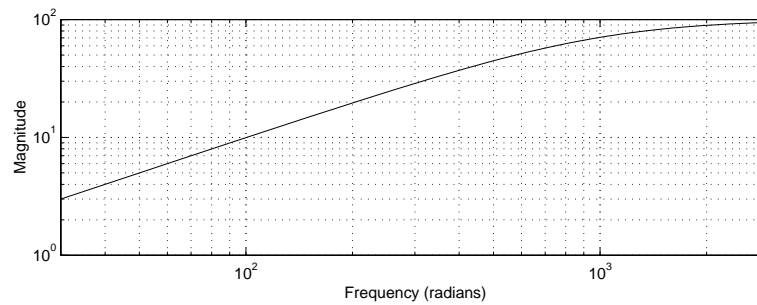**Solution:**

(a)


$$\begin{aligned}
 H(j\omega) &= -\frac{Z_f(j\omega)}{Z_i(j\omega)} = -\frac{10^4}{100 + \frac{1}{j10^{-5}\omega}} \\
 &= -\frac{j(0.1)\omega}{j0.001\omega + 1}
 \end{aligned}$$



(b,c)

---

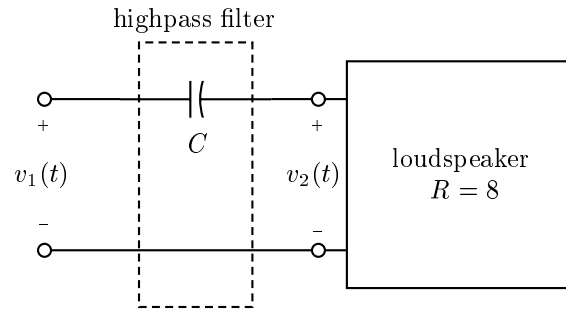
**Problem 12.4:** Many loudspeaker systems consist of two loudspeakers: the woofer, which reproduces the low frequency part of the signal, and the tweeter, which reproduces the high frequency part of the signal. A crossover network is used to select the high frequency part of the signal and feed it into the tweeter. Such a network functions as a highpass filter. The entire audio signal is applied at the terminals  $a - a'$ .



- (a) Assuming that the equivalent circuit for the tweeter consists of just a resistor with a resistance of  $R$ , plot the pole-zero pattern of the system function that relates  $v_2(t)$  to  $v_1(t)$  and sketch the frequency response curves (magnitude and angle).
- (b) If  $R = 8\Omega$ , find the value of the capacitance  $C$  so that the half-power frequency of the highpass filter is 5 kHz ( $= 2\pi(5000)$  rad/s).


---

**Solution:**

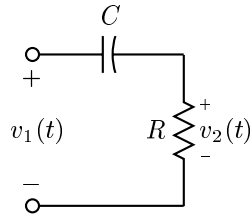


$$H(s) = \frac{R}{R + \frac{1}{Cs}} = \frac{s}{s + \frac{1}{RC}}$$

(a)

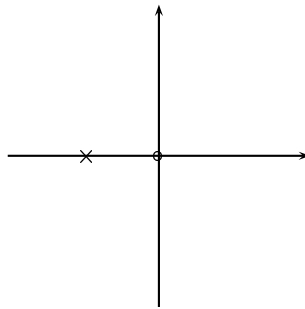

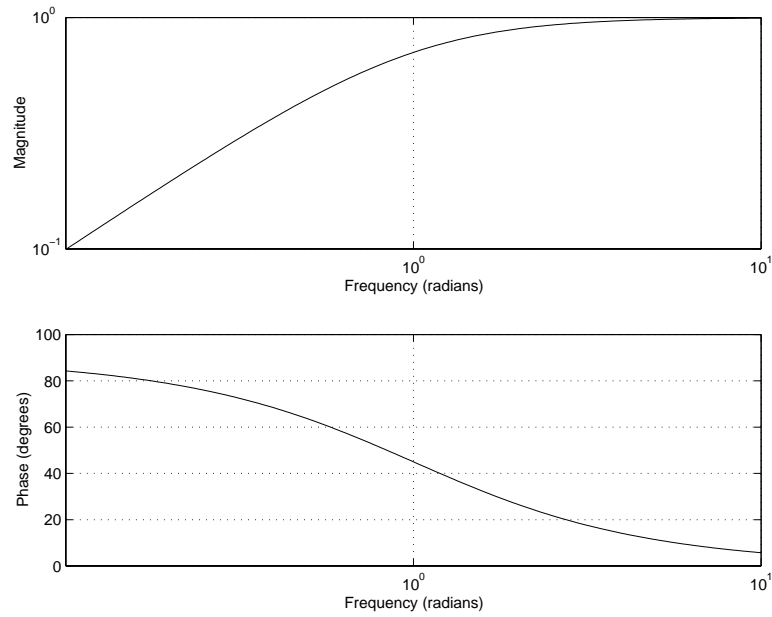Using the MATLAB function `freqs` again gives the following plot (for positive frequencies) if  $RC = 1$ .



(b)


$$\frac{1}{RC} = 2\pi(5000)$$

Thus,

$$C = \frac{1}{80,000\pi} \approx 4\mu F$$

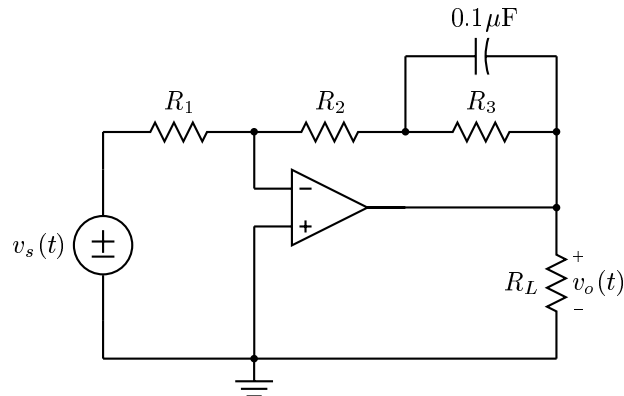**Problem 12.5:** In the circuit below the value of  $R_1$  is  $10\text{k}\Omega$ .


- Determine the values of  $R_2$  and  $R_3$  so that the gain (magnitude of the frequency response) at low frequencies is 5 and the gain at high frequencies is 2.
- Determine the frequency at which the gain is midway between these two values, i.e. the frequency at which the gain is 3.5.



---

**Solution:**

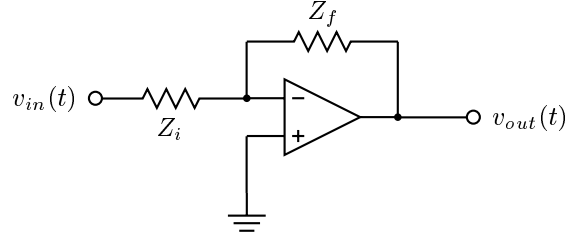(a) This circuit is a special case of an inverting amplifier as shown below.



The frequency response of such a system is known to be

$$H(j\omega) = -\frac{Z_f(j\omega)}{Z_i(j\omega)}.$$

For this circuit, the input impedance is simply

$$Z_i = R_1$$

and the other three elements contribute to the feedback impedance

$$\begin{aligned} Z_f &= R_2 + \frac{R_3 \frac{1}{j\omega C}}{R_3 + \frac{1}{j\omega C}} = R_2 + \frac{R_3}{1 + j\omega R_3 C} \\ &= \frac{(R_2 + R_3) + j\omega R_2 R_3 C}{1 + j\omega R_3 C}. \end{aligned}$$

Therefore,

$$H(j\omega) = -\frac{(R_2 + R_3) + j\omega R_2 R_3 C}{R_1(1 + j\omega R_3 C)}.$$

To measure the low frequency gain, we can let  $\omega = 0$  and take the magnitude

$$G_{LF} = \frac{R_2 + R_3}{R_1}.$$

To measure the high frequency gain, we can take the (magnitude of the) limit as  $\omega$  grows large

$$G_{HF} = \frac{R_2}{R_1}.$$

Since  $R_1 = 10k\Omega$  and we want  $G_{LF} = 5$  and  $G_{HF} = 2$ , we can substitute and solve for  $R_2$  and  $R_3$ .

$$\begin{aligned} 5 &= \frac{R_2 + R_3}{10k\Omega} \implies R_2 + R_3 = 50k\Omega \\ 2 &= \frac{R_2}{10k\Omega} \implies R_2 = 20k\Omega \end{aligned}$$

Therefore, we want to choose  $R_2 = 20k\Omega$  and  $R_3 = 30k\Omega$ .

(b) With the values substituted, the frequency response is

$$H(j\omega) = -\frac{5 + j\omega(0.6)}{1 + j\omega(0.3)}.$$

To find the value of  $\omega$  for which the magnitude is 3.5, we solve the equation

$$\frac{25 + \omega^2(0.6)^2}{1 + \omega^2(0.3)^2} = (3.5)^2.$$

This gives  $\omega = 4.14$ .

---