

GEORGIA INSTITUTE OF TECHNOLOGY  
School of Electrical and Computer Engineering

Course ECE 2040

Circuit Analysis

Assigned: September 22, 2000

Due: September 29, 2000

## Problem Set #5

---

**Reading:** Read the following sections from the class notes:

Chapter 3, Section 3.2

Chapter 4, Section 4.1, 4.2

**Reading:** Read the following sections from Dorf and Svoboda:

Chapter 3, Section 3.3–3.8; (series and parallel)

Chapter 5, Section 5.5, 5.6; (Thevenin and Norton)

Chapter 6, Section 6.3–6.5; (operational amplifiers)

---

**Announcement:** The second quiz will be held during the class hour on Friday, October 6, 2000. It will be a closed book test, although calculators are permitted (but probably not necessary). It will cover the same material that is covered in Problem Sets 3–5.

---

**Problem 5.1:** For the circuit in Figure 1 the source voltage on the left is a battery (i.e., a constant voltage source). Determine the value of  $V$  required to produce a value for  $V_o$  of 1 volt. For the

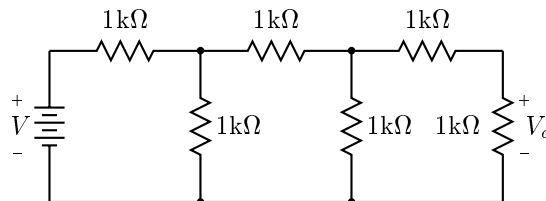


Figure 1: Circuit for Problem 5.1.

circuit in Figure 1 the source voltage on the left is a battery (i.e., a constant voltage source). Determine the value of  $V$  required to produce a value for  $V_o$  of 1 volt.

**Problem 5.2:**

- Find the Thévenin equivalent network corresponding to the two-terminal network in Figure 2.
- Find the Norton equivalent network.

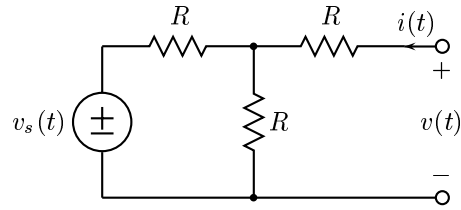


Figure 2: Circuit for Problem 5.2.

**Problem 5.3:** Sketch the Thevenin equivalent circuit corresponding to the one-port in Figure 3.

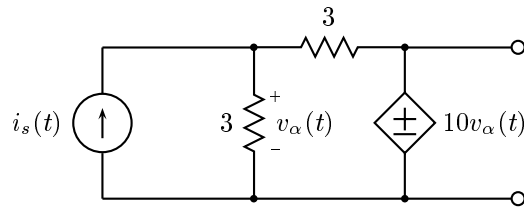


Figure 3: Circuit for Problem 5.3.

**Problem 5.4:** Consider a one-port network consisting of two capacitors with capacitances  $C_1$  and  $C_2$  connected in parallel, as shown in Figure 4.

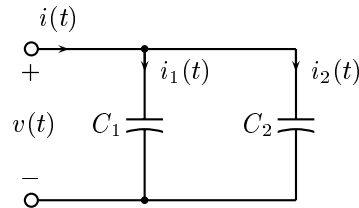


Figure 4: Two capacitors connected in parallel.

- Show that this network is equivalent to a single capacitor.
- Derive a formula for the equivalent capacitance  $C_{eq}$  in terms of  $C_1$  and  $C_2$ .
- Derive expressions for the current  $i_1(t)$  that passes through capacitor  $C_1$  and the current  $i_2(t)$  that passes through  $C_2$  in terms of the current  $i(t)$  entering the one-port.

**Problem 5.5:**

Determine  $v_{out}(t)$  in terms of  $v_{in}(t)$  for the circuit in Figure 5.

**Problem 5.6:** Find the voltage gain of the circuit in Figure 6. The voltage gain is defined as  $G = v_{out}(t)/v_{in}(t)$ .

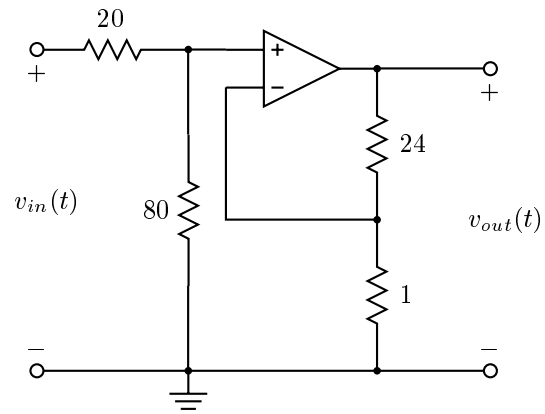


Figure 5: Circuit for Problem 5.5.

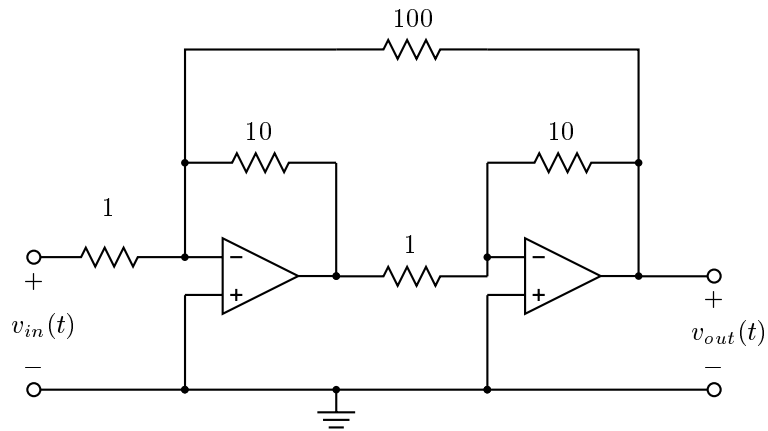


Figure 6: Circuit for Problem 5.6.