

GEORGIA INSTITUTE OF TECHNOLOGY  
School of Electrical and Computer Engineering


ECE 2040  
**Circuit Analysis**

Quiz #1 – Solutions

**Problem Q1.1:** For the circuit below the current source waveform is

$$i_s(t) = \begin{cases} e^{-t} - e^{-2t}, & t > 0 \\ 0, & t < 0 \end{cases}$$

It is known that  $v_c(-\infty) = 0$ .

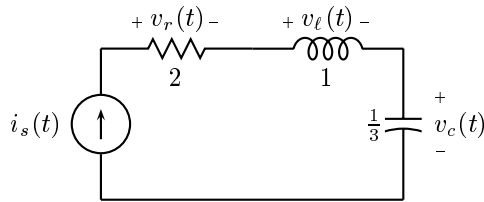

- (a) What is  $v_r(t)$ ?
- (b) What is  $v_l(t)$ ?
- (c) What is  $v_c(t)$ ?

**Solution:** The same current  $i_s(t)$  flows through all three elements.

(a)  $v_r(t) = Ri_r(t) = 2i_s(t)$ . Therefore,

$$v_r(t) = \begin{cases} 2(e^{-t} - e^{-2t}), & t > 0 \\ 0, & t < 0. \end{cases}$$

(b)  $v_l(t) = L\frac{di_s(t)}{dt}$ . Therefore,

$$v_l(t) = \begin{cases} -e^{-t} + 2e^{-2t}, & t > 0 \\ 0, & t < 0. \end{cases}$$

(c) Since


$$v_c(t) = \frac{1}{C} \int_0^t i_c(\tau) d\tau.$$

Since  $v_c(-\infty) = 0$  and  $i_c(t) = 0$ ,  $t < 0$ , we must have  $v_c(0) = 0$ . This specifies the constant of integration.

$$v_c(t) = \begin{cases} -3e^{-t} + \frac{3}{2}e^{-2t} + \frac{3}{2}, & t > 0 \\ 0, & t < 0 \end{cases}$$

---

**Problem Q1.2:**

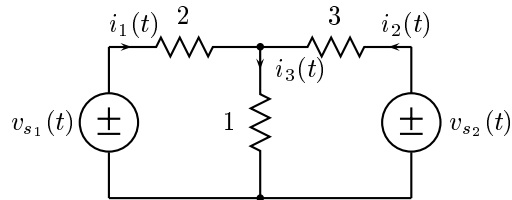

- For the above circuit write a sufficient set of KCL equations needed to find the equilibrium solution. These should be in terms of the variables  $i_1(t)$ ,  $i_2(t)$ , and  $i_3(t)$ .
- Write a sufficient set of KVL equations to find the equilibrium solution. These should also be in terms of the variables  $i_1(t)$ ,  $i_2(t)$ , and  $i_3(t)$ .
- Express your complete set of equations in matrix-vector form. You do not need to solve them.

---

**Solution:** Since we recognize that  $i_1(t)$  and  $i_2(t)$  are the currents flowing through the two voltage sources, we need only write one KCL equation and two KVL equations.

(a)

$$i_1(t) + i_2(t) - i_3(t) = 0$$

(b)

$$\text{KVL1: } 2i_1(t) + i_3(t) = v_{s1}(t)$$


$$\text{KVL2: } -i_3(t) + 3i_2(t) = -v_{s2}(t)$$

(c) In matrix-vector form these become

$$\begin{bmatrix} 1 & 1 & -1 \\ 2 & 0 & 1 \\ 0 & 3 & -1 \end{bmatrix} \begin{bmatrix} i_1(t) \\ i_2(t) \\ i_3(t) \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \\ 0 \end{bmatrix} v_{s1}(t) + \begin{bmatrix} 0 \\ 0 \\ -1 \end{bmatrix} v_{s2}(t).$$

---

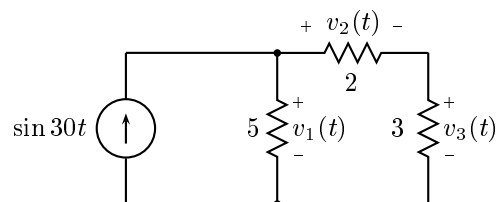**Problem Q1.3:** Solve the circuit below for  $v_1(t)$ ,  $v_2(t)$ , and  $v_3(t)$ .



---

**Solution:** We need to write 2 KCL equations and one KVL equation. If we write these in terms of the voltage variables, we save time.

$$\text{KCL1: } \frac{v_1(t)}{5} + \frac{v_2(t)}{2} = \sin 30t$$

$$\text{KCL2: } \frac{v_2(t)}{2} - \frac{v_3(t)}{3} = 0$$

$$\text{KVL: } -v_1(t) + v_2(t) + v_3(t) = 0$$

From the second equation we know that  $v_3(t) = \frac{3}{2}v_2(t)$ . Substituting this fact into the third equation gives

$$-v_1(t) + v_2(t) + \frac{3}{2}v_2(t) = 0$$

from which we learn that  $v_1(t) = \frac{5}{2}v_2(t)$ . Substituting this fact into the first equation gives

$$\frac{v_2(t)}{2} + \frac{v_2(t)}{2} = \sin 30t$$

or

$$v_2(t) = \sin 30t.$$


Therefore,

$$v_1(t) = \frac{5}{2} \sin 30t$$

$$v_3(t) = \frac{3}{2} \sin 30t.$$

---

**Problem Q1.4:**

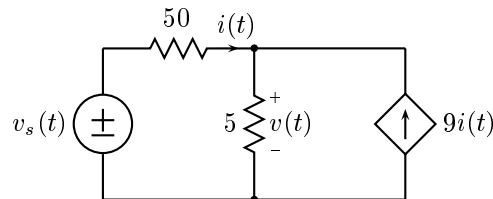

In the circuit above the only variables of interest are  $i(t)$  and  $v(t)$ .

- Using the basic network as your guide write a minimal set of KCL equations in terms of  $i(t)$  and  $v(t)$  to specify the equilibrium solution.
- Write a similar set of KVL equations.
- Solve these for  $i(t)$  and  $v(t)$ .

---

**Solution:**

- (a) Since the basic network contains only two nodes, we need only one KCL equation. We will get the same equation from either node:

$$i(t) - \frac{v(t)}{5} + 9i(t) = 0.$$

Rewriting allows us to replace this by

$$10i(t) - \frac{v(t)}{5} = 0.$$

- (b) The basic network contains only a single mesh. Therefore, we need only one KVL equation.

$$50i(t) + v(t) = v_s(t).$$

- (c) To solve these, multiply the KCL equation by 5 and add the two equations together. This gives

$$100i(t) = v_s(t)$$

or

$$i(t) = \frac{1}{100}v_s(t).$$

Substituting this result into either of the two original equations gives

$$v(t) = \frac{1}{2}v_s(t).$$

---