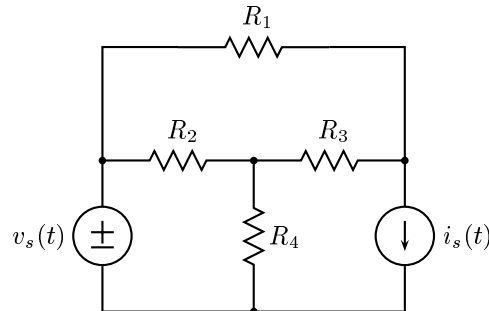


GEORGIA INSTITUTE OF TECHNOLOGY
School of Electrical and Computer Engineering

ECE 2040
Circuit Analysis

Quiz #2-Solutions

Problem Q2.1:



- For the circuit above, what is the minimum number of KCL equations that need to be written to specify the equilibrium solution?
- Select one of the nodes of the basic network as the ground node and label it. Define node potentials at the remaining nodes of the basic network and write a KCL equation at each of these nodes in terms of the node potentials (and the source waveforms).
- Put your equations in matrix-vector form with the node potentials as unknowns. You do not need to solve the equations.

Solution:


- The basic network contains three nodes. Therefore, we need to write at least two KCL equations.
- Select the (super)node at the bottom as the ground. We then write KCL equations at the two nodes connected to resistor R_3 . Let these node potentials be denoted $e_a(t)$ (left node) and $e_b(t)$ (right node). Then the two KCL equations are

$$\begin{aligned}\frac{1}{R_2}[e_a(t) - v_s(t)] + \frac{1}{R_4}e_a(t) + \frac{1}{R_3}[e_a(t) - e_b(t)] &= 0 \\ \frac{1}{R_3}[e_b(t) - e_a(t)] + \frac{1}{R_1}[e_b(t) - v_s(t)] &= -i_s(t)\end{aligned}$$

-

$$\begin{bmatrix} \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} & -\frac{1}{R_3} \\ -\frac{1}{R_3} & \frac{1}{R_1} + \frac{1}{R_3} \end{bmatrix} \begin{bmatrix} e_a(t) \\ e_b(t) \end{bmatrix} = \begin{bmatrix} \frac{1}{R_2} \\ \frac{1}{R_1} \end{bmatrix} v_s(t) + \begin{bmatrix} 0 \\ -1 \end{bmatrix} i_s(t)$$

Problem Q2.2:

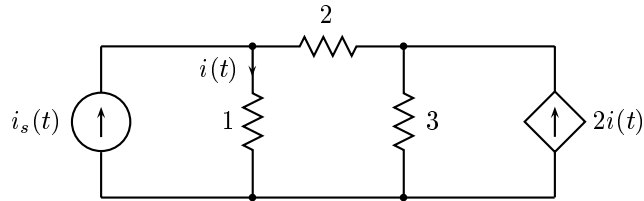

- For the circuit above, what is the minimum number of KVL equations that need to be written to specify the equilibrium solution?
- Define a mesh current for each mesh of the basic network. Write a sufficient set of KVL equations in terms of the mesh currents and the source waveforms.
- Solve your equations and use the results to determine $i(t)$.


Solution:

- There is one mesh in the basic network. Therefore, we need only a single KVL equation.
- Let $i_\alpha(t)$ be the mesh current in the center mesh.

$$[i_\alpha(t) - i_s(t)] + 2i_\alpha(t) + 3[i_\alpha(t) + 2(i_s(t) - i_\alpha(t))] = 0$$

- Unfortunately, because of a particularly poor choice of element values, the above equation is singular. It is satisfied only for the unreasonable value, $i_\alpha = \infty$, which produces an infinite value for $i(t)$. Grading for this part of the problem is based on the reasonableness of your approach.
-

Problem Q2.3:

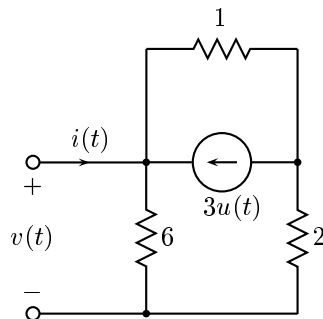

- (a) For the above two-terminal network, determine the open-circuit voltage $v_{oc}(t)$.
- (b) Determine the short-circuit current, $i_{sc}(t)$.
- (c) Determine and sketch the Norton equivalent network.

Solution:

(a) When the terminals are open circuited, the current source sees an 8Ω resistor connected in parallel with a 1Ω one. The current flowing through the 6Ω resistor is

$$\frac{1}{1+8}3u(t) = \frac{1}{3}u(t)$$


and the voltage drop across that resistor is

$$v_{oc}(t) = 6 \cdot \frac{1}{3}u(t) = 2u(t).$$


(b) When the terminals are short circuited, the current source sees a 2Ω resistor connected in parallel with a 1Ω one. The short-circuit current is the current flowing through the 2Ω resistor, which is one-third of the current coming from the source. (Be careful with the sign!)

$$i_{sc}(t) = -u(t)$$

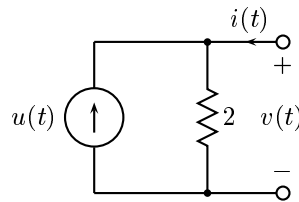(c) The Norton equivalent network is sketched below.




Problem Q2.4:

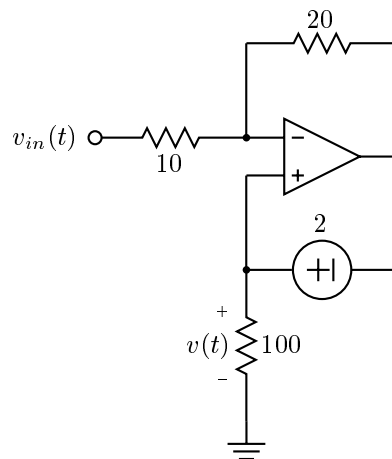

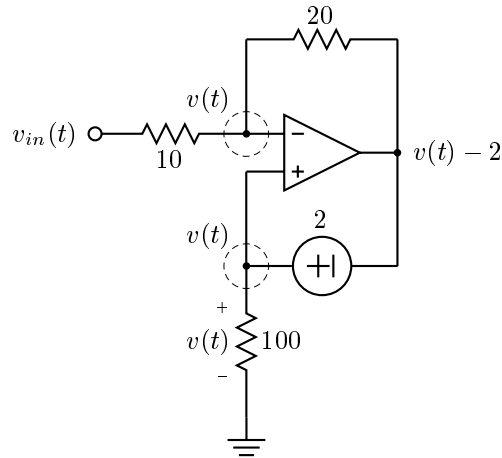- (a) Circle the nodes at which you can write valid KCL equations.
- (b) Label the potential of each node in the circuit.
- (c) Solve for $v(t)$.

Solution:

(a,b) The nodes are circled and the node potentials are labeled in the following figure.



(c) Writing a KCL equation at the upper of the two valid nodes gives:

$$\frac{v(t) - v_{in}(t)}{10} + \frac{v(t) - v(t) + 2}{20} = 0$$

or

$$v(t) = v_{in}(t) - 1.$$