

GEORGIA INSTITUTE OF TECHNOLOGY  
School of Electrical and Computer Engineering

ECE 2040  
**Circuit Analysis**

Quiz #4–Solutions

**Problem Q4.1:** A circuit with input source waveform  $x_{in}(t)$  and output  $y_{out}(t)$  has the system function

$$H(s) = \frac{s}{(s+2)^2 + 100}.$$

Determine  $y_{out}(t)$ , if

$$x_{in}(t) = 3 \cos(10t).$$

**Solution:** Since  $x_{in}(t) = \Re\{3e^{j10t}\}$ , we know that

$$\begin{aligned} y_{out}(t) &= \Re\{3H(j10)e^{j10t}\} = \Re\left\{\frac{j30}{4+j40}e^{j10t}\right\} \\ &= \Re\left\{0.7463e^{\tan^{-1}(0.1)}e^{j10t}\right\} \\ &= 0.7463 \cos(10t + \tan^{-1}(0.1)). \end{aligned}$$

**Problem Q4.2:**

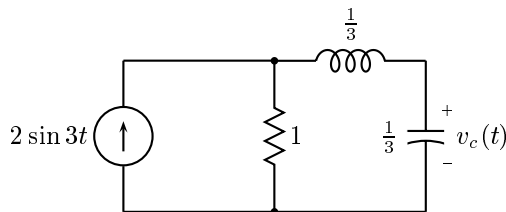


Figure 1: Circuit for Problem Q4.2.

- (a) Find the system function of the circuit in Figure 1.
- (b) Find  $v_c(t)$  for all  $t$ .

**Solution:**

(a) The system function is

$$H(s) = \frac{V_c(s)}{I_s(s)} = \frac{3}{s} \frac{1}{\frac{1}{3}s + 1 + \frac{3}{s}} = \frac{9}{s^2 + 3s + 9}$$

(b) Since

$$H(j3) = \frac{1}{j} = -j = e^{-\frac{\pi}{2}},$$

we have

$$v_c(t) = \Im(2e^{j3t - \frac{\pi}{2}}) = -2 \cos(3t).$$

**Problem Q4.3:** A circuit has the pole-zero plot shown in Figure 2.

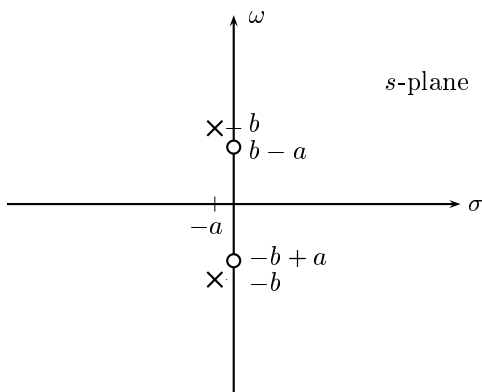


Figure 2: A pole-zero plot for Problem Q4.3.

- (a) Graph the magnitude response of the filter. Indicate key frequencies on your plot.
- (b) Determine the phase at the following frequencies:
- (i)  $\omega = 0$ .
  - (ii)  $\omega = \infty$ .
  - (iii)  $\omega = b - a - \epsilon$ ,  $\epsilon =$  a very small number.
  - (iv)  $\omega = b - a + \epsilon$ .
  - (v)  $\omega = a + b$ .

**Solution:**

- (a) The magnitude is plotted in Figure 3.


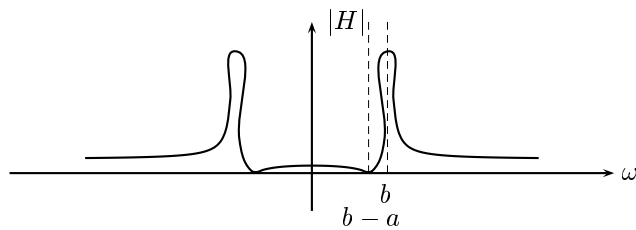


Figure 3: Magnitude response for Problem Q4.3.

- (b) (i)  $\angle H(j0) = \frac{\pi}{2} - \frac{\pi}{2} - \frac{\pi}{2} + \frac{\pi}{2} = 0$ .  
(ii)  $\angle H(j\infty) = \frac{\pi}{2} + \frac{\pi}{2} - \frac{\pi}{2} - \frac{\pi}{2} = 0$ .  
(iii) At this frequency the phase should be slightly negative.  
(iv) As the frequency response passes through the zero the phase should jump up by  $\pi$  radians. Thus the phase should be  $\pi$  greater than the result in (c).  
(v)  $\angle H(j(a+b)) \approx \frac{\pi}{2} + \frac{\pi}{2} - \frac{\pi}{2} - \frac{\pi}{4} = \frac{\pi}{4}$ .
- 

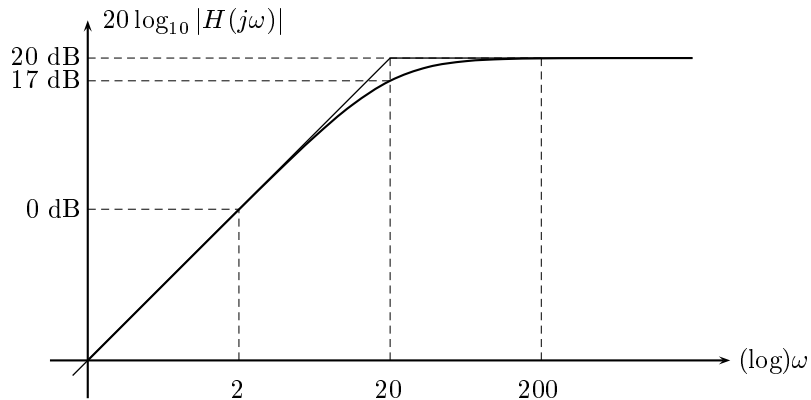**Problem Q4.4:** A stable circuit (i.e. one with all of its poles in the left half of the  $s$ -plane) has the Bode magnitude plot shown below.



- (a) Determine the locations of all of the poles and zeros of the circuit.  
(b) Determine the system function of the circuit,  $H(s)$ .  
(c) Draw the Bode phase plot (asymptotes only). Clearly label your plot.

---

**Solution:**

- (a) There is a break frequency at 20 rad/s at which the slope is reduced from 20 dB/decade to 0 dB/decade. This implies a pole at  $s = -20$ . There are no other breakpoints. The slope of 20 dB/decade extending to the left is caused by a zero at the origin. Therefore, there is a single zero at  $s = 0$  and a single pole at  $s = -20$ .  
(b)

$$H(s) = \frac{10s}{s + 20}$$

From the magnitude plot, the high frequency gain of the filter is 10 (=20 dB). Thus we need the constant 10 in the numerator.

- (c) From the system function we can plot the phase response.

