

GEORGIA INSTITUTE OF TECHNOLOGY
School of Electrical and Computer Engineering

Course ECE 2040

Circuit Analysis

Assigned: March 31, 2000

Due: April 7, 2000

Problem Set #11

Reading: Read the following sections from the class notes:

Chapter 8, Sections 8.3.3, 8.3.4

Chapter 9, Sections 9.2.2, 9.3


Reading: Read the following sections from Irwin and Wu:

Chapter 8, Sections 8.8


Chapter 12, 12.1

Chapter 14, 14.5

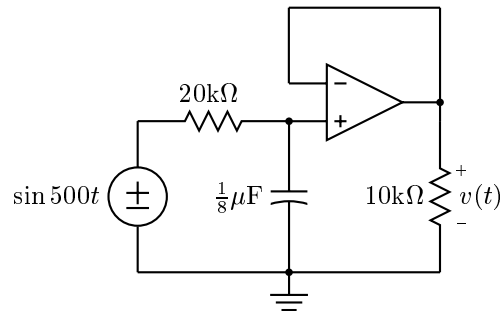Problem 11.1: For the circuit below find $v(t)$.



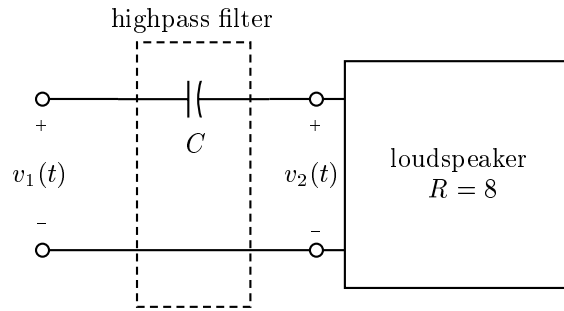
Problem 11.2: Many loudspeaker systems consist of two loudspeakers: the woofer, which reproduces the low frequency part of the signal, and the tweeter, which reproduces the high frequency part of the signal. A crossover network is used to select the high frequency part of the signal and feed it into the tweeter. Such a network functions as a highpass filter. The entire audio signal is applied at the terminals $a - a'$.



- (a) Assuming that the equivalent circuit for the tweeter consists of just a resistor with a resistance of R , plot the pole-zero pattern of the system function that relates $v_2(t)$ to $v_1(t)$ and sketch the frequency response curves (magnitude and angle).
- (b) If $R = 8\Omega$, find the value of the capacitance C so that the half-power frequency of the highpass filter is 5 kHz ($= 2\pi(5000)$ rad/s).

Problem 11.3: In the circuit below the value of R_1 is $10\text{k}\Omega$.

- (a) Determine the values of R_2 and R_3 so that the gain (magnitude of the frequency response) at low frequencies is 5 and the gain at high frequencies is 2.
- (b) Determine the frequency at which the gain is midway between these two values, i.e. the frequency at which the gain is 3.5.

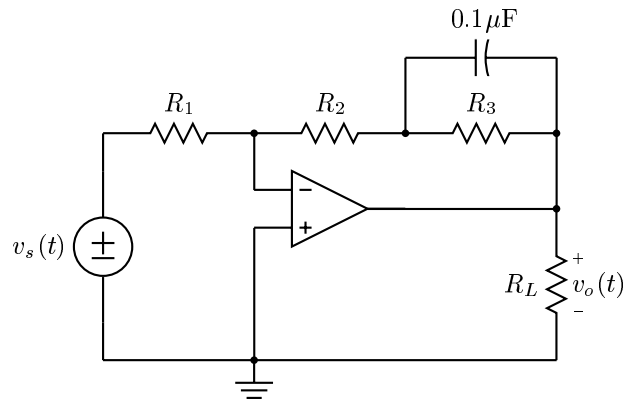

Problem 11.4: A circuit has the system function

$$H(s) = \frac{s^2 + b^2}{(s + a)^2 + b^2}$$

where $b \gg a$.

- (a) Draw the pole-zero plot. Clearly label the locations of the poles and zeros on your plots.
- (b) Sketch the magnitude of the frequency response of the filter.

Problem 11.5: An oscillator is a circuit whose system function has a pair of complex conjugate poles located on the $j\omega$ -axis in the s -plane. It is capable of supporting a sustained oscillation, i.e., once started it will continue to produce a sinusoidal output $v_{out}(t)$. In the network below determine the value of K for which the system will oscillate and determine the frequency of oscillation.

