


GEORGIA INSTITUTE OF TECHNOLOGY
School of Electrical and Computer Engineering

Course ECE 2040
Circuit Analysis

April 7, 2000

Problem Set #11–Solutions

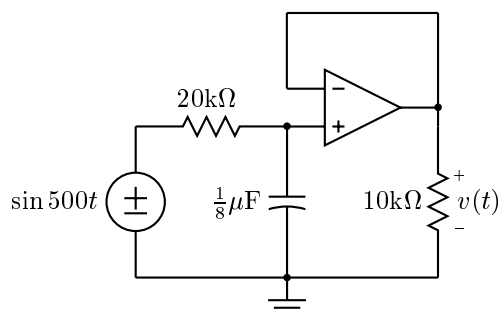Problem 11.1: For the circuit below find $v(t)$.



Solution: The opamp acts like a voltage follower, i.e., $v(t)$ is equal to the voltage across the capacitor. Furthermore, we know that $v(t)$ is of the form

$$v(t) = \Im m [V e^{j500t}].$$


To determine V , replace the source by a complex exponential time function, the elements by their equivalent impedances, and use the voltage divider.

$$V = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC}.$$

Letting $R = 20 \times 10^3$; $C = 0.125 \times 10^{-6}$, $\omega = 500$, we get


$$\begin{aligned} V &= \frac{1}{1 + j(20 \times 10^3)(0.125 \times 10^{-6})(500)} = \frac{1}{1 + j(1.25)} \\ &= 0.625 e^{-j \tan^{-1} 1.25} \\ v(t) &= 0.625 \sin(500t - \tan^{-1} 1.25). \end{aligned}$$

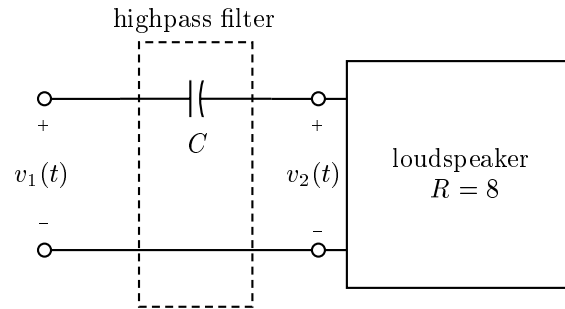Problem 11.2: Many loudspeaker systems consist of two loudspeakers: the woofer, which reproduces the low frequency part of the signal, and the tweeter, which reproduces the high frequency part of the signal. A crossover network is used to select the high frequency part of the signal and feed it into the tweeter. Such a network functions as a highpass filter. The entire audio signal is applied at the terminals $a - a'$.




- (a) Assuming that the equivalent circuit for the tweeter consists of just a resistor with a resistance of R , plot the pole-zero pattern of the system function that relates $v_2(t)$ to $v_1(t)$ and sketch the frequency response curves (magnitude and angle).
- (b) If $R = 8\Omega$, find the value of the capacitance C so that the half-power frequency of the highpass filter is 5 kHz ($= 2\pi(5000)$ rad/s).

Solution:

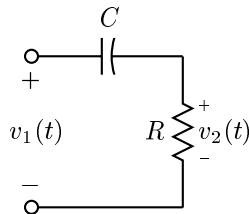


$$H(s) = \frac{R}{R + \frac{1}{Cs}} = \frac{s}{s + \frac{1}{RC}}$$

(a)

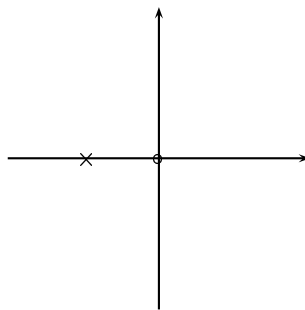

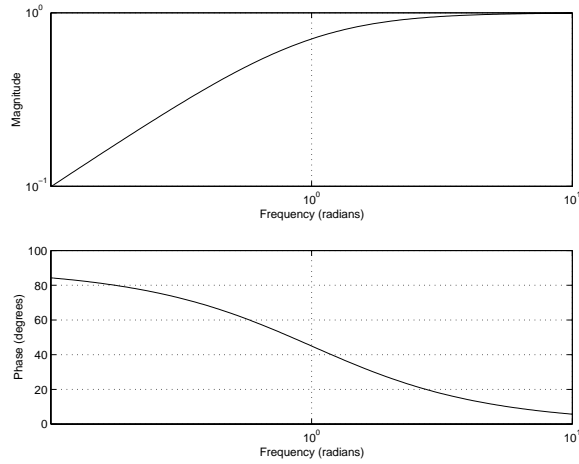Using the MATLAB function `freqs` again gives the following plot (for positive frequencies) if $RC = 1$.



(b)


$$\frac{1}{RC} = 2\pi(5000)$$

Thus,

$$C = \frac{1}{80,000\pi} \approx 4\mu F$$

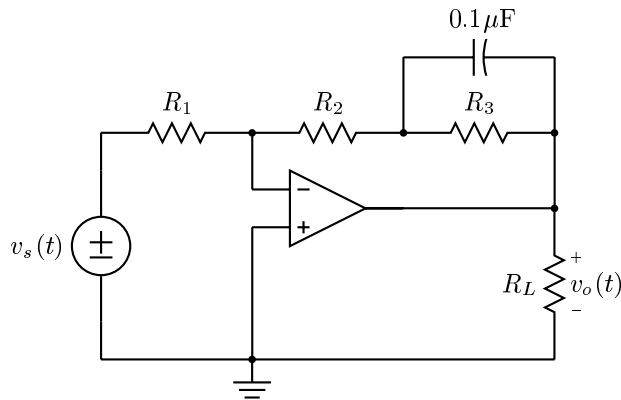
Problem 11.3: In the circuit below the value of R_1 is $10k\Omega$.

- Determine the values of R_2 and R_3 so that the gain (magnitude of the frequency response) at low frequencies is 5 and the gain at high frequencies is 2.
- Determine the frequency at which the gain is midway between these two values, i.e. the frequency at which the gain is 3.5.



Solution:

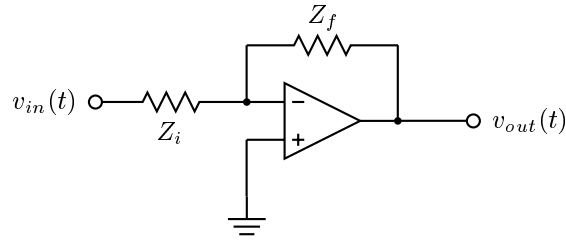- This circuit is a special case of an inverting amplifier as shown below.



The frequency response of such a system is known to be

$$H(j\omega) = -\frac{Z_f(j\omega)}{Z_i(j\omega)}.$$

For this circuit, the input impedance is simply

$$Z_i = R_1$$

and the other three elements contribute to the feedback impedance

$$\begin{aligned} Z_f &= R_2 + \frac{R_3 \frac{1}{j\omega C}}{R_3 + \frac{1}{j\omega C}} = R_2 + \frac{R_3}{1 + j\omega R_3 C} \\ &= \frac{(R_2 + R_3) + j\omega R_2 R_3 C}{1 + j\omega R_3 C}. \end{aligned}$$

Therefore,

$$H(j\omega) = -\frac{(R_2 + R_3) + j\omega R_2 R_3 C}{R_1(1 + j\omega R_3 C)}.$$

To measure the low frequency gain, we can let $\omega = 0$ and take the magnitude

$$G_{LF} = \frac{R_2 + R_3}{R_1}.$$

To measure the high frequency gain, we can take the (magnitude of the) limit as ω grows large

$$G_{HF} = \frac{R_2}{R_1}.$$

Since $R_1 = 10k\Omega$ and we want $G_{LF} = 5$ and $G_{HF} = 2$, we can substitute and solve for R_2 and R_3 .

$$\begin{aligned} 5 &= \frac{R_2 + R_3}{10k\Omega} \implies R_2 + R_3 = 50k\Omega \\ 2 &= \frac{R_2}{10k\Omega} \implies R_2 = 20k\Omega \end{aligned}$$

Therefore, we want to choose $R_2 = 20k\Omega$ and $R_3 = 30k\Omega$.

(b) With the values substituted, the frequency response is

$$H(j\omega) = -\frac{5 + j\omega(0.6)}{1 + j\omega(0.3)}.$$

To find the value of ω for which the magnitude is 3.5, we solve the equation

$$\frac{25 + \omega^2(0.6)^2}{1 + \omega^2(0.3)^2} = (3.5)^2.$$

This gives $\omega = 4.14$.


Problem 11.4: A circuit has the system function

$$H(s) = \frac{s^2 + b^2}{(s + a)^2 + b^2}$$


where $b \gg a$.

- (a) Draw the pole-zero plot. Clearly label the locations of the poles and zeros on your plots.
 (b) Sketch the magnitude of the frequency response of the filter.


Solution:

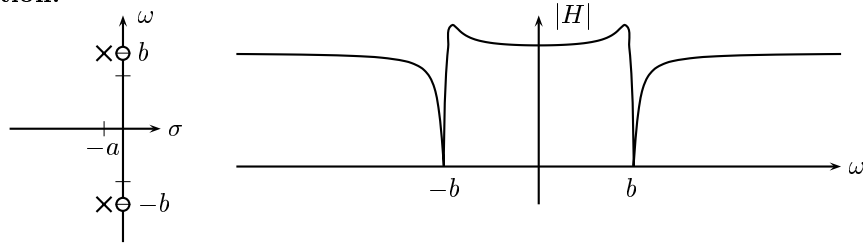

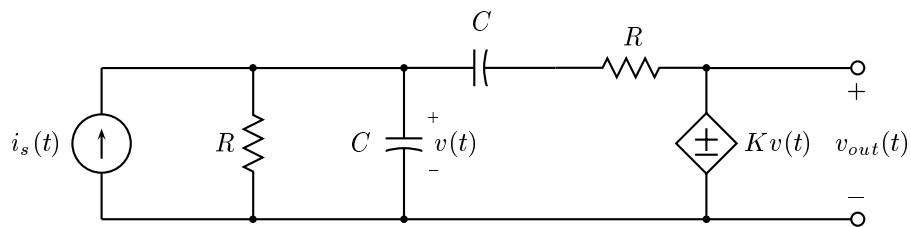Problem 11.5: An oscillator is a circuit whose system function has a pair of complex conjugate poles located on the $j\omega$ -axis in the s -plane. It is capable of supporting a sustained oscillation, i.e., once started it will continue to produce a sinusoidal output $v_{out}(t)$. In the network below determine the value of K for which the system will oscillate and determine the frequency of oscillation.



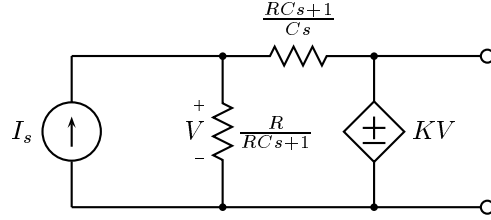Solution: To begin we can simplify the circuit in the Laplace domain by replacing the elements in series and in parallel by their equivalent impedances. This gives the circuit shown below.



Since $V_{out} = KV$, this is not included on the figure. Let the mesh current in the right mesh be $I(s)$ (and the mesh current in the left mesh be $I_s(s)$). Then

$$(I(s) - I_s(s))\frac{R}{RCs + 1} + I(s)\left(\frac{RCs + 1}{Cs}\right) - K(I(s) - I_s(s))\frac{R}{RCs + 1} = 0$$

We can solve this equation for the system function $H(s) = \frac{I(s)}{I_s(s)}$.

$$H(s) = \frac{(1 - K)RCs}{(1 - K)RCs + R^2C^2s^2 + 2RCs + 1} = \frac{\frac{1-K}{RC}s}{s^2 + \frac{3-K}{RC}s + \frac{1}{R^2C^2}}$$

From this we see that the poles will lie on the imaginary axis when $K = 3$. When $K = 3$, the poles lie at $\pm \frac{1}{RC}$, so the frequency of oscillation is $\omega_0 = \frac{1}{RC}$.
