

GEORGIA INSTITUTE OF TECHNOLOGY
School of Electrical and Computer Engineering

Course ECE 2040

Circuit Analysis

Assigned: January 21, 2000

Due: January 28, 2000

Problem Set #2


Reading: Read the following sections from the class notes:

Chapter 2, Sections 2.1.1–2.1.3


Appendix A, All sections

Note: None of the material appears in Irwin and Wu.

Problem 2.1: Find $v(t)$ in the following circuit. You may use MATLAB to help solve the equations if you wish.

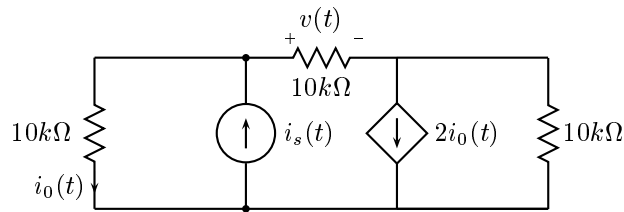

Problem 2.2: In the circuit below determine $v(t)$ in terms of $v_s(t)$ and $i_s(t)$.

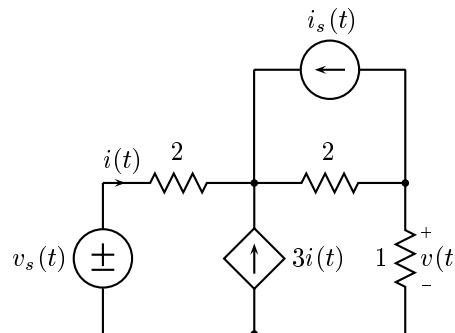

Problem 2.3: This problem is concerned with the three networks shown in Figure 1.

(a) For the network in (a)


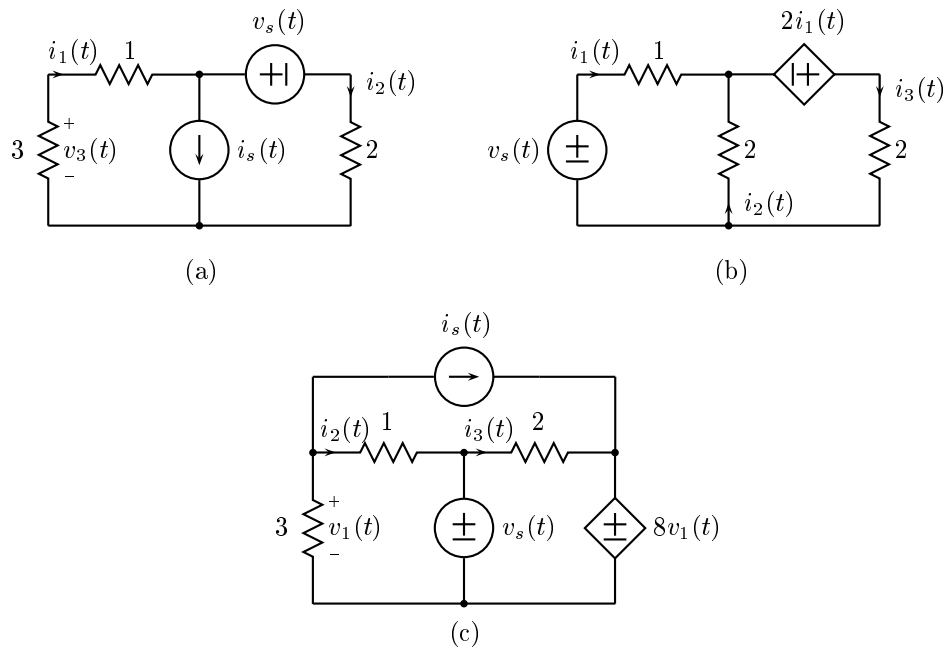


Figure 1: Networks for Problem 2.1.

- (i.) Draw the basic network.
 - (ii.) Identify the closed paths in the original network that correspond to meshes in the basic network.
 - (iii.) Identify the closed surfaces in the original network that correspond to nodes in the basic network.
- (b) Repeat for the network in (b).
- (c) Repeat for the network in (c).

Problem 2.4:

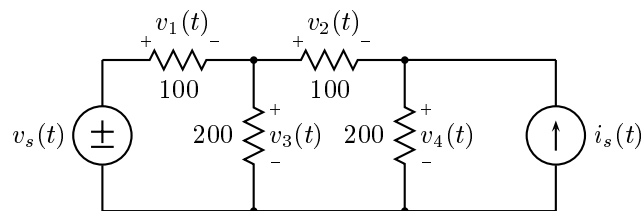

- (a) Determine the number of KCL and KVL equations that we will have to write in order to find all four voltages, $v_1(t)$, $v_2(t)$, $v_3(t)$, and $v_4(t)$.
- (b) Write a complete set of linear equations that must be solved to find the equilibrium solution.

(c) Use MATLAB to find $v_1(t)$, $v_2(t)$, $v_3(t)$, and $v_4(t)$. Each voltage should be of the form

$$v_k(t) = a_k v_s(t) + b_k i_s(t).$$

Problem 2.5: (Irwin and Wu, problem 2.101.) For the network below, choose the values of R_{in} and R_o such that $v_o(t)$ is maximized. What is the resulting ratio $|v_o(t)/v_s(t)|$?

