

GEORGIA INSTITUTE OF TECHNOLOGY  
School of Electrical and Computer Engineering

Course ECE 2040  
Circuit Analysis

February 11, 2000

Problem Set #4–Solutions

---

**Problem 4.1:** Find the  $v - i$  relation of the two-terminal network shown in Figure 1.

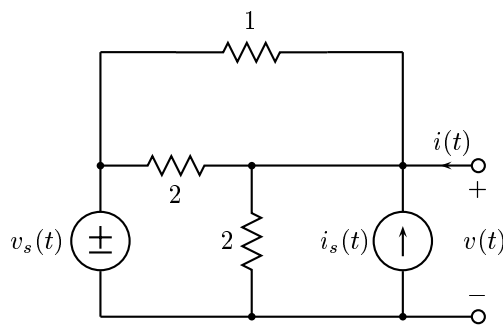


Figure 1: Two-port network for Problem 4.1.

---

**Solution:** For this circuit, we can find the  $v - i$  relation by using the node method. Let the node connected to the  $-$  terminal be the ground. Then the potential at the node connected to the  $+$  terminal is  $v(t)$ . Writing a KCL at this node provides the relation

$$\frac{1}{2}[v(t) - v_s(t)] + \frac{1}{2}v(t) - i_s(t) - i(t) + [v(t) - v_s(t)] = 0.$$

This simplifies to

$$2v(t) = \frac{3}{2}v_s(t) + i_s(t) + i(t)$$

or

$$v(t) = \frac{1}{2}i(t) + \frac{3}{4}v_s(t) + \frac{1}{2}i_s(t)$$

which is the desired  $v - i$  relation. This problem could also be solved by a number of other means including using source superposition.

---


**Problem 4.2:** You have a box containing an unlimited number of  $10\text{K}\Omega$  resistors. Show how to connect some of these together to construct equivalent resistances with the following values:

- (a)  $20\text{K}\Omega$
- (b)  $25\text{K}\Omega$
- (c)  $6667\Omega$


---

**Solution:**


(a)

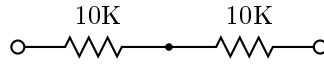

(b)

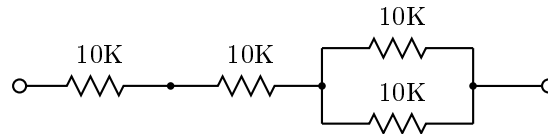

(c)

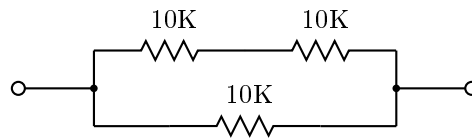

**Problem 4.3:** Consider a one-port network consisting of two capacitors with capacitances  $C_1$  and  $C_2$  connected in series, as shown in Figure 2.

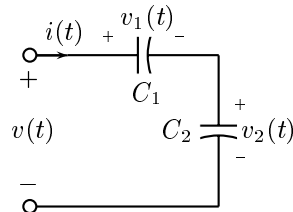


Figure 2: Two capacitors connected in series.

- (a) Show that this network is equivalent to a single capacitor.
- (b) Derive a formula for the equivalent capacitance  $C_{eq}$  in terms of  $C_1$  and  $C_2$ .
- (c) Derive expressions for the voltage  $v_1(t)$  measured across capacitor  $C_1$  and the voltage  $v_2(t)$  measured across  $C_2$  in terms of the voltage  $v(t)$  appearing across the series connection.

---

**Solution:**

(a) We know that

$$\begin{aligned}i(t) &= C_1 \frac{dv_1(t)}{dt} \implies \frac{dv_1(t)}{dt} = \frac{i(t)}{C_1} \\i(t) &= C_2 \frac{dv_2(t)}{dt} \implies \frac{dv_2(t)}{dt} = \frac{i(t)}{C_2}\end{aligned}$$

and from KVL we know

$$v(t) = v_1(t) + v_2(t).$$

Taking a derivative of both sides gives

$$\frac{dv(t)}{dt} = \frac{dv_1(t)}{dt} + \frac{dv_2(t)}{dt} = \frac{i(t)}{C_1} + \frac{i(t)}{C_2}.$$

Therefore,

$$\frac{dv(t)}{dt} = \frac{i(t)}{C_1} + \frac{i(t)}{C_2}$$

or

$$i(t) = \left( \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} \right) \frac{dv(t)}{dt}$$

and the current is seen to be proportional to the first derivative of the voltage.

(b) From part (a) we see

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}.$$

(c) We know that

$$i(t) = \left( \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} \right) \frac{dv(t)}{dt} = C_1 \frac{dv_1(t)}{dt}.$$

Therefore,

$$\frac{dv_1(t)}{dt} = \frac{\frac{1}{C_1}}{\frac{1}{C_1} + \frac{1}{C_2}} \frac{dv(t)}{dt}.$$

Integrating both sides gives the desired result:

$$v_1(t) = \frac{\frac{1}{C_1}}{\frac{1}{C_1} + \frac{1}{C_2}} v(t).$$

Similarly

$$v_2(t) = \frac{\frac{1}{C_2}}{\frac{1}{C_1} + \frac{1}{C_2}} v(t).$$

**Problem 4.4:** Two two-terminal networks,  $N_1$  and  $N_2$ , have the  $v - i$  relations

$$\begin{aligned}N_1 : \quad v(t) &= R_1 i(t) + v_{T1} \\N_2 : \quad v(t) &= R_2 i(t) + v_{T2}.\end{aligned}$$

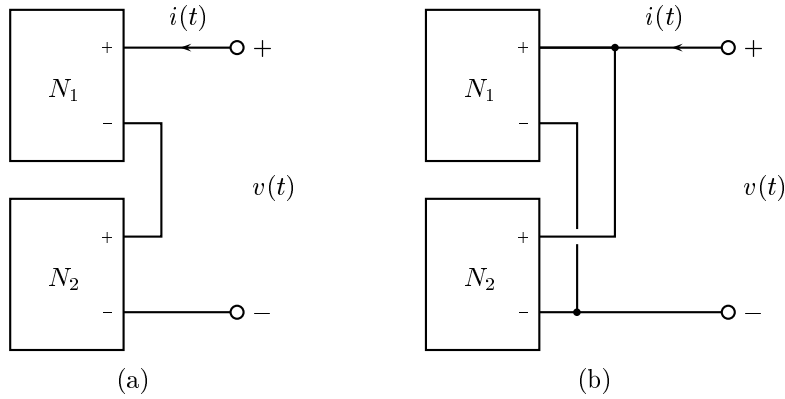


Figure 3: (a) A series connection of two two-terminal networks. (b) A parallel connection of two two-terminal networks.

- (a) The two networks are connected in series if the same current passes through both, as illustrated in Figure 3a. Determine the  $v - i$  characteristic for the series connection of  $N_1$  and  $N_2$ .
- (b) The two networks are connected in parallel if the same voltage appears across the terminals of both networks, as illustrated in Figure 3b. Determine the  $v - i$  characteristic for the parallel connection of  $N_1$  and  $N_2$ .

---

**Solution:**

- (a) Let the voltage drop across the terminals of  $N_1$  be  $v_1(t)$  and the voltage drop across the terminals of  $N_2$  be  $v_2(t)$ . The current  $i(t)$  passes through both networks. Therefore, we can rewrite the two  $v - i$  relations as

$$\begin{aligned} v_1(t) &= R_1 i(t) + v_{T1} \\ v_2(t) &= R_2 i(t) + v_{T2}. \end{aligned}$$

However,  $v(t) = v_1(t) + v_2(t)$ . Therefore, if we add the two equations,

$$\begin{aligned} v(t) &= R_1 i(t) + v_{T1} + R_2 i(t) + v_{T2} \\ &= [R_1 + R_2] i(t) + [v_{T1} + v_{T2}] \end{aligned}$$

- (b) The approach here is similar except that both networks now have the same voltage drop  $v(t)$  and currents  $i_1(t)$  and  $i_2(t)$ . Therefore,

$$\begin{aligned} v(t) &= R_1 i_1(t) + v_{T1} \\ v(t) &= R_2 i_2(t) + v_{T2}. \end{aligned}$$

By KCL

$$\begin{aligned} i(t) &= i_1(t) + i_2(t) \\ &= \frac{v(t) - v_{T1}}{R_1} + \frac{v(t) - v_{T2}}{R_2} \\ &= \left( \frac{1}{R_1} + \frac{1}{R_2} \right) v(t) - \left( \frac{1}{R_1} v_{T1} + \frac{1}{R_2} v_{T2} \right). \end{aligned}$$

This form is perfectly acceptable for the  $v-i$  relation, but if it is more convenient to have  $v(t)$  on the left, we can rewrite it as

$$v(t) = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} i(t) + \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2}} v_{T_1} + \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}} v_{T_2}.$$


---

**Problem 4.5:** Express  $v(t)$  as a function of  $i(t)$  and  $i_s(t)$  for the circuit in Figure 4.



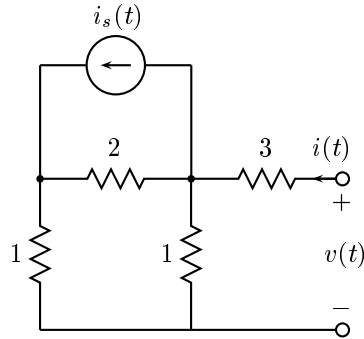


Figure 4: Circuit for Problem 4.5.


**Solution:** This problem can be worked many ways. This approach uses source substitutions, and the rules for replacing series and parallel connections of resistors by their equivalents to reduce the circuit to its Thévenin equivalent from which we can infer the  $v-i$  relation. First we replace the current source in parallel with the  $2\Omega$  resistor by a voltage source in series with a resistor.

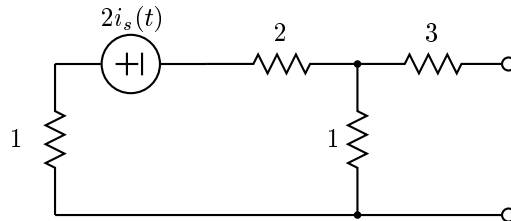

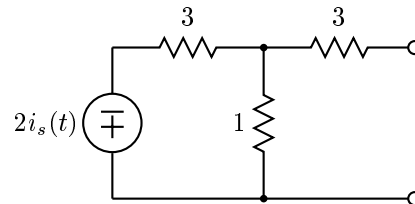
Now, by replacing the left part of the circuit by its equivalent, we get



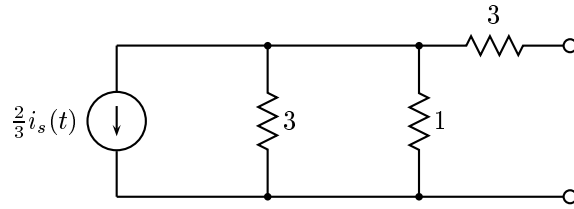
Now we can do another source substitution.



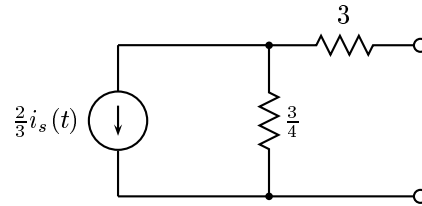
The next step is to combine the two resistors that are connected in parallel



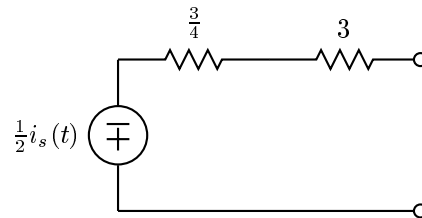Now we perform another source substitution



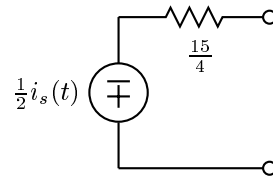Finally, combining the series resistors gives us the Thévenin equivalent.



From the circuit we see that

$$v(t) = \frac{15}{4}i(t) - \frac{1}{2}i_s(t).$$