

GEORGIA INSTITUTE OF TECHNOLOGY
School of Electrical and Computer Engineering


ECE 2040
Circuit Analysis

Quiz #2-Solutions

Wednesday, February 25, 2000

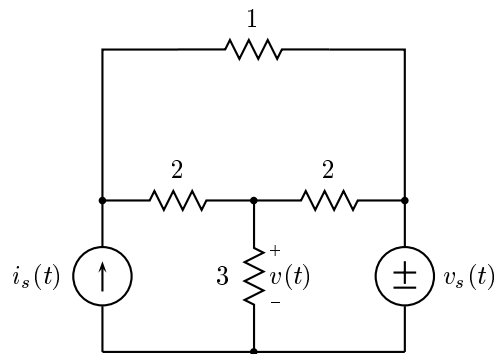Problem Q2.1:

Solve for the voltage $v(t)$ using the mesh method.



Solution: Let the mesh current (clockwise) in the upper mesh be $i_\alpha(t)$ and in the lower right mesh, let it be $i_\beta(t)$. Assign a mesh current $i_s(t)$ to the lower left mesh. Then

$$\alpha \text{ mesh: } i_\alpha(t) + 2[i_\alpha(t) - i_\beta(t)] + 2[i_\alpha(t) - i_s(t)] = 0$$

$$\beta \text{ mesh: } 3[i_\beta(t) - i_s(t)] + 2[i_\beta(t) - i_\alpha(t)] + v_s(t) = 0$$

Rearranging

$$5i_\alpha(t) - 2i_\beta(t) = 2i_s(t)$$

$$-2i_\alpha(t) + 5i_\beta(t) = -v_s(t) + 3i_s(t)$$

Multiply the first equation by 2, the lower one by 5 and add.

$$21i_\beta(t) = 19i_s(t) - 5v_s(t)$$

or

$$i_\beta(t) = \frac{19}{21}i_s(t) - \frac{5}{21}v_s(t).$$

But


$$v(t) = 3[i_s(t) - i_\beta(t)] = 3 \left[\frac{2}{21}i_s(t) + \frac{5}{21}v_s(t) \right]$$

or

$$v(t) = \frac{2}{7}i_s(t) + \frac{5}{7}v_s(t).$$

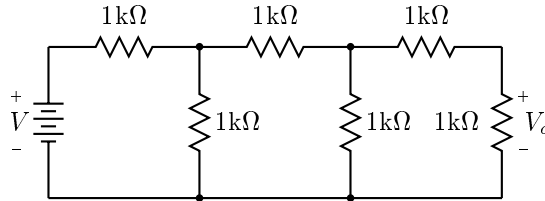Problem Q2.2:


For the circuit below the source voltage on the left is a battery (i.e., a constant voltage source).



Determine the value of V required to produce a value for V_o of 1 volt.

Solution: Number the six resistors R_1, R_2 , etc. from left to right. To get 1 volt across R_6 requires a current flowing through it of 1 mA. Since this current also flows through R_5 , there will be a 2 volt drop across the series combination of R_5 and R_6 . This means that there will be a 2 volt drop across R_4 and a 2 mA current flowing through it. Working backwards, this means that there will be a 3 mA current through R_3 and a voltage drop of 3 volts. A 3 volt drop across R_3 with a 2 volt drop across R_4 means a 5 volt drop across R_2 and a current of 5 mA. Finally there will be an 8 mA current through R_1 and an 8 volt drop. Therefore, $V = 13$ volts. (Notice that the sequence of voltages [and the sequence of currents] forms a Fibonacci series.)

Problem Q2.3:

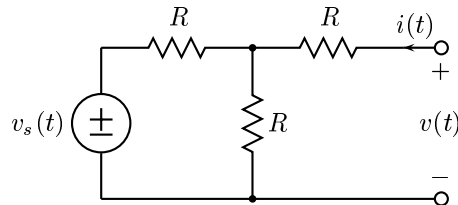


- Find the Thévenin equivalent network corresponding to the above two-terminal circuit.
- Find the Norton equivalent network.


Solution:

$$v_{oc}(t) = \frac{1}{2}v_s(t)$$
$$R_{eq} = \frac{R}{2} + R = \frac{3}{2}R$$

(a)

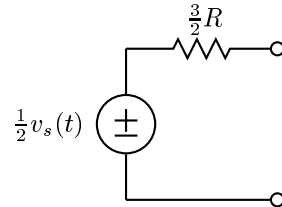


(b)

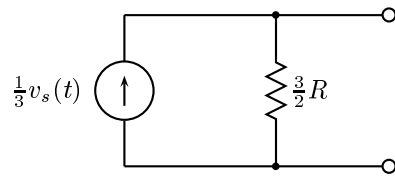

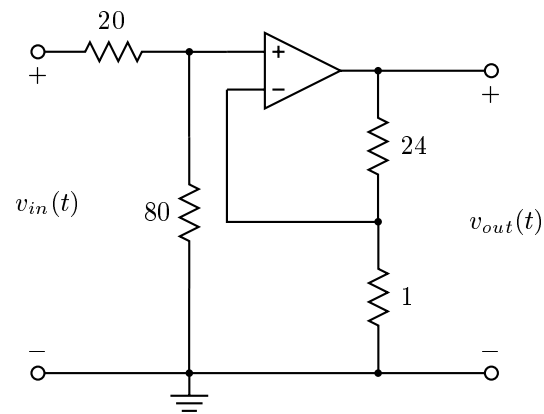Problem Q2.4:

Determine $v_{out}(t)$ in terms of $v_{in}(t)$.



Solution: Circuits containing opamps are normally analyzed using the node method, appropriately modified. For this circuit we need to write KCL equations at the two

nodes connected to the two inputs of the opamp. The potential at each of these is the same; call that potential $e(t)$.

$$+ \text{ node: } \frac{1}{20}[e(t) - v_{in}(t)] + \frac{1}{80}e(t) = 0$$

$$- \text{ node: } \frac{1}{24}[e(t) - v_{out}(t)] + e(t) = 0$$

From the first equation we find

$$e(t) = \frac{4}{5}v_{in}(t).$$

Substituting this value into the second equation gives

$$\frac{1}{24}\left[\frac{4}{5}v_{in}(t) - v_{out}(t)\right] + \frac{4}{5}v_{in}(t) = 0$$

$$\frac{5}{6}v_{in}(t) - \frac{1}{24}v_{out}(t) = 0$$

$$v_{out}(t) = 20v_{in}(t).$$
