

GEORGIA INSTITUTE OF TECHNOLOGY
School of Electrical and Computer Engineering

Course EE 2250
Electric Circuit Analysis

Assigned: April 1, 1999
Due: April 8, 1999

Problem Set #1

Reading: Read the following sections from the class notes:
Chapter 1, Sections 1.1–1.5

Reading: Read the following sections from Dorf and Svoboda:
Chapter 1, Sections 1.3–1.5; (definitions of voltage and current)
Chapter 2, Sections 2.3, 2.5; (resistors and sources)
Chapter 3, Sections 3.3; (Kirchoff's Laws)
Chapter 7, Sections 7.3, 7.6; (definitions of capacitors and inductors)

Problem 1.1: The current source in the network shown in Figure 1a has the time dependence shown in Figure 1b.

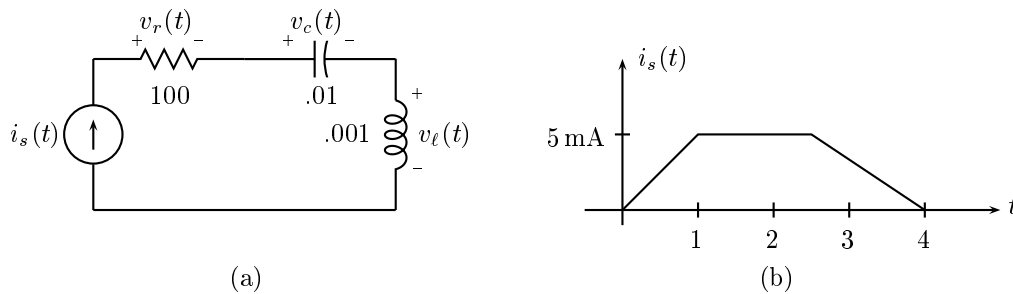


Figure 1:

- (a) Sketch $v_r(t)$.
- (b) Sketch $v_c(t)$.
- (c) Sketch $v_l(t)$.

- Problem 1.2:** (a) Write the KCL equations that constrain the currents at all of the nodes of the network in Figure 2.
- (b) Write the KVL equations that constrain the voltages for all of the meshes in that same figure.


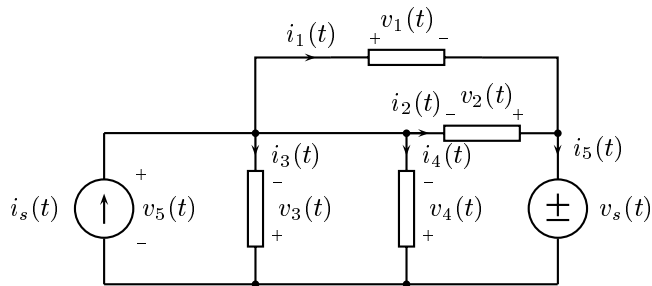


Figure 2: Figure for Problem 1.2.

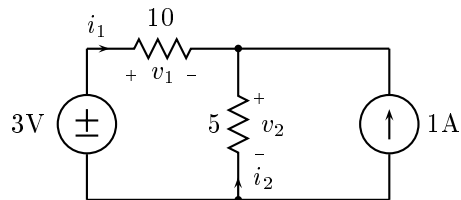- Problem 1.3:** In the circuit below both source waveforms (and all of the element variables) are constant. Compute the values of i_1 , v_1 , i_2 , and v_2 .



- Problem 1.4:** Determine the current $i(t)$ in the circuit shown in Figure 3. In order to do this you will need to define a number of element voltages and currents, write KVL and KCL equations and impose the element relations for the resistors.

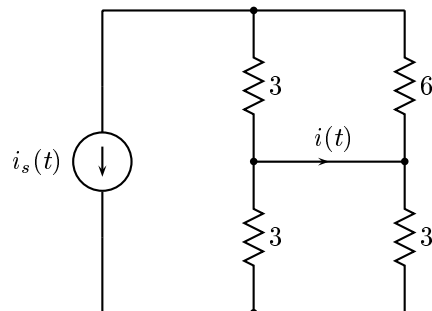


Figure 3: Figure for Problem 1.4.

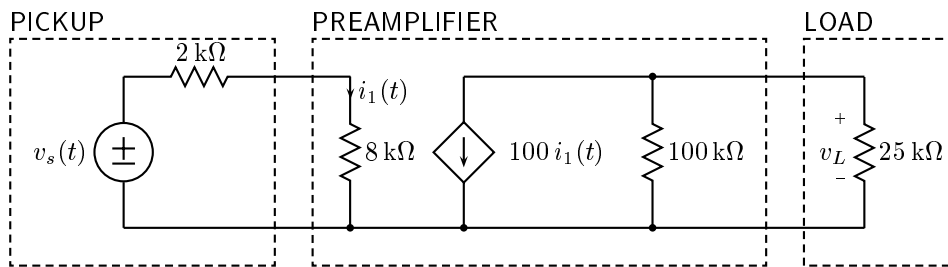


Figure 4:

Problem 1.5: In the center of Figure 4 is a model of a one-transistor preamplifier that is used to amplify the output of a low amplitude magnetic pickup, and drive a $25\text{ k}\Omega$ load. Express the voltage $v_L(t)$ measured across the load in terms of $v_s(t)$.