

GEORGIA INSTITUTE OF TECHNOLOGY
School of Electrical and Computer Engineering

Course EE 2250
Electric Circuit Analysis

Assigned: May 20, 1999

Due: May 27, 1999

Problem Set #8


Reading: Read the following sections from Dorf and Svoboda:

Chapter 10, Sections 10.10–10.11, 10.14; (Node and Mesh Methods)

Chapter 13, Sections 13.3, 13.5 (Frequency Responses of Circuits)


Announcement: Quiz #3 will be held on Thursday, May 27, 1999 during the class hour. Coverage will include that material contained on Problem Sets 5, 6, and 7. This will be a *closed book, closed notes* exam, but you are permitted to use one two-sided 8.5×11 inch handwritten sheet of notes. Calculators are also permitted.

Problem 8.1:

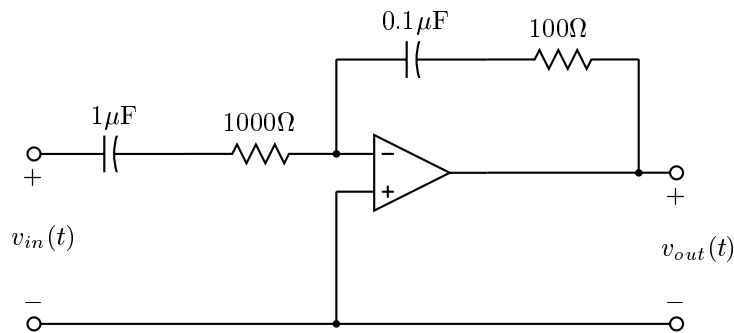


Plot the magnitude of the frequency response of the above circuit.

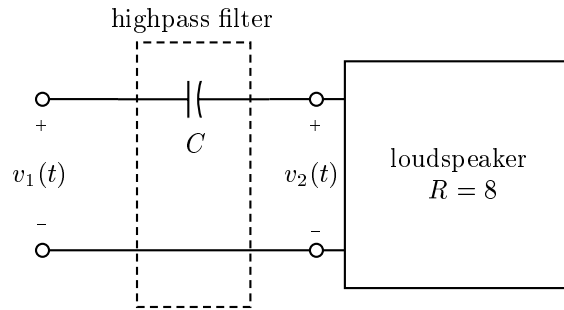Problem 8.2: Many loudspeaker systems consist of two loudspeakers: the woofer, which reproduces the low frequency part of the signal, and the tweeter, which reproduces the high frequency part of the signal. A crossover network is used to select the high frequency part of the signal and feed it into the tweeter. Such a network functions as a highpass filter. The entire audio signal is applied at the terminals $a - a'$.



- (a) Assuming that the equivalent circuit for the tweeter consists of just a resistor with a resistance of R , plot the pole-zero pattern of the system function that relates $v_2(t)$ to $v_1(t)$ and sketch the frequency response curves (magnitude and angle).
- (b) If $R = 8\Omega$, find the value of the capacitance C so that the half-power frequency of the highpass filter is 5 kHz ($= 2\pi(5000)$ rad/s).

Problem 8.3:

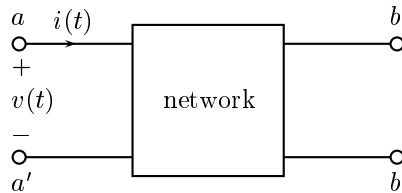

For the two-terminal pair circuit shown above the relation between $v(t)$ and $i(t)$ is

$$v(t) = i(t) + 3\frac{di(t)}{dt}$$


when the terminals b and b' are open-circuited and

$$v(t) = \frac{di(t)}{dt}$$

when the terminals b and b' are short-circuited. Determine a possible circuit having these properties.

Problem 8.4: In the circuit below the value of R_1 is $10k\Omega$.

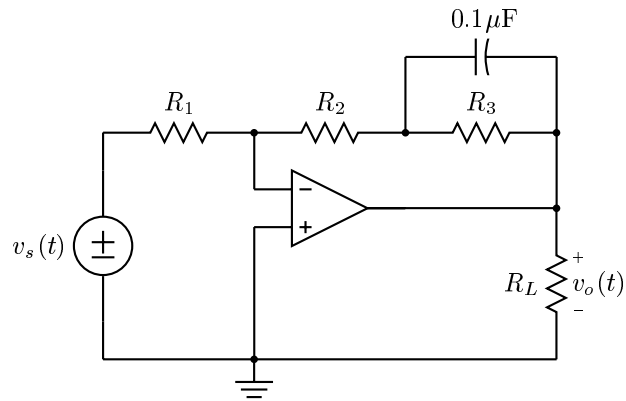- (a) Determine the values of R_2 and R_3 so that the gain (magnitude of the frequency response) at low frequencies is 5 and the gain at high frequencies is 2.
- (b) Determine the frequency at which the gain is midway between these two values, i.e. the frequency at which the gain is 3.5.



Problem 8.5: An oscillator is a circuit whose system function has a pair of complex conjugate poles located on the $j\omega$ -axis in the s -plane. It is capable of supporting a sustained oscillation, i.e., once started it will continue to produce a sinusoidal output $v_{out}(t)$. In the network below determine the value of K for which the system will oscillate and determine the frequency of oscillation.

