

GEORGIA INSTITUTE OF TECHNOLOGY
School of Electrical and Computer Engineering

Course EE 2250
Electric Circuit Analysis

Assigned: January 7, 1999
Due: January 14, 1999

Problem Set #1

Reading: Read the following sections from Dorf and Svoboda:

Chapter 1, Sections 1.3–1.5; (definitions of voltage and current)

Chapter 2, Sections 2.3, 2.5; (resistors and sources)

Chapter 3, Sections 3.3; (Kirchoff's Laws)

Chapter 7, Sections 7.3, 7.6; (definitions of capacitors and inductors)

Problem 1.1: The voltage waveform for the voltage source in Figure 1 is

$$v_s(t) = \begin{cases} \sin 2\pi(100)t, & t \geq 0 \\ 0, & t < 0 \end{cases}$$

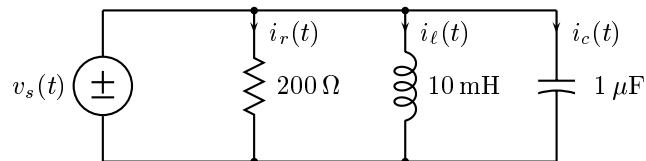


Figure 1:

- (a) Determine $i_r(t)$.
- (b) Determine $i_l(t)$.
- (c) Determine $i_c(t)$.

Problem 1.2: Consider the four terminal network N_1 shown in Figure 2.

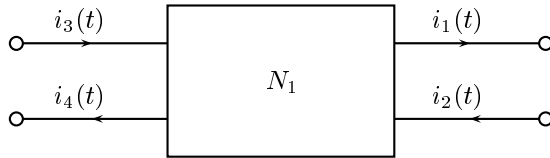


Figure 2:

- (a) When network N_1 is connected to the two subnetworks N_2 and N_3 as shown in Figure 3, what is the relation between currents $i_1(t)$ and $i_2(t)$?

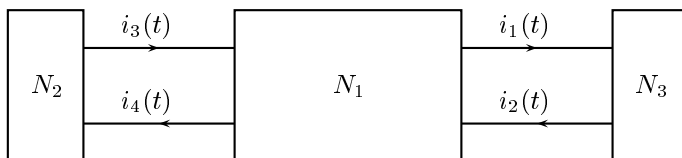


Figure 3:

- (b) Does the result that you derived in (a) apply to $i_1(t)$ and $i_2(t)$ when N_1 is embedded in a larger network as shown in Figure 4? Explain.

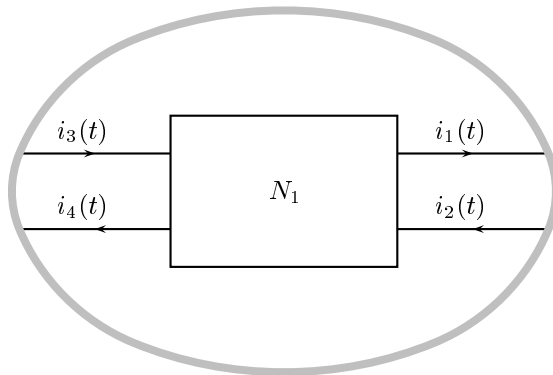


Figure 4:

- Problem 1.3:** (a) Write the KCL equations that constrain the currents at all of the nodes of the network in Figure 5.
- (b) Write the KVL equations that constrain the voltages for all of the meshes in that same figure.

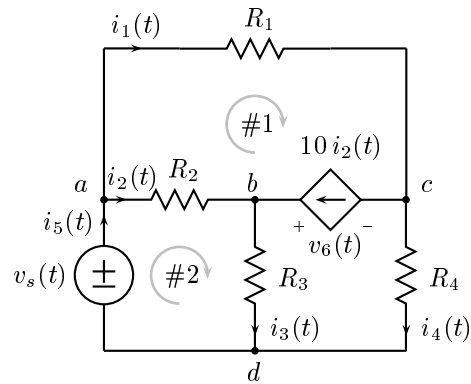


Figure 5:

- Problem 1.4:** Determine $v(t)$ and $i(t)$ in the network shown in Figure 6

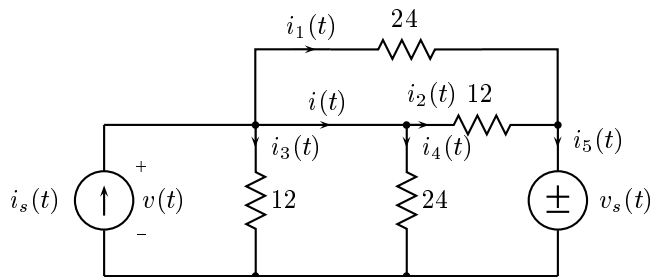


Figure 6:

- Problem 1.5:** In the center of Figure 7 is a model of a one-transistor preamplifier that is used to amplify the output of a low amplitude magnetic pickup, and drive a $25\text{ k}\Omega$ load. Express the voltage $v_L(t)$ measured across the load in terms of $v_s(t)$.

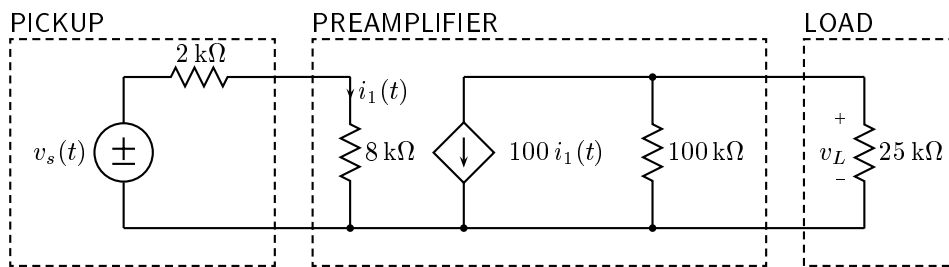


Figure 7: