

GEORGIA INSTITUTE OF TECHNOLOGY  
School of Electrical and Computer Engineering

Course EE 2250  
Electric Circuit Analysis

January 28, 1999

**Problem Set #3—Solutions**

---

**Problem 3.1:** (a) Show that the network in Figure ?? is equivalent to a single resistor.

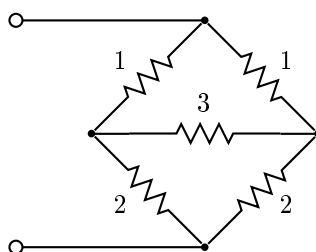


Figure 1:

(b) Determine the value of the equivalent resistance,  $R_{eq}$ .

---

**Solution:**


---

**Problem 3.2:** (a) Determine the equivalent resistance of the two-terminal network in Figure ??a as seen at the terminals  $a - a'$ .

(b) Repeat for the network in Figure ??b at the terminals  $b - b'$ .

---

**Solution:**

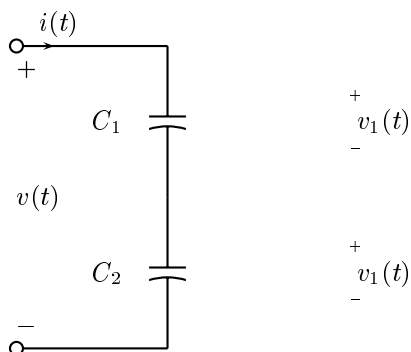

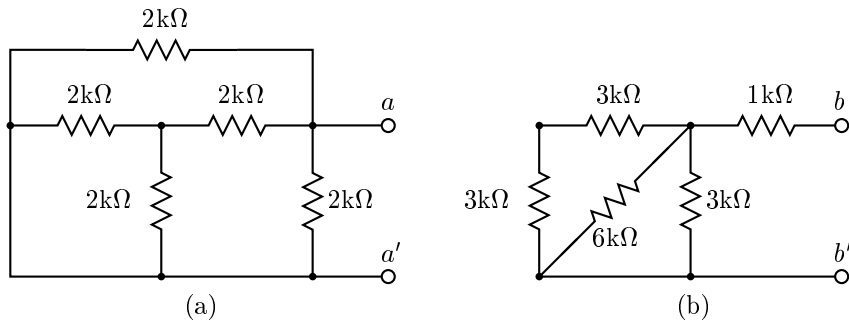


Figure 2:

**Problem 3.3:** Consider a one-port network consisting of two capacitors with capacitances  $C_1$  and  $C_2$  connected in series.

- Show that this network is equivalent to a single capacitor.
- Derive a formula for the equivalent capacitance  $C_{eq}$  in terms of  $C_1$  and  $C_2$ .
- Derive expressions for the voltage  $v_1(t)$  measured across capacitor  $C_1$  and the voltage  $v_2(t)$  measured across  $C_2$  in terms of the voltage  $v(t)$  appearing across the series connection.

**Solution:**

**Problem 3.4:** In an attempt to determine a Thévenin equivalent for a network containing only resistors and sources two experiments are performed. First, a resistor with a value of  $R$  ohms is connected across the terminals and the voltage  $v_1(t)$  is measured, as shown in Figure ???. Then a resistor with a value of  $2R$  ohms is connected across the terminals and the voltage  $v_2(t)$  is measured.

- Determine the Thévenin equivalent model for the network in terms of the measured voltages  $v_1(t)$  and  $v_2(t)$ .
- What is a good value to choose for  $R$ ? Explain your answer.

**Solution:**

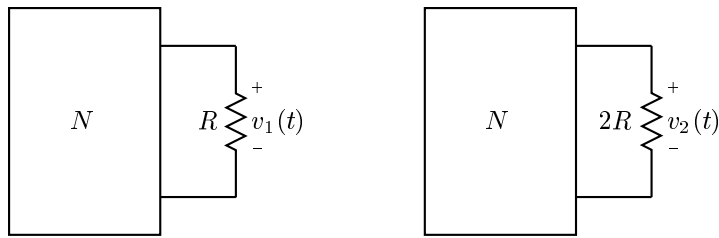


Figure 3:

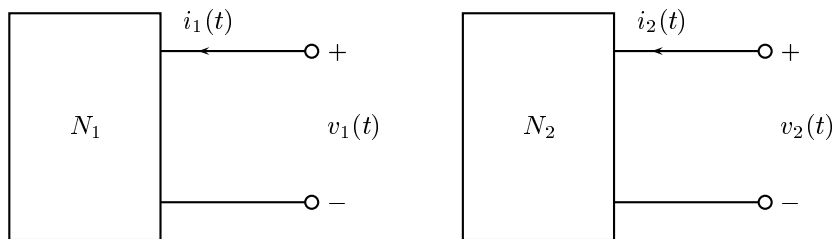


Figure 4:

**Problem 3.5:** Consider the two two-terminal networks  $N_1$  and  $N_2$  shown in Figure ???. The two networks have the  $v - i$  relations

$$N_1 : \quad v_1(t) = 4i_1(t) - 8$$

$$N_2 : \quad v_2(t) = 2i_2(t) + 3$$

- (a) Determine the equilibrium values of  $v(t)$  and  $i(t)$  if the two networks are connected as shown in Figure ??.

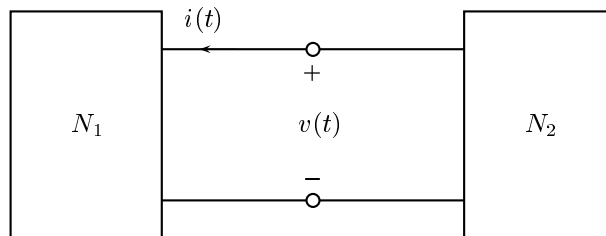


Figure 5:

- (b) Repeat part (a) for the connection shown in Figure ???.  
(c) Repeat part (a) for the connection shown in Figure ??.

---

**Solution:**

---

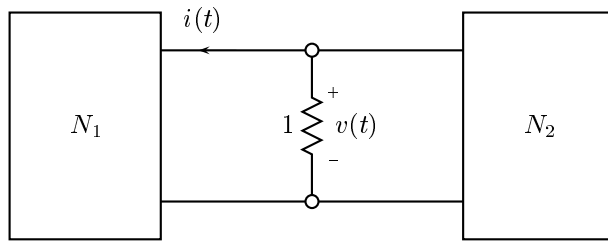


Figure 6:

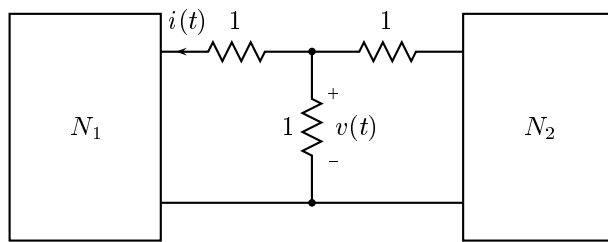


Figure 7:

**Problem 3.6:** Design a circuit with four inputs  $v_1(t)$ ,  $v_2(t)$ ,  $v_3(t)$  and  $v_4(t)$  containing a single operational amplifier, such that the output voltage  $v_{out}(t)$  satisfies

$$v_{out}(t) = k_5[k_1v_1(t) + k_2v_2(t) - k_3v_3(t) - k_4v_4(t)]$$

for positive values of the four constants. *Hint:* You might begin by trying to combine features of the differential amplifier configuration and the summing amplifier configuration.

- (b) Prove that your design in (a) works correctly.
- (c) State any additional constraints that need to be imposed on the four constants.

---

**Solution:**

---