

GEORGIA INSTITUTE OF TECHNOLOGY  
School of Electrical and Computer Engineering

Course EE 2250  
Electric Circuit Analysis

Assigned: January 28, 1999

Due: February 4, 1999


**Problem Set #4**

---


**Reading:** Read the following sections from Dorf and Svoboda:  
Chapter 10, Sections 10.3–10.9; (sinusoidal steady-state analysis)

---

**Problem 4.1:** Find  $v_o(t)$  for the circuit below in terms of the input voltages  $v_a(t)$  and  $v_b(t)$ .

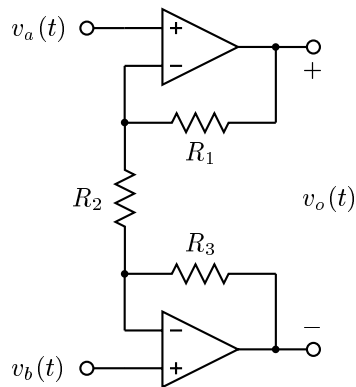

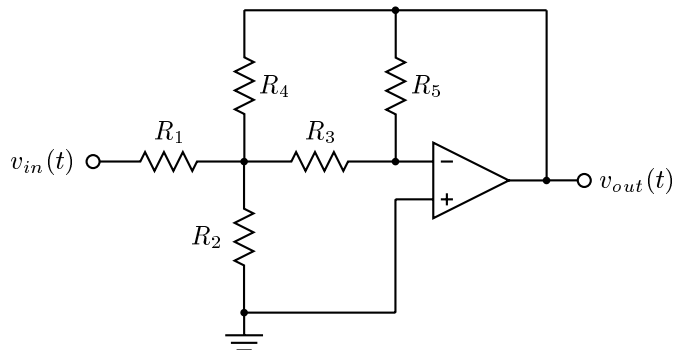
**Problem 4.2:** Determine the output voltage  $v_{out}(t)$  in terms of the input voltage  $v_{in}(t)$  for the circuit below.




**Problem 4.3:** This is Problem 6.6-16 from Dorf and Svoboda. The circuit shown below is called the inverted  $R - 2R$  ladder digital-to-analog converter (DAC). The input to this circuit is a binary code represented by  $b_1, b_2, \dots, b_n$ , where  $b_i$  is either 1 or 0. Each switch shown in the figure is controlled by one of the bits in the binary code. If  $b_i = 1$ , that switch will be in the '1' position; if  $b_i = 0$ , that switch will be in the '0' position. Depending on the position of the switch, each current  $i_k$  is diverted either to true ground (adding to the + terminal of the opamp) or to the virtual ground (adding to the - terminal.)

- (a) Show that  $i = v_R/R$  regardless of the digital input code.  
 (b) Show that the output voltage can be expressed as


$$v_{out}(t) = -\frac{R_f}{R}v_R(b_12^{-1} + b_22^{-2} + \dots + b_{n-1}2^{-n+1} + b_n2^{-n})$$

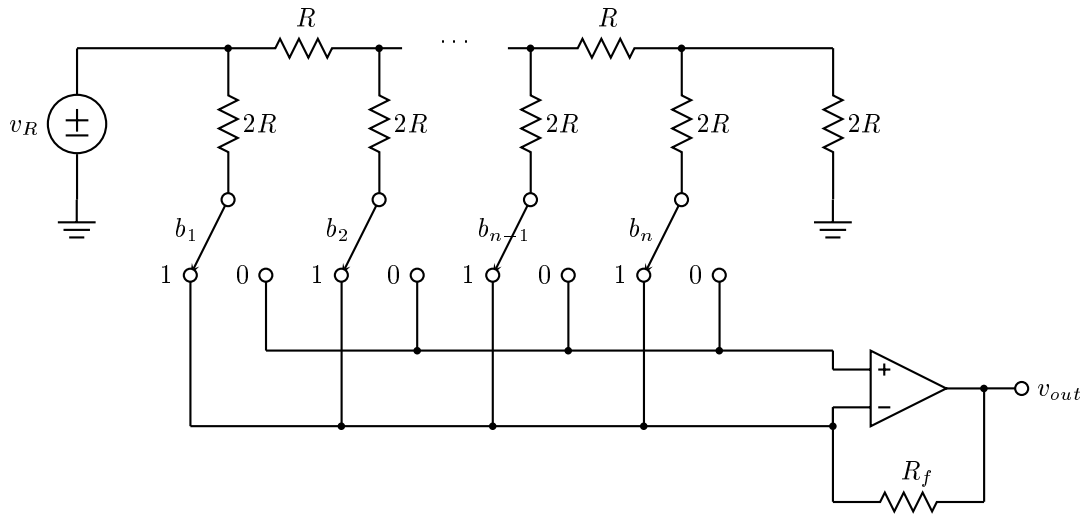

**Problem 4.4:** Find the value of the current  $v(t)$  when the current is the complex exponential time function  $i_s(t) = e^{j\omega t}$ .

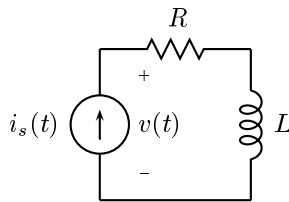

**Problem 4.5:** For the circuit below find  $v(t)$  when  $v_s(t) = \cos(\omega t)$ .

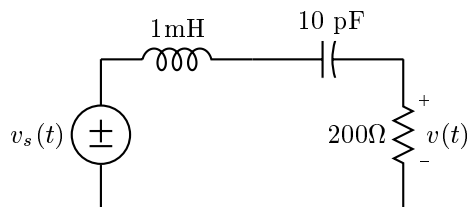

**Problem 4.6:** For the following circuit find  $i(t)$  when  $v_s(t) = \sin(\omega t)$ .

