


GEORGIA INSTITUTE OF TECHNOLOGY
School of Electrical and Computer Engineering

Course EE 2250
Electric Circuit Analysis


February 11, 1999

Problem Set #5–Solutions

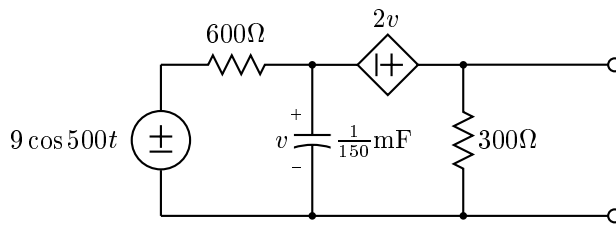Problem 5.1: Find the Thévenin equivalent circuit for the circuit shown in the figure below using the mesh current method.



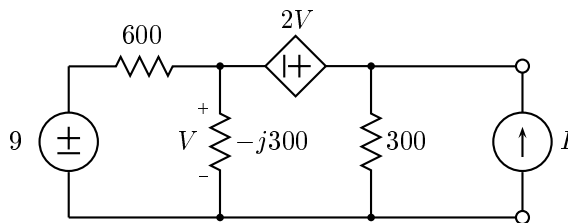Solution: We can simplify this problem considerably if we acknowledge the fact that the only frequency of interest is 500 rad/sec. Then we can replace each element by its impedance at that frequency.



To find the Thévenin equivalent we shall attach a current source with a complex current amplitude I and solve for the complex voltage amplitude V_o . Since

$$V_o = V_T + Z_T I,$$

we can get the Thévenin equivalent network from these parameters.

Let I_α and I_β be the complex amplitudes of the two mesh currents associated with the left and center meshes. Note that $V = j300(I_\beta - I_\alpha)$. The two mesh equations are

$$\begin{aligned} 600I_\alpha - j300(I_\alpha - I_\beta) &= 9 \\ -j900(I_\alpha - I_\beta) + 300(I_\beta + I) &= 0. \end{aligned}$$

These reduce to

$$\begin{aligned} (600 - j300)I_\alpha + j300I_\beta &= 9 \\ -j900I_\alpha + (300 - j900)I_\beta &= -300I. \end{aligned}$$

Using MATLAB we get

$$I_\alpha = (0.0130 + j0.0006) + (-0.1321 + j0.0377)I$$

$$I_\beta = (0.0119 - j0.0034) + (-0.2075 - j0.2264)I$$

Since $V_o = 300(I + I_\beta)$, we have

$$V_o = (237.75 - j67.92)I + (3.57 + j1.02)$$


and

$$Z_T = 237.75 - j67.92$$


$$V_T = 3.57 + j1.02$$

at $\omega = 500$ rad/s.

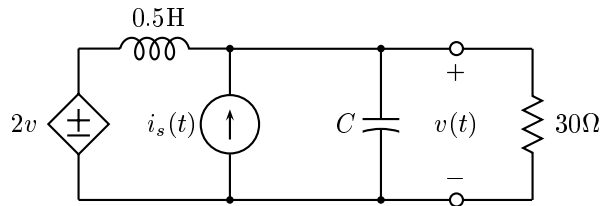Problem 5.2: Find $v(t)$ by first replacing the circuit to the left of the terminals with its Thévenin equivalent circuit when $C = 10$ mF. The current in the current source is $i_s(t) = 10 \cos 20t$.



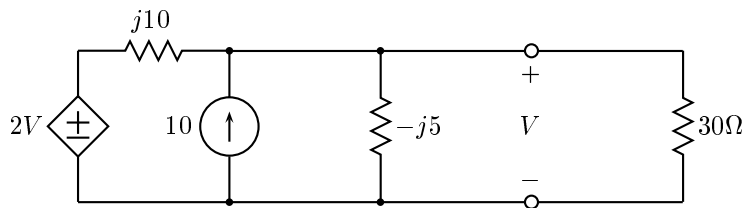Solution: Let us begin by replacing each of the elements by its equivalent impedance.



If I denotes the current entering the subnetwork from the resistor, then a KCL equation written at the node that includes the $+$ terminal is

$$\frac{2V - V}{j10} + 10 + \frac{V}{j5} + I = 0$$

or

$$j\frac{3}{10}V = I + 10.$$

From the $v - i$ relation for the 30Ω resistor, however, $I = -V/30$. Thus,


$$j\frac{3}{10}V = -\frac{1}{30}V + 10$$

$$V = \frac{300}{1 - j9} = 33.1295e^{j1.4601}$$


Thus,

$$v(t) = 33.1295 \cos(20t + 1.4601)$$

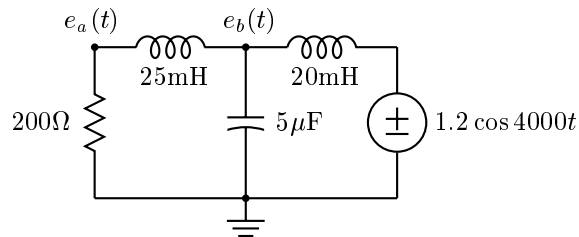Problem 5.3: Find the two node voltages $e_a(t)$ and $e_b(t)$ in the circuit below.



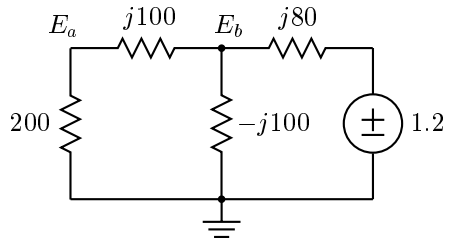Solution: Here we can replace each element by its impedance at 4000 rad/s. This allows us to redraw the circuit at



The two node equations are:

$$\frac{E_a}{200} + \frac{E_a - E_b}{j100} = 0$$

$$\frac{E_b - E_a}{j100} - \frac{E_b}{j100} + \frac{E_b - 1.2}{j80} = 0$$


These can be reduced to

$$(2 + j)E_a - 2E_b = 0$$

$$-E_a + 1.25E_b = 1.5$$

Solving these gives $E_a = 0.8276 - j2.0690$, $E_b = 1.8621 - j1.6552$.

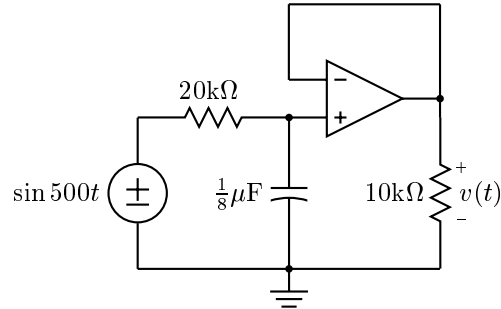Problem 5.4: For the circuit below find $v(t)$.



Solution: The opamp acts like a voltage follower, i.e., $v(t)$ is equal to the voltage across the capacitor. Furthermore, we know that $v(t)$ is of the form

$$v(t) = \Im[V e^{j500t}].$$

To determine V , replace the source by a complex exponential time function, the elements by their equivalent impedances, and use the voltage divider.


$$V = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC}.$$

Letting $R = 20 \times 10^3$; $C = 0.125 \times 10^{-6}$, $\omega = 500$, we get

$$\begin{aligned} V &= \frac{1}{1 + j(20 \times 10^3)(0.125 \times 10^{-6})(500)} = \frac{1}{1 + j(1.25)} \\ &= 0.625 e^{-j \tan^{-1} 1.25} \\ v(t) &= 0.625 \sin(500t - \tan^{-1} 1.25). \end{aligned}$$

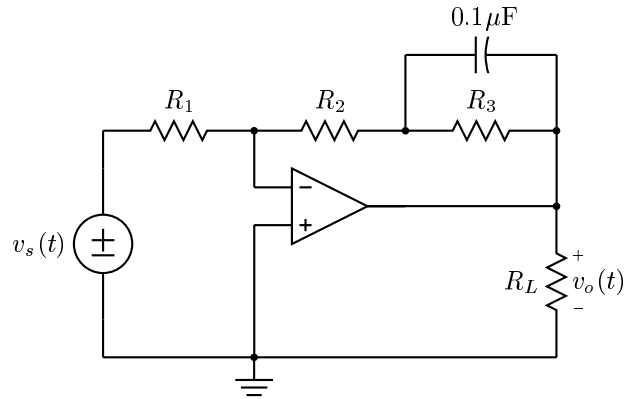
Problem 5.5: In the circuit below the value of R_1 is $10\text{k}\Omega$.

- Determine the values of R_2 and R_3 so that the gain at low frequencies is 5 and the gain at high frequencies is 2.
- Determine the frequency at which the gain is midway between these two values, i.e. the frequency at which the gain is 3.5.



Solution:

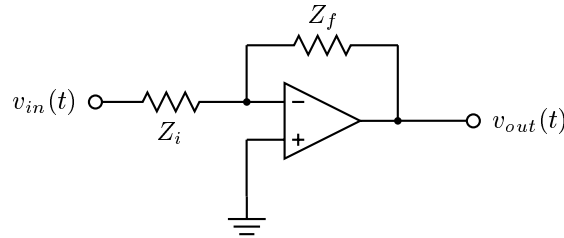(a) This circuit is a special case of an inverting amplifier as shown below.



The frequency response of such a system is known to be

$$H(j\omega) = -\frac{Z_f(j\omega)}{Z_i(j\omega)}.$$

For this circuit, the input impedance is simply

$$Z_i = R_1$$

and the other three elements contribute to the feedback impedance

$$\begin{aligned} Z_f &= R_2 + \frac{R_3 \frac{1}{j\omega C}}{R_3 + \frac{1}{j\omega C}} = R_2 + \frac{R_3}{1 + j\omega R_3 C} \\ &= \frac{(R_2 + R_3) + j\omega R_2 R_3 C}{1 + j\omega R_3 C}. \end{aligned}$$

Therefore,

$$H(j\omega) = -\frac{(R_2 + R_3) + j\omega R_2 R_3 C}{R_1 (1 + j\omega R_3 C)}.$$

To measure the low frequency gain, we can let $\omega = 0$ and take the magnitude

$$G_{LF} = \frac{R_2 + R_3}{R_1}.$$

To measure the high frequency gain, we can take the (magnitude of the) limit as ω grows large

$$G_{HF} = \frac{R_2}{R_1}.$$

Since $R_1 = 10k\Omega$ and we want $G_{LF} = 5$ and $G_{HF} = 2$, we can substitute and solve for R_2 and R_3 .

$$5 = \frac{R_2 + R_3}{10k\Omega} \implies R_2 + R_3 = 50k\Omega$$

$$2 = \frac{R_2}{10k\Omega} \implies R_2 = 20k\Omega$$

Therefore, we want to choose $R_2 = 20k\Omega$ and $R_3 = 30k\Omega$.

(b) With the values substituted, the frequency response is


$$H(j\omega) = -\frac{5 + j\omega(0.6)}{1 + j\omega(0.3)}$$

To find the value of ω for which the magnitude is 3.5, we solve the equation

$$\frac{25 + \omega^2(0.6)^2}{1 + \omega^2(0.3)^2} = (3.5)^2.$$

This gives $\omega = 4.14$.

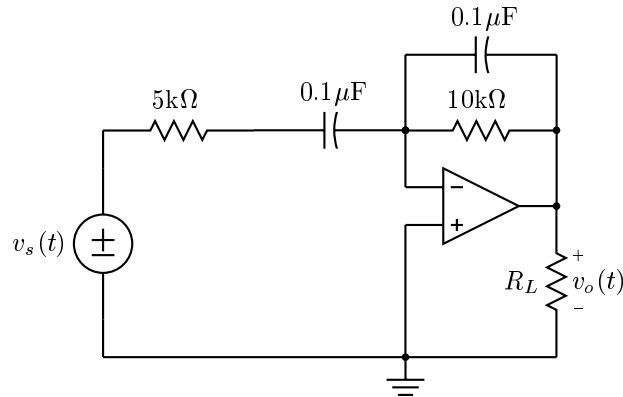Problem 5.6: Sketch the asymptotes for the magnitude Bode plot of the frequency response of the circuit below.



Solution: This circuit also has the form of an inverting amplifier

$$H(j\omega) = -\frac{Z_f(j\omega)}{Z_i(j\omega)} = -\frac{\frac{R_2 \frac{1}{jC_2\omega}}{R_2 + \frac{1}{jC_2\omega}}}{R_1 + \frac{1}{jC_1\omega}}$$

$$= -\frac{\frac{jR_2 C_1\omega}{1 + jR_2 C_2\omega}}{1 + jR_1 C_1\omega}$$

$$= -\frac{jR_2 C_1\omega}{(1 + jR_2 C_2\omega)(1 + jR_1 C_1\omega)}$$

But

$$\begin{aligned}R_1C_1 &= (5000)(10^{-7}) = 5 \times 10^{-4} \\R_2C_2 &= (10000)(10^{-7}) = 10^{-3} = R_2C_1\end{aligned}$$

Therefore,

$$20 \log_{10} |H(j\omega)| = 20 \log_{10}(10^{-3}\omega) - 20 \log_{10} |1 + j(5 \times 10^{-4})\omega| - 20 \log_{10} |1 + j(10^{-3})\omega|$$

The Bode magnitude plot is seen to consist of the sum of three terms.

The first term, $20 \log_{10}(10^{-3}\omega)$ increases at 20 dB/decade for all frequencies. Its value is 0 at $\omega = 1000$ rad/s.

The second term, $-20 \log_{10} |1 + j(5 \times 10^{-4})\omega|$ has a value that is nearly constant at 0 dB for $\omega < 2000$ rad/s, and it decreases at 20 dB/decade for frequencies above that.

The third term is similar to the second except that it has its break at 1000 rad/s.

Adding these three terms together gives a Bode plot that increases with a slope of 20 dB/decade until $\omega = 1000$ rad/s, where it has a value of 0 dB, then is constant until $\omega = 2000$ rad/s, then decreases with a slope of -20 dB/decade for higher frequencies.
