


# ECE3055

## Computer Architecture and Operating Systems



### Chapter 5: Datapath Part I

---

 

Prof. Hsien-Hsin Sean Lee  
School of Electrical and Computer Engineering  
Georgia Institute of Technology


## The Processor: Datapath and Control

---

- We're ready to look at an implementation of the MIPS
- Simplified to contain only:
  - memory-reference instructions: `lw, sw`
  - arithmetic-logical instructions: `add, sub, and, or, slt`
  - control flow instructions: `beq, j`
- Generic Implementation:
  - use the program counter (PC) to supply instruction address
  - get the instruction from memory
  - read registers
  - use the instruction to decide exactly what to do
- All instructions use the ALU after reading the registers  
Why? memory-reference? arithmetic? control flow?

## More Implementation Details

- Abstract / Simplified View:

 


Two types of functional units:

- Elements that operate on data values (combinational)
- Elements that contain state (sequential)


 
## State Elements

- Unlocked vs. Clocked
- Clocks used in synchronous logic
  - when should an element that contains state be updated?



# D flip-flop

- Output changes only on the clock edge

  


# Our Implementation

- An edge triggered methodology
- Typical execution:
  - read contents of some state elements,
  - send values through some combinational logic
  - write results to one or more state elements



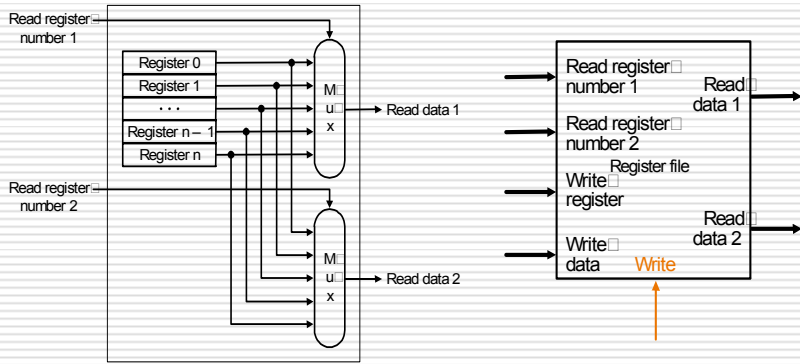
# Register File

- Built using D flip-flops (remember ECE 2030!)



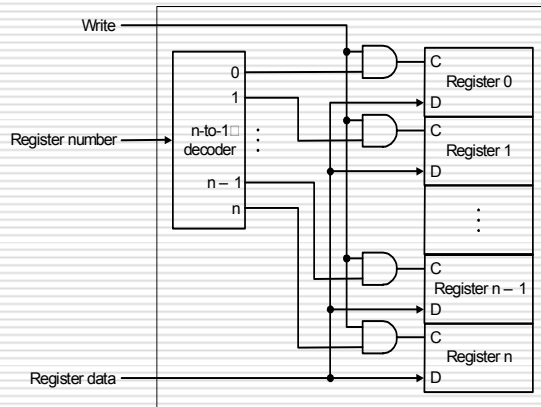
# Register File

- Note: we still use the real clock to determine when to write



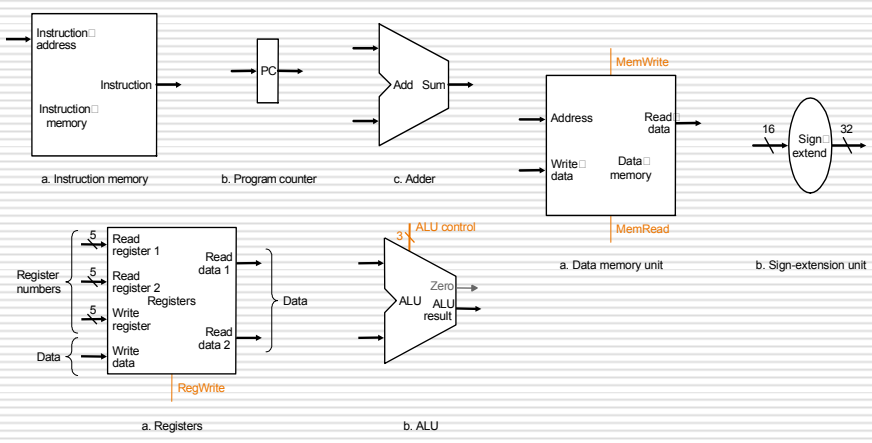
# Simple Implementation

- Include the functional units we need for each instruction




# Executing R-Format Instructions

 


op	rs	rt	rd	shamt	funct
----	----	----	----	-------	-------

# Executing I-Format Instructions

 

# Program Counter Update

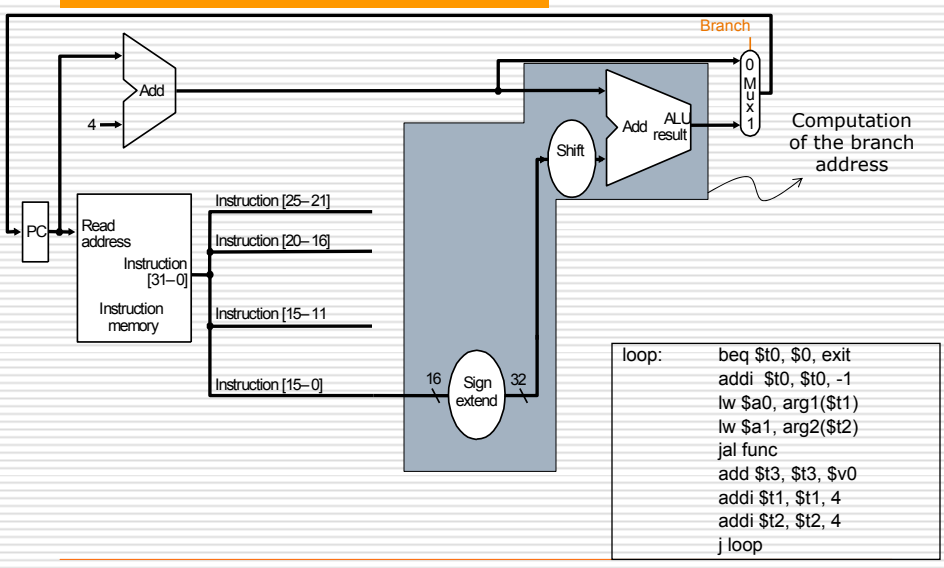


```


loop:  beq $t0, $0, exit
       addi $t0, $t0, -1
       lw $a0, arg1($t1)
       lw $a1, arg2($t2)
       jal func
       add $t3, $t3, $v0
       addi $t1, $t1, 4
       addi $t2, $t2, 4
       j loop
    
```

# Building the Datapath

Use multiplexers to stitch them together

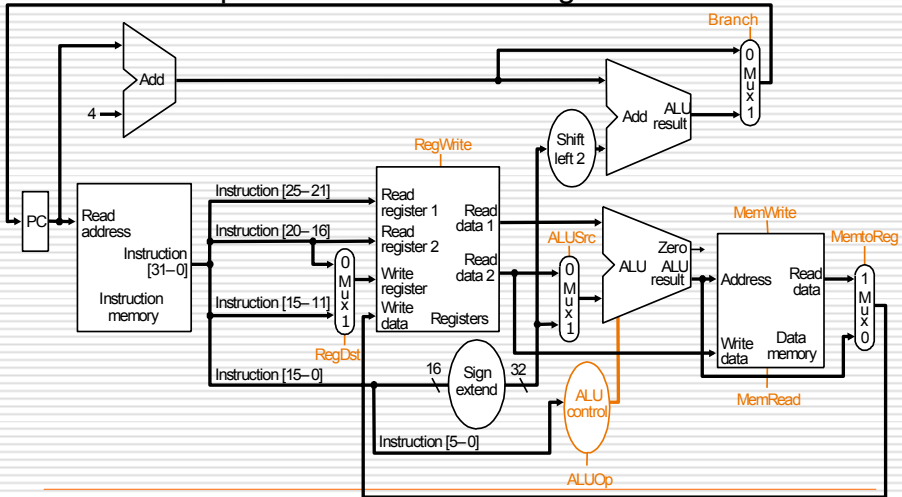

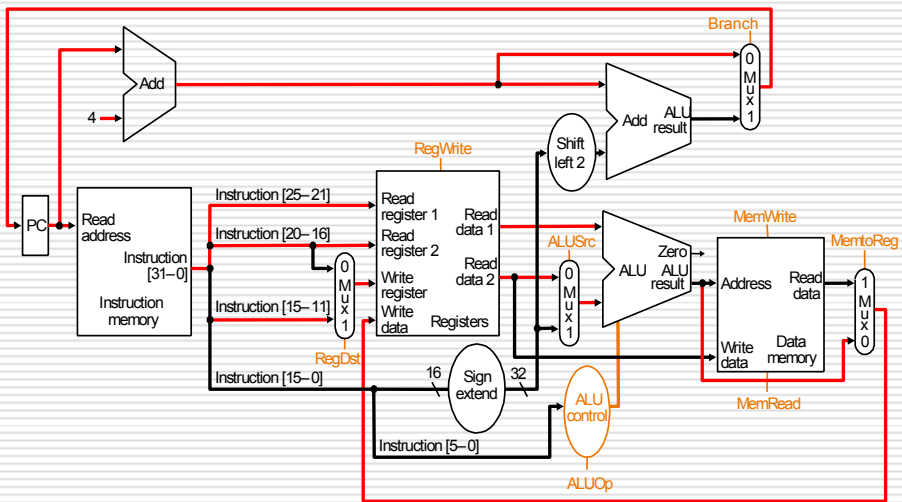
# R-Type Instructions (e.g. add \$2, \$3, \$4; Not JR/JALR)




# I-Type Instructions

(e.g. lw \$4, 1000(\$15))

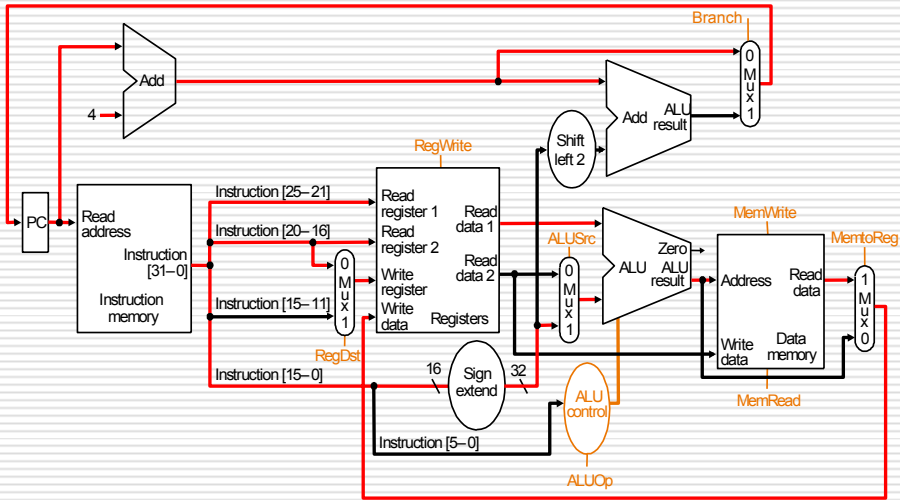


# I-type Instruction for Branches

(e.g. beq \$4, \$5, Label7)

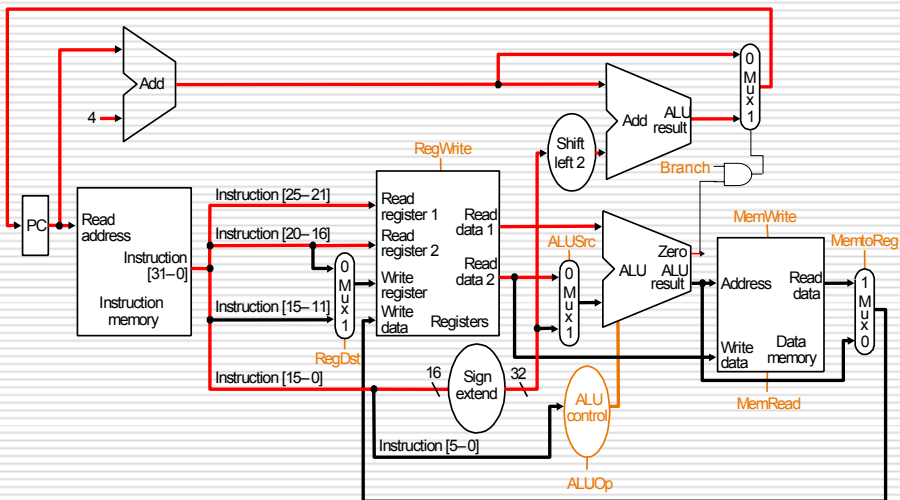
 
# Control


- Selecting the operations to perform (ALU, read/write, etc.)
- Controlling the flow of data (multiplexer inputs)
- Information comes from the 32 bits of the instruction
- Example:



- ALU's operation based on instruction type and function code

 
# Control

- e.g., what should the ALU do with this instruction
- Example: lw \$1, 100(\$2)



- ALU control input

000	AND
001	OR
010	add
110	subtract
111	set-on-less-than

 

- Why is the code for subtract 110 and not 011? What do you need for slt instruction?

# Control the ALU


- Must describe hardware to compute 3-bit ALU control input
    - given instruction type
      - 00 = lw, sw
      - 01 = beq,
      - 11 = arithmetic (incl. slt)
    - function code for arithmetic
- ALUOp  
computed from instruction type
- Describe it using a truth table (can turn into gates):



	ALUOp		Funct field					ALU Control		
	ALUOp1	ALUOp0	F5	F4	F3	F2	F1			F0
lw/sw	0	0	X	X	X	X	X	X	010	add
beq	X	1	X	X	X	X	X	X	110	sub
arith	1	X	X	X	0	0	0	0	010	add
	1	X	X	X	0	0	1	0	110	sub
	1	X	X	X	0	1	0	0	000	and
	1	X	X	X	0	1	0	1	001	or
	1	X	X	X	1	0	1	0	111	slt

Generated from inst[5:0]  
Decoding inst[31:26]
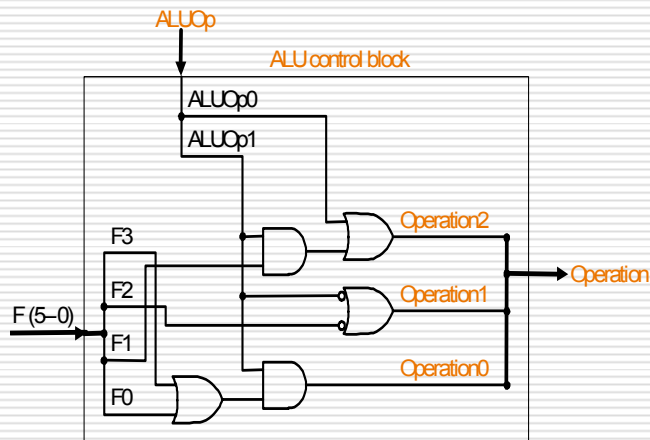
# ALU Control

- Simple combinational logic (truth tables)



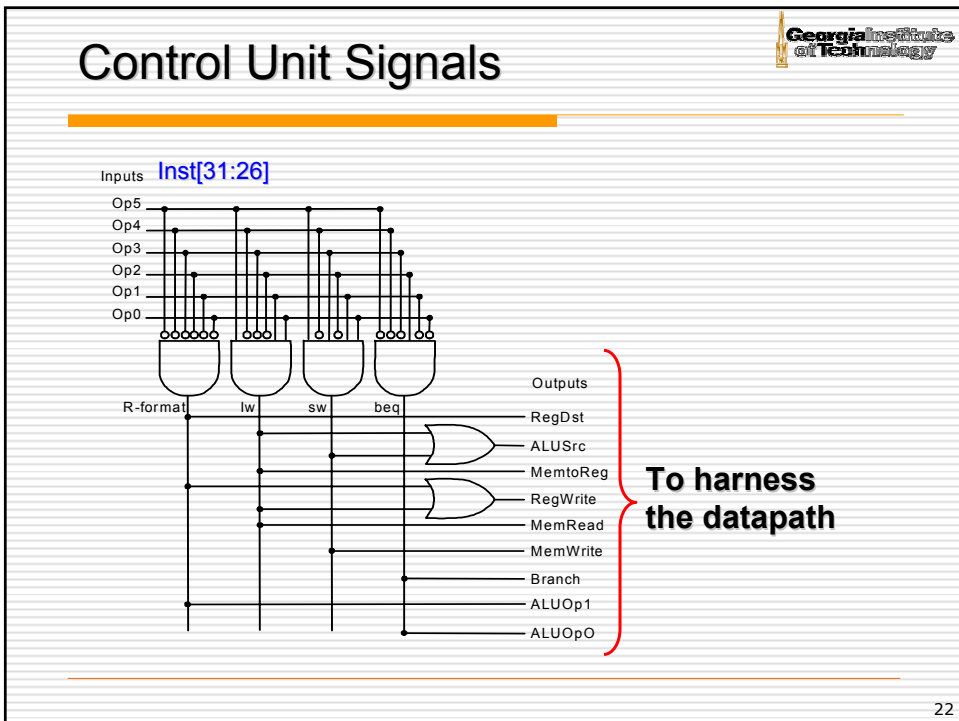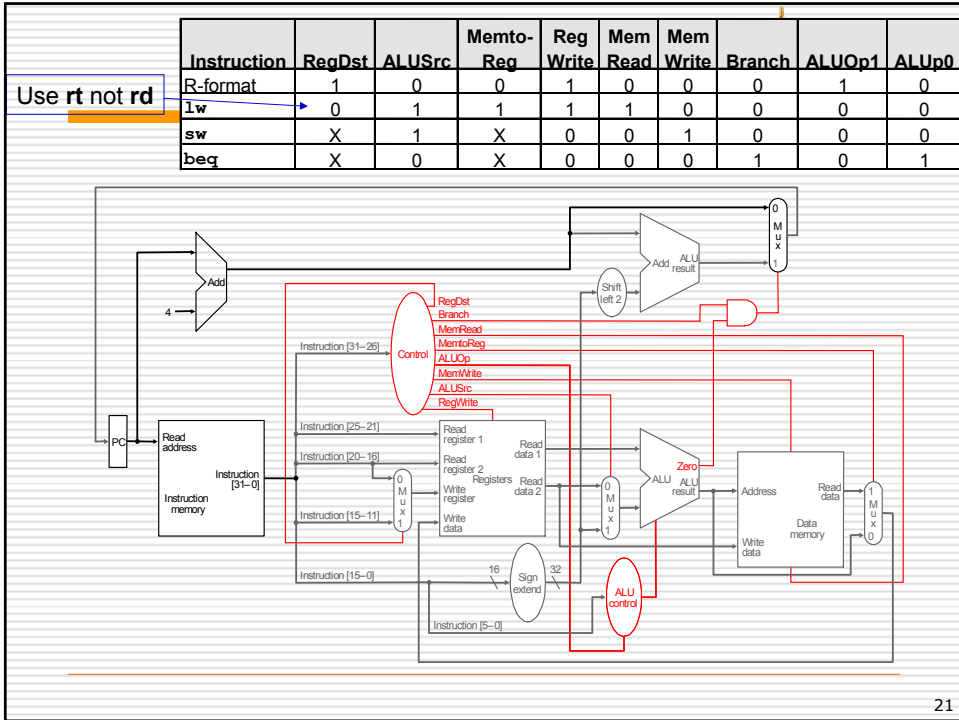

## Controller Implementation

```

□ LIBRARY IEEE;
□ USE IEEE.STD_LOGIC_1164.ALL;
□ USE IEEE.STD_LOGIC_ARITH.ALL;
□ USE IEEE.STD_LOGIC_SIGNED.ALL;

□ ENTITY control IS
□ PORT(
□     SIGNAL Opcode           : IN     STD_LOGIC_VECTOR( 5 DOWNTO 0 );
□     SIGNAL RegDst           : OUT    STD_LOGIC;
□     SIGNAL ALUSrc           : OUT    STD_LOGIC;
□     SIGNAL MemtoReg         : OUT    STD_LOGIC;
□     SIGNAL RegWrite         : OUT    STD_LOGIC;
□     SIGNAL MemRead          : OUT    STD_LOGIC;
□     SIGNAL MemWrite         : OUT    STD_LOGIC;
□     SIGNAL Branch           : OUT    STD_LOGIC;
□     SIGNAL ALUOp            : OUT    STD_LOGIC_VECTOR( 1 DOWNTO 0 );
□     SIGNAL clock, reset     : IN     STD_LOGIC );

□ END control;

```

23

## Controller Implementation (cont.)

```

□ ARCHITECTURE behavior OF control IS
□     SIGNAL R_format, Lw, Sw, Beq : STD_LOGIC;

□ BEGIN
□     -- Code to generate control signals using opcode bits
□     R_format <= '1' WHEN Opcode = "000000" ELSE '0';
□     Lw       <= '1' WHEN Opcode = "100011" ELSE '0';
□     Sw       <= '1' WHEN Opcode = "101011" ELSE '0';
□     Beq      <= '1' WHEN Opcode = "000100" ELSE '0';
□     RegDst   <= R_format;
□     ALUSrc   <= Lw OR Sw;
□     MemtoReg <= Lw;
□     RegWrite <= R_format OR Lw;
□     MemRead  <= Lw;
□     MemWrite <= Sw;
□     Branch   <= Beq;
□     ALUOp( 1 ) <= R_format;
□     ALUOp( 0 ) <= Beq;

□ END behavior;

```




*Implementation  
of each table  
column*

24
 
## Our Simple Control Structure

- All of the logic is combinational
- We wait for everything to settle down, and the right thing to be done
  - ALU might not produce “right answer” right away
  - we use write signals along with clock to determine when to write
- Cycle time determined by length of the longest path




*We are ignoring some details like **setup** and **hold times***

## Extending the Datapath

- Add new instructions
  - j or jal
- Modifications to the datapath
  - Determine data flows
  - Add control elements (muxes)
  - Modify datapath control
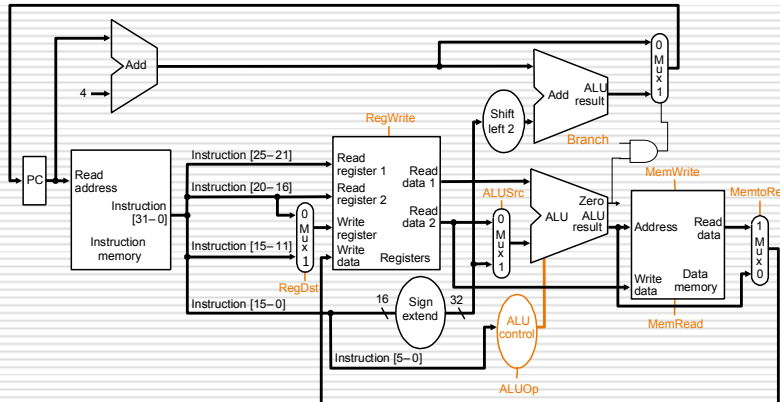
# Single Cycle Implementation

- Calculate cycle time assuming negligible delays except:
  - memory (2ns), ALU and adders (2ns), register file access (1ns)



# Where we are headed

- Single Cycle Problems:
  - what if we had a more complicated instruction like floating point?
  - wasteful of area
- One Solution:
  - use a “smaller” cycle time
  - have different instructions take different numbers of cycles
  - a “multicycle” datapath:

