



# ECE 3042

## Homework Assignment No. 3

Fall 2009 Homework for Experiment No. 3



**Due Week of September 14**

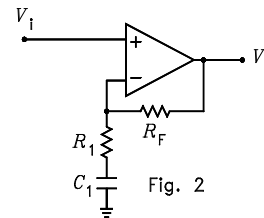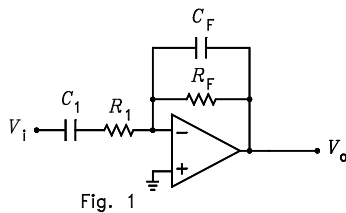1. Design an inverting bandpass op amp amplifier/filter with a midband voltage gain with a magnitude of 15, a lower  $-3\text{dB}$  frequency of  $100\text{ Hz}$ , and an upper  $-3\text{dB}$  frequency of  $10\text{ kHz}$ . The circuit shown in Fig. 1 is suggested. Pick the capacitor  $C_1 = 0.1\ \mu\text{F}$  and compute the other components. Perform an ac analysis with either Cadence or National Instruments SPICE to plot the magnitude of the voltage gain as a function of frequency as the frequency ranges from  $1\text{ Hz}$  to  $1\text{ MHz}$ . Assume that the op amp is ideal. Plot the magnitude and phase of the frequency response with Mathcad.



2. Design an op amp noninverting high pass shelving amplifier/filter. The dc gain is to be 1, the infinite frequency gain 15, and the pole frequency  $10\text{ kHz}$ . The circuit shown in Fig. 2 is suggested. Pick  $C_1 = 0.1\ \mu\text{F}$  and solve for the other circuit components. Perform an ac analysis with either Cadence or National Instruments SPICE to plot the magnitude of the voltage gain as a function of frequency as the frequency ranges from  $1\text{ Hz}$  to  $1\text{ MHz}$ . Assume that the op amp is ideal. Plot the magnitude and phase of the frequency response with Mathcad.

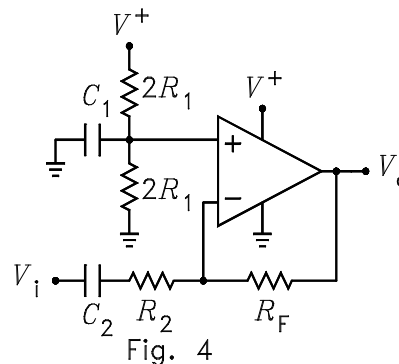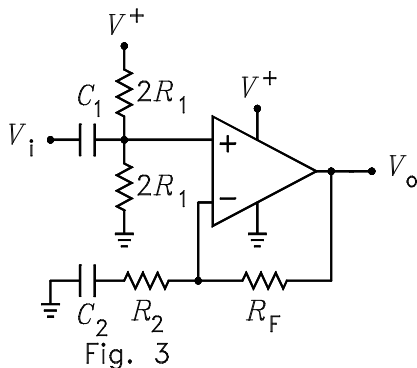3. Design an opamp noninverting amplifier/filter that uses a single dc power supply. The input is to be capacitively coupled to prevent dc voltage from appearing on the source. The circuit is to have a high pass characteristic with a high frequency gain of 15 and a pole frequency of  $10\text{ kHz}$ . The circuit shown in Fig. 3 is suggested. Pick  $C_1 = C_2 = 0.1\ \mu\text{F}$  and compute the other circuit components. Perform an ac analysis with either Cadence or National Instruments SPICE to plot the magnitude of the voltage gain as a function of frequency as the frequency ranges from  $1\text{ Hz}$  to  $1\text{ MHz}$ . Assume that the op amp is ideal. Plot the magnitude and phase of the frequency response with Mathcad.



4. Design an opamp inverting amplifier/filter that uses a single dc power supply. The input is to be capacitively coupled to prevent dc voltage from appearing on the source. The circuit is to have a high pass characteristic with a high frequency gain with a magnitude of 15 and a pole frequency of  $10\text{ kHz}$ . The circuit shown in Fig. 4 is suggested. Pick  $C_1 = C_2 = 0.1\ \mu\text{F}$  and compute the other circuit components. Perform an ac analysis with either Cadence or National Instruments SPICE to plot the magnitude of the voltage gain as a function of frequency as the frequency ranges from  $1\text{ Hz}$  to  $1\text{ MHz}$ . Assume that the op amp is ideal. The value of  $R_1$  is irrelevant. Plot the magnitude and phase of the frequency response with Mathcad.