

ECE 3042

Homework Assignment No. 6

Fall 2009 Homework Problem Set for Experiment No. 5

Due Week of October 19

1. Use either Cadence or National Instruments SPICE to plot the voltage transfer characteristic V_o versus V_i for the circuit shown below for $-9\text{ V} \leq V_i \leq 9\text{ V}$. Assume that the op amp is ideal and that each of the four diodes is a 1N4148 (use the PSpice model for the 1N4148 diode). The component values are: $V^+ = 15\text{ V}$, $V^- = -15\text{ V}$, $R_1 = 4.7\text{ k}\Omega$, $R_2 = 5.6\text{ k}\Omega$, $R_3 = 11\text{ k}\Omega$, and $R_4 = 15\text{ k}\Omega$. Compare the simulation results with the theoretically expected values with regard to break points and slopes. Also plot the currents in the four diodes as functions of V_i .

2. Use either Cadence or National Instruments SPICE to plot the output voltage $v_o(t)$ as a function of time for the circuit shown below if the input is

$$v_i(t) = A \sin(\omega t)$$

where $A = 3.7\text{ V}$ and $f = 1\text{ kHz}$ for two cycles of $v_i(t)$. Compare the peak value of the output with the theoretically expected value.

