

First Order Low Pass Active Filter
Specifications

$f_{crit} := 10.2\text{kHz}$ $j := \sqrt{-1}$

Non Inverting DC Gain 20dB 3dB Frequency f_{crit}

$K := 10^{\frac{20}{20}} = 10$ Pick $C := 0.1\mu\text{F}$ Pick $R_B = 3\text{k}\Omega$ $R_A = 27\text{k}\Omega$



$T(s) = K \cdot \frac{1}{1 + s\tau}$ $\tau = RC$

$K = T(0)$ $f_3 = \frac{1}{2\pi\tau}$

$f_3 := f_{crit}$
 $R := \frac{1}{2 \cdot \pi \cdot f_3 \cdot C} = 154.82\Omega$

$K = 1 + \frac{R_A}{R_B}$

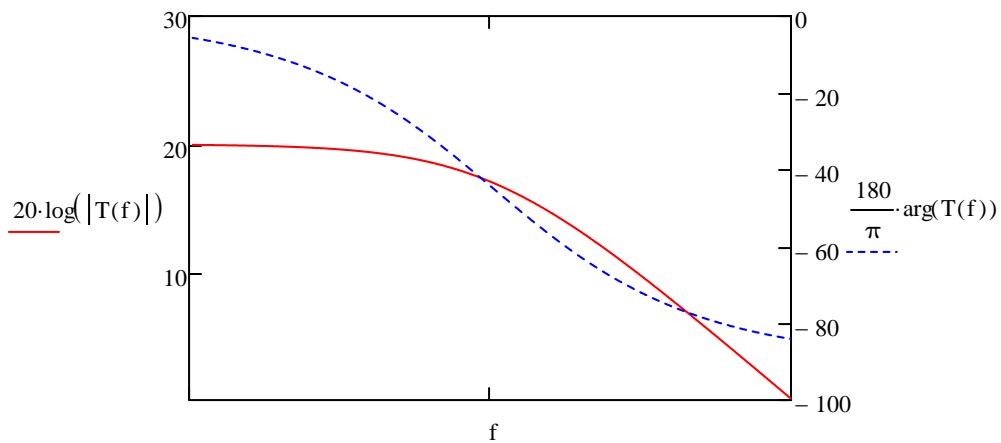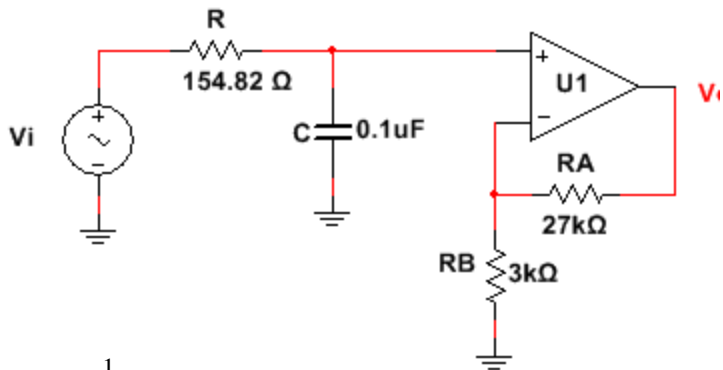$T(f) := K \cdot \frac{1}{1 + j \cdot \frac{f}{f_3}}$



A

B

C


D

E

F

G



H

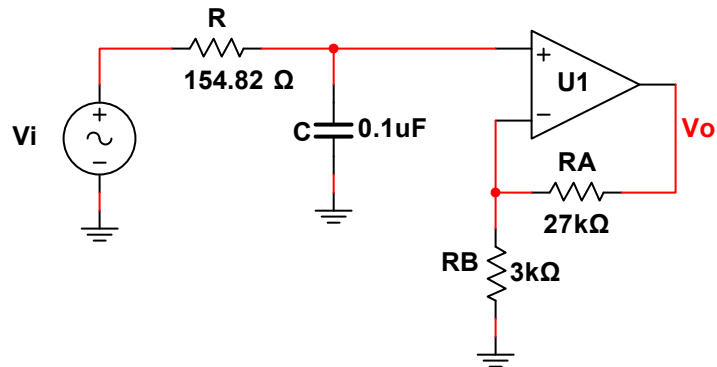

First Order

LPF_1st_Order
AC Analysis

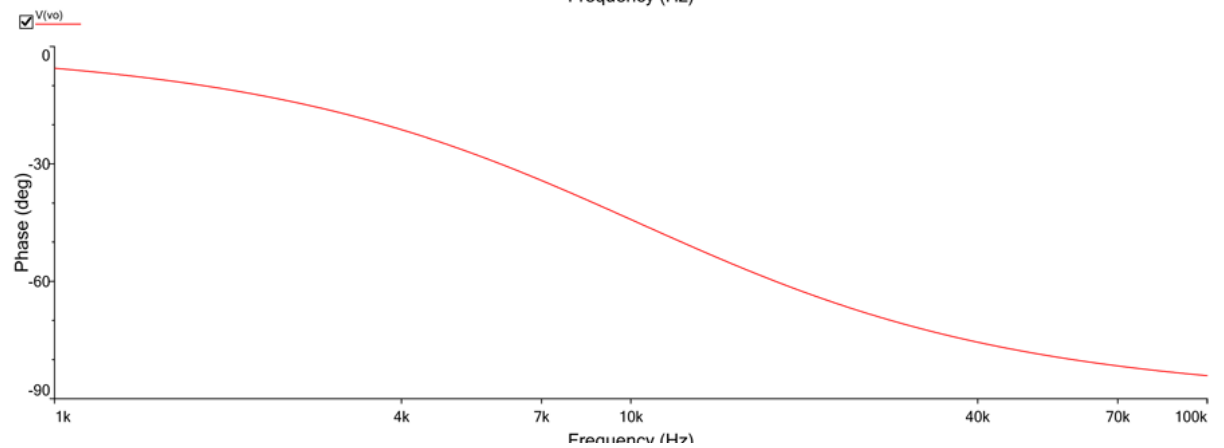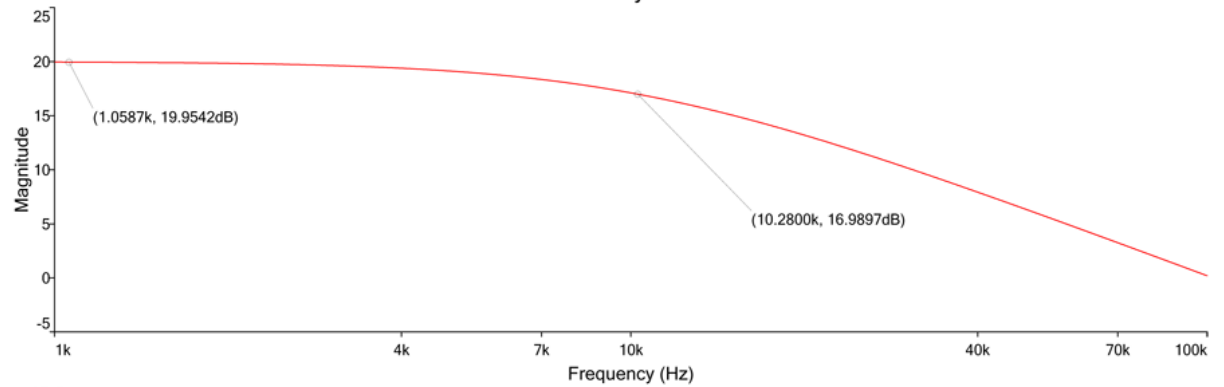
Printing Time: Tuesday, June 05, 2012, 8:15:25 PM



Low Pass Shelving Filter

$$j := \sqrt{-1}$$

$$f_{crit} := 10.28\text{kHz}$$

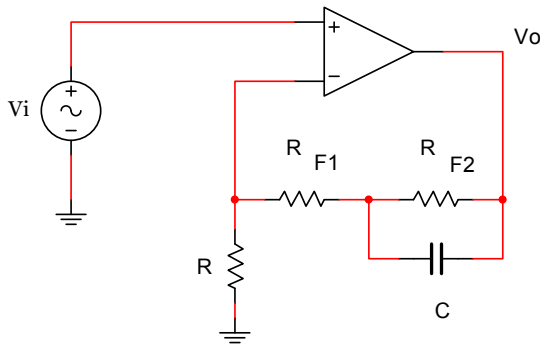

$$T(s) = K \cdot \frac{1 + s\tau_Z}{1 + s\tau_P}$$

$$T(0) = K = 1 + \frac{R_{F1} + R_{F2}}{R}$$

$$T(\infty) = 1 + \frac{R_{F1}}{R}$$

$$\tau_P = R_{F2}C$$

$$\tau_Z = [R_{F2} \parallel (R_{F1} + R)] \cdot C$$

$$f_p = \frac{1}{2\pi \cdot \tau_P}$$

$$f_z = \frac{1}{2\pi \tau_Z}$$

Specification

$$f_p := f_{crit}$$

DC gain

20dB

∞ frequency gain

6dB

Solution

Pick

$$C := 0.015\mu\text{F}$$

$$\tau_P := \frac{1}{2 \cdot \pi \cdot f_p}$$

$$R_{F2} := \frac{\tau_P}{C} = 1.032\text{k}\Omega$$

$$K := 10^{\frac{20}{20}} = 10$$

$$K_H := 10^{\frac{6}{20}} = 1.995$$

$$R := \frac{R_{F2}}{K - K_H} = 128.94\Omega$$


$$R_{F1} := R \cdot (K_H - 1) = 128.329\Omega$$


$$\tau_Z := \frac{K_H}{K} \cdot \tau_P$$

$$f_z := \frac{1}{2 \cdot \pi \cdot \tau_Z}$$

$$T(f) := K \cdot \frac{1 + j \cdot \frac{f}{f_z}}{1 + j \cdot \frac{f}{f_p}}$$

$$f_z = 51.522\text{kHz}$$

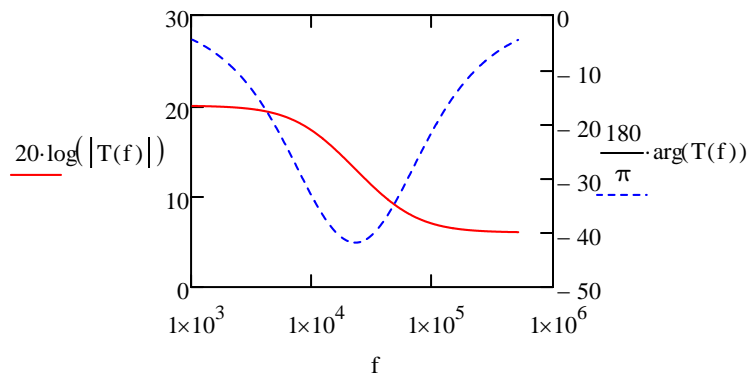


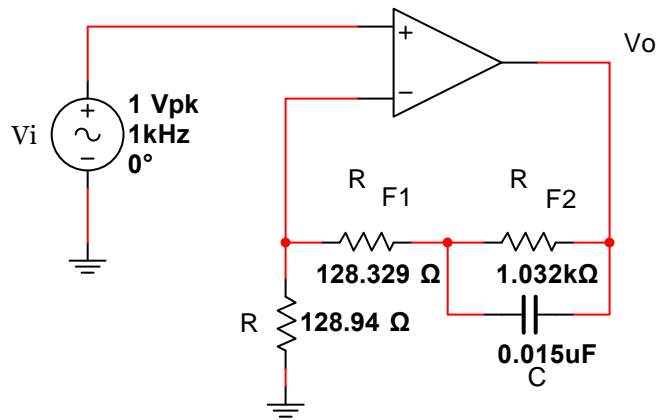


Low Pass Shelving Filter



Design1
AC Analysis

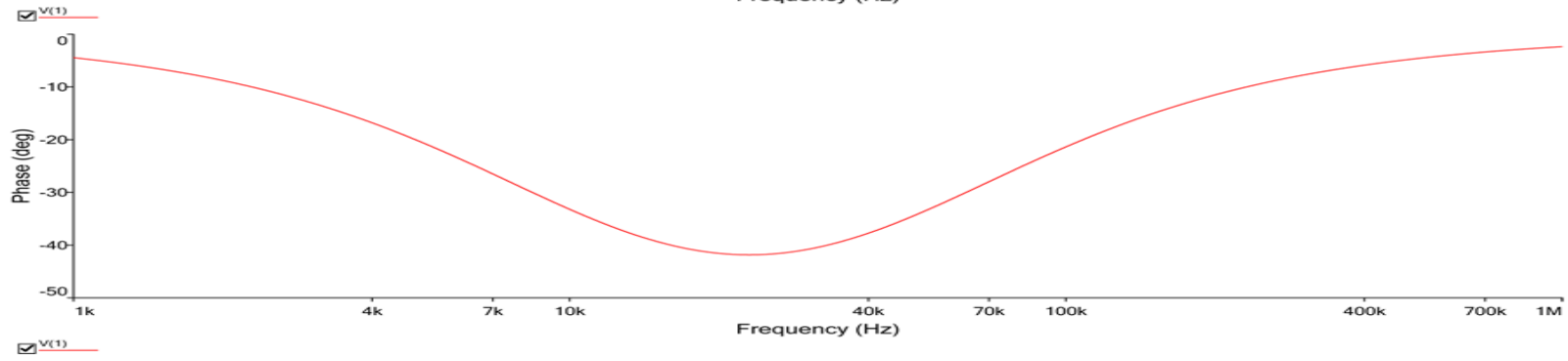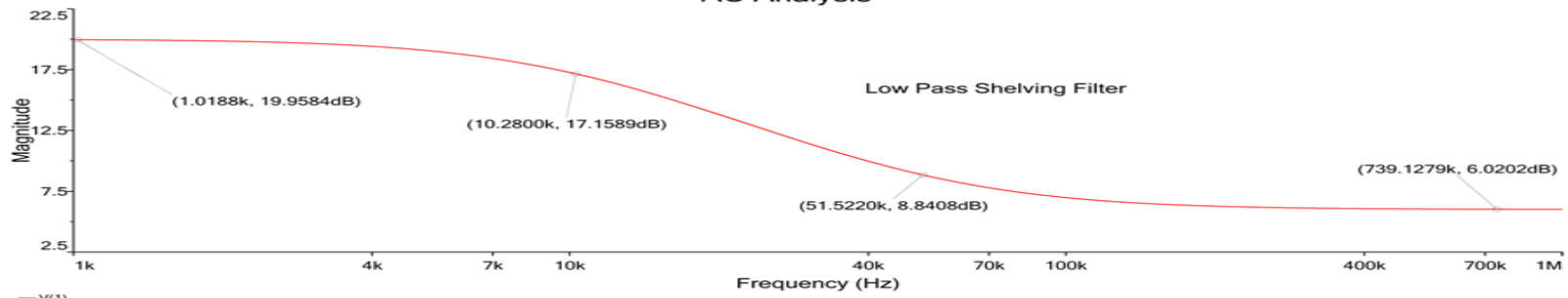
Printing Time: Monday, June 04, 2012, 7:46:34 PM



High Pass Shelving Filter

$$j := \sqrt{-1}$$

$$f_{crit} := 10.28 \text{ kHz}$$

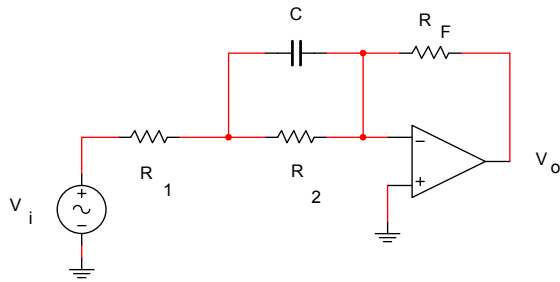

$$T(s) = K \cdot \frac{1 + s\tau_Z}{1 + s\tau_P}$$

$$T(0) = K = \frac{-R_F}{R_1 + R_2}$$

$$T(\infty) = \frac{-R_F}{R_1} \quad \tau_Z = R_2 C$$

$$\tau_P = (R_2 || R_1) \cdot C$$

$$f_p = \frac{1}{2\pi \cdot \tau_P}$$

$$f_z = \frac{1}{2\pi \tau_Z}$$

Specification

$$f_z := f_{crit}$$

DC gain 6dB

∞ frequency gain 20dB

Solution

Pick

$$C := 0.015 \mu\text{F}$$

$$\tau_Z := \frac{1}{2 \cdot \pi \cdot f_z}$$

$$R_2 := \frac{\tau_Z}{C} = 1.032 \text{ k}\Omega$$

$$K := -(10)^{\frac{6}{20}} = -1.995$$

$$K_H := -10^{\frac{20}{20}} = -10$$

$$R_F := \frac{R_2}{\frac{1}{K_H} - \frac{1}{K}} = 2.573 \text{ k}\Omega$$


$$R_1 := \frac{-R_F}{K_H} = 257.27 \Omega$$


$$\tau_P := \frac{K}{K_H} \cdot \tau_Z$$

$$f_p := \frac{1}{2 \cdot \pi \cdot \tau_P}$$


$$T(f) := K \cdot \frac{1 + j \cdot \frac{f}{f_z}}{1 + j \cdot \frac{f}{f_p}}$$

$$f_p = 51.522 \text{ kHz}$$

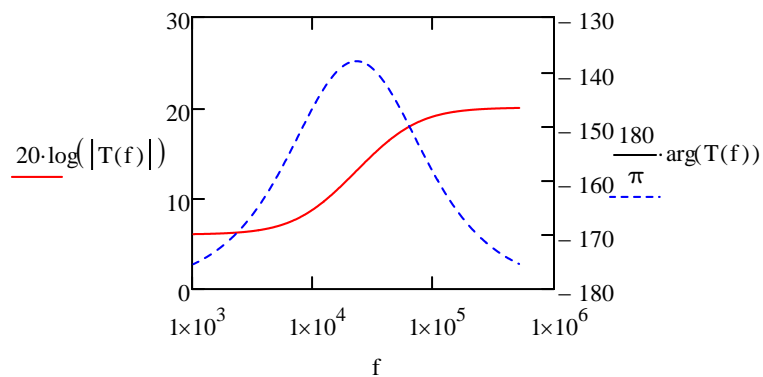

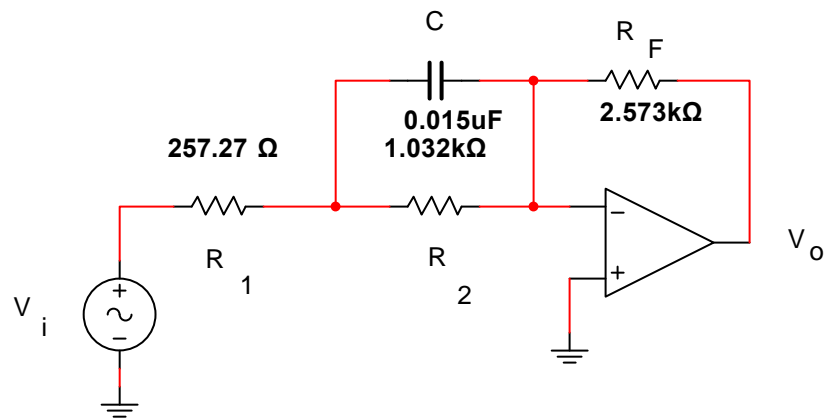


High Pass Shelving Filter

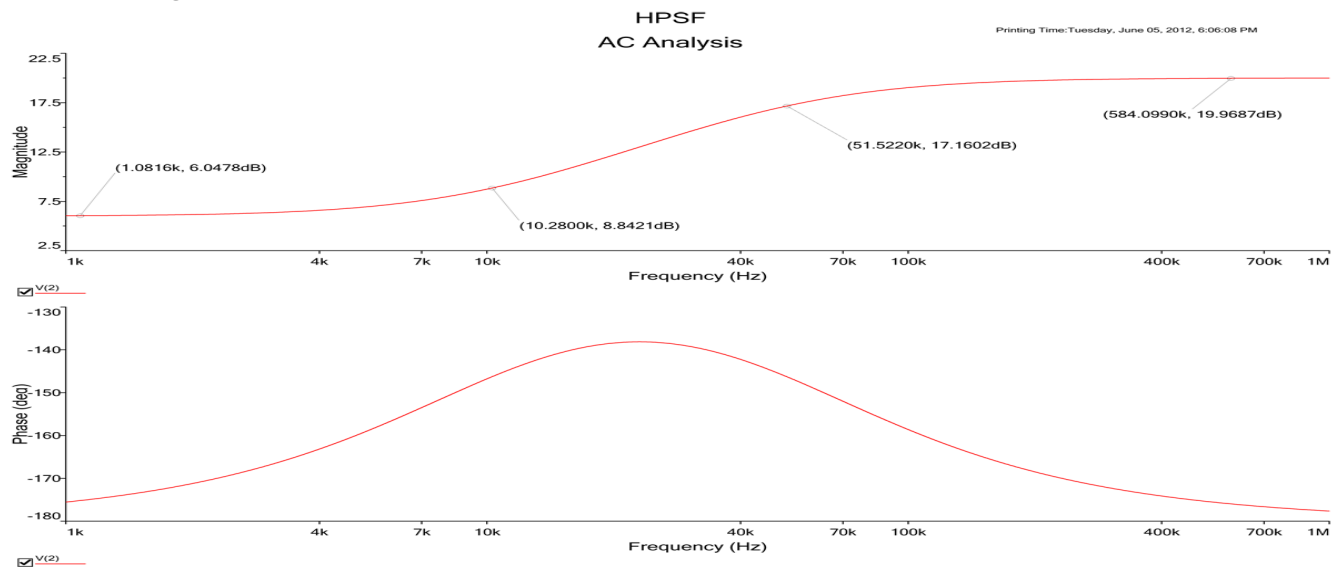

First Order All Pass Filter Inverting Phase

$$j := \sqrt{-1}$$

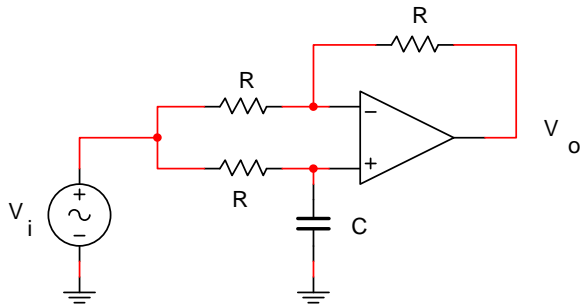

$$T(s) = K \cdot \frac{1 - s\tau}{1 + s\tau}$$

$$K = 1 \quad \tau = RC$$

Frequency at which phase shift is - 90 degrees

$$f_0 = \frac{1}{2\pi \tau}$$

Specification

$$f_{\text{crit}} := 10.28 \text{ kHz}$$

$$f_0 := f_{\text{crit}}$$


Pick


$$C := 0.015 \mu\text{F}$$

$$K := 1$$

$$R := \frac{1}{2 \cdot \pi \cdot C \cdot f_0} = 1.032 \text{ k}\Omega$$
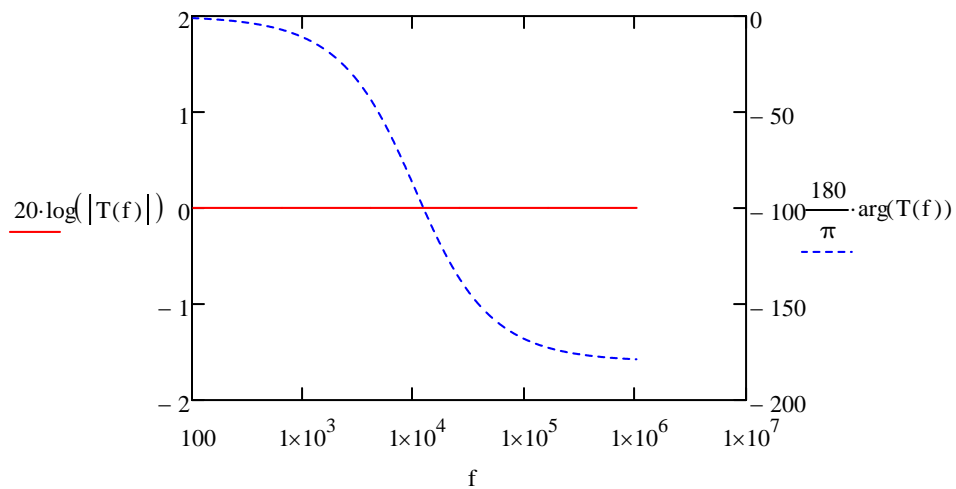
$$T(f) := K \cdot \frac{1 - j \cdot \frac{f}{f_0}}{1 + j \cdot \frac{f}{f_0}}$$





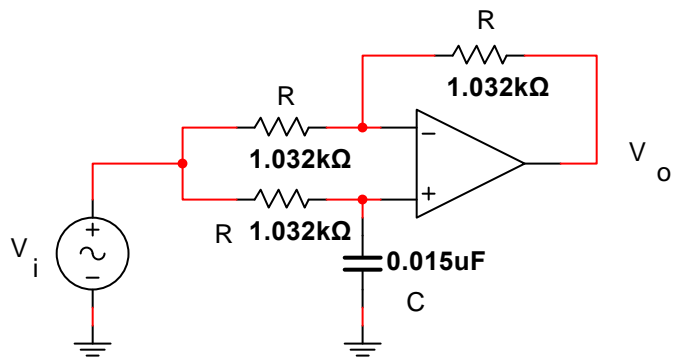

First Order Inverting All Pass Filter

Design1
AC Analysis

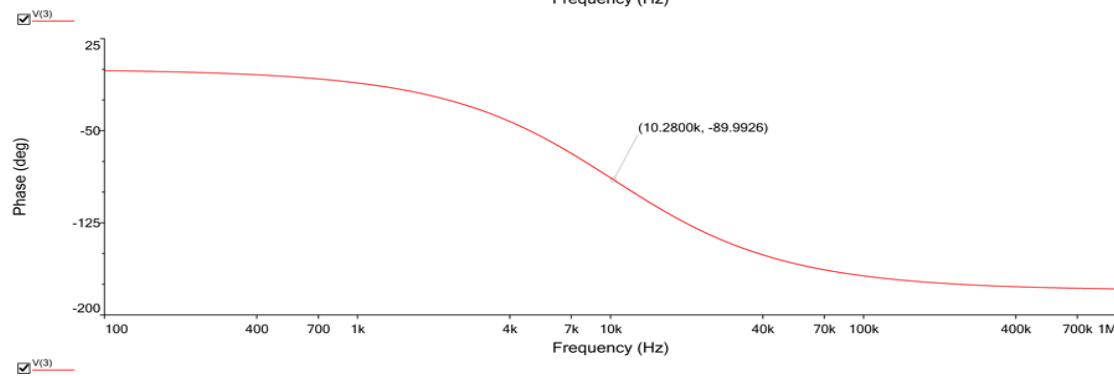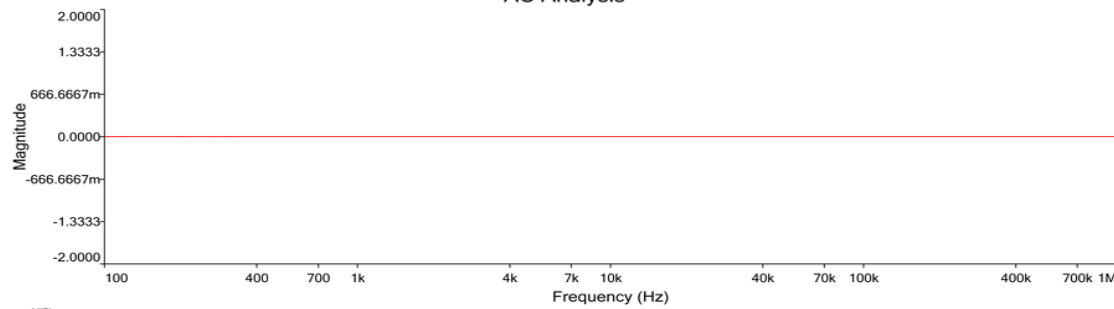Printing Time: Tuesday, June 05, 2012, 7:41:08 PM



Georgia Institute of Technology

School of Electrical and Computer Engineering

ECE 3043

Electrical and Electronic Circuits Laboratory

Verification Sheet

NAME: _____

SECTION: _____

AD LOGIN: _____

Experiment 7: First Order Active Filters

| Procedure | Time Completed | Date Completed | Verification (Must demonstrate circuit) | Points Possible | Points Received |
|------------------------------|----------------|----------------|---|-----------------|-----------------|
| 1. Low Pass | | | | 20 | |
| 2. High Pass | | | | 20 | |
| 3. High Pass Shelving | | | | 20 | |
| 4. Low Pass Shelving | | | | 20 | |
| 5. All-Pass | | | | 20 | |

If you were born on or before June 30, your critical frequency is found from your birthday as Month.Day kHz. If you were born after June 30, your critical frequency is (Month.Day/2) kHz. Ex 1: If you were born on March 3, your critical frequency is 3.03 kHz. Ex 2: If you were born on December 18, your critical frequency is 6.09 kHz.

Enter your critical frequency below:

| | |
|------------|--|
| f_{crit} | |
|------------|--|

To be permitted to complete the experiment during the open lab hours, you must complete at least **three** procedures during your scheduled lab period or spend your entire scheduled lab session attempting to do so. A signature below by your lab instructor, Dr. Brewer, or Dr. Robinson permits you to attend the open lab hours to complete the experiment and receive full credit on the report. Without this signature, you may use the open lab to perform the experiment at a 50% penalty.

SIGNATURE: _____

DATE: _____

ECE 3043 Check-off Requirements for Experiment 7

Make sure you have made all required measurements before requesting a check-off. For all check-offs, you must demonstrate the circuit or measurement to a lab instructor. All screen captures must have a time/date stamp.

1 & 2. Low Pass and High Pass Filters

- ✓ Bode magnitude plot
- ✓ Table showing measured pass band gain and -3dB frequencies compared to design values

3 & 4. Low and High Pass Shelving Filters

- ✓ Bode magnitude plot
- ✓ Table showing measured low frequency gain, high frequency gain, and gain at f_{crit} compared to design values

5. All Pass Filter

- ✓ Bode Phase Plot
- ✓ Measure frequency where phase shift is 90 degrees. Compare to f_{crit} .