

ECE 3043

Spring 2077

Section L01 Tu 12-3

Homework No 1

Due February 31




Thomas E. Brewer

AD Login: gt1234

ECE 3043 Spring 2077
Homework Problem Set No 1 for Experiment No. 2

Due Week of February 31

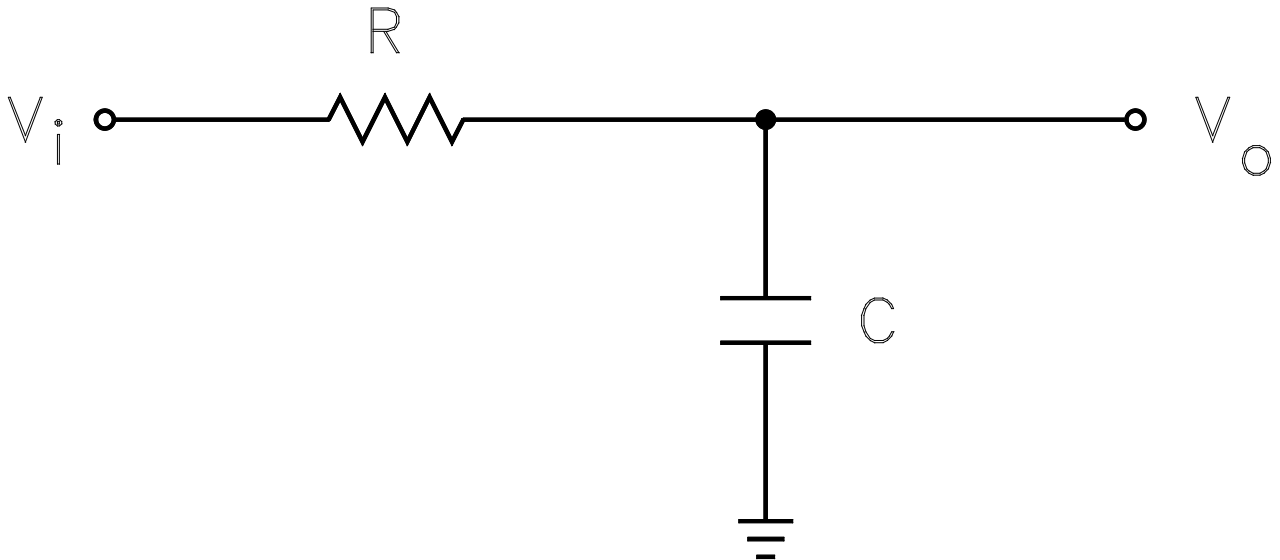


1. For the circuit shown above derive the complex transfer function $T(s) = V_o/V_i$. Express it as a function of the symbols for the resistor and capacitor and the complex frequency variable s . Simplify it as

$$T(s) = K \frac{1 + s\tau_z}{1 + s\tau_p} \quad (1)$$

Compute the dc gain in dB and the pole and zero frequencies in Hz.

2. Plot the Bode plot for the circuit using Mathcad. Plot the frequency response one decade below the lowest critical frequency and one decade above the highest critical frequency. Plot the magnitude in dB and the phase in degrees. The values of the circuit components are $R = 10 \text{ k}\Omega$ and $C = 0.1 \mu\text{F}$.
3. Make the same plot as in Problem 2 using Matlab.
4. Make the same plot as in Problem 2 using National Instruments SPICE (Multisim).
5. Make the same plot as in Problem 2 using LTSpice (text editor input mode).

Derivation of Transfer Function

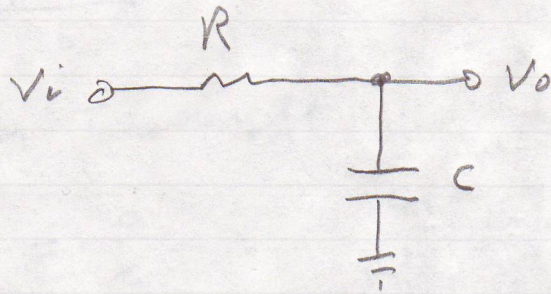

$$R = 10 \text{ k}\Omega$$
$$C = 0.1 \mu\text{F}$$

$$T(\omega) = \frac{V_o}{V_i} = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} = \frac{1}{1 + sRC}$$

$$T(s) = K \frac{1 + s\tau_z}{1 + s\tau_p} \quad K = 1 \quad \tau_z = 0$$
$$\tau_p = RC$$


$$\text{DC gain} = 20 \log_{10} |T(0)| = 0 \text{ dB}$$

$$\omega_p = \frac{1}{2\pi\tau_p} = \frac{1}{2\pi RC} = 159.1549 \text{ Hz}$$


```
-----  
Your MATLAB license will expire in 53 days.  
Please contact your system administrator or  
MathWorks to renew this license.  
-----
```

```
>> %Transfer Function Direct Evaluation  
>> f=logspace(0,4,100);%Specify Frequency Range 10^0 to 10^4 100 pts per decade  
>> j=sqrt(-1);R=10e3;C=0.1e-6;%Specify Component Values  
>> tau=R*C;fo=1/(2*pi*tau);%Compute Pole frequency  
>> T=1./(1+j*f/fo);%Transfer Function Specification  
>> plot(f,20*log10(abs(T)));%Plot Mag of Transfer Function Change Freq to log in Graph  
Properties  
>> plot(f,180*angle(T)/pi);%Plot Phase of Transfer Function Change Freq to log in Graph  
Properties  
>> %Transfer Function Using Bode Function  
>> N=[1];D=[tau 1];bode(N,D);%Numerator Poly, Denominator Poly, bode function  
>> %Use Graph Properties to change freq units to Hz
```

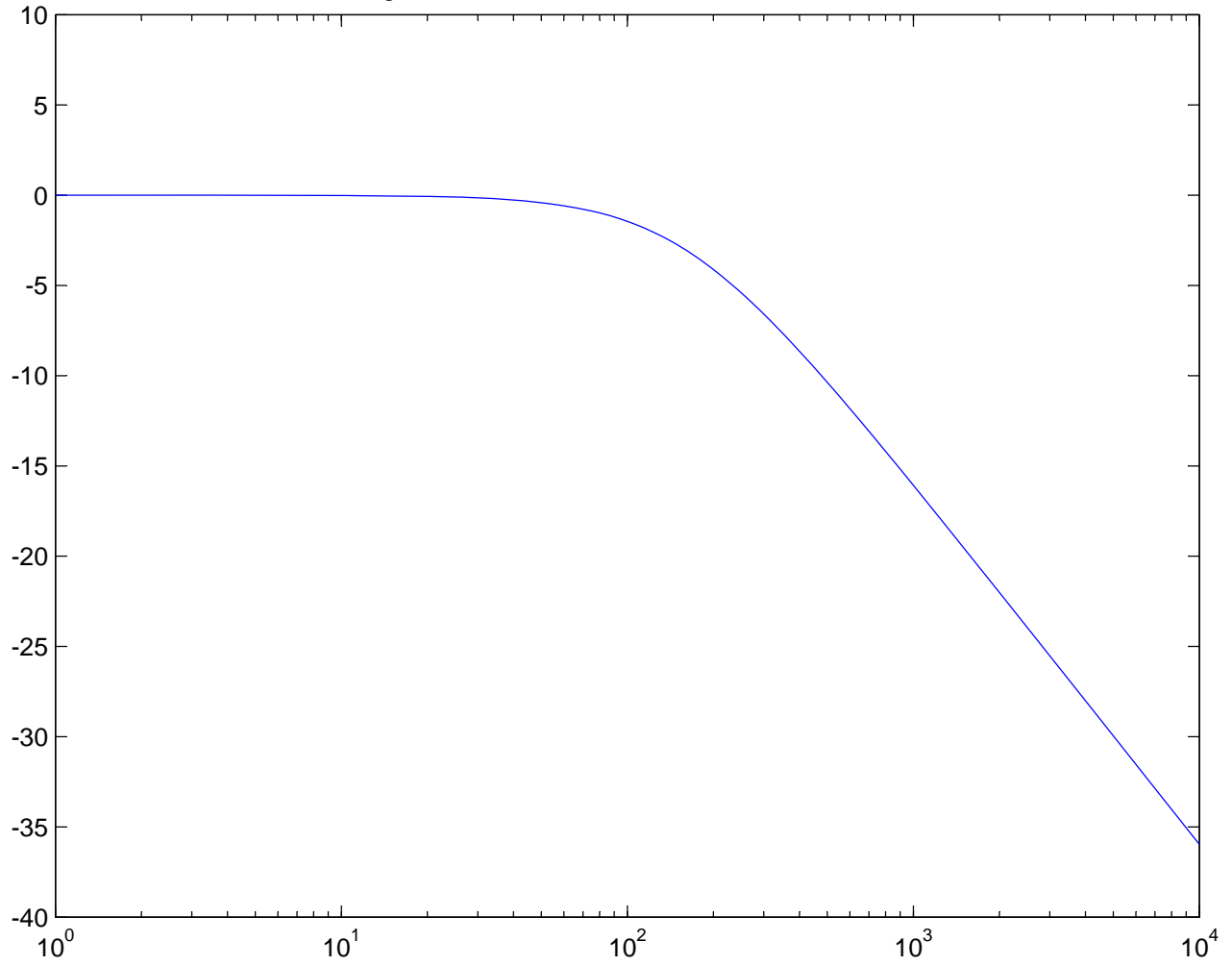
Magnitude of Transfer Function Direct Calculation



Phase versus Frequency Direct Evaluation

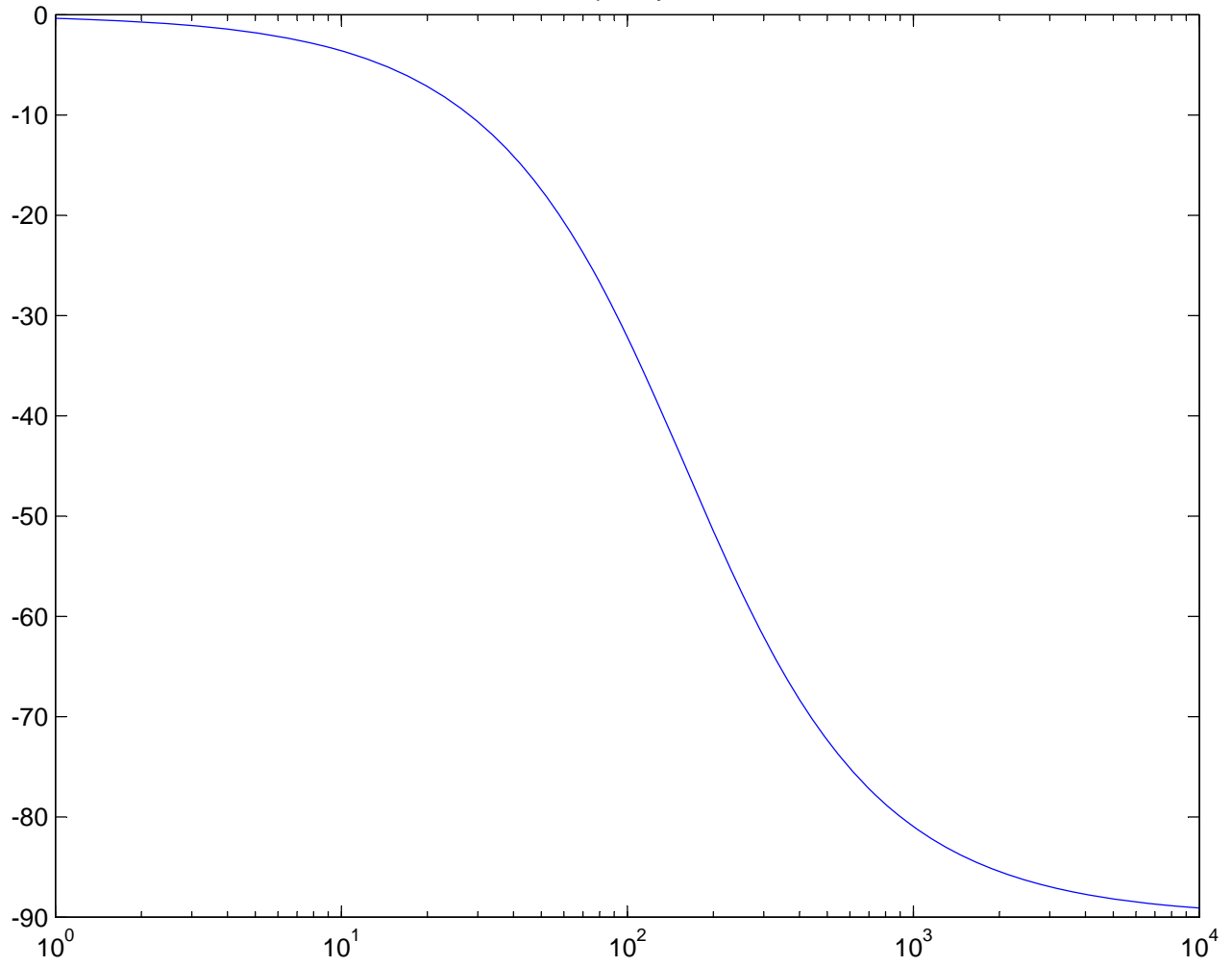

Bode Diagram Using Bode Function

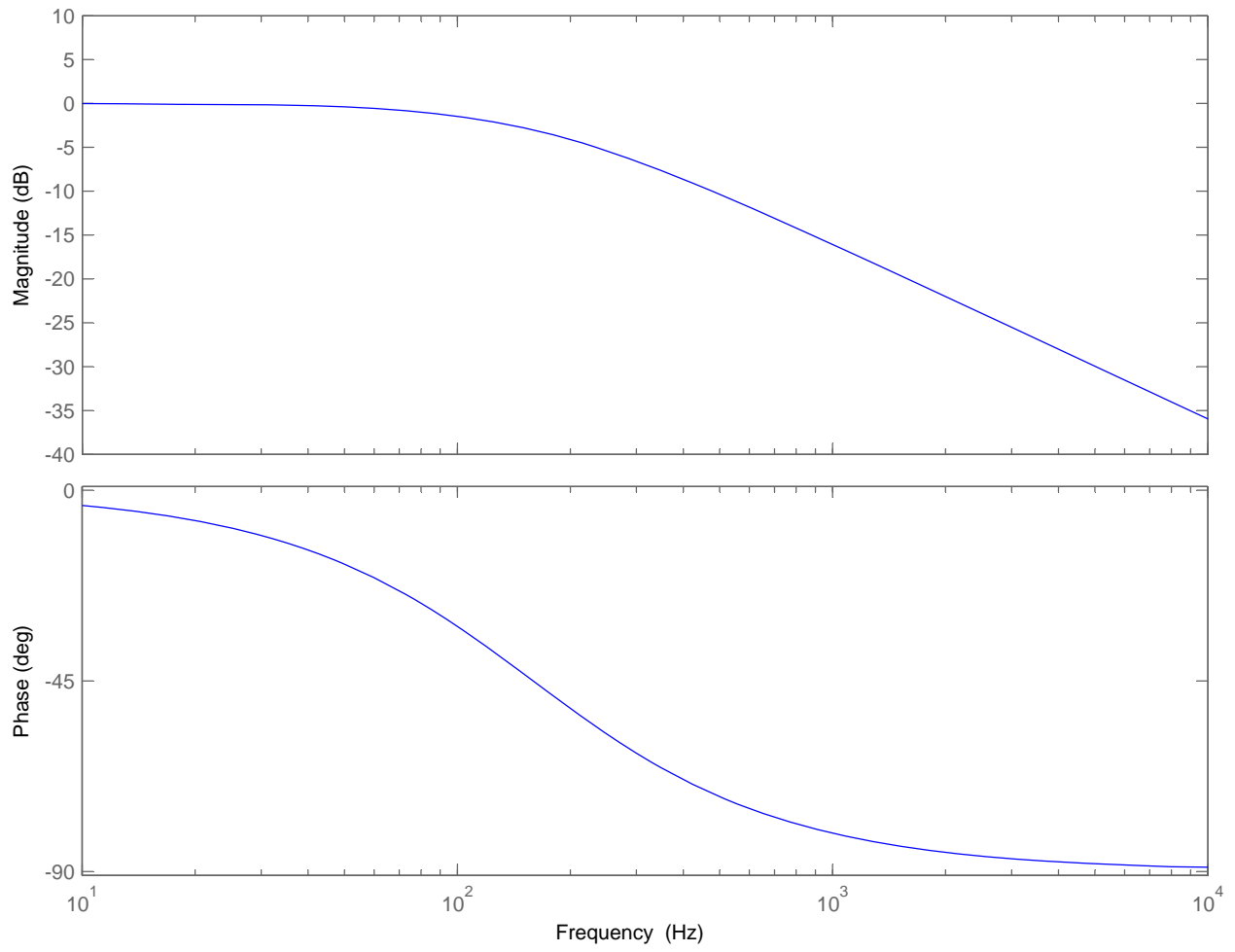

Spring 2077 Hwk No 1 Transfer Function
Mathcad

$$j := \sqrt{-1}$$

$$R := 10\text{k}\Omega$$

$$C := 0.1 \cdot \mu\text{F}$$

$$K := 1$$

$$R_p(A, B) := \frac{A \cdot B}{A + B}$$

$$\tau_p := R \cdot C$$

$$T(f) := K \cdot \frac{1}{1 + \tau_p \cdot (j \cdot 2 \cdot \pi \cdot f)}$$

$$f_p := \frac{1}{2 \cdot \pi \cdot \tau_p} = 159.155 \cdot \text{Hz}$$

$$f_{\text{start}} := 10\text{Hz}$$

$$f_{\text{stop}} := 10\text{kHz}$$


$$N := 1024$$

$$i := 0 \dots N - 1$$

$$f_i := f_{\text{start}} \left(\frac{f_{\text{stop}}}{f_{\text{start}}} \right)^{\frac{i}{N-1}}$$

$$M(f) := 20 \cdot \log(|T(f)|)$$
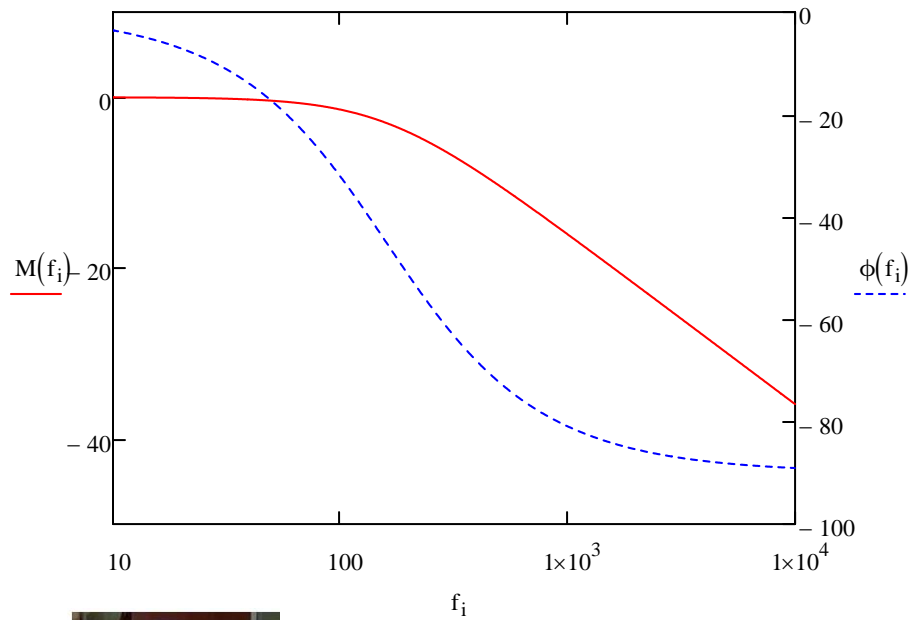
$$\phi(f) := \frac{180}{\pi} \cdot \arg(T(f))$$




Thomas E. Brewer
Academic Factotum

	0	1	2	3	4	5	6	7	8													
A	<div data-bbox="583 235 955 495" data-label="Diagram"> </div> <div data-bbox="1283 204 1577 483" data-label="Image"> </div> <div data-bbox="1010 716 1661 889" data-label="Table"> <table border="1"> <tr> <td colspan="3">Title:Example</td> </tr> <tr> <td>Size:</td> <td>Document N:</td> <td>Revision:</td> </tr> <tr> <td>A</td> <td>0001</td> <td>1.0</td> </tr> <tr> <td>Date:</td> <td>12/11/2012</td> <td>Sheet 1 of 1</td> </tr> </table> </div>										Title:Example			Size:	Document N:	Revision:	A	0001	1.0	Date:	12/11/2012	Sheet 1 of 1
Title:Example																						
Size:											Document N:	Revision:										
A											0001	1.0										
Date:											12/11/2012	Sheet 1 of 1										
B																						
C																						
D																						
E																						
F																						
G																						
	0	1	2	3	4	5	6	7	8													

Example


Printing Time: Tuesday, December 11, 2012, 6:22:47 PM

AC Analysis

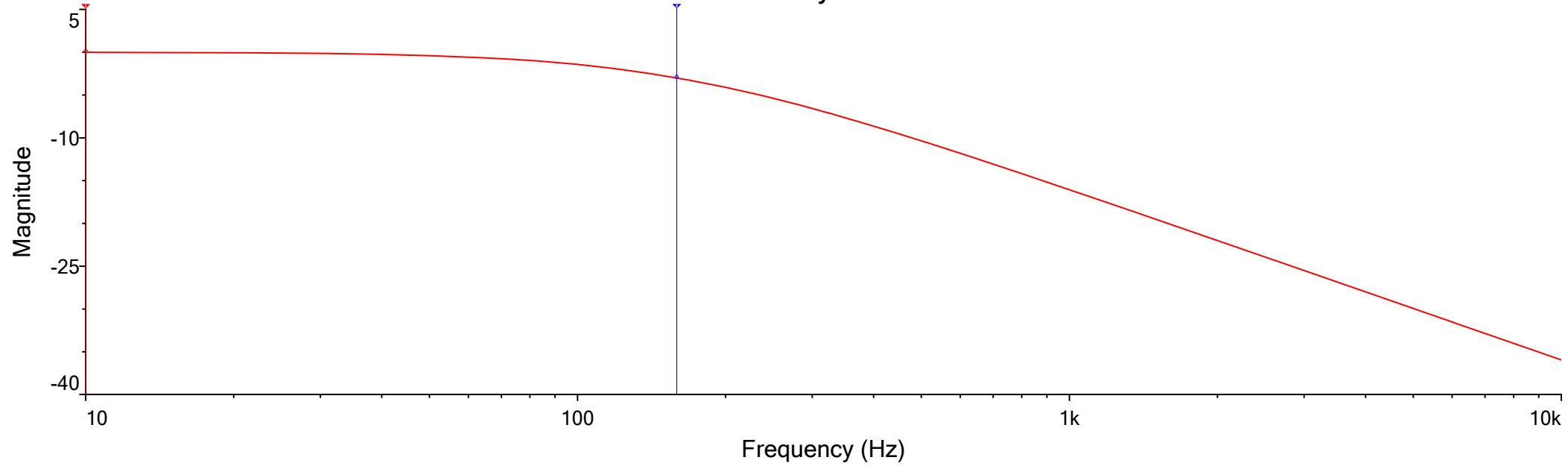

V(1)

	x1	y1	x2	y2	dx	dy	dy/dx	1/dx
V(1):	10.0000	-17.1116m	159.0903	-3.0087	149.0903	-2.9916	-20.0656m	6.7073m

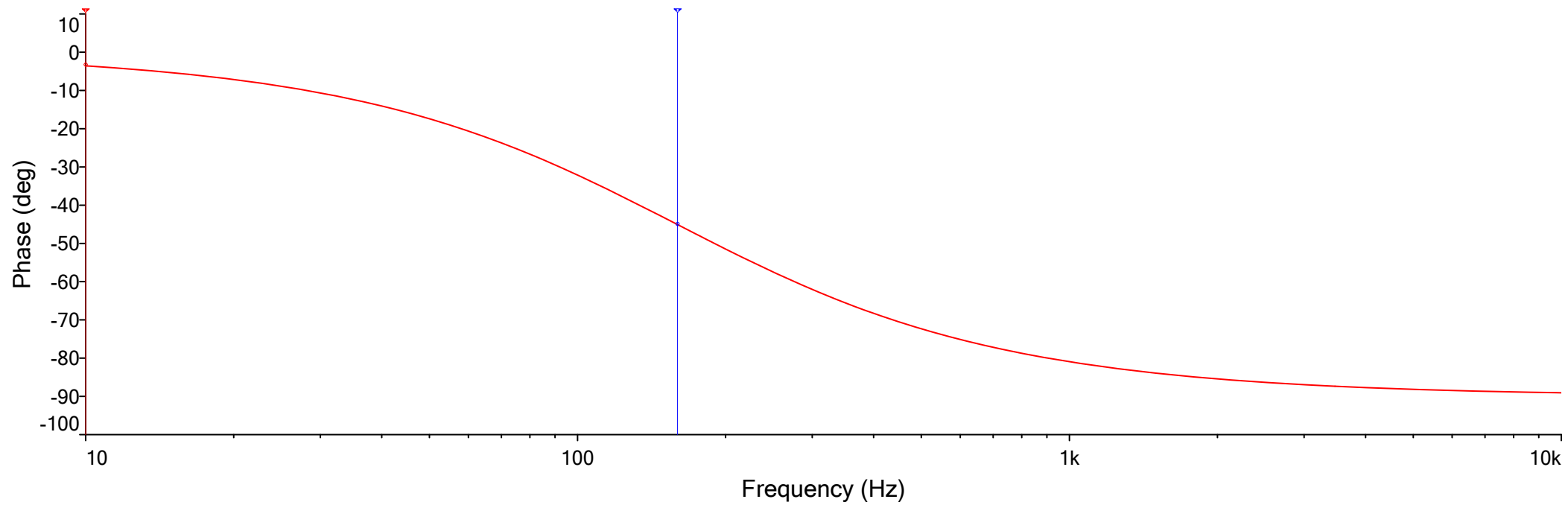

V(1)

	x1	y1	x2	y2	dx	dy	dy/dx	1/dx
V(1):	10.0000	-3.5953	159.6937	-45.0968	149.6937	-41.5015	-277.2430m	6.6803m

```
George P. Burdell  
Vi 1 0 ac 1  
R 1 2 10k  
C 2 0 0.1u  
.ac dec 100 10 10k  
.probe  
.end
```

