

# ECE 4043

## Spring 2020

### Homework for 7 for Experiment No. 7

Due Week of March 2

1. Shown below is a single stage common source amplifier biased by a current mirror current source. Bias the circuit so that the dc drain current is 1.86 mA, viz pick  $R_T$  so that the drain current in each transistor has this value. The small-signal input impedance is specified to be  $50\text{ k}\Omega$  and the small signal output impedance is  $5.1\text{ k}\Omega$  (Assume  $\lambda = 0$  for this specifications). The load resistor is  $10\text{ k}\Omega$ . The dc power supply voltages are  $V^+ = +15\text{ V}$  and  $V^- = -15\text{ V}$ . The parameters of the each transistor are:  $K = 1\text{ mA/V}^2$ ,  $V_{TO} = 1\text{ V}$ ,  $\lambda = 0.001\text{ V}^{-1}$ ,  $C_{GDO} = 2.5\text{ nF/m}$ , and  $C_{GSO} = 2.5\text{ nF/m}$ . Pick  $C_1 = C_2 = 22\text{ }\mu\text{F}$ , and  $C_3 = 330\text{ }\mu\text{F}$ .

Verify the design with a SPICE analysis using National Instruments SPICE Multisim .

For the SPICE analysis use a DC analysis to determine the bias. Use an AC analysis to plot the gain versus the frequency. Choose the lower frequency as 1 Hz and the upper frequency 10 GHz. Mark the midband gain and the  $-3\text{ dB}$  frequencies. The SPICE parameters are  $KP$  ( $2K$ ),  $V_{TO}$  ( $V_{TO}$ ),  $LAMBDA$  ( $\lambda$ ),  $CGDO$  ( $C_{GDO}$ ), and  $CGSO$  ( $C_{GSO}$ ). If the version of SPICE used requires the width ( $W$ ) and length ( $L$ ) of the channel use  $10\text{ }\mu\text{m}$  for each. Perform a transient analysis to determine the upper and lower clipping levels. (Remember the SPICE parameter  $KP = 2K$ .)

