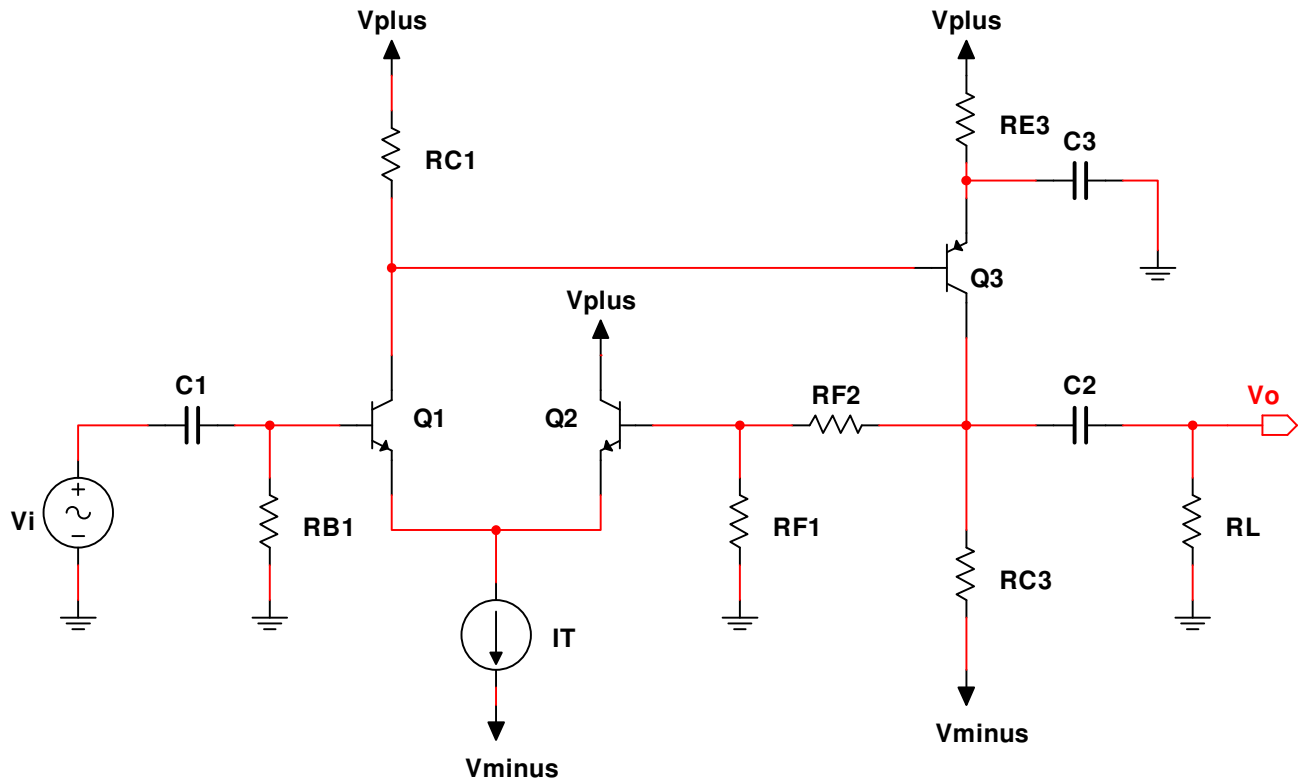


ECE 4043 Spring 2020

Homework Problem Set No 8 for Experiment No. 8

Due March 9, 2020



1. Shown above is a Series-Shunt feedback amplifier. The dc power supplies are $\pm 15\text{ V}$ and the ideal current source $I_T = 2\text{ mA}$. The component values are: $C_1 = C_2 = 22\ \mu\text{F}$, $R_{B1} = 51\ \text{k}\Omega$, $R_{C1} = 10\ \text{k}\Omega$, $R_{F1} = 10\ \text{k}\Omega$, $R_{F2} = 100\ \text{k}\Omega$, $R_{E3} = 3.1167\ \text{k}\Omega$, $R_{C3} = 5\ \text{k}\Omega$, and $R_L = 10\ \text{k}\Omega$. Compute the open loop gain and the feedback factor. Perform a SPICE simulation to obtain the Q point, small signal gain, and clipping behavior using National Instruments SPICE Multisim. The SPICE parameters for both the NPN and PNP BJTs are: Assume that the SPICE parameters for the NPN BJT are: saturation current, $6.734\ \text{fA}$; forward beta, 100; Early voltage, $170\ \text{V}$, zero-bias base collector capacitance, $3.638\ \text{pF}$; forward transit time, $301.2\ \text{ps}$, and base spreading resistance, $10\ \Omega$.

An exceedingly useful reference for this problem can be found at (Series-Shunt Example 4).

<https://leachlegacy.ece.gatech.edu/ece3050/notes/feedback/FBExamples.pdf>