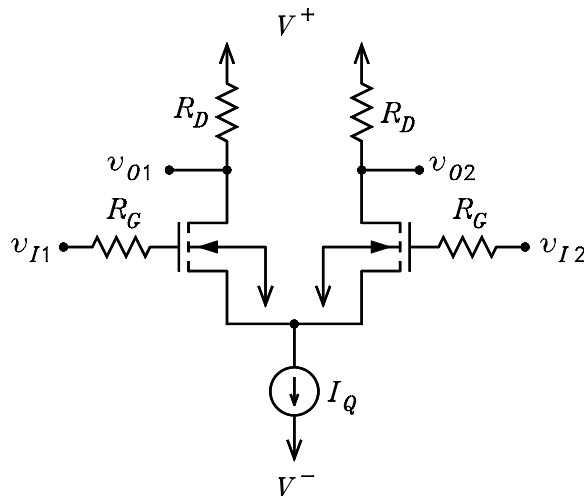


ECE3040 – Assignment 6

1. The figure shows a MOSFET differential amplifier. It is given that $K = 0.001 \text{ A/V}^2$, $V_{TH} = 2 \text{ V}$, $\lambda = 0$, $V^+ = 18 \text{ V}$, $V^- = -18 \text{ V}$, $I_Q = 3 \text{ mA}$, $R_D = 6.2 \text{ k}\Omega$, and $R_G = 100 \text{ k}\Omega$.



- (a) Show that $V_{GS} = 3.225 \text{ V}$ and $V_{DS} = 11.93 \text{ V}$.
 (b) For an ac small-signal analysis, show that

$$v_{o1} = -v_{o2} = -7.593 (v_{i1} - v_{i2})$$

- (c) Use the pi or T model of the MOSFETs to investigate whether the body effect cancels out if a resistor R_S is placed in series with the source lead of each MOSFET.

2. For the BJT, show that the base-to-collector current gain can be written

$$\beta = \frac{I_C - I_{CBO}}{I_B + I_{CBO}}$$

3. Calculate the values of β and I_S for the transistor shown if $V_{CB} = V_{BE} = 0.7 \text{ V}$, $I_B = 0.2 \text{ mA}$, and $I_E = 10 \text{ mA}$. [$\beta = 49$, $I_S = 6.78 \times 10^{-15} \text{ A}$]



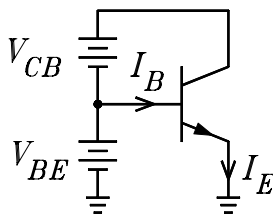


Figure 1:

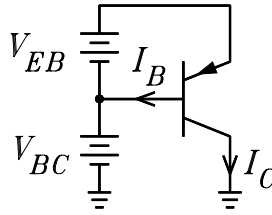
4. Calculate the values of β and I_S for the transistor shown if $V_{EB} = V_{BC} = 0.7 \text{ V}$, $I_B = 50 \mu\text{A}$, and $I_C = 2.5 \text{ mA}$. [$\beta = 50$, $I_S = 1.73 \times 10^{-15} \text{ A}$]



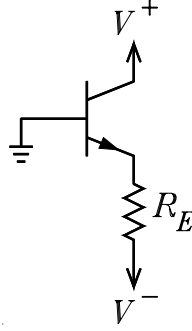
5. Calculate the collector, emitter, and base currents if $V^+ = 3.3\text{ V}$, $V_{EE} = -3.3\text{ V}$, $V_{BE} = 0.7\text{ V}$, $R_E = 47\text{ k}\Omega$, and $\beta = 90$. [$I_E = 55.3\ \mu\text{A}$, $I_B = 0.608\ \mu\text{A}$, $I_C = 54.7\ \mu\text{A}$]



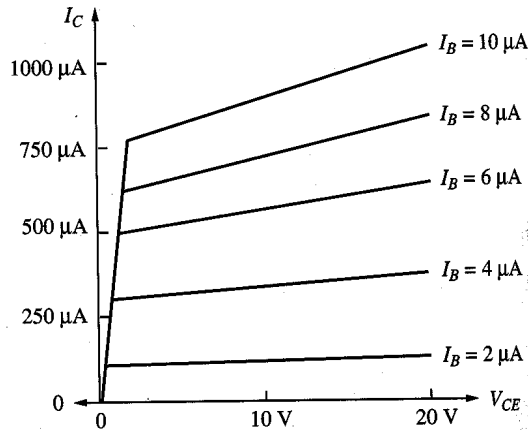
6. An npn transistor is operated in the active mode with a base current of $3\ \mu\text{A}$. It is found that $I_C = 240\ \mu\text{A}$ for $V_{CE} = 5\text{ V}$ and $I_C = 265\ \mu\text{A}$ for $V_{CE} = 10\text{ V}$. What are the values of β_0 and V_A for this transistor? [$\beta_0 = 71.7$, $V_A = 43.1\text{ V}$]
7. A BJT has the parameters $\beta_0 = 75$, $V_A = 100\text{ V}$, and $V_{CE} = 10\text{ V}$. Show that $\alpha = 0.9880$.
8. The output characteristics of a BJT are shown. (a) What are the values of β and β_0 at $I_B = 4\ \mu\text{A}$ and $V_{CE} = 10\text{ V}$? [$\beta = 90$, $\beta_0 = 120$] (b) What are the values of β and β_0 at $I_B = 8\ \mu\text{A}$ and $V_{CE} = 10\text{ V}$? [$\beta = 95$, $\beta_0 = 75$]



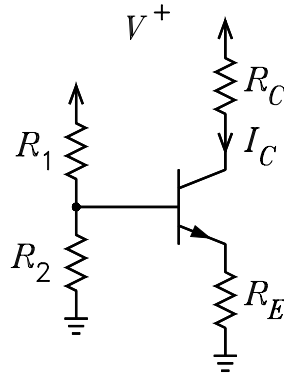9. Solve for I_C and V_{CB} for the values $V^+ = 18\text{ V}$, $R_E = 1\text{ k}\Omega$, $R_1 = 130\text{ k}\Omega$, $R_2 = 36\text{ k}\Omega$, $R_C = 2.4\text{ k}\Omega$, $V_{BE} = 0.7\text{ V}$, and $\beta = 99$. Is the BJT biased in the active mode? [$I_C = 2.474\text{ mA}$, $V_{CB} = 8.863\text{ V}$]



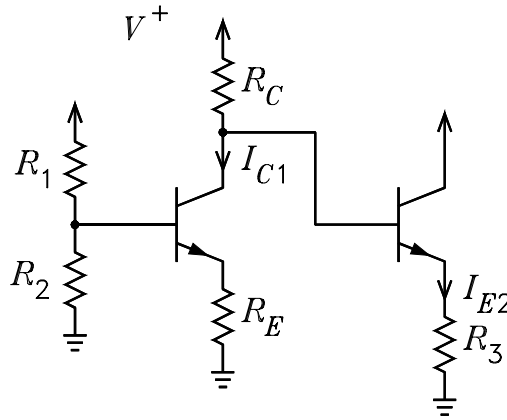10. Add a second npn transistor to the circuit of problem 9 as shown with $R_3 = 1\text{ k}\Omega$. Assume the same V_{BE} and β . Solve for I_{E2} . Solve for V_{CB} for both transistors and verify they are in the active mode. [$I_{E2} = 11.10\text{ mA}$, $V_{CB2} = 6.204\text{ V}$, $V_{CB1} = 8.597\text{ V}$]



11. For $R_1 = 10\text{ k}\Omega$, $R_2 = 47\text{ k}\Omega$, $R_C = 1.5\text{ k}\Omega$, $R_E = 2\text{ k}\Omega$, and $V^+ = 9\text{ V}$, solve for I_C and V_{CB} for $\beta = 99$ and $\beta = \infty$. Verify that the BJT is biased in the active mode. Assume $V_{BE} = 0.7\text{ V}$ for each case. [$I_C = 1.968\text{ mA}$, $V_{CB} = 1.212\text{ V}$, $I_C = 2.038\text{ mA}$, $V_{CB} = 1.016\text{ V}$]

