

## ECE 3040 Microelectronic Circuits Quiz 9


July 14, 2004

Professor Leach

Name \_\_\_\_\_

**Instructions.** Print your name in the space above. The quiz is closed-book and closed-notes. The quiz consists of one problem. **Honor Code Statement:** *I have neither given nor received help on this quiz.*  
 Initials \_\_\_\_\_

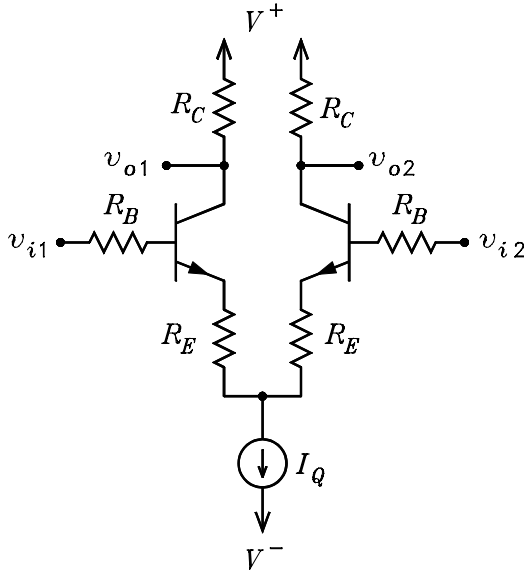1. It is given that  $V^+ = 18\text{ V}$ ,  $V^- = -18\text{ V}$ ,  $I_Q = 1\text{ mA}$ ,  $R_B = 1\text{ k}\Omega$ ,  $R_E = R_C/200$ ,  $\beta = 99$ ,  $r_0 = \infty$ , and  $V_T = 25\text{ mV}$ . Solve for  $R_C$  such that  $v_{o1} = -v_{o2} = -50(v_{i1} - v_{i2})$ .



In the simplified T model of each BJT,  $r'_e$  is given by

$$r'_e = \frac{R_B}{1 + \beta} + \frac{2V_T}{I_Q} = 60\ \Omega$$

From the simplified T model circuit

$$i'_{e1} = -i'_{e2} = \frac{v_{I1} - v_{I2}}{2(r'_e + R_E)} = \frac{v_{I1} - v_{I2}}{2(r'_e + R_C/200)}$$


The two output voltages are given by

$$v_{o1} = -v_{o2} = -\alpha i'_{e1} R_C = \frac{-\alpha R_C}{2(r'_e + R_C/200)} (v_{I1} - v_{I2}) = -50(v_{i1} - v_{i2})$$


It follows that

$$\alpha R_C = 2 \times 50 \left( r'_e + \frac{R_C}{200} \right) \implies (\alpha - 0.5) R_C = 100 r'_e \implies R_C = \frac{100 r'_e}{\alpha - 0.5} = 12.24\text{ k}\Omega$$

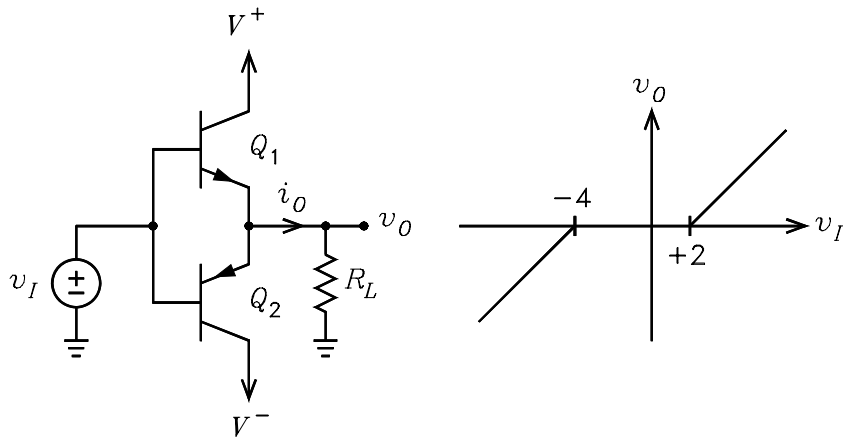2. (a)  $Q_1$  and  $Q_2$  both have the cutin voltage  $V_\gamma = 0.5\text{ V}$ . How can the circuit be modified to produce the given  $v_O$  versus  $v_I$  graph? Draw and label the circuit. You may add any circuit element or elements to achieve the desired graph.



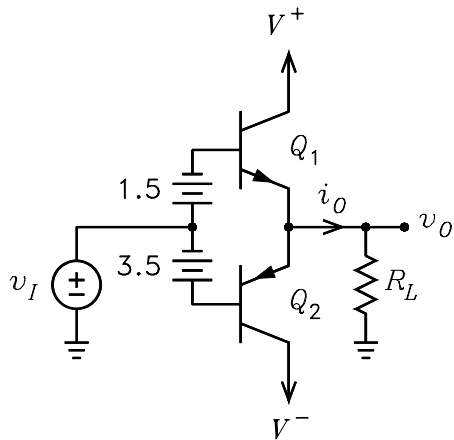The simplest circuit uses two batteries as shown.



Transistors with the base-emitter junctions in series could also be used. It would tke 4 NPN transistors and 8 PNP transistors.

- (b) Let  $v_I$  be a sine wave with a peak voltage of  $10\text{ V}$ . On the same axes, draw and label the graphs of  $v_I$  and  $v_O$  versus time. For the given graph of  $v_O$  versus  $v_I$ , assume that the two lines have a slope  $m = +1$ .

