
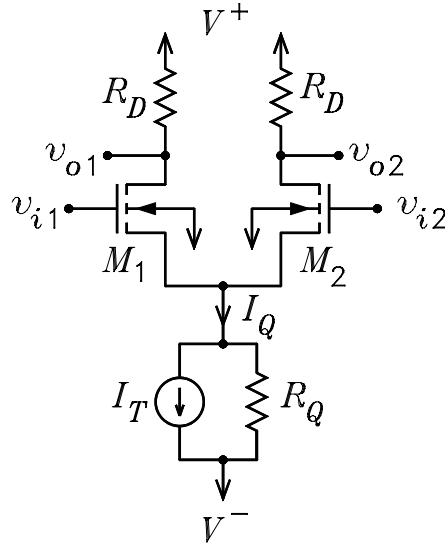


## ECE3050 Assignment 12

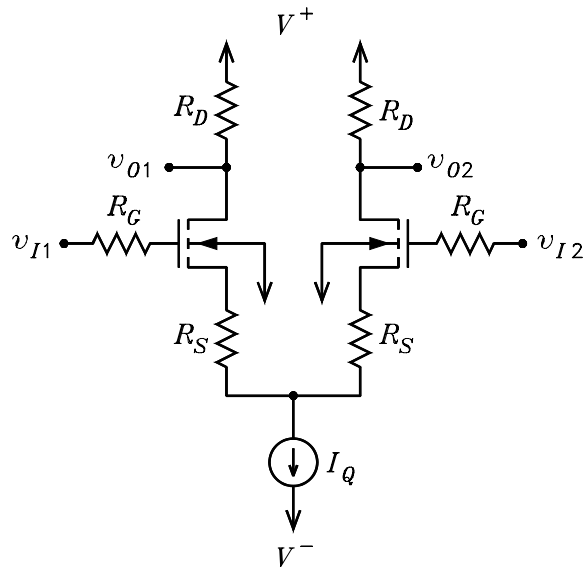1. The figure shows a differential amplifier. Each MOSFET has the parameters  $g_m = 1/400 \text{ S}$ ,  $r_0 = 40 \text{ k}\Omega$ , and  $\chi = 0.5$ . It is given that  $R_D = 10 \text{ k}\Omega$  and  $R_Q = 20 \text{ k}\Omega$ . The answers given assume the  $r_0$  approximations.



- (a) Show that the resistance seen looking out of each source is  $R_{ts} = 263.16 \Omega$ , the resistance seen looking into each drain is  $r_{id} = 79.74 \text{ k}\Omega$ , and the output resistance seen looking into the two outputs with  $v_{i1} = v_{i2} = 0$  is  $r_{out1} = r_{out2} = 8.886 \text{ k}\Omega$ .
- (b) For the differential inputs  $v_{i1} = v_{id}/2$  and  $v_{i2} = -v_{id}/2$ , show that  $v_{o1}/v_{id} = -v_{o2}/v_{id} = -11.11$ .
- (c) For the common-mode inputs  $v_{i1} = v_{icm}$  and  $v_{i2} = v_{icm}$ , show that  $v_{o1}/v_{icm} = v_{o2}/v_{icm} = -0.147$ .
2. For a MOSFET diff amp, show that the body effect cancels out with differential inputs if there is no external resistor in series with the source leads, i.e.  $R_S = 0$ . Hint: For differential inputs, the currents can be calculated with the sources connected to signal ground. This is the case in the preceding problem.
3. The figure shows a MOSFET differential amplifier. For the MOSFETs, it is given that  $k' = 0.008 \text{ A/V}^2$ ,  $W/L = 1$ ,  $V_{TO} = 1.5 \text{ V}$ ,  $\lambda = 0$ , and  $\chi = 0.4$ . For the circuit, it is given that  $V^+ = 20 \text{ V}$ ,  $V^- = -20 \text{ V}$ ,  $I_Q = 2.5 \text{ mA}$ ,  $R_G = 5 \text{ k}\Omega$ ,  $R_S = 100 \Omega$ , and  $R_D = 12 \text{ k}\Omega$ . Assume the dc components of each input are zero, i.e.  $V_{I1} = V_{I2} = 0$ .
- (a) With  $v_{I1} = v_{I2} = 0$ , calculate  $V_{GS}$  for each transistor. Answer:  $V_{GS} = 1.956 \text{ V}$ .
- (b) With  $v_{I1} = v_{I2} = 0$ , calculate  $V_D$  for each transistor. Answer:  $V_D = 5 \text{ V}$ .
- (c) Use the value of  $V_{GS}$  found in part (a) and the value of  $V_D$  found in part (b) to solve for  $V_{DS}$  for each transistor. Verify that  $V_{DS} > V_{GS} - V_{TO}$ . Answers:  $V_{DS} = 6.956 \text{ V}$  and  $V_{GS} - V_{TO} = 0.456 \text{ V}$ .
- (d) Calculate  $g_m$ ,  $r_s$ ,  $r'_s$ ,  $r_0$ , and the resistance  $R_{ts}$  seen looking out of each source. Answers:  $g_m = 5.477 \text{ mS}$ ,  $r_s = 182.6 \Omega$ , and  $r'_s = 130.4 \Omega$ ,  $r_0 = \infty$ , and  $R_{ts} = 330.4 \Omega$ .



(e) With  $v_{i2} = 0$ , show that

$$\frac{v_{o1}}{v_{i1}} = -\frac{v_{o2}}{v_{i1}} = -18.6 \quad r_{out} = 12 \text{ k}\Omega$$

(f) With  $v_{i1} = 0$ , use the Norton drain circuit to show that

$$\frac{v_{o2}}{v_{i2}} = -\frac{v_{o1}}{v_{i2}} = -18.6 \quad r_{out} = 12 \text{ k}\Omega$$

(g) For the differential input signals  $v_{i1} = v_{id}/2$  and  $v_{i2} = -v_{id}/2$ , show that

$$\frac{v_{o1}}{v_{id}} = -\frac{v_{o2}}{v_{id}} = -18.6$$

(h) For the common mode inputs  $v_{i1} = v_{i2} = v_{icm}$ , why is the common-mode gain equal to zero? Answer: Because the tail supply is a perfect current source.