

## ECE 3050 Analog Electronics Quiz 7


February 25, 2009

Professor Leach

Name \_\_\_\_\_


**Instructions.** Print your name in the space above. **Honor Code:** *I have neither given nor received help on this quiz.* Initials \_\_\_\_\_

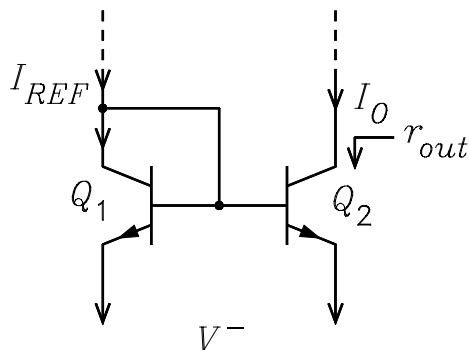1. The figure shows a basic two-BJT current mirror.
  - (a) Assume the two transistors are identical and that the Early effect can be neglected, i.e.,  $V_A = \infty$ . Label the branch currents and derive the equation for the output current  $I_O$ .
  - (b) If the Early effect is not neglected, what would be the output resistance  $r_{out}$ ?



$$I_{REF} = I_O + \frac{I_O}{\beta} + \frac{I_O}{\beta} \implies I_O = \frac{I_{REF}}{1 + 2/\beta} \quad r_{out} = r_{o2}$$

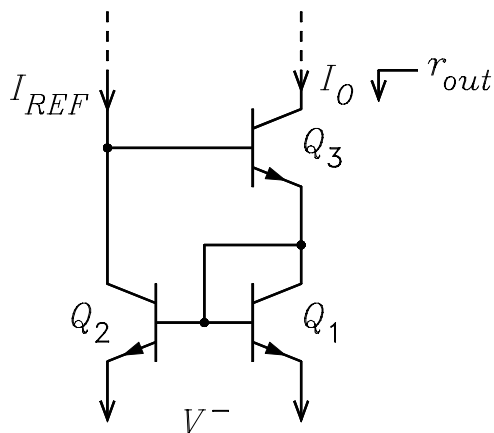2. The figure shows a Wilson current mirror.
  - (a) Assume the two transistors are identical and that the early effect can be neglected, i.e.,  $V_A = \infty$ . Making use of the results of Problem 1, label the branch currents and derive the equation for the output current  $I_O$ .
  - (b) Aside from the difference in the equation for  $I_O$ , what is the major difference between the Wilson mirror and the two-BJT current mirror?



Make use of the answer for Problem 1 to solve for  $I_{C2}$ .

$$I_{REF} = \frac{I_O}{\beta} + \frac{I_O/\alpha}{1 + 2/\beta} \implies I_O = \frac{I_{REF}}{\frac{1}{\beta} + \frac{1/\alpha}{1 + 2/\beta}}$$

The output resistance is much higher than for the two-BJT current mirror. This is caused by a positive feedback effect.