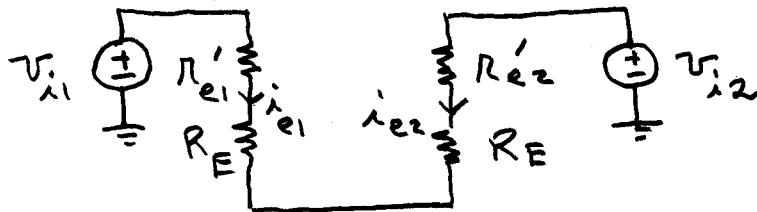


1-06/16/03

Approximate Analysis of the BJT Diff Amp

Assume $r_o = \infty$. Use the simplified T model to solve for \hat{i}_e . Then use $\hat{i}_c = \alpha \hat{i}_e$ to solve for \hat{i}_c .

Looking into the emitter of the two transistors with $r_o = \infty$, we see r_e' in series with v_{EB} .




$$r_{e1}' = r_{e2}' = r_e' = \frac{R_B + R_x}{1 + \beta} + r_e$$

$$r_e = \frac{V_T}{I_E} = \frac{2V_T}{I_Q}$$

$$\hat{i}_{e1} = -\hat{i}_{e2} = \frac{v_{i1} - v_{i2}}{2(r_e' + R_E)}$$

$$\hat{i}_{c1} = -\hat{i}_{c2} = \alpha \hat{i}_{e1} = \frac{\alpha}{2(r_e' + R_E)} (v_{i1} - v_{i2})$$

2-6/13/03

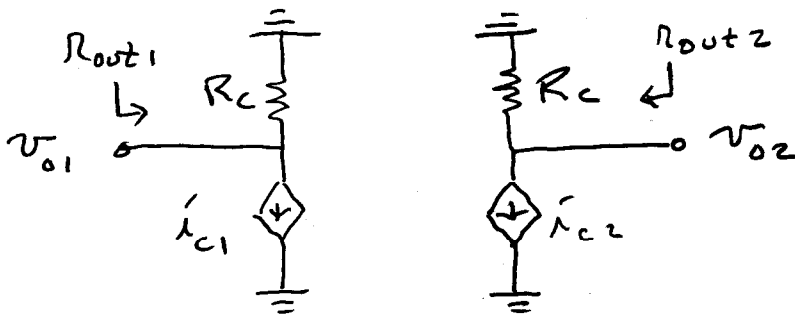

$$v_{o1} = -v_{o2} = -i_{c1} R_c = \frac{-\alpha R_c}{2(R'_e + R_E)} (v_{i1} - v_{i2})$$

With $v_{i2} = 0$ $R_{in1} = R_{x1} + (1+\beta)(R'_e + R_{te1})$

where $R_{te1} = 2R_E + R'_e$


With $v_{i1} = 0$, $R_{in2} = R_{in1}$.

$$R_{out1} = R_{out2} = R_c$$

3 - 6/16/03

Differential and Common-Mode Analysis of the BJT Diff Amp

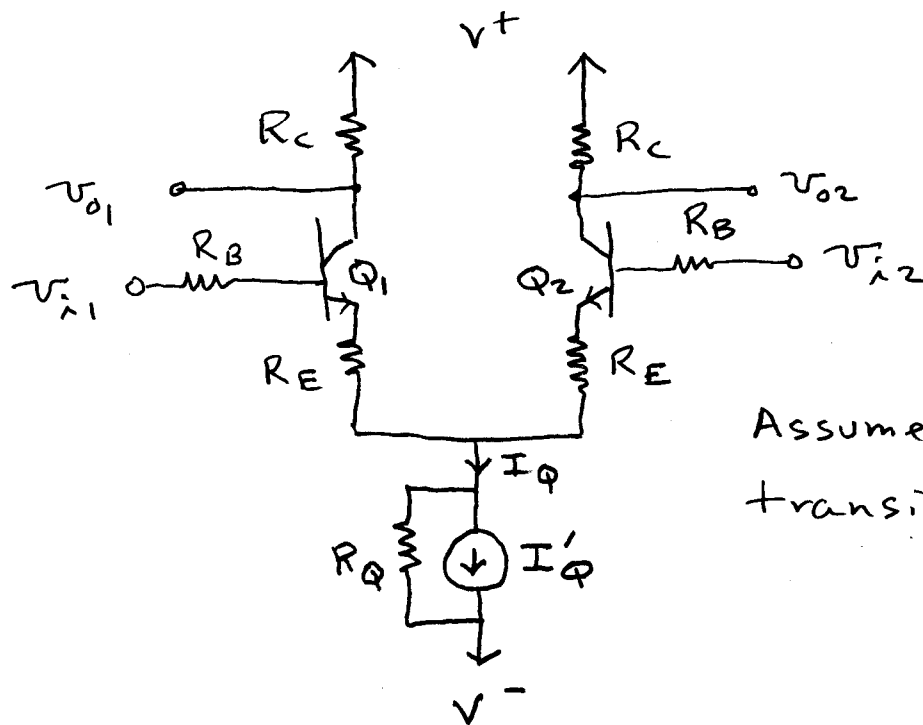Consider the case where the tail supply is not a perfect current source. Let it exhibit a parallel resistance R_Q .




Assume identical transistors.

For the dc analysis, set $v_{i1} = v_{i2} = 0$. Divide the tail supply into 2 identical current sources ($I_Q/2$ in parallel with $2R_Q$). By symmetry the circuit for either Q_1 or Q_2

4-6/16/03

reduces to

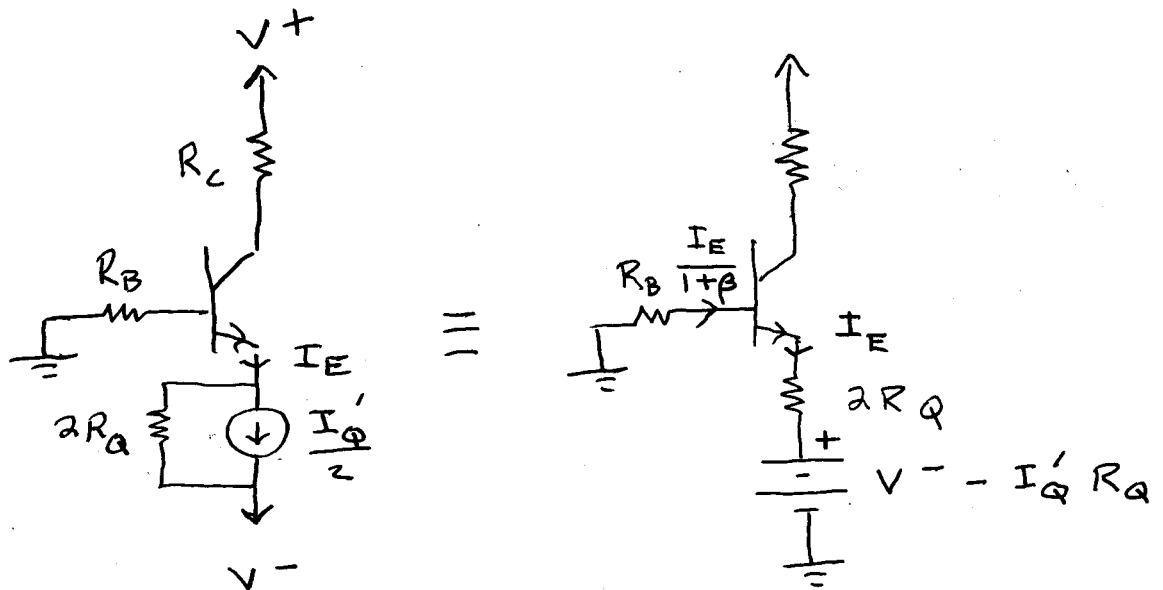

The dc bias equation is

$$0 - (V^- - I_Q' R_Q) = \frac{I_E}{1+\beta} R_B + V_{BE} + I_E 2R_Q$$

$$\Rightarrow I_E = \frac{-V^- + I_Q' R_Q - V_{BE}}{\frac{R_B}{1+\beta} + 2R_Q}$$

$$R_{21} = R_{22} = R_e = \frac{V_T}{I_E}$$

For the BJT's to be biased in the active mode, $V_{CB} > 0$.

5 - 6/16/03

$$\begin{aligned}V_{CB} &= V_C - V_B = (V^+ - \alpha I_E R_C) - \left(-\frac{I_E}{1+\beta} R_B\right) \\ &= V^+ - I_E \left(\alpha R_C - \frac{R_B}{1+\beta}\right)\end{aligned}$$

This must be > 0 , often it is taken to be $\frac{1}{2}V^+$ for a resistively loaded diff amp.

Small-Signal AC Analysis

Let us define the differential and common-mode input voltages as follows:

$$\text{Differential : } v_{id} = v_{i1} - v_{i2}$$


$$\text{Common-Mode : } v_{icm} = \frac{1}{2}(v_{i1} + v_{i2})$$

It follows from these definitions that

$$\begin{aligned}v_{i1} &= v_{icm} + \frac{1}{2}v_{id} \\ v_{i2} &= v_{icm} - \frac{1}{2}v_{id}\end{aligned}$$

6 - 6/16/03

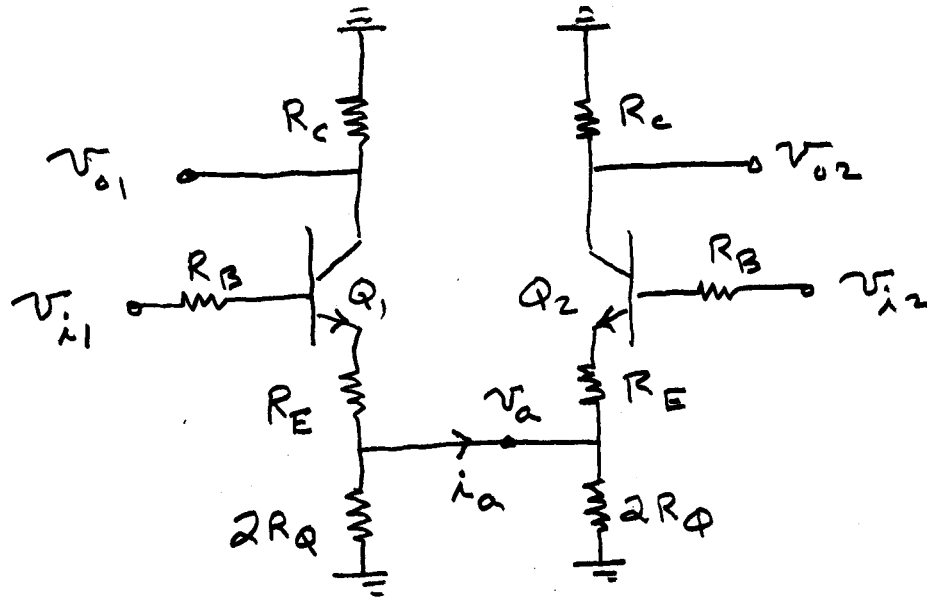To solve for v_{o1} & v_{o2} , we can use superposition of v_{id} and v_{icm} . The AC signal circuit is




Differential Analysis

Let $v_{i1} = \frac{1}{2} v_{id}$ and $v_{i2} = -\frac{1}{2} v_{id}$

\Rightarrow v_{i1} increases v_a and v_{i2} decreases v_a . The net effect is that $v_a = 0$. Thus we can ground the v_a node. The circuit becomes

7-6/16/03

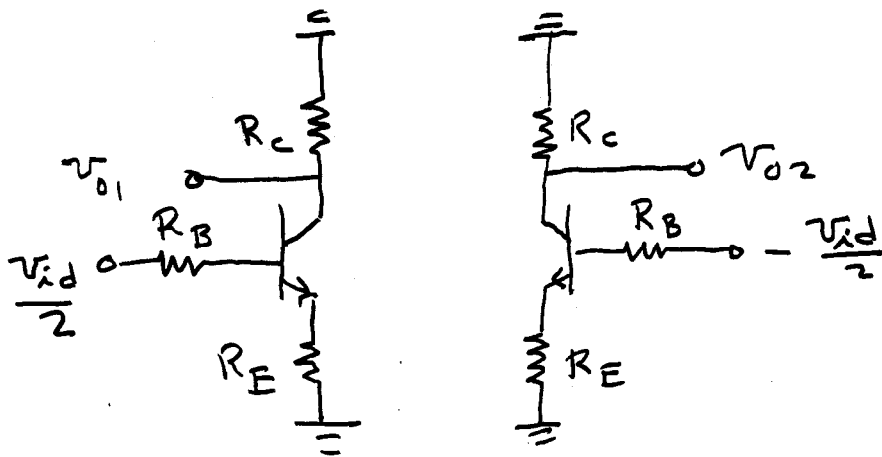

Thus the circuit consists of two CE amplifiers. By symmetry, $v_{o2} = -v_{o1}$. From our CE amplifier analysis, we have

$$v_{o1} = -i_{c(sc)} r_{ic(d)} \parallel R_C$$

$$i_{c(sc)} = G_{mb(d)} \frac{v_{id}}{2}$$

$$\Rightarrow v_{o1} = \left[-\frac{1}{2} G_{mb(d)} r_{ic(d)} \parallel R_C \right] v_{id}$$

where $G_{mb(d)}$ and $r_{ic(d)}$ are calculated with $R_{tb} = R_B$ and $R_{te} = R_E$. By symmetry


$$v_{o2} = \left[\frac{1}{2} G_{mb(d)} r_{ic(d)} \parallel R_C \right] v_{id}$$

8 - 6/16/03

Common-Mode Analysis

Let $v_{i1} = v_{i2} = v_{icm}$.

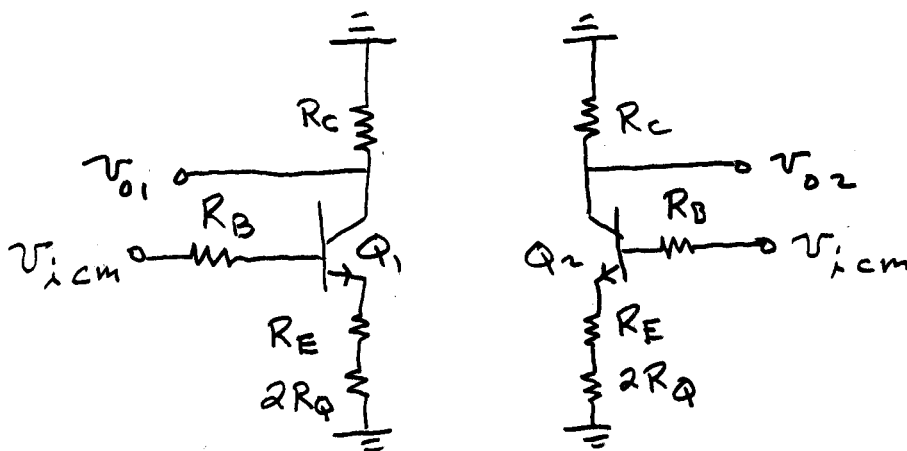$\Rightarrow v_{i1}$ increases i_a and v_{i2} decreases i_a . The net effect is that $i_a = 0$. Thus we can open the i_a branch. The circuit becomes



Thus the circuit again consists of two CE amplifiers. By symmetry, $v_{o1} = v_{o2}$. From our CE analysis, we have

$$v_{o1} = -i_{c1(sc)} R_{ic(cm)} \parallel R_C$$

$$i_{c1(sc)} = G_{mb(cm)} v_{icm}$$

9-6/16/03

$$\Rightarrow v_{o1} = \left[-G_{mb(cm)} R_{ic(cm)} \parallel R_c \right] v_{icm}$$

where $G_{mb(cm)}$ and $R_{ic(cm)}$ are calculated with $R_{tb} = R_B$ and $R_{te} = R_E + 2R_Q$. By symmetry

$$v_{o2} = \left[-G_{mb(cm)} R_{ic(cm)} \parallel R_c \right] v_{icm}$$

Total Solution for v_{o1} :

We add the differential and common-mode solutions to obtain

$$\begin{aligned} v_{o1} &= \left[-\frac{1}{2} G_{mb(d)} R_{ic(d)} \parallel R_c \right] (v_{i1} - v_{i2}) \\ &\quad + \left[-G_{mb(cm)} R_{ic(cm)} \parallel R_c \right] \frac{v_{i1} + v_{i2}}{2} \\ &= A_1 v_{i1} + A_2 v_{i2} \end{aligned}$$

where A_1 and A_2 are given by

10 - 6/16/03

$$A_1 = -\frac{1}{2} \left[G_{mb(d)} R_{ic(d)} \parallel R_c + G_{mb(cm)} R_{ic(cm)} \parallel R_c \right]$$

$$A_2 = +\frac{1}{2} \left[G_{mb(d)} R_{ic(d)} \parallel R_c - G_{mb(cm)} R_{ic(cm)} \parallel R_c \right]$$

For the case $R_Q \rightarrow \infty$, $G_{mb(cm)} \rightarrow 0$
and we have

$$A_1 = -A_2 = A = -\frac{1}{2} G_{mb(d)} R_{ic(d)} \parallel R_c$$

In this case, v_{o1} is given by

$$v_{o1} = A (v_{i1} - v_{i2})$$

All solutions for v_{o2} can be obtained by interchanging v_{i1} and v_{i2} in the solutions for v_{o1} .

The Common-Mode Rejection Ratio
or CMRR

Let the output be taken from

11-6/16/03

the v_{o1} output. This is given by

$$\begin{aligned}v_{o1} &= -\frac{v_{id}}{2} [G_{mb(d)} R_{ic(d)} \parallel R_c] \\ &\quad - v_{icm} [G_{mb(cm)} R_{ic(cm)} \parallel R_c] \\ &= A_d v_{id} + A_{cm} v_{icm}\end{aligned}$$

where A_d and A_{cm} are given by

$$A_d = -\frac{1}{2} G_{mb(d)} R_{ic(d)} \parallel R_c$$

$$A_{cm} = -G_{mb(cm)} R_{ic(cm)} \parallel R_c$$

The CMRR is defined by

$$CMRR = \frac{A_d}{A_{cm}} = \frac{\frac{1}{2} G_{mb(d)} R_{ic(d)} \parallel R_c}{G_{mb(cm)} R_{ic(cm)} \parallel R_c}$$

For $R_Q \rightarrow \infty$, it follows that $CMRR \rightarrow \infty$. The larger the CMRR, the lower the common mode gain

12-6/16/03

and the closer the diff amp is to an ideal diff amp with the output $v_{o1} = -A(v_{i1} - v_{i2})$.

For $\text{CMRR} < \infty$, the gains for the two inputs are not equal. For $\text{CMRR} \rightarrow \infty$, the gains are equal.

In practice a CMRR of 60 to 80 dB ($20 \log(A_d/A_{cm})$) can be achieved.