

## ECE 3050 Analog Electronics Quiz 1


May 20, 2009

Professor Leach      Last Name: \_\_\_\_\_ First Name: \_\_\_\_\_

**Instructions. Print** your name in the spaces above. Place a box around any answer. **Honor Code Statement:**

*I have neither given nor received help on this quiz.* Initials \_\_\_\_\_

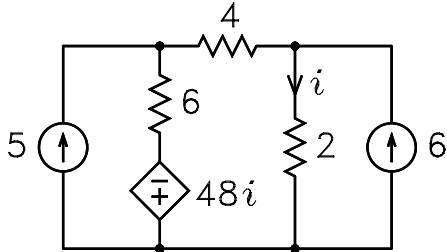1. Use superposition, Ohm's Law, voltage division, and current division to solve for  $i$ .



$$i = 5 \frac{6}{6 + 4 + 2} + 6 \frac{6 + 4}{6 + 4 + 2} - \frac{48i}{6 + 4 + 2} = \frac{90}{12} - \frac{48i}{12}$$

$$i = \frac{90/12}{1 + 48/12} = 1.5 \text{ A}$$

2. There are three small-signal parameters derived from slopes of curves that model the terminal characteristics of the BJT. These are the transconductance  $g_m$ , the base-emitter resistance  $r_\pi$ , and the collector-emitter resistance  $r_0$ .

- (a) What are the names of the three curves?

the transfer characteristics, or the plot of  $i_C$  versus  $v_{BE}$

the output characteristics, or the plot of  $i_C$  versus  $v_{CE}$

the input characteristics, or the plot of  $i_B$  versus  $v_{BE}$

- (b) How is each parameter defined in terms of the slope of a curve at the dc operating point?

$g_m$  is the slope of the transfer characteristics at the Q-point

$r_0$  is the reciprocal of the output characteristics at the Q-point

$r_\pi$  is the reciprocal of the input characteristics at the Q-point