

ECE 3050 Analog Electronics Quiz 2

May 27, 2009

Professor Leach Last Name: _____ First Name: _____


Instructions. Print your name in the spaces above. Place a box around any answer. **Honor Code Statement:**

I have neither given nor received help on this quiz. Initials _____

$$i'_c = g_m v_\pi = \beta i_b = \alpha i'_e \quad g_m = \frac{I_C}{V_T} \quad \beta = g_m r_\pi \quad a = \frac{\beta}{1 + \beta}$$

$$r_\pi = \frac{V_T}{I_B} \quad r_e = \frac{V_T}{I_E} \quad r'_e = \frac{R_{tb} + r_x}{1 + \beta} + r_e \quad I_C = \beta I_B = \alpha I_E$$

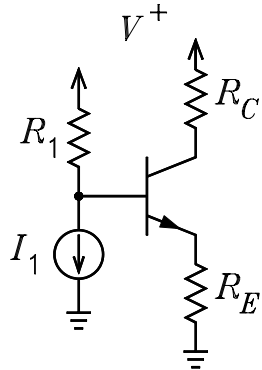- 1 of 2. Replace the circuit seen looking out of the base with a Thévenin equivalent and solve for the collector current I_C for $V^+ = 15\text{ V}$, $R_1 = 4\text{ k}\Omega$, $I_1 = 3\text{ mA}$, $R_C = 1.2\text{ k}\Omega$, $R_E = 1.1\text{ k}\Omega$, $V_{BE} = 0.65\text{ V}$, and $\beta = 49$.




$$V_p := 15 \quad R_1 := 4000 \quad R_E := 1100 \quad R_C := 1200 \quad V_{BE} := 0.65 \quad \beta := 49$$

$$I_1 := 0.003 \quad \alpha := \frac{\beta}{1 + \beta} \quad \alpha = 0.98$$

$$I_C := \frac{(V_p - I_1 \cdot R_1) - V_{BE}}{\frac{R_1}{\beta} + \frac{R_E}{\alpha}} \quad I_C = 1.952 \cdot 10^{-3}$$

$$V_{CB} := (V_p - I_C \cdot R_C) - \left(\frac{I_C}{\alpha} \cdot R_E + V_{BE} \right) \quad V_{CB} = 9.817$$

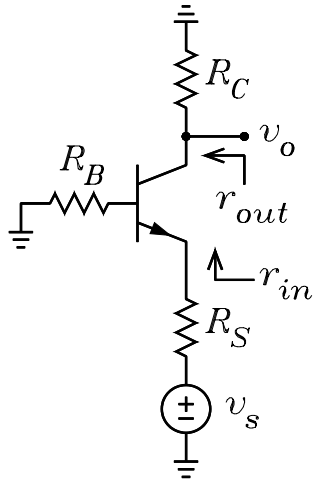2 of 2. For the ac signal circuit circuit shown, use the simplified T model to solve for $A_v = v_o/v_s$, r_{in} , and r_{out} for $R_S = 75\ \Omega$, $R_B = 100\ \Omega$, $R_C = 12\ \text{k}\Omega$, $I_E = 1\ \text{mA}$, $r_x = 50\ \Omega$, $\alpha = 0.99$, $r_0 = \infty$, and $V_T = 0.025\ \text{V}$.



$$R_S := 75 \quad R_B := 100 \quad R_C := 12000 \quad I_E := 0.001 \quad r_x := 50 \quad V_T := 0.025$$

$$\alpha := 0.99 \quad \beta := \frac{\alpha}{1 - \alpha} \quad \beta = 99$$

$$r_e := \frac{V_T}{I_E} \quad r_e = 25 \quad r'_e := \frac{R_B + r_x}{1 + \beta} + r_e \quad r'_e = 26.5$$

$$v_s := 1 \quad i'_e := \frac{-v_s}{R_S + r'_e} \quad i'_e = -9.852 \cdot 10^{-3} \quad i'_c := \alpha \cdot i'_e \quad i'_c = -9.754 \cdot 10^{-3}$$

$$v_o := -i'_c \cdot R_C \quad v_o = 117.044 \quad \text{This is the voltage gain } \frac{v_o}{v_s}.$$

$$r_{in} := r'_e \quad r_{in} = 26.5 \quad r_{out} := R_C \quad r_{out} = 1.2 \cdot 10^4$$