

## ECE 6416 Quiz 2

November 16, 2009

Professor Leach

Name \_\_\_\_\_

**Instructions.** Print your name in the space above and at the top of all other pages in your quiz. Place a box around each answer. Express each numerical answer as a decimal number. Numerical values are  $4kT_0 = 1.6 \times 10^{-20}$  J,  $q = 1.6 \times 10^{-19}$  C, and  $V_T = 25$  mV. **Honor Code:** *I have neither given nor received help on this quiz.* Initials \_\_\_\_\_

1. An amplifier has a voltage gain of 300 and an input resistance of  $5 \text{ k}\Omega$ . A white noise source with an output resistance  $R_S = 2 \text{ k}\Omega$  is connected to the amplifier input. With the source voltage zeroed, the rms amplifier noise output voltage is  $0.470 \text{ mV}$ . With the rms spot noise output voltage of the source set to  $v_s = 0.1 \mu\text{V}/\sqrt{\text{Hz}}$ , the rms amplifier output voltage is  $4.82 \text{ mV}$ . Solve for the noise factor and the noise figure of the amplifier.

$$v_{no1}^2 = \left( \frac{AR_i}{R_S + R_i} \right)^2 4kTR_S B_n \times F \quad v_{no2}^2 = \left( \frac{AR_i}{R_S + R_i} \right)^2 (S_v B_n + 4kTR_S B_n \times F)$$

Take ratios and solve for  $F$ .

$$F = \frac{S_v}{\left( \frac{v_{no2}^2}{v_{no1}^2} - 1 \right) 4kTR_S} = \frac{(0.1 \times 10^{-6})^2}{\left[ \frac{(4.82 \times 10^{-3})^2}{(0.470 \times 10^{-3})^2} - 1 \right] \times 1.6 \times 10^{-20} \times 2000} = 3$$
$$NF = 10 \log(F) = 4.77$$

2. An amplifier has  $v_n = 3 \text{ nV}/\sqrt{\text{Hz}}$ ,  $i_n = 6 \text{ pA}/\sqrt{\text{Hz}}$ , and  $\rho = 0.15$ . The amplifier is driven from a voltage source with an output resistance  $R_S = 1 \text{ k}\Omega$ . Assume the noise bandwidth  $B_n = 1 \text{ Hz}$ .
  - (a) Calculate the noise factor  $F$  and noise figure  $NF$ .

$$F = \frac{4kTR_S + v_n^2 + 2v_n i_n R_S \rho + i_n^2 R_S^2}{4kTR_S} = 4.15 \quad NF = 10 \log(F) = 6.18$$

- (b) Calculate the optimum source resistance  $R_{so}$ .

$$R_{so} = \frac{v_n}{i_n} = 500 \Omega$$

- (c) A resistor is added in parallel with the amplifier input to make the source resistance seen by the amplifier equal to  $R_{so}$ . What is the required value of the resistor?

$$R_p = \frac{R_S R_{so}}{R_S - R_{so}} = 1000 \Omega$$

- (d) What are the new noise figure and noise factor?

$$V_{i(oc)} = \frac{R_p}{R_S + R_p} V_s + V_{tso} + V_n + I_n R_{so} = \frac{R_p}{R_S + R_p} \left[ V_s + \frac{R_S + R_p}{R_p} (V_{tso} + V_n + I_n R_{so}) \right]$$
$$V_{ni} = \frac{R_S + R_p}{R_p} (V_{tso} + V_n + I_n R_{so})$$
$$F = \frac{\left( \frac{R_S + R_p}{R_p} \right)^2 (4kTR_{so} + v_n^2 + 2v_n i_n R_{so} \rho + i_n^2 R_{so}^2)}{4kTR_S} = 7.18 \quad NF = 10 \log(F) = 8.56$$

3. The figure shows the ac signal circuit of a common-base amplifier. The BJT has the parameters  $\beta = 150$ ,  $r_x = 50 \Omega$ , and  $r_0 = \infty$ . It is given that  $R_s = 50 \Omega$  and  $R_C = 30 \text{ k}\Omega$ .

(a) If flicker noise is neglected, calculate the optimum bias current  $I_{C(opt)}$  and the rms equivalent noise voltage in series with  $V_s$  for the band  $0 \text{ Hz} \leq f \leq 50 \text{ kHz}$ .

$$I_{C(opt)} = \frac{V_T}{R_s + r_x} \frac{\beta}{\sqrt{1 + \beta}} = 3.05 \text{ mA}$$

$$v_{ni}^2 = 4kT(R_s + r_x) B_n \frac{\sqrt{1 + \beta}}{\sqrt{1 + \beta} - 1} = 8.71 \times 10^{-14} \text{ V}^2 \quad v_{ni} = 2.95 \times 10^{-7} \text{ V}$$

(b) What is the noise factor and noise figure for the band  $0 \text{ Hz} \leq f \leq 50 \text{ kHz}$ ?

$$F = \frac{v_{ni}^2}{4kTR_s B_n} = 2.18 \quad NF = 10 \log(F) = 3.38$$

(c) What is the rms noise voltage at the amplifier output for the band  $0 \text{ Hz} \leq f \leq 50 \text{ kHz}$ ?

$$A_v = \frac{i'_e i'_c v_o}{v_s i'_e i'_c} = \left( -\frac{1}{r'_e + R_s} \right) \alpha (-R_C) = +510 \quad v_{no} = A_v v_{ni} = 0.150 \text{ mV}$$

