

# LECTURE 210 – CLOCK AND DATA RECOVERY CIRCUITS - II


(References [6])

## VOLTAGE CONTROLLED OSCILLATORS FOR CDR APPLICATIONS

### Comparison of VCOs

| Comparison of VCO Topologies |                |                |                |                |
|------------------------------|----------------|----------------|----------------|----------------|
|                              | Relaxation     | Ring           | LC             | Quadrature LC  |
| Control Voltage              | Differential ↑ | Differential ↑ | Single-ended ↓ | Differential ↑ |
| Phase Noise                  | High ↓         | High ↓         | Low ↑          | Moderate       |
| Tuning Range                 | Wide ↑         | Wide ↑         | Narrow ↓       | Medium         |
| VCO Gain                     | High ↓         | High ↓         | Low ↑          | Medium         |
| PVT Variations               | High ↓         | High ↓         | Low ↑          | Low ↑          |

### Ring Oscillator Example<sup>†</sup>

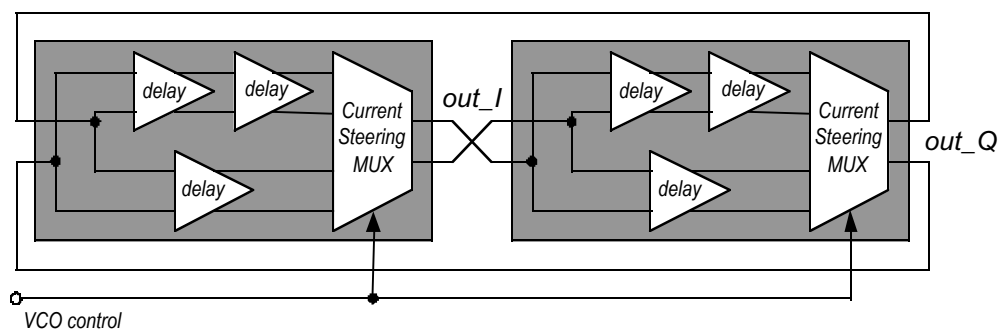


#### Comments:

- Tuning can be split into fine and coarse control
- Very wide tuning range
- Differential control
- Moderate phase noise

<sup>†</sup> R. Walker, *ISSCC* 1997, pp. 246-247.


## LC VCO Example

 

Comments:



- Fine tuning is through varactor control
- Coarse tuning is achieved by binary weighted capacitor array
- Low tuning range
- Single-ended control
- Very good phase noise characteristics

## Quadrature LC VCO Example

 

T.P. Liu, *IEEE VLSI* 1999, pp. 55-56

  - Two identical LC VCOs are coupled in quadrature.
- VCO tuning is achieved through:
  - Adjusting the coupling between the two oscillator cores
  - Changing the LC-tank capacitance



A.L. Coban, et. al., *VLSI* 2001, pp. 119-120

## A Design Procedure for VCOs for CDR Applications

The following procedure seeks to maximize the tuning range and minimize the phase noise with the knowledge of four parameters:

- Load capacitance,  $C_L$
- Required output voltage swing
- Center frequency,  $f_o$
- Power

The first two parameters may require a buffer as shown below.

 


Fig. 210-01

## Design Procedure for VCOs – Continued

Other circuits that the VCO may have to drive include a flip-flop in a divider chain, two flipflops in the demultiplexer and a  $50\Omega$  output driver:

 


Fig. 210-02

Procedure:

1.) With the power budget and hence the value of  $I_{DD}$  the width of M1 and M2 is chosen to yield an average CM level of approximately  $0.5V_{DD}$  at the X and Y nodes. Note that when  $V_X = V_Y$ , that  $V_{DG1} = V_{DG2} = 0$ .

$$I_D = \frac{K'W}{2L} (V_{GS} - V_T)^2: V_{GS} = 0.5V_{DD} \text{ and } I_{DD} \rightarrow \frac{W}{L} \rightarrow g_m$$

2.) Design the inductors,  $L_1$  and  $L_2$ . To maximize the tuning range (and  $Q$ ) the inductance must be minimized. To get the oscillator to start-up, the following must hold:

$$(g_m R_{p,min})^2 = 1$$

However,  $R_{p,min}$  is the parallel resistance of the tank and is primarily due to the inductor.

$$R_{p,min} \approx QL_{min}\omega_{osc} \rightarrow (g_m QL_{min}\omega_{osc})^2 = 1 \rightarrow L_{min} = \frac{1}{g_m Q \omega_{osc}}$$

The above assumes that the  $Q$  is approximately constant with the value of  $L_{min}$ .

### VCO Design Procedure – Continued

3.) With  $L = L_{min}$ , the oscillation amplitude is quite small in order to maintain unity loop gain. If the amplitude grows, the transistor nonlinearities reduce the loop gain which may prevent full swing. One must also be careful of the variation of  $g_m$  and  $Q$  with PVT corners possibly prohibiting oscillation at some corners. Therefore, the values of  $L$  and  $R_p$  must sufficiently exceed  $L_{min}$  and  $R_{p,min}$  to provide the required voltage swings and start under worst case conditions.

4.) The value of  $R_p$  can be related to the required output swing as follows. M1 and M2 each have an average current of  $0.5I_{DD}$ . If the drain currents are approximated by sinusoids varying between  $I_{DD}$  and zero, the  $V_X$  and  $V_Y$  swing from  $0.5V_{DD}-I_{DD}R_p$  and  $0.5V_{DD}+I_{DD}R_p$ . For this voltage sinusoid, the largest peak voltage is  $0.5V_{DD}=I_{DD}R_p$  giving

$$R_{p,swing} = \frac{V_{DD}}{2I_{DD}} \quad (\text{minimum parallel tank resistance giving maximum swing})$$

$$\therefore L_{opt} = \frac{V_{DD}}{2I_{DD}} \cdot \frac{1}{Q\omega_{osc}}$$

5.) With  $W/L$  and  $L_{opt}$  known, the varactor capacitance can be found as

$$C_{tot} = \frac{1}{\omega_{osc}^2 L_{opt}}$$

where  $C_{tot} = C_{var} + C_{gs} + C_{bds} + 4C_{gd} + C_{inductor} + C_{buffer}$

### Designing a VCO for CDR Applications

Use the above procedure to design a VCO for 5GHz using 0.18 $\mu$ m CMOS technology having  $K_N' = 120\mu\text{A}/\text{V}^2$  and  $V_{TN} = 0.5\text{V}$ . Assume the  $Q$  of the inductor is 5,  $V_{DD} = 1.8\text{V}$  and the power is to be 5mW. Assume that  $C_{gs} + C_{bds} + 4C_{gd} = 300\text{fF}$ ,  $C_{inductor} = 50\text{fF}$ , and  $C_{buffer} = 200\text{fF}$ .

#### Solution

1.) From the specifications we get  $I_{DD} = 5\text{mW}/1.8\text{V} = 2.78\text{mA}$ . The  $W/L$  can be found as,

$$\frac{W}{L} = \frac{I_{DD}}{K_N'(0.5V_{DD}-V_{TN})^2} = \frac{2.78\text{mA}}{0.12\text{mA}/\text{V}^2 (0.9-0.5)^2} = 144.67 \approx 145$$

$$g_m = \sqrt{2K_N'(0.5I_{DD})145} = 6.95\text{mS}$$

2.) The minimum inductance can be found as

$$L_{min} = \frac{1}{g_m Q \omega_{osc}} = \frac{1}{6.95\text{mS} \cdot 5 \cdot 2\pi \cdot 5 \times 10^9} = 0.916\text{nH}$$

3.) The value of  $R_p$  for maximum swing is

$$R_{p,swing} = \frac{V_{DD}}{2I_{DD}} = \frac{1.8}{2 \cdot 2.78\text{mA}} = 323.7\Omega$$

$$\therefore L_{opt} = \frac{V_{DD}}{2I_{DD}} \cdot \frac{1}{Q\omega_{osc}} = 323.7\Omega \left( \frac{1}{5 \cdot 10\pi \times 10^9} \right) = 2.06\text{nH}$$

**Example - Continued**

4.) The value of  $C_{tot}$  is,

$$C_{tot} = \frac{1}{\omega_{osc}^2 L_{opt}} = \frac{1}{(10\pi \times 10^9)^2 (2.06 \text{ nH})} = 491.6 \text{ fF}$$

Unfortunately, we see that  $C_{var} = 491.6 \text{ fF} - 550 \text{ fF} = -58 \text{ fF}$

Our only choices are:

- a.) Decrease the inductor size which will reduce the output swing.
- b.) Decrease the buffer input capacitance which will degrade the drive capability.
- c.) Decrease the W/L of the transistors by decreasing the power dissipation

5.) Since the inductance capacitance is small compared to the buffer input capacitance, we will choose to reduce the buffer input capacitance by a half giving

$$C_{var} = 491.6 \text{ fF} - 450 \text{ fF} = 42 \text{ fF}$$

**A 2.5-GB/s CLOCK AND DATA RECOVERY CIRCUIT<sup>†</sup>****Introduction**

Important considerations in this design are:

- Jitter
- VCO tuning range
- 2.5 GHz speed in 0.25 $\mu\text{m}$  CMOS technology
- Skew in phase detector and decision circuit

General block diagram of the architecture:

 


Fig. 4.2-23

<sup>†</sup> B. Razavi, "A 2.5-Gb/s 15-mW clock recovery circuit," *IEEE Journal of Solid-State Circuits*, vol. 31, pp. 472 - 480, April 1996.

## Jitter Issues

Source of jitter:


- Input jitter, VCO device noise, VCO jitter due to ripple on control, supply and substrate noise.

Trade-offs in the choice of VCO gain,  $K_{VCO}$ :

- Low supply voltage necessitates high  $K_{VCO}$  for a given tuning range.
- For a given ripple on the control line, higher  $K_{VCO}$  results in higher jitter.

Solution:

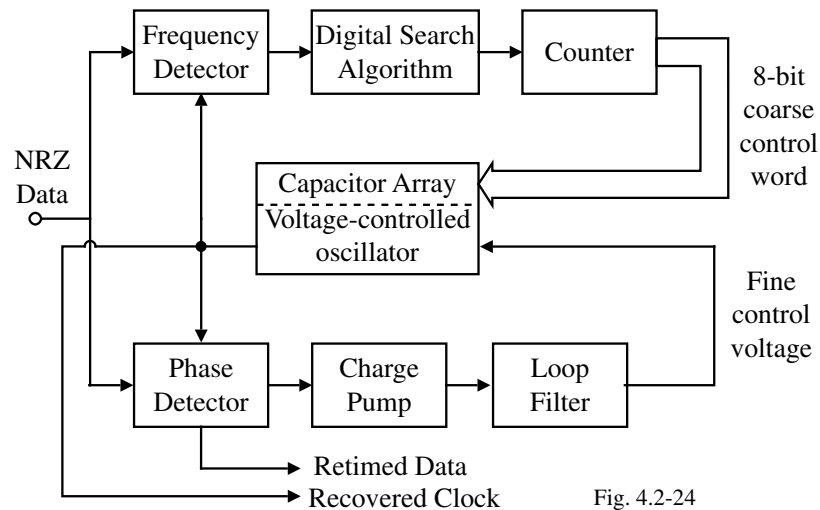Decompose the control line into fine and coarse control lines. The coarse control will be driven by the frequency detector and will remain quiet.



## Frequency Detector

Use the Pottbacker quadrature frequency detector:


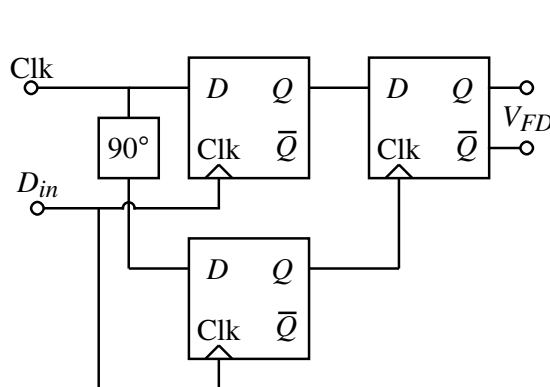


Fig. 4.2-25

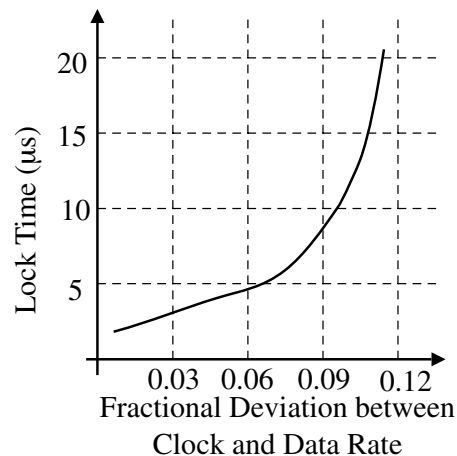

### Frequency Detector – Continued

Add a charge pump to the previous circuit to get:

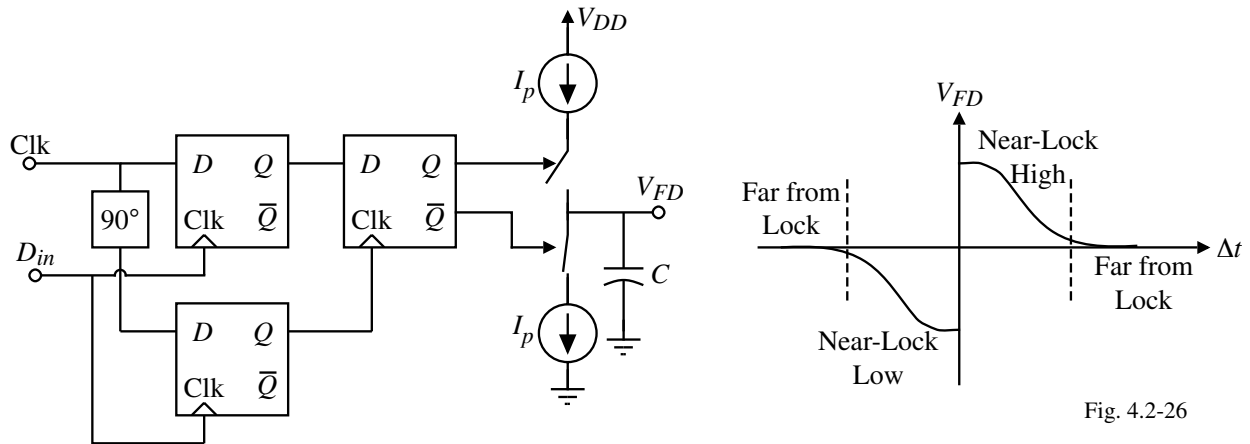


Fig. 4.2-26

Comments:

- In the near-lock regions, the output carries enough DC content to signify the polarity of the frequency difference.
- In the far-from-lock regions, the output carries little information.

### Digital Search Algorithm with a Broad Range

 


Fig. 4.2-27

Comments:

- 8 bits of resolution in the capacitor array allows a frequency step of 2.1 MHz.
- The fine VCO control can have a gain of only 50MHz/V.

 


Fig. 4.2-28

## VCO Circuit Implementation

 


Fig. 4.2-29

### Comments:

- Continuous frequency tuning is obtained by varying the coupling between oscillators.
- The VCO has a fully differential control.
- The input V/I converter, M1-M2, linearizes the input transconductance with M3-M4.

## Capacitor Array

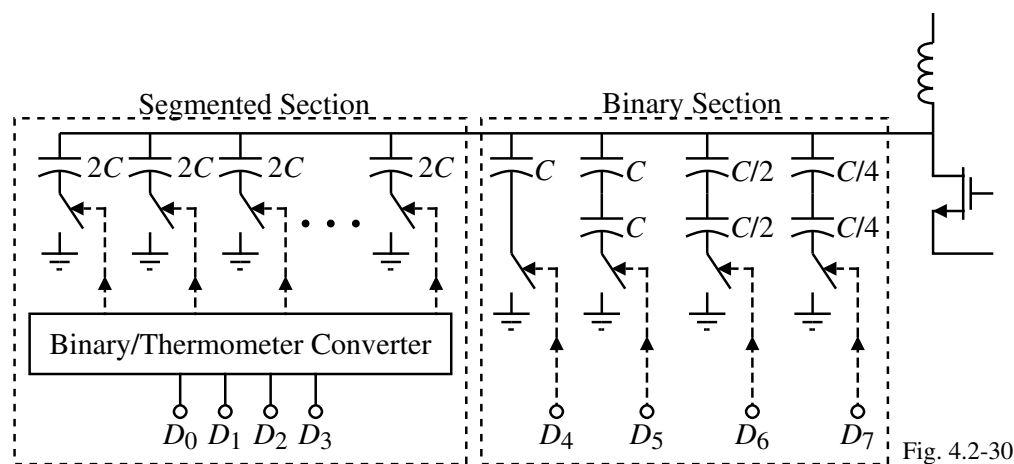


Fig. 4.2-30

### Comments:

- The capacitors are divided into a 4-bit (MSB) segmented section and a 4-bit (LSB) binary-weighted section.
- Monotonicity guaranteed with up to 12.5% capacitor mismatch.
- Requires only 20 switched elements and has a worst case  $Q$  of 10.



### Quadrature Frequency Detector Implementation

Use dummy loading to balance out delays.


 



Fig. 4.2-31

Circuit Implementation:

Symmetric XOR

 


Delay Cell

 

### Charge Pump Implementation

Charge-Pump Circuit:

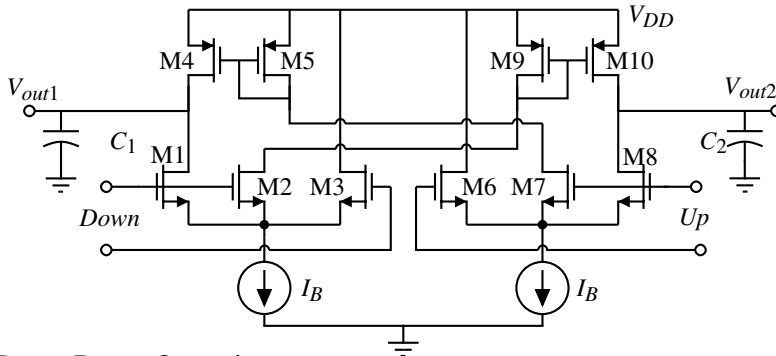

Pump-Down Operation:


 


Fig. 4.2-33


No Up or Down Pulses:

 

This charge-pump has no current mismatch or charge mismatch.

### Implementation of the Charge Pump – Continued

Conventional Implementation:

 

This implementation:

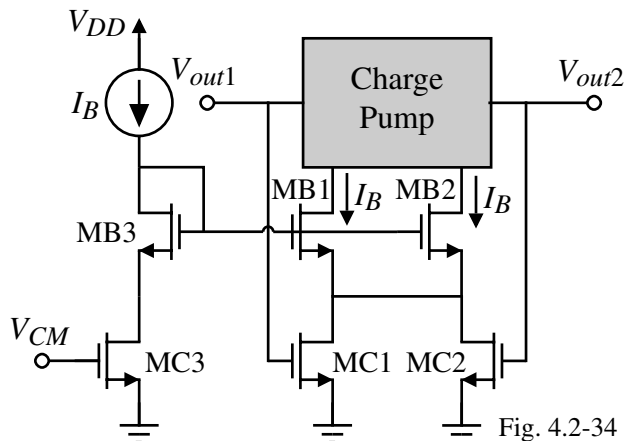


Fig. 4.2-34

The modified implementation stabilizes the common-mode output of the charge pump to a specific value,  $V_{CM}$ .

### Theoretical Jitter Analysis (Open Loop)

Block diagram of the jitter model:

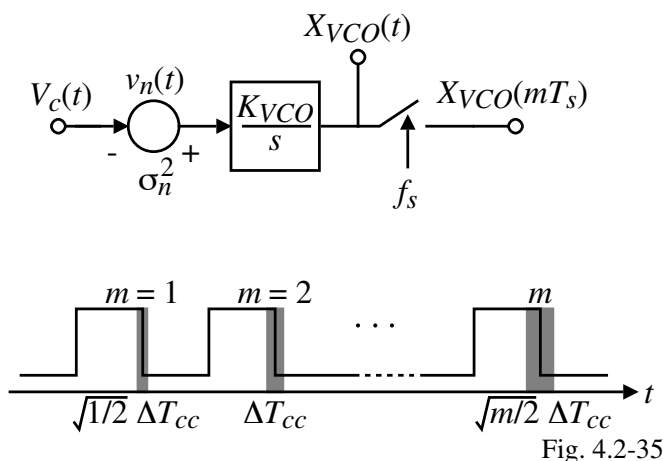


Fig. 4.2-35

The variation of the jitter as a function of  $mT_s$  can be written as,

$$\Delta T(mT_s) \approx K_{VCO} \sqrt{\frac{mT_s}{2}} \sigma_n \frac{T_s}{2\pi}$$

Therefore,

$$\Delta T(t) \approx \sqrt{\frac{f_{\sigma} t}{2}} \Delta T_{cc}$$

### Jitter Analysis – Continued

Recall that timing jitter creates phase noise, i.e.,

 


Fig. 4.2-36

$$S_{\phi}(f) \approx \frac{K_{VCO}^2 \sigma_n^2}{2(2\pi)^2 (f - f_0)^2}$$

$$\sigma_T^2 = \Delta T_{cc}^2 \approx \frac{2}{f_0^3} S_{\phi}(f) (f - f_0)^2$$

Illustration:

 


Fig. 4.2-37

### Simulated Open- and Closed-Loop Jitter

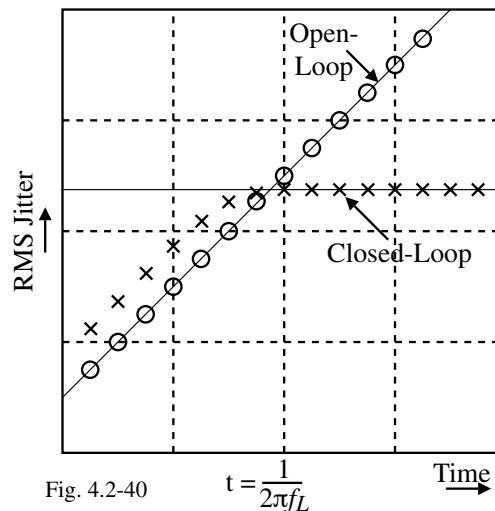



Fig. 4.2-40

$$t = \frac{1}{2\pi f_L}$$


$$\text{Maximum closed-loop jitter} = \sqrt{\frac{f_0}{2}} \Delta T_{cc} \sqrt{\frac{1}{2\pi f_L}}$$

(J. McNeill, JSSCC, June 1997)

## Measured VCO Characteristics

 


## Chip Microphotograph

 


### Jitter Measurements

PRBS of length  $2^{23}-1$ :

 


81 ps/div

 


20 ps/div

### Recovered Clock Spectrum

 


### Eye Diagram

 


### Theoretical Jitter versus Measured Jitter

#### Phase Noise

 

- Measured free-running VCO phase noise = -85 dBc/Hz
- Closed-loop bandwidth = 3.1 MHz
- Theoretical closed-loop jitter = 5.08 ps

#### Timing Jitter

 

Experimental closed-loop jitter = 5.1 ps

## Summary of Experimental Results

| Specification                     | Value             |
|-----------------------------------|-------------------|
| Bit Rate                          | 2.5 Gb/s          |
| Capture Range                     | 540 MHz           |
| Phase Noise at 1-MHz Offset       | -92 dBc/Hz        |
| Jitter for PRBS $2^{23}-1$        | 5.1 ps            |
| Power Dissipation:                |                   |
| VCO                               | 11mW              |
| VCO Buffer                        | 8mW               |
| Phase detector and charge pump    | 28.5mW            |
| Frequency detector and comparator | 7.5mW             |
| Total                             | 55mW              |
| Supply Voltage                    | 2.5V              |
| Die Area                          | 0.9 mm x 0.6 mm   |
| Technology                        | 0.25 $\mu$ m CMOS |

## Summary of 2.5 Gb/s Example

- A method to resolve the conflict between a wide tuning range and low VCO sensitivity is described utilizing a dual-loop topology.
- An LC-based VCO with a segmented capacitor array is used to discretely tune the oscillation frequency.
- A charge pump that reduces drift in the event of no UP or DOWN pump signal is introduced.
- A method is proposed to estimate the closed-loop jitter based on the phase noise of the free-running VCO.

(To be continued)