


### Homework Assignment No. 3 - Solutions

#### Problem 1 - (10 points)

Assume an LPLL has  $F(s) = 1$  and the PLL parameters are  $K_d = 0.8\text{V/radians}$ ,  $K_o = 100\text{ MHz/V}$ , and the oscillation frequency,  $f_{osc} = 500\text{MHz}$ . Sketch the control voltage at the output of the phase detector if the input frequency jumps from  $500\text{MHz}$  to  $650\text{MHz}$ .
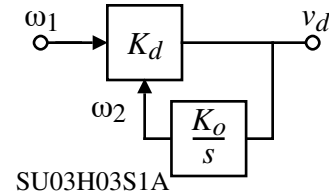
#### Solution

Find the transfer function from the input frequency,  $f_{in}$ , to the output of the phase detector,  $v_d$ .



$$V_d = K_d(\theta_1 - \theta_2) = K_d\theta_1 - \frac{K_d K_o}{s} V_d$$

$$V_d \left( 1 + \frac{K_d K_o}{s} \right) = K_d \theta_1 = K_d \left( \frac{\omega_1}{s} \right)$$

$$\therefore \frac{V_d}{\omega_1} = \frac{K_d}{s + K_d K_o} \rightarrow V_d(s) = \frac{K_d}{s + K_d K_o} \omega_1(s) = \frac{K_d}{s + K_d K_o} \frac{\Delta\omega_1}{s} = \frac{k_1}{s} + \frac{k_2}{s + K_d K_o}$$


By partial fraction expansion we can show that  $k_1 = -k_2 = \frac{K_d \Delta\omega_1}{K_d K_o} = \frac{K_d \Delta\omega_1}{K_v} = 1.5\text{V}$

Note the units of  $\frac{K_d \Delta\omega_1}{K_v}$  are  $\frac{(\text{V/rad})(\text{rad/sec})}{1/\text{sec}} = \text{V}$

and  $K_v = (2\pi \cdot 100\text{MHz/V})(0.8\text{V/rad.}) = 502.65 \times 10^6 \text{ (1/sec.)}$


$$\therefore v_d(t) = \frac{K_d \Delta\omega_1}{K_v} (1 - e^{-K_v t}) = 1.5(1 - e^{-502.65 \times 10^6 t})$$

A plot of  $v_d(t)$  is shown below.

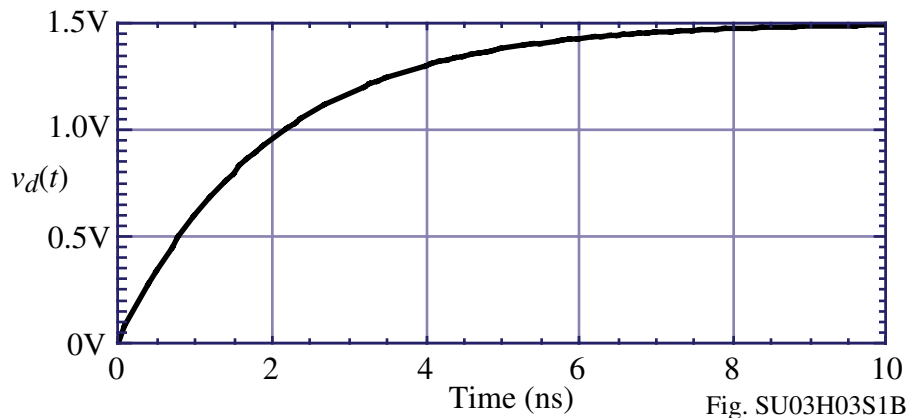

Problem 2 – (10 points)

A Type I PLL incorporates a VCO with  $K_o = 100\text{MHz/V}$ , a phase detector with  $K_d = 1\text{V/rad}$ , and a first-order, lowpass filter with  $\omega_{LPF} = 2\pi \times 10^6$  radians/s shown below. A divider of 100 has been placed in the feedback path to implement a frequency synthesizer. (a.) Find the value of the natural damping frequency,  $\omega_n$ , and the damping factor,  $\zeta$ , for the transfer function  $\phi_{out}(s)/\phi_{in}(s)$ , for this PLL. (b.) If a step input of  $\Delta\phi_{in}$  is applied at  $t = 0$ , what is the steady-state phase error at the output of the phase detector,  $\phi_e$ ? The steady-state error is evaluated by multiplying the desired phase by  $s$  and letting  $s \rightarrow 0$ .

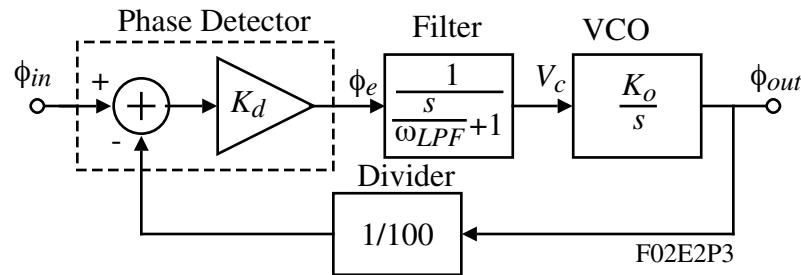Solution

$$(a.) \phi_{out} = \frac{K_o}{s} \left( \frac{1}{\frac{s}{\omega_{LPF}} + 1} \right) K_d \left( \phi_{in} - \frac{\phi_{out}}{N} \right) \rightarrow \phi_{out} \left[ 1 + \frac{K_o}{sN} \left( \frac{K_d}{1 + \frac{s}{\omega_{LPF}}} \right) \right] = \frac{K_o}{s} \left( \frac{K_d}{\frac{s}{\omega_{LPF}} + 1} \right) \phi_{in}$$

$$\therefore \frac{\phi_{out}(s)}{\phi_{in}(s)} = \frac{K_o K_d}{s \left( 1 + \frac{s}{\omega_{LPF}} \right) + \frac{K_o K_d}{N}} = \frac{K_o K_d \omega_{LPF}}{s^2 + \omega_{LPF} s + \frac{K_o K_d \omega_{LPF}}{N}} = \frac{\omega_n^2}{s^2 + 2\zeta \omega_n s + \omega_n^2}$$

$$\text{Thus, } \omega_n^2 = \frac{K_o K_d \omega_{LPF}}{N} = \frac{2\pi \times 10^6 \cdot 2\pi \times 10^8}{100} = 4\pi^2 \times 10^{12} \rightarrow \omega_n = 2\pi \times 10^6$$

$$\zeta = \frac{\omega_{LPF}}{2\omega_n} = \frac{\omega_{LPF}}{2\sqrt{\frac{K_o K_d \omega_{LPF}}{N}}} = \frac{1}{2} \sqrt{\frac{N \omega_{LPF}}{K_o K_d}} = \frac{1}{2} \sqrt{\frac{100 \cdot 2\pi \times 10^6}{1.2\pi \times 10^8}} = 0.5$$

$$\therefore \boxed{\omega_n = 2\pi \times 10^6 \text{ and } \zeta = 0.5}$$

(b.) First we must solve for  $\phi_e(s)$  which is found as



$$\phi_e(s) = \frac{s \left( 1 + \frac{s}{\omega_{LPF}} \right)}{K_o} \phi_{out}(s) = \frac{s \left( 1 + \frac{s}{\omega_{LPF}} \right)}{K_o} \frac{K_o K_d \omega_{LPF}}{s^2 + \omega_{LPF} s + \frac{K_o K_d \omega_{LPF}}{N}} \phi_{in}(s)$$

$$\text{If } \phi_{in}(s) = \frac{\Delta\phi_{in}}{s}, \text{ then we can write } s\phi_e(s) = \frac{K_d (s^2 + \omega_{LPF} s) \Delta\phi_{in}}{s^2 + \omega_{LPF} s + \frac{K_o K_d \omega_{LPF}}{N}}$$

Therefore, we see that the steady-state error is  $\boxed{\phi(t=\infty) = 0.}$

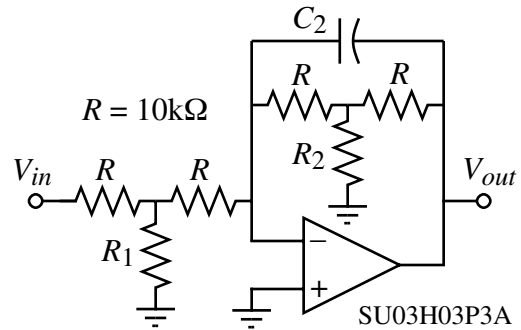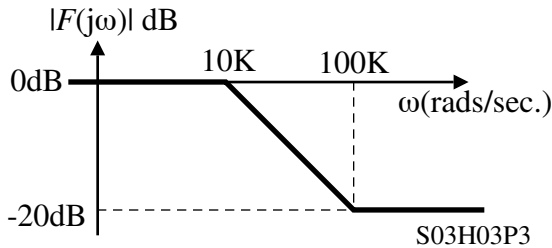Problem 3 – (10 points)

Modify the active filter shown of Problem 4 of Homework 2 to design the lag-lead loop filter shown below. The capacitors can be no larger than 10pF. Give the values of  $R_1$ ,  $R_2$ ,  $C_1$  and  $C_2$ .



Solution


The transfer function corresponding to the above Bode plot is,

$$F(s) = \frac{\frac{s}{10^5} + 1}{\frac{1}{10^4} + 1}$$

The modification of the filter is shown where from Prob. 4 of Homework 2,

$$R_{Ti} = \frac{2RR_i + R^2}{R_i}$$

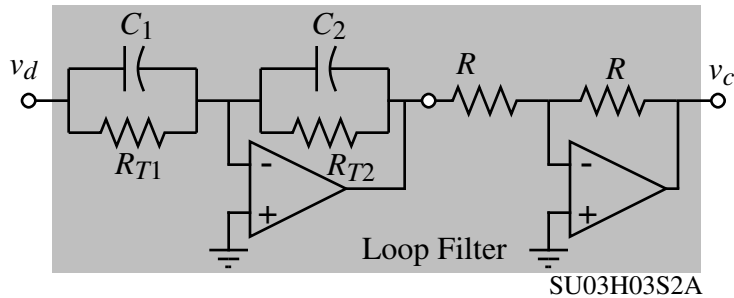The transfer function of this filter is found as,



$$F(s) = \frac{V_c(s)}{V_d(s)} = \left(\frac{R_{T2}}{R_{T1}}\right) \frac{sR_{T1}C_1 + 1}{sR_{T2}C_2 + 1} \Rightarrow R_{T2} = R_{T1} = R_T, R_T C_1 = 10^{-5} \text{ and } R_T C_2 = 10^{-4}$$


We see if  $R_{T2} = R_{T1}$ , then  $C_2 = 10C_1$ . Choosing  $C_2 = 10\text{pF}$  gives  $C_1 = 1\text{pF}$ . This gives

$$R_T = \frac{10^{-4}}{C_2} = \frac{10^{-4}}{10^{-11}} = 10^7$$

$$R_T = \frac{2RR_i + R^2}{R_i} = 2R + \frac{R^2}{R_1} = 20 \times 10^3 + \frac{100 \times 10^6}{R_1} = 10^7 \Rightarrow R_1 = \frac{100 \times 10^6}{10^7 - 20 \times 10^3} = 10.02 \Omega$$

Therefore,  $R_1 = R_2 = \underline{10.02 \Omega}$ ,  $C_1 = \underline{1\text{pF}}$  and  $C_2 = \underline{10\text{pF}}$

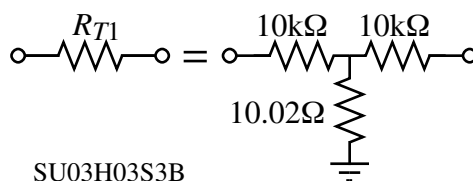The realization is completed by replacing each of the  $R_T$  resistors with the following equivalent:



SU03H03S3B

Problem 4 – (10 points)

Using the filter of Problem 3, find the value of  $\omega_n$  and  $\zeta$  of the PLL if  $K_d = 1\text{V/radians}$ ,  $K_o = 2\text{Mradians/V}\cdot\text{sec}$ . What is the steady state phase error in degrees if a frequency ramp of  $10^9$  radians/sec.<sup>2</sup> is applied to the PLL?

Solution

Using the definition give in the notes for the time constants of the passive lag-lead filter we get,

$$F(s) = \frac{\frac{s}{10^5} + 1}{\frac{1}{10^4} + 1} = \frac{s\tau_2 + 1}{s(\tau_1 + \tau_2) + 1} \quad \Rightarrow \quad \tau_2 = 10^{-5} \text{ sec. and } \tau_1 = 9 \times 10^{-5} \text{ sec.}$$

$$\therefore \omega_n = \sqrt{\frac{K_o K_d}{\tau_1 + \tau_2}} = \sqrt{\frac{2 \times 10^6}{10^{-4}}} = \sqrt{2} \times 10^5 = \underline{\underline{141.4 \times 10^3 \text{ radians/sec.}}}$$

$$\zeta = \frac{\omega_n}{2} \left( \tau_2 + \frac{1}{K_o K_d} \right) = \frac{\sqrt{2} \times 10^5}{2} \left( 10^{-5} + \frac{1}{2 \times 10^6} \right) = \frac{1}{\sqrt{2}} \left( 1 + \frac{1}{20} \right) = \underline{\underline{0.742}}$$

Assuming the PLL has a high loop gain, then the steady-state phase error can be found as

$$\theta_e(\infty) = \frac{\Delta \dot{\omega}}{\omega_n^2} = \frac{10^9}{2 \times 10^{10}} = \frac{1}{20} \text{ radians} = \underline{\underline{2.86^\circ}}$$

Problem 5 – (10 points)

Solve for the crossover frequency of the PLL of Problems 3 and 4 and find the phase margin. Use SPICE to find the open-loop frequency response of the PLL and from your plot determine the crossover frequency and phase margin and compare with your calculated values.

Solution

The crossover frequency can be found as,

$$\begin{aligned}\omega_c &= \omega_n \sqrt{2\xi^2 + \sqrt{4\xi^4 + 1}} = \sqrt{2} \times 10^5 \sqrt{2 \cdot 0.742^2 + \sqrt{4 \cdot 0.742^4 + 1}} \\ &= \sqrt{2} \times 10^5 (1.6089) = 2.275 \times 10^5 \text{ radians/sec.} = 36.208 \text{ kHz}\end{aligned}$$

The open loop transfer function is given as


$$LG(s) = \frac{K_v (1+s\tau_1)}{s (1+s\tau_2)} = \frac{\sqrt{2} \times 10^5 (1+s10^{-5})}{s (1+s10^{-4})}$$

The phase margin can be written as,

$$PM = 180^\circ - 90^\circ + \tan^{-1}\left(\frac{\omega_c}{10^5}\right) - \tan^{-1}\left(\frac{\omega_c}{10^4}\right) = 90^\circ + 66.27^\circ - 87.48^\circ = \underline{\underline{68.79^\circ}}$$

SPICE Results:

```
Problem H3P5-Open Loop Response of an LPLL with Lead-Lag Filter
VS 1 0 AC 1.0
R1 1 0 10K
* Loop bandwidth = Kv =2xE+6    Tau1=1E-4    Tau2=1E-5
ELPLL 2 0 LAPLACE {V(1)}=
+{(2E+6/(S+0.001))*((1+1E-5*S)/(1+1E-4*S))}
* Note: The 0.001 added to "S" in the denominator is to prevent
* blowup of the problem at low frequencies.
R2 2 0 10K
*Steady state AC analysis
.AC DEC 20 10 100K
.PRINT AC VDB(2) VP(2)
.PROBE
.END
```

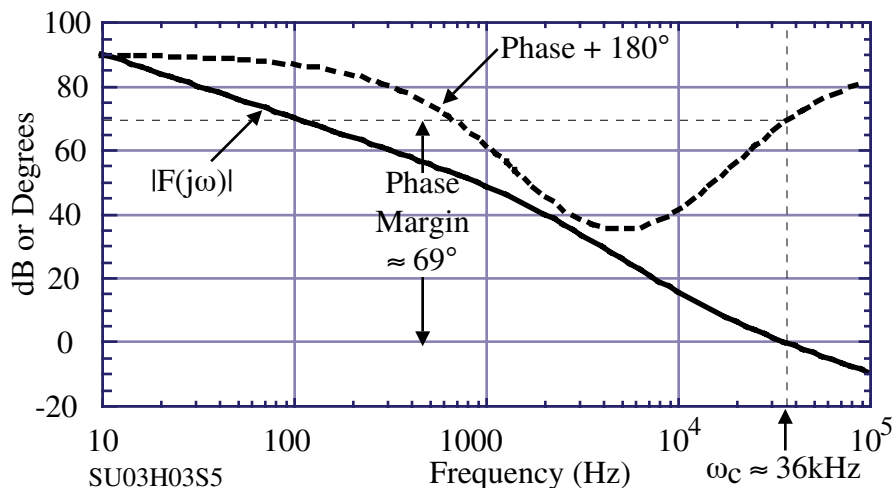

The simulation results agree well with the calculated results.