

**Homework Assignment No. 3**


This homework assignment is due in class on Wednesday, June 4, 2003.

Problem 1 - (10 points)

Assume an LPLL has  $F(s) = 1$  and the PLL parameters are  $K_d = 0.8\text{V/radians}$ ,  $K_o = 100\text{MHz/V}$ , and the oscillation frequency,  $f_{osc} = 500\text{MHz}$ . Sketch the control voltage at the output of the phase detector if the input frequency jumps from 500MHz to 650MHz.



Problem 2 – (10 points)

A Type I PLL incorporates a VCO with  $K_o = 100\text{MHz/V}$ , a phase detector with  $K_d = 1\text{V/rad}$ , and a first-order, lowpass filter with  $\omega_{LPF} = 2\pi \times 10^6\text{ radians/s}$  shown below. A divider of 100 has been placed in the feedback path to implement a frequency synthesizer. (a.) Find the value of the natural damping frequency,  $\omega_n$ , and the damping factor,  $\zeta$ , for the transfer function  $\phi_{out}(s)/\phi_{in}(s)$ , for this PLL. (b.) If a step input of  $\Delta\phi_{in}$  is applied at  $t = 0$ , what is the steady-state phase error at the output of the phase detector,  $\phi_e$ ? The steady-state error is evaluated by multiplying the desired phase by  $s$  and letting  $s \rightarrow 0$ .

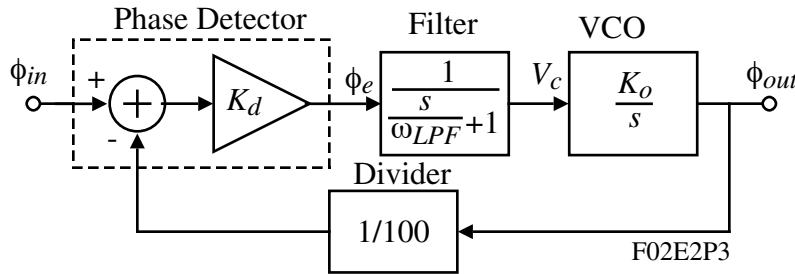

Problem 3 – (10 points)

Modify the active filter shown of Problem 4 of Homework 2 to design the lag-lead loop filter shown below. The capacitors can be no larger than 10pF. Give the values of  $R_1$ ,  $R_2$ ,  $C_1$  and  $C_2$ .

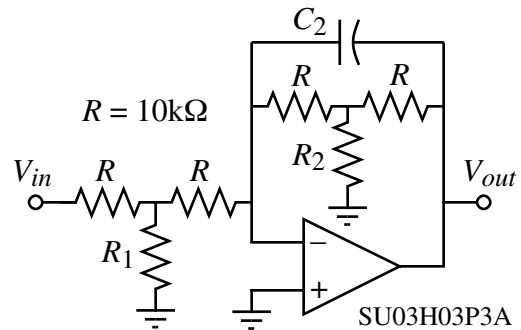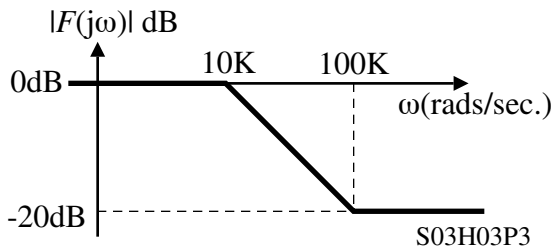

Problem 4 – (10 points)

Using the filter of Problem 3, find the value of  $\omega_n$  and  $\zeta$  of the PLL if  $K_d = 1\text{V/radians}$ ,  $K_o = 2\text{Mradians/V}\cdot\text{sec}$ . What is the steady state phase error in degrees if a frequency ramp of  $10^8\text{ radians/sec}^2$  is applied to the PLL?

Problem 5 – (10 points)

Solve for the crossover frequency of the PLL of Problems 3 and 4 and find the phase margin. Use SPICE to find the open-loop frequency response of the PLL and from your plot determine the crossover frequency and phase margin and compare with your calculated values.