

MONOLITHIC INDUCTOR DESIGN IN SI TECHNOLOGY

Objective

The objective of this presentation is:


- 1.) Illustrate the design and analysis of on-chip spiral inductor.
- 2.) Show an inductor design example using ASITIC.

Outline

- Spiral Inductors
- Inductor Modeling
- Design Guidelines for CMOS Spiral Inductors
- ASITIC overview
- Design Example
- References

Spiral Inductors

 The most widely used on-chip inductor is a spiral inductor.




- D: diameter
- W: width of a spiral
- S: spacing between turns
- N: number of turns

- Design Parameters
 - Diameter, D , is mainly decided from area restriction.
 - Remaining parameters, W , S , and N are optimized to get
 - i) Desired inductance value, L
 - ii) High quality factor, Q
 - iii) High self-resonant frequency, f_{SR}

Spiral Inductors

Implementation

 
- Spiral inductor is implemented using metal layers in Si technology.
- Topmost metal is preferred because of its low resistivity.
- More than one metal layers can be connected together to reduce resistance or area.
- The accurate analysis of a spiral inductor requires complex electro-magnetic simulation.



 (a) top view (b) cross-sectional view of a spiral inductor using three metal process [3]

Inductor Modeling

A lumped circuit model can be developed to show spiral inductor conceptually and to be used in circuit design.



$$L \approx \frac{37.5\mu_0 N^2 a^2}{11D - 14a}$$

$$R_s \approx \frac{l}{W \cdot \sigma \cdot \delta (1 - e^{-l/\delta})}$$

$$C_p = N \cdot W^2 \cdot \frac{\epsilon_{ox}}{t_{ox}}$$

$$C_{ox} = W \cdot L \cdot \frac{\epsilon_{ox}}{t_{ox}}$$

$$R_1 \approx \frac{2}{W \cdot L \cdot G_{sub}}$$

$$C_1 \approx \frac{W \cdot L \cdot C_{sub}}{2}$$

where

$\mu_0 = 4\pi \times 10^{-7}$, σ is the conductivity of the material

a is the distance from the center of the inductor to the middle of the windings

L is the total length of the spiral, t is the thickness of the metal,

δ is the skin depth given by $\delta = \sqrt{\frac{2}{W\mu_0\sigma}}$, $G_{sub}(C_{sub})$ is process-dependent parameters.

Inductor Modeling

- Components
 - R_s : low-frequency resistive loss of a metal and skin effect.
 - C_p : arises from the overlap of the cross-under with the rest of the spiral. The lateral capacitance from turn to turn is included.
 - C_{ox} : capacitance between the spiral and the substrate
 - R_1 : substrate loss
 - C_1 : capacitance of the substrate
- Design specifications
 - L: desired inductance value
 - Q: quality factor. Simple approximation is

$$Q = \frac{\omega L}{R_s}$$

- f_{SR} : self-resonant frequency. The resonant frequency of LC combination represents the upper useful frequency limit of the inductor. Inductor operation frequency should be lower than f_{SR} , $f < f_{SR}$

Design Guidelines for CMOS Spiral Inductors [4]

- D: outer diameter
 - $D \uparrow$ - $Q \uparrow$ for small D, but self-resonant frequency, $f_{SR} \downarrow$, as parasitic capacitance between the substrate and the spiral increases.
 - A good design usually has $D < 200\mu\text{m}$.
- W: metal width
 - Metal width should be as wide as possible.
 - $W \uparrow$ - $Q \uparrow$ as $R_s \downarrow$
 - However, as $W > W_{opt}$, skin effects appear in metal traces, increasing R_s .
 - A good design uses $10\mu\text{m} < W < 20\mu\text{m}$.
- S: spacing between turns
 - Spacing should be as small as possible.
 - $S \uparrow$ - $L \uparrow$ as M (mutual inductance) \downarrow
 - Use minimum metal spacing allowed in the technology (ex., $S_{min} \approx 1\sim 5\mu\text{m}$ in CMOS). Make sure the inter-winding capacitance between turns is not significant.
- N: number of turns
 - Use a value that gives a layout convenient to work with other parts of circuits.

ASITIC

• Overview

- An analysis and simulation tool for spiral inductors and transformers for ICs
- Developed by Ali M. Niknejad at UC Berkeley
- Document: <http://formosa.eecs.berkeley.edu/~niknejad/asitic.html>

• Procedure

- Log on to UNIX account.
- Make a directory for ASITIC files (ex. 'my_asitic')
- Copy a technology file (CMOS.tek) to working directory. This is the default tech file that can be replaced for other processes.
> cp /a/yamsrv1.ece.gatech.edu/export/home3/asitic/common/tek/CMOS.tek .
- Start ASITIC program with following command
> /a/yamsrv1.ece.gatech.edu/export/home3/asitic/asitic_sun -8 -t CMOS.tek
- ASITIC window will pop up and command line shows a prompt for the program.
ASITIC>
- Create, analyze and optimize inductors using commands.
- Useful command: sq, optl, pix and etc. For reference, refer 'Command Reference' section of the documentation.

Design Example

A 2GHz LC tank will be designed as a part of LC oscillator. C value is given as 3pF.

(a) Find L value. (b) Design a spiral inductor with L value ($\pm 5\%$ range) from (a) using ASITIC. Optimize design parameters, W, S, D and N to get a high Q ($Q_{\min} = 5$). Show L, Q, f_{SR} value obtained from simulation. (c) Show the layout. (d) Give a lumped circuit model.

Solution

(a) LC tank oscillation frequency is given as 2GHz.

$$\omega_{osc} = \frac{1}{\sqrt{LC}}, \quad L = \frac{1}{\omega_{osc}^2 \cdot C} = \frac{1}{(2\pi \cdot 2 \times 10^9)^2 \cdot (3 \times 10^{-12})} = 2.11 \times 10^{-9}$$

L = 2.11nH is desired.


(b) L = 2.11nH ($\pm 5\%$) is used as input parameter. Several design parameters are tried to get high Q and f_{SR} values. Final design has

- Parameters: W = 19um, S = 1um, D = 200um, N = 3.5
- Resulting inductor: L = 2.06nH, Q = 7.11, $f_{SR} = 9.99\text{GHz}$ @ 2GHz


This design is acceptable as $Q > Q_{\min}$ and $f < f_{SR}$.

Design Example

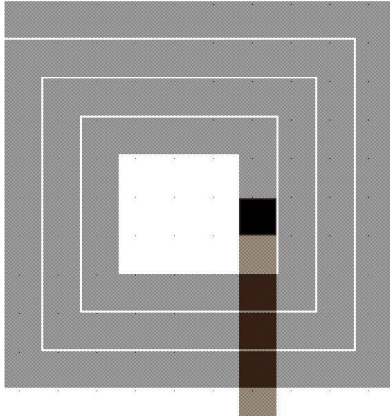(c) ASITIC generates a layout automatically. It can be saved and imported to use in other tools such as Cadence, ADS and Sonnet.



(d) Analysis in ASITIC gives a pi model.

 

Pi model is usually not symmetrical and this can be used for differential configuration where none of the two ports is ac-grounded.

References

- [1] Thomas H. Lee, *The Design of CMOS Radio-Frequency Integrated Circuits*, Cambridge
- [2] Behzad Razavi, *Design of Integrated Circuits for Optical Communications*, McGraw Hill
- [3] Joachim N. Burghartz and et al, "RF Circuit Design Aspects of Spiral Inductors on Silicon", *IEEE J. Solid-State Circuits*, vol. 33, no.12, pp. 2028-2034, 1998
- [4] Jaime Aguilera and et al, "A Guide for On-Chip Inductor Design in a Conventional CMOS Process for RF Applications", *Applied Microwave & Wireless*, pp. 56-65, October 2001