

Lecture 190 – All Digital Frequency Synthesizer for Bluetooth

What is bluetooth?







- A short-range technology for integration into mobile and handheld devices that is targeted to replace cables.
- Radio specification
 - Frequency range: 2400 ~ 2483.5 MHz
 - Spectrum spreading: FHSS (Frequency Hopping Spectrum Spreading)
 - $f_k = 2.402 + k$ MHz, $k = 0, \dots, 78$ (dwell time: .625 ms)
 - Channel bandwidth: 1 MHz
 - Modulation: GFSK (BT = 0.5; $0.28 < h < 0.35$)
 - Receiver sensitivity: -70 dBm @ 0.1% BER
 - Coverage area: Up to 10 m
 - Transmit power: 0 dbm (up to 20 dbm with power control)



Frequency synthesizer specification for bluetooth application


- Frequency range: 2.402 ~ 2.480 GHz
- Settling time ≤ 220 usec
- Phase noise ≤ -89 dBc/Hz @ 500 KHz offset
 ≤ -121 dBc/Hz @ 2 MHz offset
- Channel bandwidth: 1 MHz, Error tolerance: ± 20 ppm (96 KHz)

Architecture selection

- Direct digital frequency synthesizer: limit of speed by Nyquist sampling theorem
- Integer-N frequency synthesizer (Channel spacing = reference freq.)
 - Channel spacing  Divide ratio  In-band phase noise 
 - Channel spacing  Loop bandwidth  Switching time 
- Fractional-N frequency synthesizer (Channel spacing \ll reference freq.)
 - Lower in-band noise
 - Faster lock
 - Fractional spurs eliminated by modulating divide ratio using high-order $\Sigma\Delta$ modulator

System level design using linear model

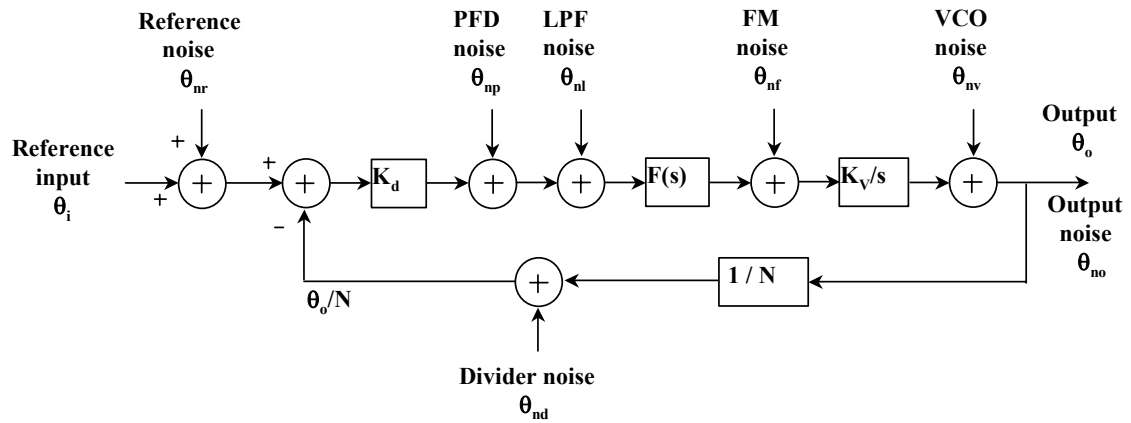- When PLL is in lock state, the linear model can be used to analyze it.
- Reference signal frequency » Loop bandwidth \Rightarrow Continuous model



$$B(s) = \frac{\theta_o(s)}{\theta_i(s)} = \frac{G(s)}{1 + G(s)H(s)}, \text{ where } G(s) = \frac{K_d K_v F(s)}{s} \text{ and } H(s) = \frac{1}{N}$$


- Output noise power, θ_{no}

$$\theta_{no}^2 = N^2 (\theta_{nr}^2 + \theta_{n,eq}^2) \cdot \left(\frac{O(s)}{1 + O(s)} \right)^2 + \theta_{nv}^2 \left(\frac{1}{1 + O(s)} \right)^2$$

Low-pass transfer function $\left(\frac{O(s)}{1 + O(s)} \right)^2$ High-pass transfer function $\left(\frac{1}{1 + O(s)} \right)^2$


where $\theta_{n,eq}^2 = \frac{1}{K_d^2} (\theta_{np}^2 + \theta_{nl}^2) + \frac{1}{K_d^2 F(s)^2} \theta_{nf}^2 + \theta_{nd}^2$ and $O(s) = G(s) \cdot H(s) = \frac{K_d K_v F(s)}{sN}$.

 - Reference noise and VCO inherent noise are the two major sources of phase noise in a PLL




Direct Digital Frequency Synthesizer

 - Direct Digital Frequency Synthesizer (DDFS)
 - Advantage: high frequency resolution, fast switching time
 - Disadvantage: high power consumption, limitation of highest frequency by Nyquist sampling theorem, discrete narrow band spurious signals
- The DDFS methods are combined with PLLs to achieve fine frequency steps with reasonable phase noise



PLL Based Frequency Synthesizer

 
- PLL is negative feedback system whose output frequency is locked onto an input signal
 - PD: error amplifier
 - LPF: suppress high frequency component of PD
 - VCO: Voltage Controlled Oscillator
- Low cost and good spurious suppression
- Coarse frequency resolution or frequency step and bad phase noise
- Slow switching speed for negative feedback loop



PLL Based Frequency Synthesizer (continued)


- Closed loop transfer function
 
$$B(s) = \frac{A(s)}{1 + A(s) \cdot \beta(s)} = \frac{K_{PD} \cdot K_{VCO} \cdot G(s) / s}{1 + \frac{K_{PD} \cdot K_{VCO} \cdot G(s)}{N \cdot s}} = \frac{N\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$




Charge-Pump Frequency Synthesizer

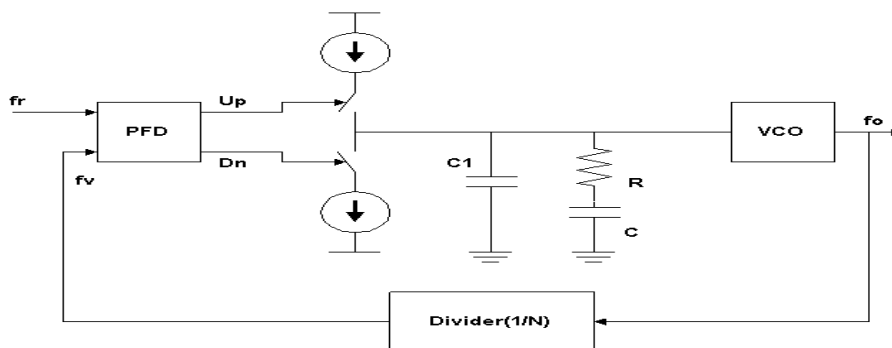- Charge-pump phase locked loop (type 2, 3rd order PLL)
 - Advantage: low phase noise
 - Disadvantage: process dependency, slow locking speed, large passive external elements (Rs and Cs)




Integer-N Frequency Synthesizer

- Integer-N Frequency Synthesizer
 - $f_{out} = N \cdot f_{ref}$, N : integer number
 - Frequency step size = reference frequency
 - Inverse relationship between step size and phase noise
 - To achieve a small channel spacing \rightarrow a low $f_{ref} \rightarrow$ narrow loop BW \rightarrow increasing the settling time, and reducing VCO noise suppression
 - Low reference \rightarrow large integer $N \rightarrow$ increasing in-band phase noise

 

Dual Loop Frequency Synthesizer

 - Dual Loop Frequency Synthesizer
 - Mixer is incorporated into the PLL \rightarrow alter the relationship between the channel spacing and the reference frequency of integer N synthesizer
 - 2 dual loop types: combination of 2 PLLs by a single side band mixer in parallel and in series
 - Adding fixed high offset frequency and low variable frequency




Dual Loop Frequency Synthesizer

- Dual Loop Frequency Synthesizer
 - Parallel configuration: (a fixed frequency + changeable frequency) @the output → large spurs during mixing
 - Series configuration: changeable frequency is added inside the loop → longer time to settle, small sideband from the mixer
 - The loop BW of the high frequency loop can be large → more reduction of phase noise close to the carrier
 - The division number of the divider can be reduced ← fixed offset frequency
 - The sidebands produced from non-ideal SSB mixing and larger power consumption

Fractional-N Frequency Synthesizer

- Fractional-N Frequency Synthesizer
 - Doesn't require more current, complexity or bigger dies
 - The reference $f_{ref} \gg$ frequency step time, f_{step}
 - $f_{VCO} = f_{ref}(N + (K/F))$

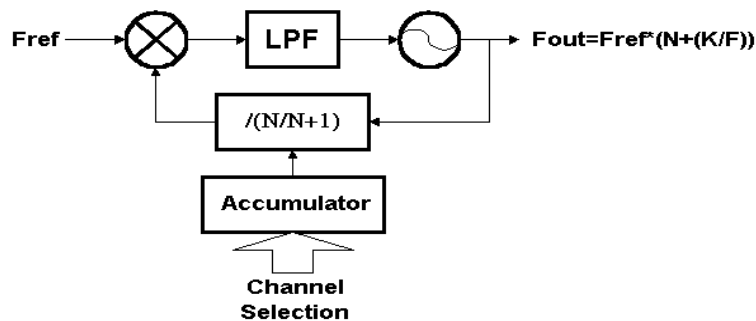
$$N_{fractional} = \frac{N \cdot (F - K) + (N + 1) \cdot K}{F} = N + \frac{K}{F}, F \geq K \geq 0$$



All Digital Frequency Synthesizer


- Apply digital filter to achieve a single-chip freq. synthesizer
 - Fully-integrated freq. synthesizer
 - Easy to implement Multi-mode application (ex. W-CDMA/GPRS/GSM)
 - Increase design robustness
- Apply MASH
 - Reduced spurs
 - Fast locking time
- Apply switched-current Oscillator
 - Wide locking range
 - Fast locking time

Block diagram


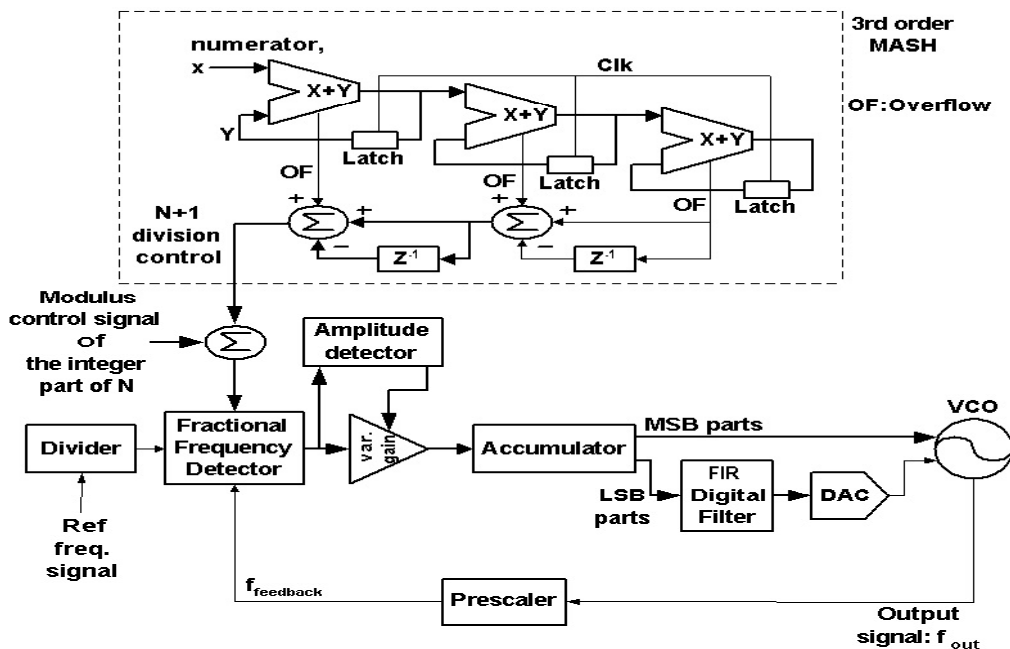


Linear model of the proposed freq. syn.


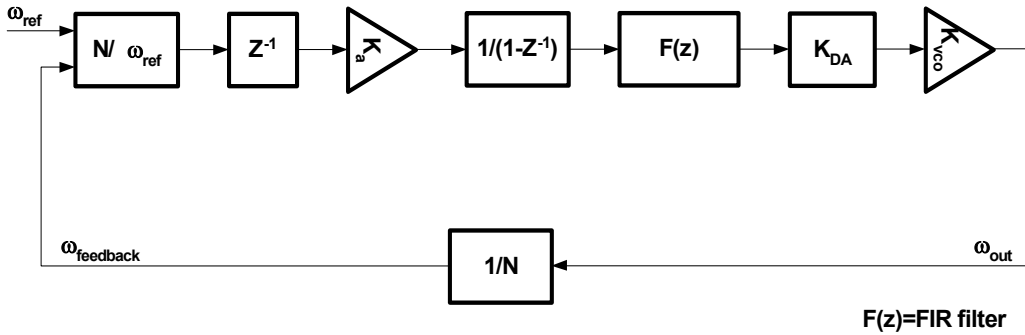
$$H(z) = \frac{\omega_{feedback}}{\omega_{ref}} = \frac{K \cdot F(z) \cdot z^{-1}}{1 - z^{-1}(1 - K \cdot F(z))}, K = \frac{K_{DA} \cdot K_{VCO} \cdot K_a}{\omega_{ref}}$$



 
 
System level unit step response and pole-zero plot



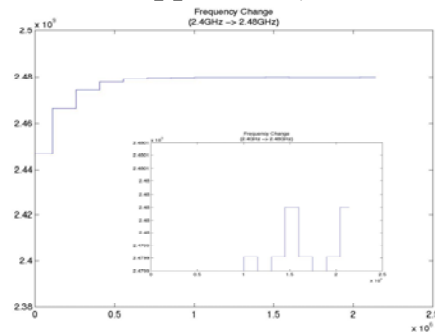 System level locking time simulation (Bluetooth application)



  System level noise simulation (Bluetooth application)





$Fractional = \frac{Num}{Den} = 32/64$

$0/64$


Block design: High-order ΣΔ Modulator

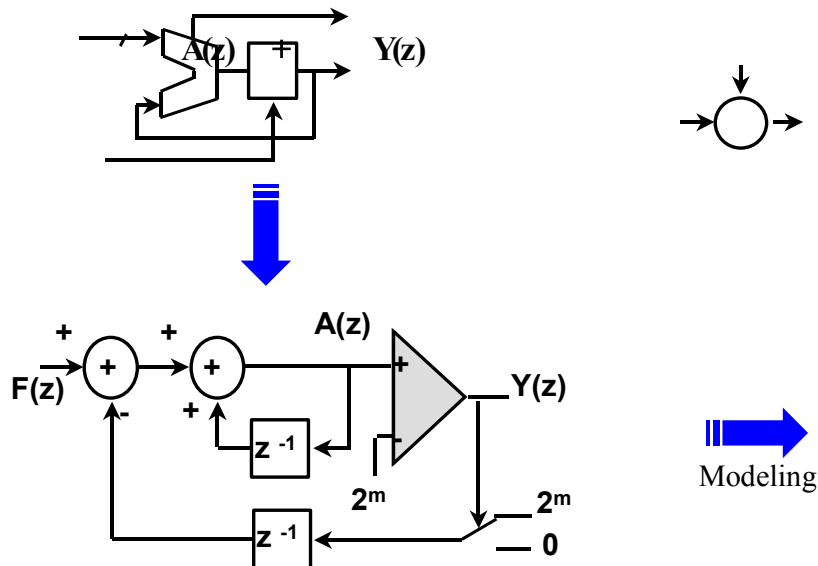- Used to eliminate fractional spurs by modulating divide ratio
- Higher-order modulator is used to meet higher spurs specification
- First-order ΣΔ modulator $Q(z)$



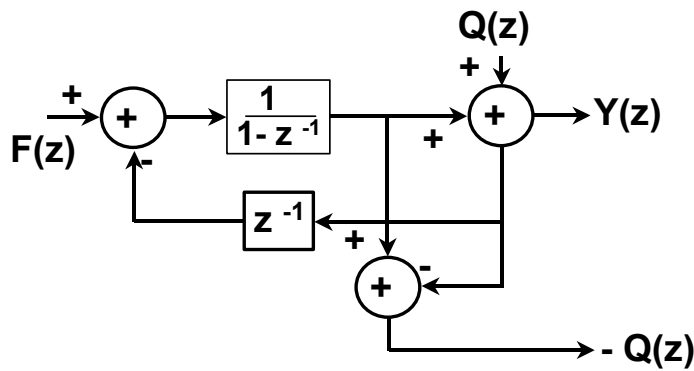

 - Third-order $\Sigma\Delta$ modulator system-level simulation result






Block Design (continued):

- 3rd order MASH system level simulation

$$y(z) = x(z) + (1 - z^{-1})^3 q_3(z)$$


$$y(z) = x(z) + H_{noise}(z) q_3(z)$$

  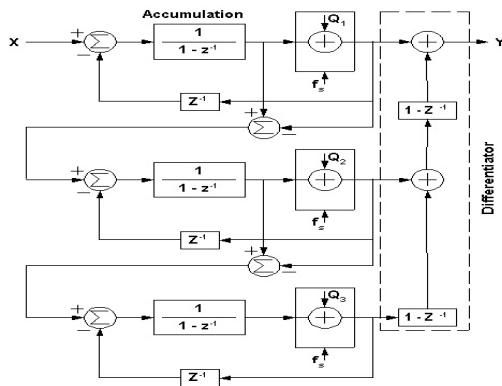

Block Design (continued)

- Conventional CMOS static logic
 - Wide noise margins
 - High packaging density
 - Zero static-power-dissipation
 - Coupling between the analog blocks and the digital blocks
 - Susceptible to power-supply noise

 - Current Mode Logic
 - Constant current source
 - Differential input & output




Block Design (continued)

- 8-bit Digital-to-Analog Converter
 - Symmetric 2-stage current-cell matrix architecture
 - A 4-MSB current-cell matrix and a 4-LSB current-cell matrix
 - Use thermometer-code
 - Monotonic conversion characteristic

$$I_{out} = I_{MSB}(2^3 B_7 + 2^2 B_6 + 2^1 B_5 + 2^0 B_4) + I_{LSB}(2^3 B_3 + 2^2 B_2 + 2^1 B_1 + 2^0 B_0)$$

$$I_{MSB} = 16 \cdot I_{LSB}$$

$$V_{out} = I_{out} \cdot R_{LOAD}$$


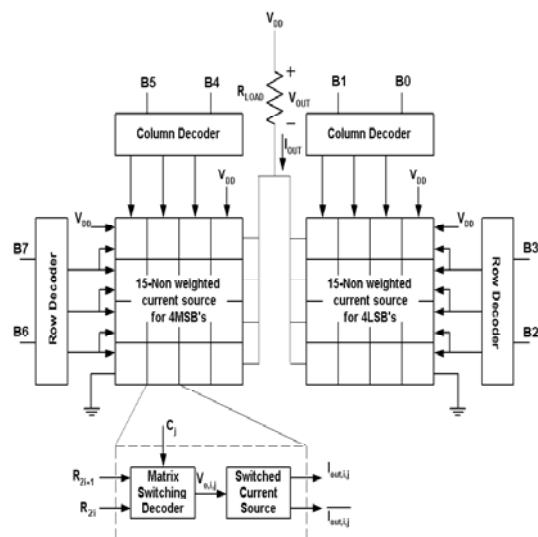


Block Design (continued)

- Prescaler: high operating frequency, low power dissipation, low phase-noise contribution
- Feedback CML: Transistors, MF₁ and MF₂


$$A(f) = \frac{A_d(f)}{1 + F_b \cdot A_d(f)} = \frac{A_d(0)}{1 + F_b \cdot A_d(0)} \cdot \frac{1}{1 - j\left(\frac{\omega}{\omega_p}\right)\left(\frac{1}{1 + F_b A_d(0)}\right)}$$

  - F_b: the gain of the feedback transistors
- The BW of the feedback CML is wider than the BW of the conventional CML



Block Design (Continued)

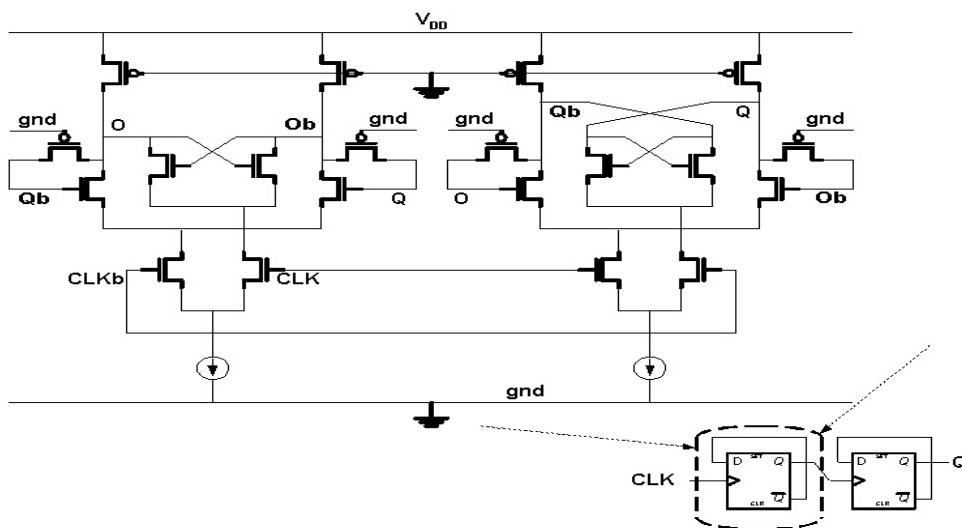- Feedback Current Mode Logic in D Flip-Flop





Block Design (Continued)

- FIR digital filter

(a) Single flow graph of nth order

(b) Linear Phase transpose direct form

 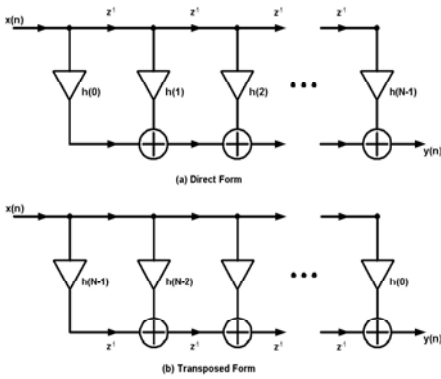

- Floating point coefficient