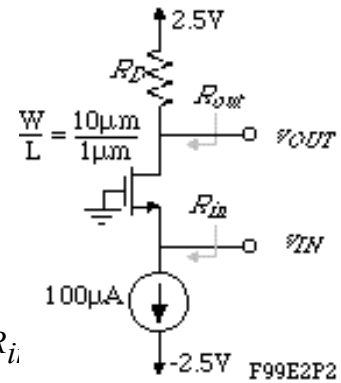


Homework # 5

Problem 1


The following questions relate to the MOSFET circuit shown. Assume the MOSFET is saturated and has the large signal parameters of $K_N' = 24 \mu\text{A}/\text{V}^2$, $V_{TN} = 0.75 \text{ V}$, and $\lambda_N = 0.01 \text{ V}^{-1}$.

- (a.) What is the dc value of v_{IN} ?
- (b.) What is the largest value of R_D for which the MOSFET is saturated?
- (c.) If $R_D = 10\text{k}\Omega$, what is the numerical value of the small-signal voltage gain, v_{out}/v_{in} ?
- (d.) What is the numerical value of the small-signal input resistance, R_i ?
- (e.) What is the numerical value of the small-signal output resistance, R_{out} ?




Problem 2

A BJT amplifier is shown. (a.) Find the value of V_{BB} that will give $I_C = 1\text{mA}$. (b.) Assume that $I_C = 1\text{mA}$ and find the small signal input resistance, R_{in} , output resistance, R_{out} , and the midband voltage gain, $A_v(0)$. (c.) If $C_\pi = 10\text{pF}$ and $C_\mu = 1\text{pF}$, use Miller's approximation to find the -3dB frequency of this amplifier in Hertz.

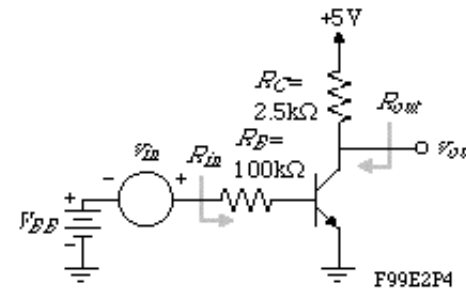

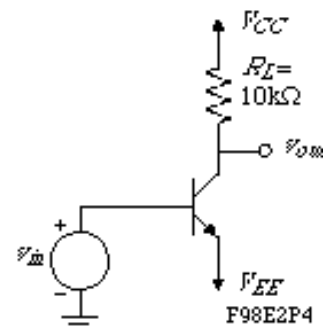Problem 3

Find the -3dB frequency of the circuit shown in Hz. The values of the hybrid-pi model are $r_b = 100\Omega$, $r_\pi = 10\text{k}\Omega$, $g_m = 10\text{mS}$, $r_o = 100\text{k}\Omega$, $C_\mu = 1\text{pF}$, and $f_T = 100\text{MHz}$. (Hint: Use the Miller approximation on C_μ and ignore the output pole.)




Homework # 5 - Solutions

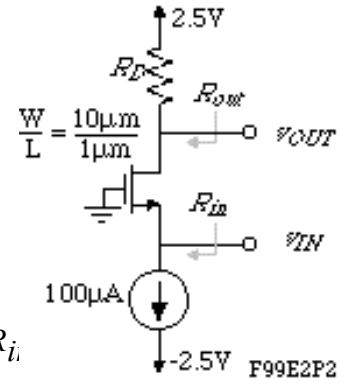Problem 1

The following questions relate to the MOSFET circuit shown. Assume the MOSFET is saturated and has the large signal parameters of $K_N' = 24 \mu\text{A}/\text{V}^2$, $V_{TN} = 0.75 \text{ V}$, and $\lambda_N = 0.01 \text{ V}^{-1}$.

- What is the dc value of v_{IN} ?
- What is the largest value of R_D for which the MOSFET is saturated?
- If $R_D = 10\text{k}\Omega$, what is the numerical value of the small-signal voltage gain, v_{out}/v_{in} ?
- What is the numerical value of the small-signal input resistance, R_i ?
- What is the numerical value of the small-signal output resistance, R_{out} ?



Solution:

(a.) $V_{IN} = -V_{GS} = -\sqrt{\frac{2I_D}{K'(W/L)}} - V_T = -0.913 - 0.75 = -1.663\text{V} \rightarrow \boxed{V_{IN} = -1.663\text{V}}$

(b.) Remember that the drain can be a value of V_T below the gate when the transistor is on the edge of saturation.

$\therefore R_D = \frac{2.5 - (-0.75)}{100\mu\text{A}} = 32\text{k}\Omega \rightarrow \boxed{R_D \leq 32\text{k}\Omega}$


(c.) Small-signal model:

Noting that $v_{gs} = -v_{in}$, we can sum the currents at the output node a

$$g_m v_{in} + g_{ds}(v_{in} - v_{out}) = G_D v_{out} \rightarrow \frac{v_{out}}{v_{in}} = \frac{g_m + g_{ds}}{G_D + g_{ds}}$$

$g_m = \sqrt{2 \cdot 100 \cdot 24 \cdot 10} = 219\mu\text{S}$, $g_{ds} = 100 \cdot 0.01 = 1\mu\text{S}$, and $G_D = 10\text{S}$

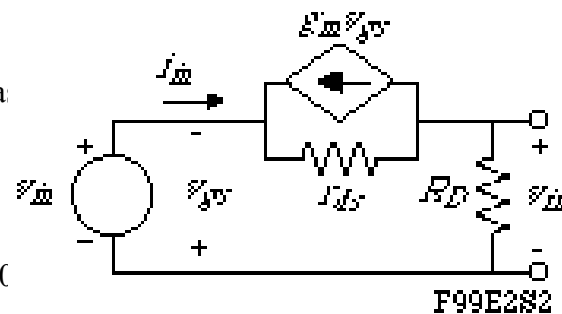$\therefore \frac{v_{out}}{v_{in}} = +2.18\text{V/V} \rightarrow \boxed{\frac{v_{out}}{v_{in}} = +2.18\text{V/V}}$



(d.) Summing the currents at the input gives $i_{in} = g_m v_{in} + g_{ds}(v_{in} - v_{out})$

Noting that $v_{out} = i_{in} R_D$ gives

$$i_{in}(1 + g_{ds} R_D) = (g_m + g_{ds}) v_{in} \rightarrow \frac{v_{in}}{i_{in}} = \frac{1 + g_{ds} R_D}{g_m + g_{ds}} = \frac{1 + 0.1}{219 + 1} \times 10^6 = 4591\Omega$$

$$\therefore R_{in} = 4591\Omega$$

(e.) The output resistance is simplified if we recall that $v_{in} = 0$ which means that $v_{gs} = 0$. Therefore the output resistance is simply

$$R_{out} = \frac{1}{g_{ds} + G_D} = \frac{10^6}{1 + 100} = 9.9k\Omega$$


Problem 2

A BJT amplifier is shown. (a.) Find the value of V_{BB} that will give $I_C = 1mA$. (b.) Assume that $I_C = 1mA$ and find the small signal input resistance, R_{in} , output resistance, R_{out} and the midband voltage gain, $A_v(0)$. (c.) If $C_\pi = 10pF$ and $C_\mu = 1pF$, use Miller's approximation to find the -3dB frequency of this amplifier in μs .

Solution:

$$(a.) V_{BB} = \frac{R_B I_C}{\beta} + V_t \ln\left(\frac{I_C}{I_S}\right) = \frac{100 \cdot 1}{100} + 0.656 = 1.656V$$

$$\rightarrow V_{BB} = 1.656V$$

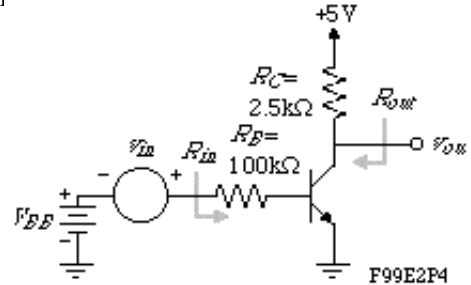


(b.) Small-signal model:

$$g_m = \frac{I_C}{V_t} = \frac{1mA}{25.9mV} = 38.6mS,$$

$$r_\pi = \frac{1 + \beta}{g_m} = \frac{101}{0.0386} = 2.616k\Omega,$$
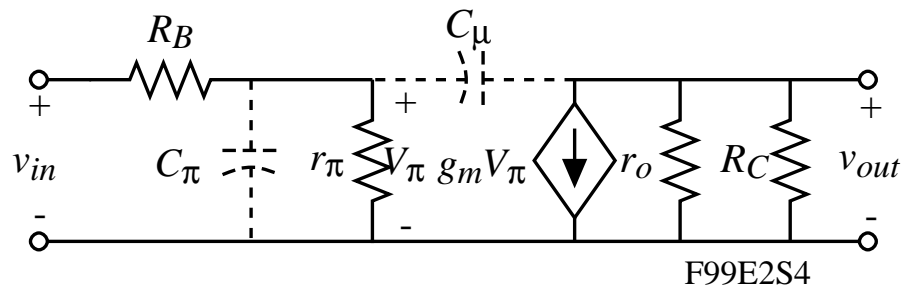
$$r_o = \frac{V_A}{I_C} = \frac{100V}{1mA} = 100k\Omega$$



$$\text{First: } R_{in} = R_B + r_\pi = 102.62k\Omega \text{ and } R_{out} = r_o || R_C = 100k\Omega || 2.5k\Omega = 2.44k\Omega$$

$$\text{Next: } A_v(0) = \frac{V_{out}}{V_{in}} = \frac{-g_m r_\pi R_{out}}{r_\pi + R_B} = \frac{-0.0386(2.44 \times 10^3)2.616}{102.616} = -2.4V/V \rightarrow A_v(0) = -2.4V/V$$

(c.) With the capacitors included in the model,


$$\begin{aligned} \omega_{-3dB} &= \frac{1}{(R_B || r_\pi)[C_\pi + C_\mu(1 + g_m R_{out})]} = \frac{10^{12}}{(2.549 \times 10^3)[10 + 1(1 + 93.18)]} \\ &= 3.766 \times 10^6 \text{ rads/sec.} \rightarrow f_{-3dB} = 0.599 \text{ MHz} \end{aligned}$$

Problem 3

Find the -3dB frequency of the circuit shown in Hz. The values of the hybrid-pi model are $r_b = 100\Omega$, $r_\pi = 10k\Omega$, $g_m = 10mS$, $r_o = 100k\Omega$, $C_\mu = 1pF$, and $f_T = 100MHz$. (Hint: Use the Miller approximation on C_μ and ignore the output pole.)

Solution:

Small signal model:

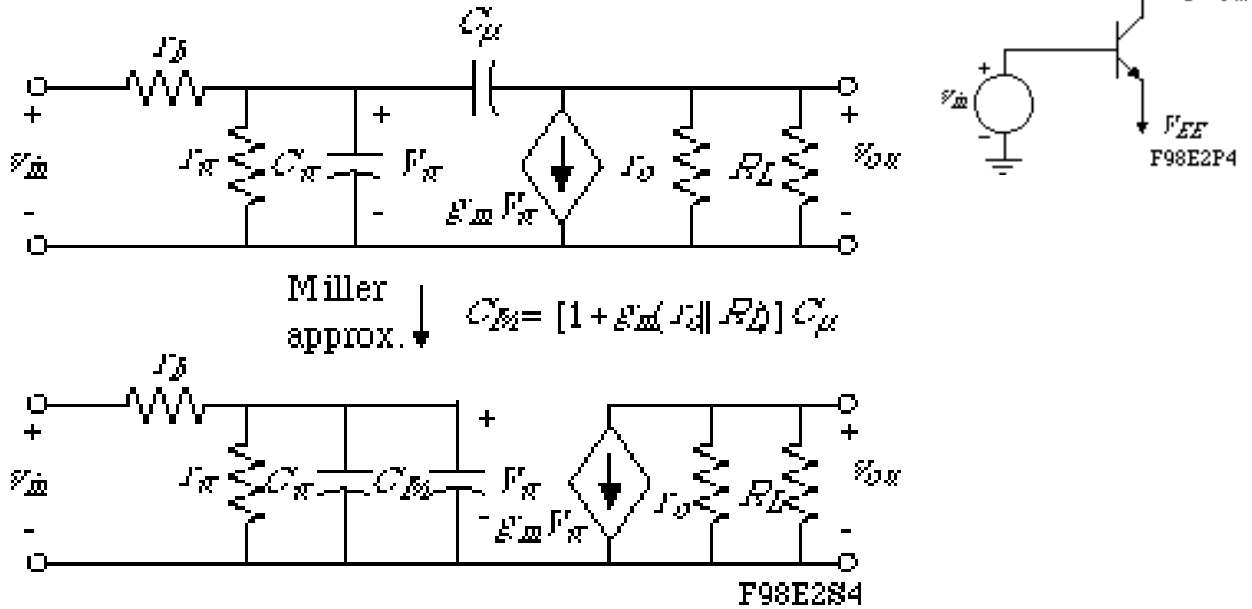

Miller approx. ↓ $C_M = [1 + g_m(r_b || R_D)] C_\mu$

$$C_\pi = \frac{g_m}{\omega_T} - C_\mu = \frac{10 \times 10^{-3}}{2\pi \times 10^8} - 1pF = 14.9pF$$

Method 1 –Miller Approx.: $C_M = [1 + 10^{-2}(100k\Omega || 10k\Omega)]1pF = (1+90.9)1pF = 91.9pF$

Thus, $\omega_{-3dB} \approx \frac{1}{(r_b || r_\pi)(C_\pi + C_M)} = \frac{1}{99\Omega \cdot 106.8pF} = 94.6 \times 10^6 \text{ rads/sec.}$

$$\therefore f_{-3dB} \approx \frac{94.6 \times 10^6}{2\pi} = 15.1MHz$$

Method 2 – Classical Approach (two-node problem):

$$V_{out}(g_o + G_L + sC_\mu) = (sC_\mu - g_m)V_{out} \quad \& \quad g_b V_{in} = (g_\pi + g_b + sC_\pi + sC_\mu)V_\pi - sC_\mu V_{out}$$

Solving: $\frac{V_{out}}{V_{in}} = \frac{g_b(sC_\mu - g_m)}{s^2 C_\mu C_\pi + s[(C_\mu + C_\pi)(g_o + G_L) + (g_\pi + g_b)C_\mu + g_m C_\mu] + (g_\pi + g_b)(g_o + G_L)}$

& denominator is: $D(s) = 14.9 \times 10^{-24}(s^2 + 14.66 \times 10^8 s + 7.4564 \times 10^{16})$, which has two roots.

The smallest is -527.6×10^6 rads/sec which gives

$$f_{-3\text{dB}} = \frac{527 \times 10^6}{2\pi} = 8.4\text{MHz}$$